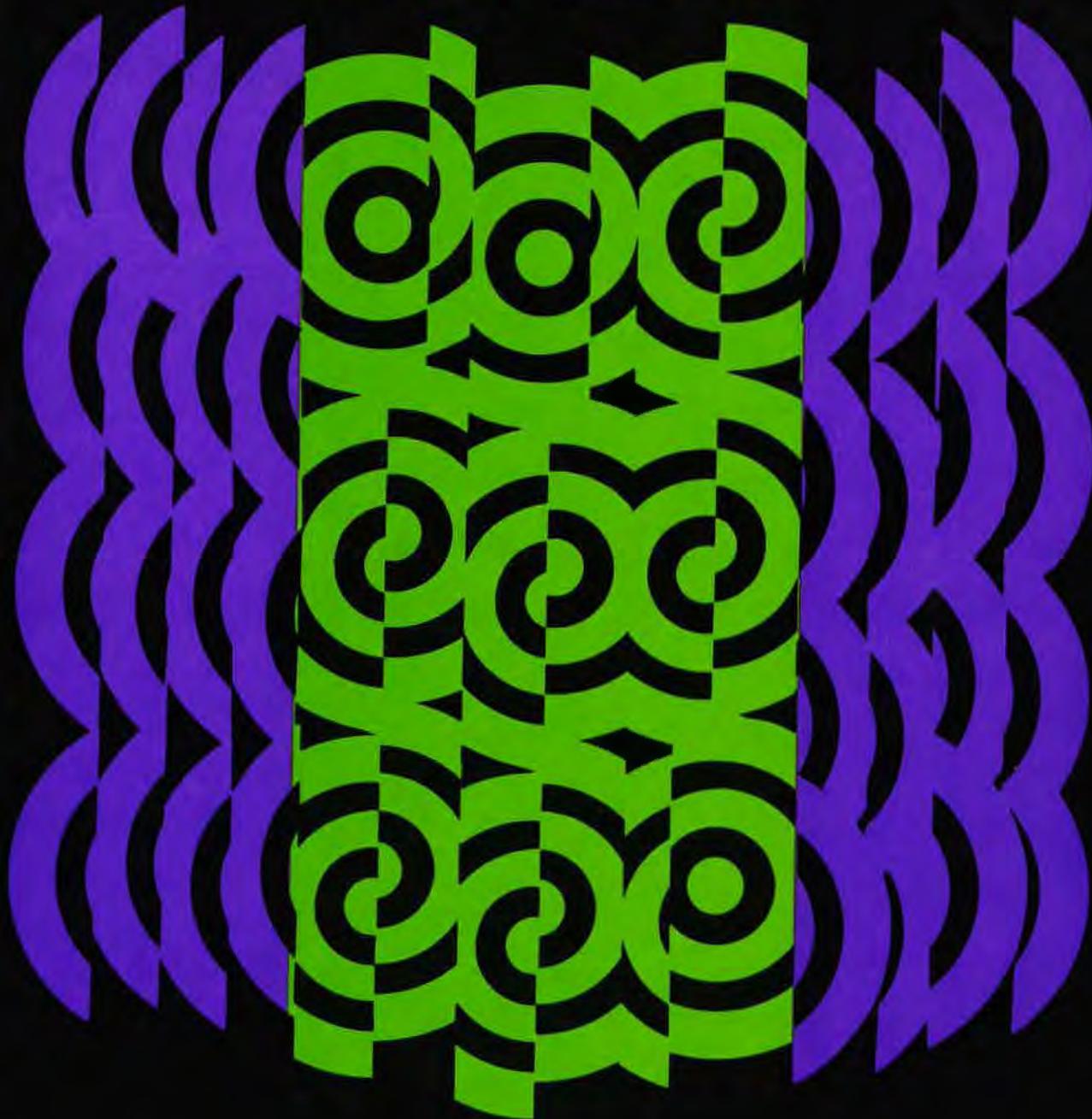


HANDBOOK OF ELECTRONIC DESIGN AND ANALYSIS PROCEDURES USING PROGRAMMABLE CALCULATORS

BRUCE K. MURDOCK



INTRODUCTION

This book provides programming techniques and programs to make the fully programmable calculator a valuable design tool for the working engineer. This book is not specifically intended to be a textbook on calculator programming, although documented programs can serve this purpose. Three books can be recommended for programming methods and algorithms: Jon M. Smith, "Scientific Analysis on the Pocket Calculator," Wiley 1975, John Ball, "Algorithms for RPN Calculators," Wiley 1978, and Richard W. Hamming, "Numerical Methods for Scientists and Engineers," McGraw-Hill 1973.

Many programs in this book are meant to be used in sets, i.e., the output of one program becomes the input for another through common storage register allocations. The description of each program is meant to stand alone, and consists of the following parts:

- 1) Problem description with pertinent equations,
- 2) Program operating instructions,
- 3) One or more program examples,
- 4) Equation and method derivation, or references,
- 5) Annotated program listing, which is its own flowchart.

Part 4 is not present in every program.

This program ordering was chosen so the variable definitions and operating instructions are immediately available to the experienced user. Should the user wish more information or background on the program and equations, or the details of the program operation, this material is also available, but is placed after the operating instructions.

Although the program language, and resulting program flow is tailored to the Hewlett-Packard (HP) fully programmable calculators, the HP-67/97, the annotated program listing/flowchart can be used as a basis for generating programs in other languages.

The language of the Texas Instruments (TI) fully programmable calculator, the TI-59, is not very different from the HP-67/97 language

when considered on a gross scale, therefore, the HP-67/97 programs may be easily translated into the language of the TI-59. While it is easy to write a program from equations and flowcharts, the new program must still be debugged. Translating a program that has already been tested and debugged can lead to a new program that has no bugs at all. The TI program translation will also closely follow the flow of the original HP program.

The differences between the HP and TI languages are mainly in format and not in form. Because the TI-59 has few merged keycodes, must use parentheses to set hierarchy, and must branch to a label or line number as the result of a true conditional test, the TI-59 program will be longer than the mating HP-67/97 program. This increased program length is generally not a detriment as it is accommodated by the larger program memory available in the TI-59. Because the TI-59 always starts label searches from the top of the program, the program execution time can also be longer unless direct addressing is used, or the labeled subroutines are placed at the beginning of the program.

Since the TI-59 does not have a stack to hold the results of an equals operation, a set of scratchpad registers must be set aside to hold those intermediate results normally retained in the HP-67/97 stack. Results residing in the TI-59 display register after the equals operation will permanently disappear unless stored before subsequent operations are performed.

The arithmetic hierarchy of the Algebraic Operating System (AOS) can sometimes be a problem which becomes particularly apparent when calling subroutines. If an equals operation does not precede the subroutine call, the subroutine hierarchy will be dependent on the hierarchy set up in the main program. To make the subroutine hierarchy independent of the main program, the subroutine should always start with an open parenthesis and terminate with a close parenthesis. This rule can be extended to the "go to" command also. The last statement prior to the unconditional jump should be an equals to terminate all pending operations. It will cause no harm to have an open parenthesis as the first statement after the label that is the jump destination. The TI-59 has enough program memory so that, whenever in doubt, parenthesis can be inserted to establish unconditional arithmetic hierarchy.

The TI-59 does not have the equivalent of the HP-67/97 flag 3 function where flag 3 is automatically set whenever numeric data

is entered from the keyboard. Because of this difference, the convenience feature existing in most of the HP-67/97 programs herein where the execution of a user definable key such as "A" without numeric entry results in the currently stored parameter value being displayed cannot be translated to the TI-59 program.

None of the TI-59 flags are test cleared, while flags 2 and 3 of the HP-67/97 are test cleared, thus, clear flag statements may be required in the TI-59 program and subroutines involving the use of flags 2 and 3.

The HP-67/97 and the TI-59 both have user definable labels A through E, and a through e (the latter are designated A' through E' on the TI-59). Executing these keys from the keyboard acts like a subroutine call on either machine: the program pointer jumps to the designated label, and program execution begins. The HP-67/97 and the TI-59 are different in the labels called "common labels" by TI, i.e., labels other than the user definable ones. HP uses the label designators 0 through 9, and a given label may be used more than once as label searches start from the present place in program memory, hence a "local label" such as label 6 in Program 2-4 is used many times within the program. The TI-59 cannot use numeric labels, but uses other function keys as labels, e.g., "sin," "fix," etc. There are 62 such keys available for labels. The TI-59 always starts label searches from the top of the program, hence, a given label can only be used once within the program.

The TI-59 is internally set up to be most efficient, time wise, when jumps and branches are made to line numbers rather than to labels. The HP-67/97 appears to be as fast in a label search as the TI-59 is in a line number search. The HP-67/97 cannot go to a specified line number under program control, hence, it is restricted to label searches only. There is a simple program trick shown on page IV-98 of the TI-59 owner's manual where a program is initially written with labels, and the label calls have "NOP" statements following so the program can easily be modified for line number addressing after the program is debugged and complete.

Care should be exercised when translating program coding containing rectangular-to-polar ($\rightarrow P$) and polar-to-rectangular ($\rightarrow R$) conversions as the TI-59 and HP-67/97 operate on the variables in opposite manner. The HP-67/97 takes the x and y coordinates from the x and y registers

and places the magnitude and angle equivalents back into the x and y registers respectively for the $\rightarrow P$ conversion, and vice-versa for the $\rightarrow R$ conversion. The TI-59 uses the t and x registers for the two variables, and takes the x and y coordinates from the t and x registers and places the equivalent magnitude and angle back into the t and x registers respectively for the $\rightarrow P$ conversion, and vice-versa for the $\rightarrow R$ conversion. Both machines display the contents of the x register, so the TI-59 will display angle or y coordinate whereas the HP-67/97 will display magnitude or x coordinate after respective $\rightarrow P$ or $\rightarrow R$ conversions.

To guide the reader in this translation, several programs in this book have been translated into the TI-59 language. These programs have user instructions, examples, and program coding in both languages. Program 1-1 has been flowcharted in addition to provide a common point of reference between the two program listings.

The preceding paragraphs mention anomalies in the TI-59 language. The HP-67/97 language has its idiosyncracies also. Reading the program listings, one will notice some "non-standard" program coding. The prime consideration was to fit the algorithm into the program memory. Within this constraint, the program coding was selected to minimize program execution time whenever possible. Numeric entries within the body of the program are to be avoided, and should be recalled from register storage. Entry of each numeric digit requires 72 milliseconds to execute while a register recall only requires 35 milliseconds typically. Numeric entries such as "10," "100," or any other power of 10 should be entered as a power of ten through the "EEX" key. The number "1" should be entered as "EEX" alone and requires only 48 milliseconds to execute. Similarly, the "CLX" function will result in a zero in the display, and only requires 30 milliseconds to execute. Multiplication of a number by two ($2, \times$) requires 179 milliseconds to execute, while addition of a number to itself ($ENT \uparrow, +$) requires 82 milliseconds execution time and yields the same result. Register arithmetic is executed faster than stack arithmetic when the register recalls are considered, and register arithmetic can save program steps. Whenever the algorithm allows, subroutine calls should be minimized as they typically require 240 milliseconds for the label search and return. Likewise unconditional jumps such as GTOA require 160 milliseconds for the label search typically. By paying attention to small details such as these, the program

execution time can be shortened considerably especially when iteration or looping is required. For more information on execution times and programming hints with the HP-67/97, see "Better Programming on the HP-67/97" edited by William Kolb, John Kennedy, and Richard Nelson, and available from the PPC Club (new name for the HP-65 Users Club), 2541 W. Camden Place, Santa Ana, Calif. 92704.

Even though the program coding has been chosen for minimum execution time, the program LNAP may require more than a minute of computation time before output is provided when the number of branches is large. Likewise, the same time requirement may exist for the filter programs when the filter order is large.

An attempt has been made to choose self-explanatory label descriptions for the user definable keys; hence, once familiar with a particular program, the user need only refer to the magnetic card label markings to run the program.

To restate a point made in the preface of this book, it is not possible to include programs and descriptions covering all areas of engineering analysis and design. The programs herein are only representative of areas in networks and circuits (the terms "networks" and "circuits" may be used interchangeably). The 39 programs contained in this book have been selected from the author's library, and have proved to be quite useful to the author; hopefully, they will prove equally useful to the reader.

The program description not only shows the equations used by the program, but gives a reference, or has a derivation of the equations so these programs may serve as a base for the generation of other related programs as may be needed by the reader for his or her particular application.

Because the programs herein cover several different disciplines in electrical engineering, a problem with nomenclature arises. To the control systems oriented engineer, the term "transfer function" implies system output divided by system input. On the other hand, to the filter design engineer, "transfer function" implies system input divided by system output, or the reciprocal of the control system engineer's definition. To avoid confusion, the term "transmission function" is used to mean system output divided by input and "transfer function" is used to mean system input divided by output. This convention will be followed

throughout the book.

The appendix has a list of a list of abbreviations used, along with the bibliography give the reader an easily found place to go should confusion or uncertainty to variable or abbreviation meaning arise.

HANDBOOK OF ELECTRONIC DESIGN AND ANALYSIS PROCEDURES USING PROGRAMMABLE CALCULATORS

Part 1
NETWORK ANALYSIS

PROGRAM 1-1 LOSSY TRANSMISSION LINE INPUT IMPEDANCE.

Program Description and Equations Used

This program uses Eq. (1-1.1) to determine the complex input impedance, Z_s , of a lossy transmission line of length ℓ , loaded with a complex impedance Z_r , and having a characteristic impedance Z_0 , an attenuation constant α_{dB} in dB per unit length, and a phase constant β in radians per unit length (or velocity of propagation C_m). For solid dielectric cables, C_m is typically 1/2 to 2/3 the free-space speed of light, and is approximated by Eq. (1-1.9) for low loss coaxial cables, or calculated from Eqs. (1-1.5) and (1-1.6) if the cable impedance and admittance per unit length are known at the operating frequency. The unit of length has purposely not been given because it is to be selected by the user. As long as the same length unit is used throughout, length will cancel out of Eq. (1-1.1). Figure 1-1.1 shows the general circuit topology.

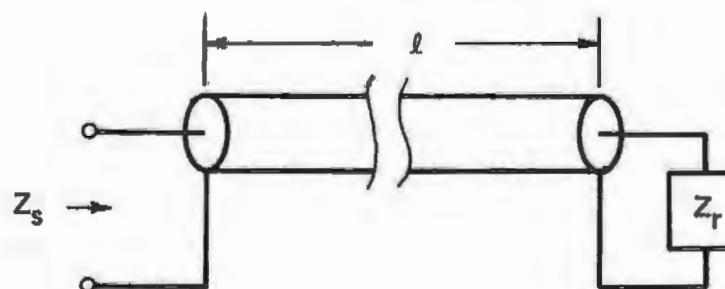


Figure 1-1.1 Transmission line setup.

The equation that describes the problem is:

$$Z_s = Z_o \frac{1 + \rho e^{-2\gamma l}}{1 - \rho e^{-2\gamma l}} \quad (1-1.1)$$

where ρ is the reflection coefficient and γ is the propagation function. These quantities are given by the following equations:

$$\rho = \frac{Z_r/Z_o - 1}{Z_r/Z_o + 1} \quad (1-1.2)$$

$$\gamma = \alpha + j\beta \quad (1-1.3)$$

$$\alpha = (\alpha_{db})/(20 \log e) \quad (1-1.4)$$

$$\beta = \frac{2\pi}{\lambda} = \frac{2\pi f}{C_m} \quad (1-1.5)$$

If the per unit length series impedance, $\bar{R} + j\omega\bar{L}$, and shunt admittance, $\bar{G} + j\omega\bar{C}$, are available at the frequency of operation, then the propagation function is given by:

$$\gamma = \sqrt{(\bar{R} + j\omega\bar{L})(\bar{G} + j\omega\bar{C})} \quad (1-1.6)$$

If Z_r is desired in terms of Z_s , Z_r is replaced by Z_s in Eq. (1-1.1), Z_s is replaced by Z_r in Eq. (1-1.2), and l is replaced by $-l$ in Eq. (1-1.1).

This quasi-symmetrical property allows the use of the same program to calculate the transmission line input impedance with a complex load by using a positive line length, or to calculate the complex load that will provide a specified input impedance by using a negative line length.

A duality also exists with Eq. (1-1.1) and Eq. (1-1.2). The same equation form holds for the transmission line input or output admittance providing each Z is replaced by the corresponding Y , i.e., $Y_s = 1/Z_s$, $Y_r = 1/Z_r$, and $Y_o = 1/Z_o$. The admittance forms of Eqs. (1-1.1) and (1-1.2) are as follows:

$$Y_s = Y_o \frac{1 + \rho' e^{-2\gamma l}}{1 - \rho' e^{-2\gamma l}} \quad (1-1.7)$$

where

$$\rho' = \frac{Y_r/Y_o - 1}{Y_r/Y_o + 1} \quad (1-1.8)$$

$$(\rho' = -\rho)$$

Because the equation form is the same, the program will work with admittances as well as impedances.

In this HP-67/97 program, keys "A" through "E" and "a" through "c" on the calculator have a dual function role. Execution of these keys following a data entry from the keyboard is interpreted as data input by the program, and the numeric entry is stored. Execution of these keys following a nonnumeric entry, or following the "e" (clear) key is interpreted as an output request, and the currently stored values are printed (HP-97 only) and displayed. This feature cannot be translated into the TI-59 program.


The data required by the program is entered in either cartesian (real and imaginary) or polar (magnitude and angle) form through keys "b" and "c," or "B" and "C" respectively. On large coax cables such as underwater telephone cable, both the cable attenuation and phase constants are provided as a function of frequency by the manufacturer, and are loaded into the program using the units of dB per unit length and radians per unit length respectively. If β is unknown, it can be calculated from the velocity of propagation in the transmission line. If the transmission line has less than 1 dB loss in the length being used, and is of coaxial construction, the velocity in the medium (phase velocity) may be approximated by

$$C_m \approx \frac{\text{speed of light in free space}}{\sqrt{\epsilon_r \mu_r}} \quad (1-1.9)$$

where ϵ_r and μ_r are the relative dielectric constant and relative permeability of the cable dielectric and conductors respectively. For cables constructed of nonmagnetic parts, or for cables with a steel strength member within the center conductor of the cable and operating at frequencies where the skin effect keeps currents from flowing within the strength member, the relative permeability, μ_r becomes unity.

1-1 User Instructions

HP-67/97 PROGRAM

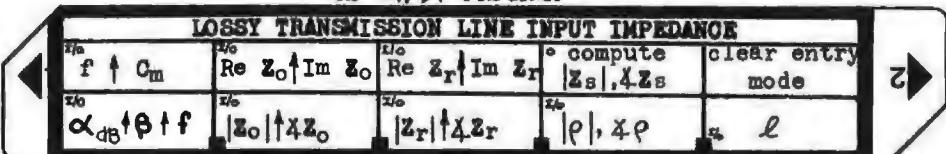

STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
1	Load both sides of program card			
2	Enter transmission line parameters line loss in dB/unit length α _{dB} phase constant in radians/unit length β frequency in hertz f If velocity of propagation is known instead of phase constant, enter dummy value of 1 for phase constant in step 3 above, then Enter frequency in hertz f Enter propagation velocity* C _m		f ↓ A	α _{dB} β f C _m
	* note: The units of length must be consistent throughout the data, i.e., all in meters, or feet, or miles, etc.			
3	Enter the transmission line characteristics at the chosen analysis frequency magnitude of Z _o in ohms Z _o phase angle of Z _o in degrees 4Z _o OR real part of Z _o in ohms Re Z _o imaginary part of Z _o in ohms Im Z _o		↑ B	Z _o 4Z _o Re Z _o Im Z _o
4	Enter load impedance magnitude of load impedance in ohms Z _r phase angle of load impedance in degrees 4Z _r OR real part of load impedance in ohms Re Z _r imaginary part of load impedance in Ω Im Z _r		↑ C	Z _r 4Z _r Re Z _r Im Z _r

1-1 User Instructions

LOSSY TRANSMISSION LINE INPUT IMPEDANCE

HP-67/97
CONTINUED




STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
5	Enter transmission line length +l to calculate Z _s given Z _r -l to calculate Z _r given Z _s	± l	E	
6	Optional, printout or enter refl. coef ρ entry ρ printout Of the three variables Z _o , Z _r , & ρ either Z _o & Z _r or Z _o & ρ are required.	ρ entry ρ printout	D D	1ρ1, 4ρ°
7	Compute Z _s , 4Z _s (length positive) Z _r , 4Z _r (length negative)		f D	Z , 4Z°
8	To clear input mode and initialize program		f E	
9	To review input data		f E f A A f B B f C C f D D f E E	f, C _m α _{dB} , β, f Re Z _o , Im Z _o Z _o , 4Z _o Re Z _r , Im Z _r Z _r , 4Z _r 1ρ1, 4ρ° l

NOTE:

The angular mode of the program is degrees.
All angular data input and output is in
degrees with the exception of β. The
angular mode should not be changed as program
malfunction will occur because of R>D and
D>R conversions that are used.

1-1 User Instructions

→ TI-59 TRANSLATION ←

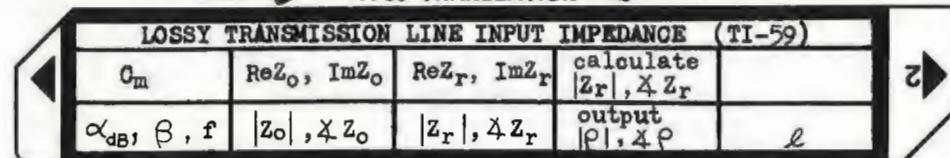

STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
1	Load both sides of magnetic card			
2	Load line loss in dB/unit length Load line phase constant in rad/unit length If C_m , the velocity in the medium, is known instead, load dummy β of 1	α_{dB} β	A R/S	
	Load analysis frequency in hertz	f	R/S	
3	If C_m is known instead of β , load C_m	C_m	2nd A	
4	Enter Z_0 , the transmission line characteristic impedance in polar or rectangular co-ords polar co-ordinates: magnitude $ Z_0 , \Omega$ phase angle $\angle Z_0, ^\circ$		B R/S	
	rectangular co-ordinates: real part $Re Z_0, \Omega$ imaginary part $Im Z_0, \Omega$		2nd B R/S	
5	Enter load impedance at the analysis freq as either polar or rectangular data polar co-ordinates: $ Z_r , \Omega$ $\angle Z_r, ^\circ$		C R/S	
	rectangular co-ordinates: $Re Z_r, \Omega$ $Im Z_r, \Omega$		2nd C R/S	
6	Load transmission line length + ℓ to calculate Z_s given Z_r - ℓ to calculate Z_r given Z_s	$\pm \ell$	E	
7	Optional: output reflection coefficient		D R/S*	$ \rho $ $\angle \rho, ^\circ$
8	To calculate Z_s (or Z_r given negative length) * If the TI-59 is attached to the PC-100A printer, the second value will be printed without the R/S command.		2nd D R/S*	$ Z , \Omega$ $\angle Z, ^\circ$

Example 1-1.1

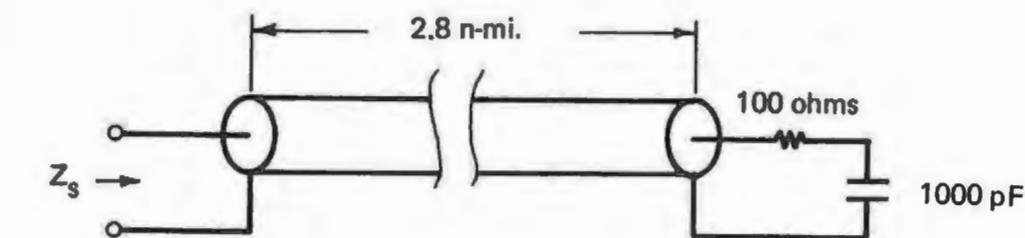


Figure 1-1.2 SD coaxial cable circuit for Ex. 1-1.1.

Type SD underwater telephone coax is to be used at 0.72 MHz. The cable section is 2.8 nautical miles (n-mi.) long and is loaded by a series RC network of 100 ohms and 1000 pF as shown in Fig. 1-1.2. Find the cable input impedance, Z_s , at this frequency.

At 0.72 MHz the electrical parameters of SD coax are:

$$\alpha_{dB} = 2.070 \text{ dB/n-mi.}$$

$$\beta = 42.511 \text{ radians/n-mi.}$$

$$Z_0 = 44.625 \text{ ohms at } -0.315 \text{ degree}$$

The RC load impedance is:

$$Re Z_r = 100 \text{ ohms}$$

$$Im Z_r = -j/(2\pi fC) = -j221 \text{ ohms}$$

The input impedance of the loaded coax is $66.902 + j11.167$ ohms as obtained from using the program and shown in the printout below:

PROGRAM INPUT	PROGRAM OUTPUT
2.070 ENT1 α_{dB} , dB/n-mi. 42.511 ENT1 β , rad/n-mi. .72+06 GSBA frequency, Hz	GSBd calculate Z_s 67.827 *** $ Z_s $, ohms 9.476 *** $\angle Z_s$, degrees
44.265 ENT1 $ Z_0 $, ohms -.315 GSBE $\angle Z_0$, degrees	X2Y convert to rect +R
100.000 ENT1 $Re Z_r$, ohms -221.000 GSBe $Im Z_r$, "	66.902 *** $Re Z_s$, ohms 11.167 *** $Im Z_s$, "
2.800 GSBE length, n-mi.	GSBa calculate C_m 720000.000 *** frequency, Hz 106417.008 *** C_m , n-mi./sec

Example 1-1.2

Using the type SD underwater telephone coax of Example 1-1.1, find the load impedance at 0.72 MHz that will result in an input impedance of $60 + j0$ ohms. The length of the coax is 2.8 n-mi. as in the previous example.

When using a lossy cable, a negative real part in Z_r will be required to obtain values of Z_s greatly different than Z_o . Furthermore, if αl is greater than 30 dB, the input impedance will be nearly Z_o , independent of the load impedance.

In this example, a negative line length is loaded to use the quasi-symmetric properties of Eqs. (1-1.1) and (1-1.2) for calculating Z_r given Z_s .

The HP-97 printout reproduced next shows a load impedance of $67.396 - j73.338$ ohms is required. The equivalent load network is also shown.

PROGRAM INPUT	PROGRAM OUTPUT
2.070 ENT† α_{dB} , dB/n-mi. 42.511 ENT† β , rad/n-mi. .72+0j GSBA frequency, Hz	GSBa calculate load Z_r 99.603 *** $ Z_r $, ohms -47.418 *** $\angle Z_r$, degrees
44.265 ENT† $ Z_o $, ohms -.315 GSBE $\angle Z_o$, degrees	X2Y convert to rect 67.396 *** Re Z_r , ohms -73.338 *** Im Z_r , "
60.000 ENT† Re Z_s , ohms 0.000 GSBe Im Z_s , "	2.000 Pi calculate .72+0j X equivalent X capacitor 1/X
-2.800 GSBE	3.014-09 *** C, farad

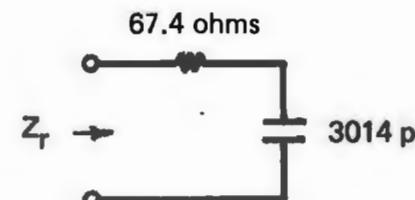


Figure 1-1.3 Equivalent load network.

Example 1-1.3, TI-59 Program Example

This example is the same as Example 1-1.2 where the problem is to determine load impedance, Z_r , that results in an input impedance, Z_s , of $60 + j0$ ohms. The line length is 2.8 n-mi. Because Z_r is to be calculated given Z_s , a negative line length is used. The PC-100A printer output is shown below.

PROGRAM INPUT

2.07	α_{dB} , dB/n-mi.
42.511	β , rad/n-mi.
7.2 05	frequency, Hz
106417.0079	C_m (output), n-mi./sec
44.265	$ Z_o $, ohms
-.315	$\angle Z_o$, degrees


60.	Re Z_s , ohms
0.	Im Z_s , "
-2.8	line length, n-mi.

PROGRAM OUTPUT


.1509385583	$ \rho $, dimensionless
1.019762234	$\angle \rho$, degrees
99.60303649	$ Z_r $, ohms
-47.41754913	$\angle Z_r$, degrees

Note: the PC-100A printer will not print the mnemonic representing the input key. The HP-97 does this automatically when in the "norm" mode.



PROGRAM FLOW DIAGRAM

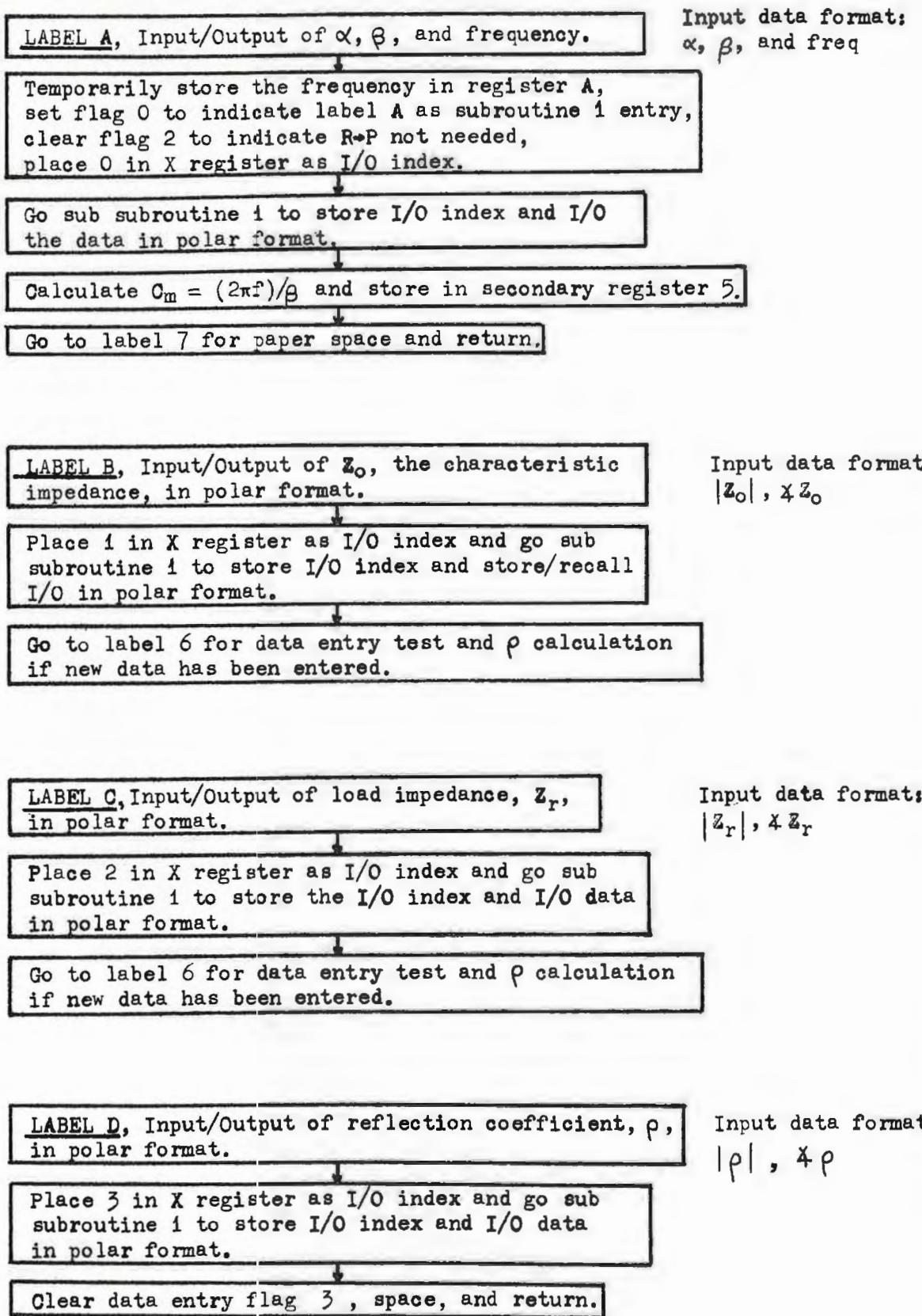



PROGRAM FLOW DIAGRAM

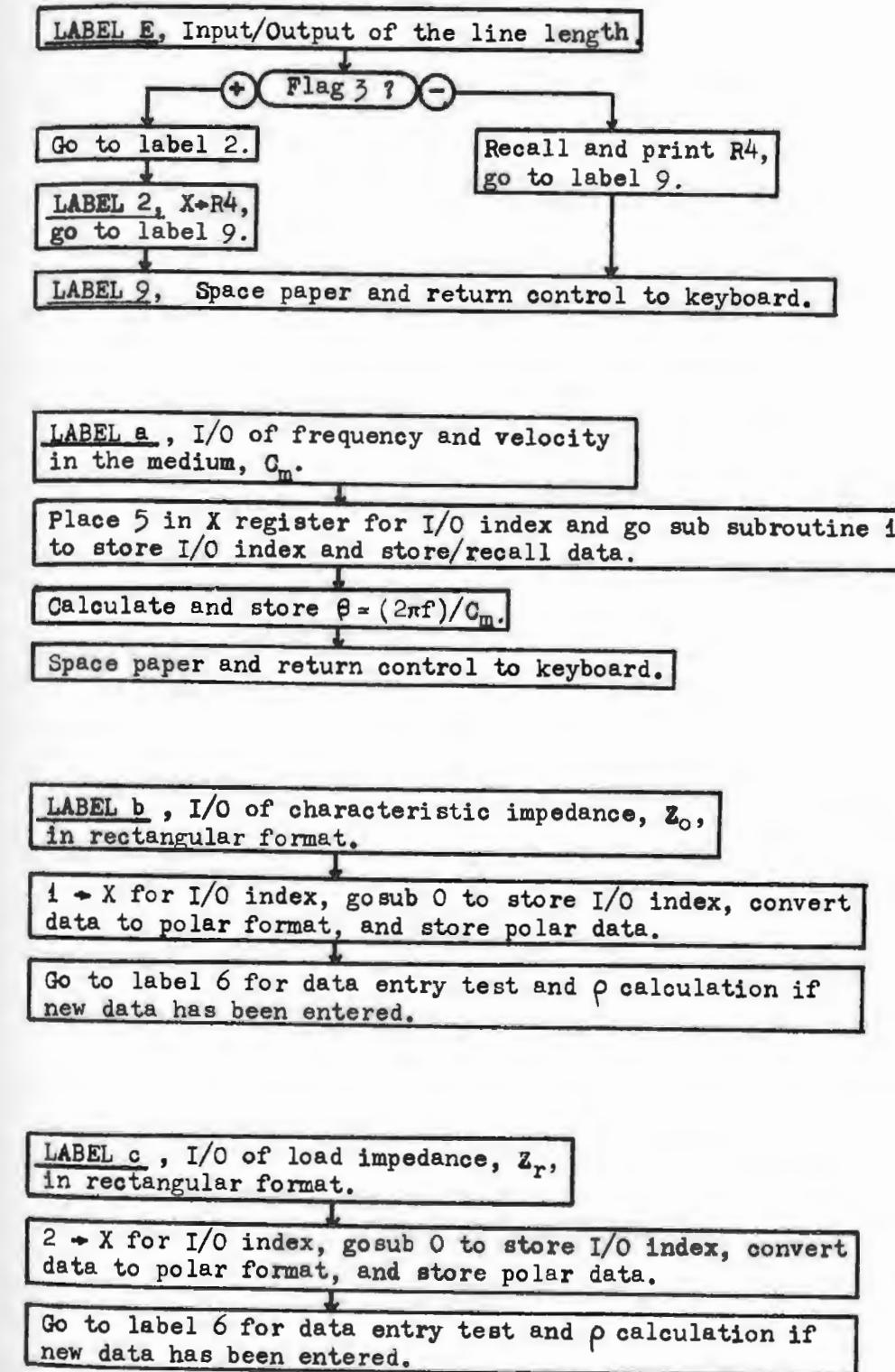

PROGRAM FLOW DIAGRAM

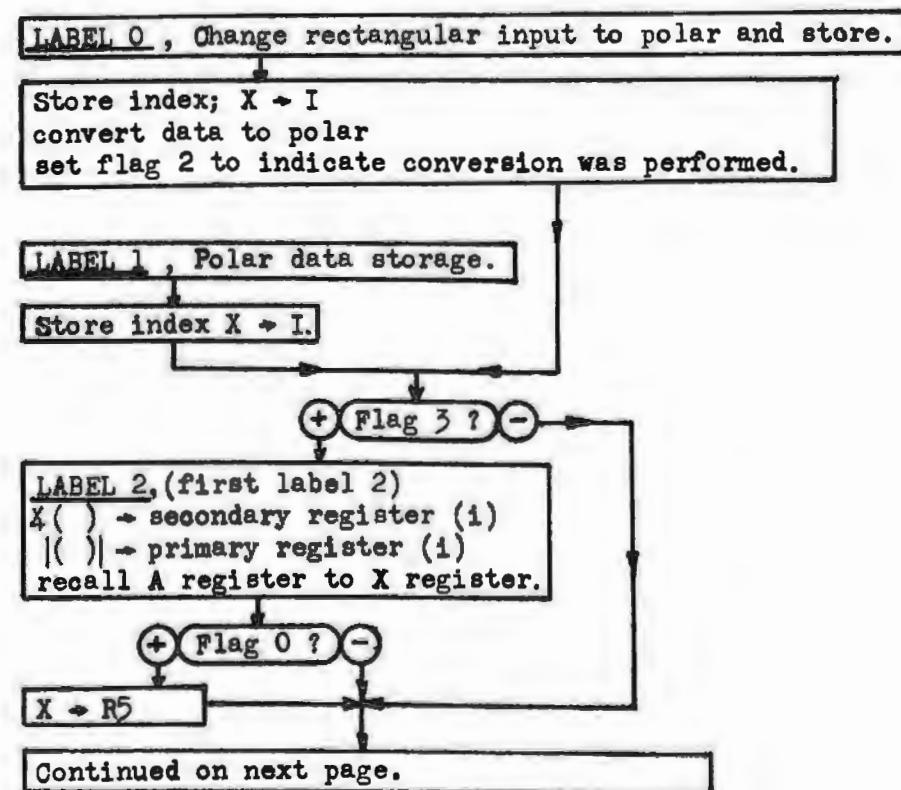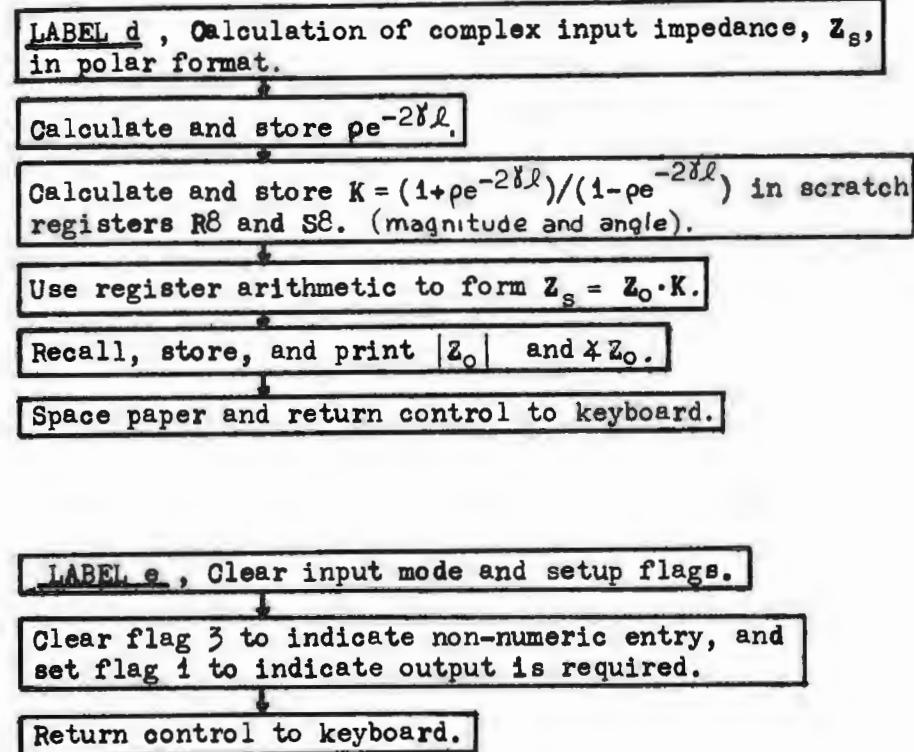

PROGRAM FLOW DIAGRAM

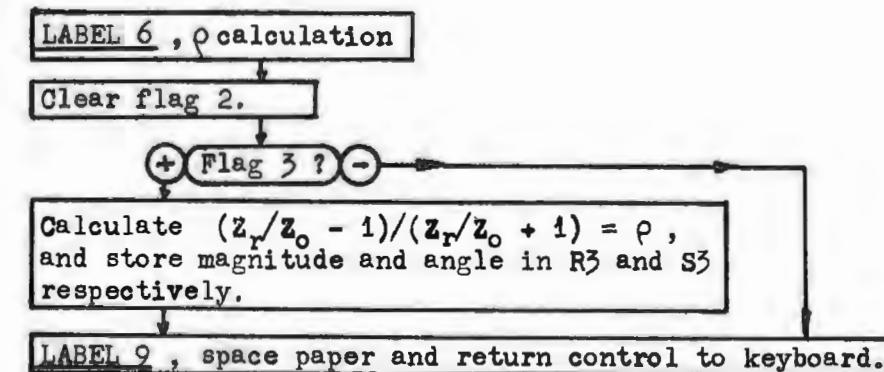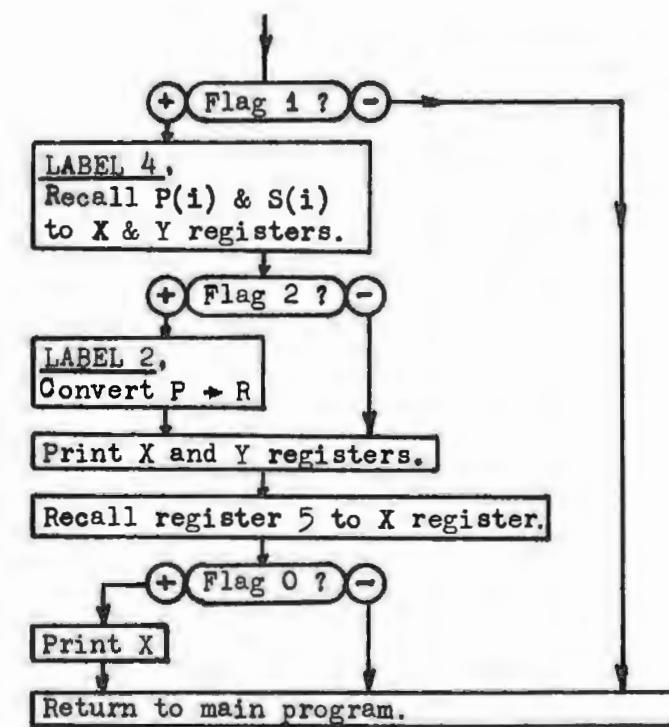

1-1 Program Listing I

001	*LBLA	I/O OF α_{dB} , β , AND FREQ	057	GSB0	IN CARTESIAN CO-ORDINATES
002	ST0A		058	GT06	
003	R↓		059	*LBLc	I/O OF $Re Z_r$, $Im Z_r$, THE
004	SF0		060	2	LOAD IMPEDANCE IN
005	CF2		061	GSB0	CARTESIAN CO-ORDINATES
006	0		062	GT06	
007	GSB1		063	*LBLd	CALCULATION OF $ Z_s $, $\angle Z_s$,
008	CF0		064	RCL3	THE COMPLEX INPUT
009	CF3		065	RCL0	IMPEDANCE
010	P↓		066	RCL4	
011	P↓		067	X	
012	+		068	EEX	
013	RCL5		069	1	
014	X		070	÷	
015	P±S		071	CHS	
016	RCL0		072	10 ^X	$e^{-2\alpha l}$
017	÷		073	X	
018	ST05		074	ST0A	$ ρ \cdot e^{-2\alpha l} = ρe^{-2\alpha l} $
019	GT07		075	P±S	
020	*LBLB	I/O OF $ Z_r $, $\angle Z_r$, THE	076	RCL3	4ρ
021	EEX	CHARACTERISTIC IMPEDANCE	077	RCL0	β , radians/length
022	GSB1	IN POLAR CO-ORDINATES	078	R+D	β , degrees/length
023	GT06		079	P±S	
024	*LBLC	I/O OF $ Z_r $, $\angle Z_r$, THE	080	RCL4	l
025	2	LOAD IMPEDANCE IN	081	X	
026	GSB1	POLAR CO-ORDINATES	082	ENT↑	
027	GT06		083	+	$2\alpha l$
028	*LBLD	I/O OF $ \rho $, $\angle \rho$, THE	084	-	$4\rho - 2\alpha l = 4(\rho e^{-2\alpha l})$
029	3	COMPLEX REFLECTION COEF	085	RCLA	
030	GSB1	IN POLAR CO-ORDINATES	086	+R	
031	CF3		087	ST0A	$Re(\rho e^{-2\alpha l})$
032	GT09		088	EEX	
033	*LBLE	I/O OF THE LINE LENGTH	089	+	$1 + Re(\rho e^{-2\alpha l})$
034	F3?		090	X±Y	
035	GT02		091	ST0B	$Im(\rho e^{-2\alpha l})$
036	RCL4		092	X±Y	
037	GT08		093	+P	
038	*LBL2		094	ST07	$ 1 + \rho e^{-2\alpha l} $
039	ST04		095	X±Y	
040	GT09		096	ST09	$4(1 + \rho e^{-2\alpha l})$
041	*LBLa	I/O OF FREQUENCY AND	097	RCLB	
042	5	VELOCITY IN THE MEDIUM, c_m	098	CHS	$Im(1 - \rho e^{-2\alpha l})$
043	GSB1		099	EEX	
044	CF3		100	RCLA	
045	RCL5		101	-	$Re(1 - \rho e^{-2\alpha l})$
046	ENT↑		102	+P	
047	+		103	ST÷7	
048	P↓		104	X±Y	
049	X		105	ST-9	
050	P±S		106	RCL1	$ Z_o $
051	RCL5		107	ST×7	
052	÷		108	P±S	
053	ST08		109	RCL1	$\angle Z_o$
054	GT07		110	P±S	
055	*LBL6	I/O OF $Re Z_o$, $Im Z_o$, THE	111	ST+9	
056	EEX	CHARACTERISTIC IMPEDANCE	112	RCL9	$\angle Z_s$

CHARACTERISTIC IMPEDANCE

α , dB/ell	$ z_0 $	$ z_r $	$ \rho $	ℓ	freq	χ^0 , scratch	$\pi z $	$ z $	$\sum z$
$S_0 \frac{rad}{\ell}$	$S_1 \chi z_0$	$S_2 \chi z_r$	$S_3 \chi \rho$	$S_4 .$	$S_5 c_m$	S_6	S_7	$S_8 \chi z$	S_9
A scratchpad	B scratchpad	C scratchpad	D	E	F	G	H	I	index

Program Listing II

113 RCL7 Z _s	168 RCL5 recall frequency
114 →R } eliminates neg magnitude	169 F0? print required ?
115 →P }	170 PRTX print frequency
116 ST08 Z _s	171 RTN
117 PRTX	172 *LBL2 convert polar data to
118 XZY	173 →R rectangular format and
119 P±S	174 PRTX print results
120 ST08 × Z _s	175 R↓
121 P±S	176 *LBL8 print and space subroutine
122 GSB8	177 PRTX
123 GT09	178 GT09 goto space subroutine
124 *LBL6 CLEAR INPUT MODE	179 *LBL6 φ calculation
125 CF3 initialize and set flags	180 CF2
126 SF1	181 F3? φ calculation needed ?
127 RTN	182 F3?
128 *LBL8 change rectangular input	183 GT09 goto space and return subr
129 ST01 to polar format	184 P±S
130 R↓	185 RCL2 × Z _r
131 XZY	186 RCL1 × Z _o
132 →P	187 - × (Z _r - Z _o)
133 XZY	188 P±S
134 SF2	189 RCL2 Z _r
135 GT02	190 RCL1 Z _o
136 *LBL1 data I/O in polar mode	191 X=0? exit if Z _o is zero
137 ST01	192 GT09
138 R↓	193 ÷ Z _r /Z _o
139 *LBL2	194 →R
140 F3? test for input	195 ST0A Re(Z _r /Z _o)
141 GSB2 goto input routine	196 EEX
142 F1? test for output	197 - Re(Z _r /Z _o - 1)
143 GSB4 goto output routine	198 XZY
144 SF1	199 ST0B Im(Z _r /Z _o - 1)
145 RTN	200 XZY
146 *LBL2 input data storage routine	201 →P
147 SF3 (data stored in polar form)	202 ST03 Z _r /Z _o - 1
148 P±S	203 XZY
149 ST01	204 ST06 × (Z _r /Z _o - 1)
150 P±S	205 RCLB Im(Z _r /Z _o)
151 R↓	206 RCLA Re(Z _r /Z _o)
152 ST01	207 EEX
153 RCLA	208 + Re(Z _r /Z _o + 1)
154 F0?	209 →P
155 ST05	210 ST÷3 ρ
156 CF1	211 XZY
157 RTN	212 ST-6 × ρ
158 *LBL4 data output routine	213 RCL6
159 P±S	214 P±S
160 RCL1	215 ST03
161 P±S	216 *LBL7 P±S & space subroutine
162 RCL1	217 P±S
163 F2? P → R required ?	218 *LBL9 space and return subr
164 GT02	219 SPC
165 PRTX	220 RTN
166 R↓	
167 PRTX	

LABELS FLAGS SET STATUS

$\frac{1}{I/O: \alpha_{dB}, \beta, f}$	$\frac{B}{I/O: 11.4 Z_0}$	$\frac{C}{I/O: 11.4 Z_r}$	$\frac{D}{I/O: 11.4 \rho}$	$\frac{E}{I/O: \text{length}}$	0	label A ?	FLAGS	TRIG	DISP
$\frac{1}{I/O: f, C_m}$	$\frac{B}{I/O: \text{ReIm} Z_0}$	$\frac{C}{I/O: \text{ReIm} Z_r}$	$\frac{D}{\text{calc. } Z_s}$	$\frac{E}{\text{clear input mode}}$	1	input or output	ON OFF	DEG ■	FIX ■
$P \rightarrow R$	$I/O \text{ index}$	local lbl	3	$^4 \text{ print in polar}$	5	cartesian data fmt	0	GRAD	SCI
5	$^6 \text{ calc } \rho$	$^7 \text{ pzs, spc, rt}$	$^8 \text{ prt, spc, rt}$	$^9 \text{ spc, rtn}$	0	data entry	1	RAD	ENG
					n_3		2		
							3		

1-1 TI-59 PROGRAM LISTING

000	76	LBL	LOAD α_{dB}
001	11	A	
002	42	STD	store and print
003	00	00	α_{dB}
004	99	PRT	
005	91	R/S	LOAD β
006	42	STD	store and print
007	10	10	β
008	99	PRT	
009	91	R/S	LOAD FREQUENCY
010	42	STD	store and print
011	05	05	frequency
012	99	PRT	
013	65	X	calculate and
014	02	2	store $2\pi f$
015	65	X	
016	89	¶	
017	95	=	
018	42	STD	
019	26	26	
020	55	÷	calculate and
021	43	RCL	store C_m
022	10	10	
023	95	=	$C_m = \frac{2\pi f}{\beta}$
024	42	STD	
025	15	15	
026	02	2	set flag 7 if
027	00	0	calculator
028	69	OP	attached to
029	07	07	printer
030	69	OP	
031	19	19	
032	25	CLR	
033	43	RCL	recall C_m and go
034	15	15	to R/S or print
035	71	SBR	routine
036	68	NOP	
037	98	ADV	
038	92	RTN	
039	76	LBL	LOAD C_m
040	16	A*	
041	42	STD	store and print
042	15	15	C_m
043	99	PRI	
044	35	1/X	calculate and
045	65	X	store β
046	43	RCL	$\beta = \frac{2\pi f}{C_m}$
047	26	26	
048	95	=	
049	42	STD	
050	10	10	
051	71	SBR	go to print or R/S
052	68	NOP	routine
053	98	ADV	
054	92	RTN	
055	76	LBL	LOAD $ Z_o $
056	12	B	
057	42	STD	store and print
058	01	01	$ Z_o $
059	99	PRI	
060	91	R/S	LOAD $\frac{1}{Z_o}$
061	42	STD	store and print
062	11	11	$\frac{1}{Z_o}$
063	99	PRT	
064	98	ADV	
065	61	GTO	goto ρ calculation
066	70	RAD	subroutine
067	76	LBL	LOAD $Re Z_o$
068	17	B*	
069	99	PRT	print and store
070	32	XIT	$Re Z_o$
071	91	R/S	LOAD $Im Z_o$
072	22	INV	convert to polar
073	37	P/R	
074	42	STD	store $\frac{1}{Z_o}$
075	11	11	
076	32	XIT	recall and store
077	42	STD	$ Z_o $
078	01	01	
079	98	ADV	go to ρ calculation
080	61	GTO	subroutine
081	70	RAD	
082	76	LBL	LOAD $ Z_r $
083	13	C	
084	42	STD	store and print
085	02	02	$ Z_r $
086	99	PRI	
087	91	R/S	LOAD $\frac{1}{Z_r}$
088	42	STD	store and print
089	12	12	$\frac{1}{Z_r}$
090	99	PRT	
091	98	ADV	
092	61	GTO	goto ρ calculation
093	70	RAD	subroutine
094	76	LBL	LOAD $Re Z_r$
095	18	C*	
096	99	PRT	store and print
097	32	XIT	$Re Z_r$
098	91	R/S	LOAD $Im Z_r$
099	99	PRT	print $Im Z_r$

NOTE: The register assignments are the same as the HP-97 program.
Read S0 as R10, and RA as R20, etc. R26 - R28 are scratchpads

1-1 TI-59 PROGRAM LISTING

100	98	ADV	
101	22	INV	convert to polar
102	37	P/R	
103	42	STD	store $\frac{1}{Z_r}$
104	12	12	
105	32	XIT	store $ Z_r $
106	42	STD	
107	02	02	
108	76	LBL	ρ calculation
109	70	RAD	
110	43	RCL	calculate & store:
111	12	12	
112	75	-	$4(Z_r - Z_o)$
113	43	RCL	
114	11	11	
115	95	-	
116	32	XIT	
117	43	RCL	calculate & store:
118	02	02	
119	55	÷	$ Z_r / Z_o $
120	43	RCL	
121	01	01	
122	95	=	
123	32	XIT	
124	37	P/R	convert to rect
125	42	STD	
126	27	27	store $Im(Z_r/Z_o)$
127	32	XIT	
128	42	STD	store $Re(Z_r/Z_o)$
129	28	28	
130	75	-	calculate & store:
131	01	1	
132	95	=	$Z_r/Z_o - 1$
133	32	XIT	
134	22	INV	convert to polar
135	37	P/R	
136	42	STD	store $4(Z_r/Z_o - 1)$
137	13	13	
138	43	RCL	recall & store:
139	27	27	$Im(Z_r/Z_o + 1)$
140	32	XIT	
141	42	STD	store $ Z_r/Z_o - 1 $
142	03	03	
143	43	RCL	
144	28	28	form $Z_r/Z_o + 1$
145	85	+	
146	01	1	
147	95	=	
148	32	XIT	
149	22	INV	convert to polar
150	37	P/R	
151	22	INV	use register
152	44	SUM	arithmetic to form:
153	13	13	$4e$
154	32	XIT	use register
155	22	INV	arithmetic to form:
156	49	PRD	$ e $
157	03	03	
158	92	RTN	rtn to main pgm
159	76	LBL	e OUTPUT ROUTINE
160	14	D	
161	43	RCL	recall $ e $
162	03	03	
163	71	SBR	goto print or R/S
164	68	NOP	
165	43	RCL	recall $4e$
166	13	13	
167	71	SBR	goto print or R/S
168	68	NOP	
169	98	ADV	space and return
170	92	RTN	
171	76	LBL	CALCULATE Z_s
172	19	D*	
173	43	RCL	form α_l in dB
174	00	00	
175	65	X	
176	43	RCL	
177	04	04	
178	55	÷	convert to nepers
179	53	(
180	01	1	
181	22	INV	
182	23	LNX	
183	28	LOG	
184	65	X	
185	01	1	
186	00	0	
187	54)	
188	95	=	
189	94	+/-	calculate:
190	22	INV	$e^{-2\alpha l}$
191	23	LNX	
192	65	X	calculate & store:
193	43	RCL	
194	03	03	$ e e^{-2\alpha l}$
195	95	=	
196	32	XIT	
197	43	RCL	recall $4e$
198	13	13	
199	75	-	

1-1 TI-59 PROGRAM LISTING

200	53	(250	01	01	use register arith
201	43	RCL	251	49	PRD	to form $ Z_r $
202	10	10	252	07	07	
203	65	x	253	43	RCL	use register arith
204	43	RCL	254	11	11	to form $\times Z_r$
205	04	04	255	44	SUM	
206	65	x	256	09	09	
207	03	3	257	43	RCL	recall $ Z_r $
208	06	6	258	07	07	
209	00	0	259	32	XIT	
210	55	÷	260	43	RCL	recall $\times Z_r$
211	89	1	261	09	09	
212	54	2	262	37	P/R	eliminate negative
213	95	=	263	22	INV	magnitude
214	37	P/R	264	37	P/R	
215	42	STO	265	42	STO	store $\times Z$
216	21	21	266	18	18	
217	32	XIT	267	32	XIT	store $ Z $
218	42	STO	268	42	STO	
219	20	20	269	08	08	
220	85	+	270	71	SBR	goto print or R/S
221	01	1	271	68	NOP	
222	95	=	272	43	RCL	recall $\times Z$
223	32	XIT	273	18	18	
224	22	INV	274	71	SBR	goto print or R/S
225	37	P/R	275	68	NOP	
226	42	STO	276	98	ADV	space & return
227	09	09	277	92	RTN	
228	32	XIT	278	76	LBL	print or R/S
229	42	STO	279	68	NOP	subroutine
230	07	07	280	87	IFF	jump if flag 7 set
231	01	1	281	07	07	
232	75	-	282	38	SIN	
233	43	RCL	283	91	R/S	stop & await start
234	20	20	284	92	RTN	return to main pgm
235	95	=	285	76	LBL	
236	32	XIT	286	38	SIN	
237	43	RCL	287	99	PRT	print
238	21	21	288	92	RTN	rtn to main program
239	94	+/-	289	76	LBL	LOAD LINE LENGTH
240	22	INV	290	15	E	
241	37	P/R	291	42	STO	store line length
242	22	INV	292	04	04	
243	44	SUM	293	99	PRT	print line length
244	09	09	294	98	ADV	
245	32	XIT	295	92	RTN	rtn to keyboard
246	22	INV				
247	49	PRD				
248	07	07				
249	43	RCL				
		recall $ Z_0 $				

PROGRAM 1-2 VOLTAGE ALONG A LOSSY LOADED TRANSMISSION LINE.

Program Description and Equations Used

This program calculates the voltage $V(x)$ in dBV, at any distance, x , along a doubly loaded transmission line (a line with terminating Y's or Z's at both ends). Both the source and load impedances are allowed to be complex quantities. This program is parasitic to Program 1-1, and that program must be run first to properly load the registers for this program. The same line length and units must be used with both programs.

Given a section of transmission line of length ℓ (Fig. 1-2.1) which may be a coax as shown, or open wire line, stripline, microstrip, or other, the input impedance, Z_s , can be expressed in terms of the load impedance, Z_r , and the cable parameters as given by Eqs. (1-1.1) and (1-1.2). With the input impedance, Z_s known, and given the transmitter source impedance, Z_t , the voltage at the input of the transmission line, V_s , is given by:

$$V_s = V_t \left[\frac{Z_s}{Z_s + Z_t} \right] \quad (1-2.1)$$

where Z_s is given by Eq. (1-1.1).

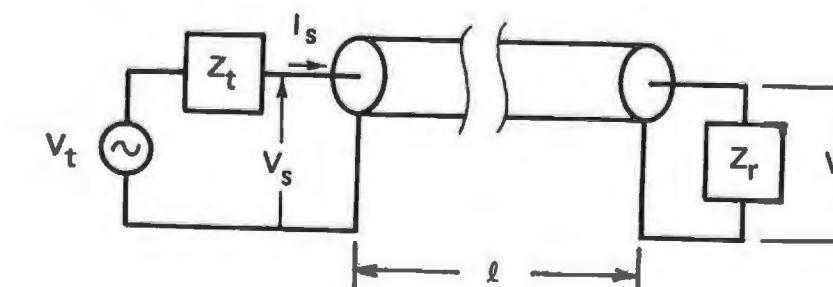


Figure 1-2.1 Transmission line circuit topology.

The voltage and current distribution of the transmission line can be written in terms of the voltage and current at any point along the transmission line as the reference. Most commonly, the voltage at the receiving end is taken as the reference, but for this problem, the voltage and current at the transmitting end are more convenient references. The voltage at any distance, x , from the transmitting end is given by Eq. (1-2.2), where the reflection coefficient at the transmitter is designated ρ_t and is defined by Eq. (1-2.3). The derivation of Eq. (1-2.2) is given later.

$$V(x) = \frac{V_s}{1 + p_t} \cdot \left[e^{-\gamma x} + p_t e^{\gamma x} \right] \quad (1-2.2)$$

$$P_t = \frac{Z_s/Z_o - 1}{Z_s/Z_o + 1} \quad (1-2.3)$$

In Eq. (1-2.2), γ is as defined in Eq. (1-1.3). With these equations in mind, the program operation is now described (Program 1-1 has already calculated and stored Z_s using Eq. (1-1.1)).


The routines under labels "A," "a," and "B" provide for data entry and storage. All impedances are stored in polar form; hence, impedances entered in cartesian form (real and imaginary) under label "a" are converted to polar form and stored using the routine under label "A," which is the polar impedance entry and storage routine. The routine under label "B" causes the source voltage strength in volts to be stored.

Label "E" is the start of the data output routine. On the first execution of label "E" after program loading and data entry, ρ_t is calculated and stored. Flag 2 is tested on each execution of label "E" to determine if the reflection coefficient calculation is needed (ρ_t). Since flag 2 is test cleared, and is only set by card loading, the ρ_t calculation is skipped after the first execution of label "E."

Following the ρ_t calculation decision, is a routine to evaluate Eq. (1-2.2) without the V_s term (lines 050 and 096 in the program listing). V_s is calculated using Eq. (1-2.1) in lines 097 through 118 and combined with the results of Eq. (1-2.2) in lines 119 to 125. The output is provided as magnitude (in dBV) of $V(x)$ and its angle.

Label 9 is a space and return subroutine used by labels "a," "A," "B," and "E."

User Instructions

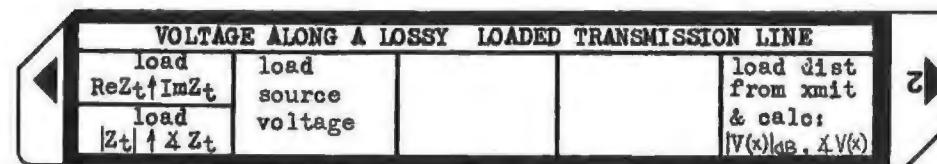

STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
	This program is to be used in conjunction with Program 1-1. Run that program first using the frequency, cable parameters, and total line length which are germane to this program			
1	Load and run Program 1-1			
2	Load both sides of Program 1-2 magnetic card			
3	Load transmitter output impedance a) If data is in cartesian coordinates: real part of impedance in ohms $\text{Re } Z_t$ imaginary part of impedance in ohms $\text{Im } Z_t$ or b) If data is in polar coordinates: magnitude of impedance in ohms $ Z_t $ angle of impedance in degrees $\angle Z_t$		<input type="button" value="ENT"/> <input type="button" value="A"/>	
4	Load source voltage of transmitter in volts V_t		<input type="button" value="B"/>	
5	Load length between transmitter and analysis point using the same units as used with Program 1-1 x		<input type="button" value="E"/>	$20 \log V(x) $ $\angle V(x)^\circ$
6	Go back to step 5 for another case			

Example 1-2.1

Given the coax cable with source and load impedances as shown in Fig. 1-2.2, find the voltages on the cable at the transmitting end, the receiving end, and 1 n-mi. from the transmitting end.

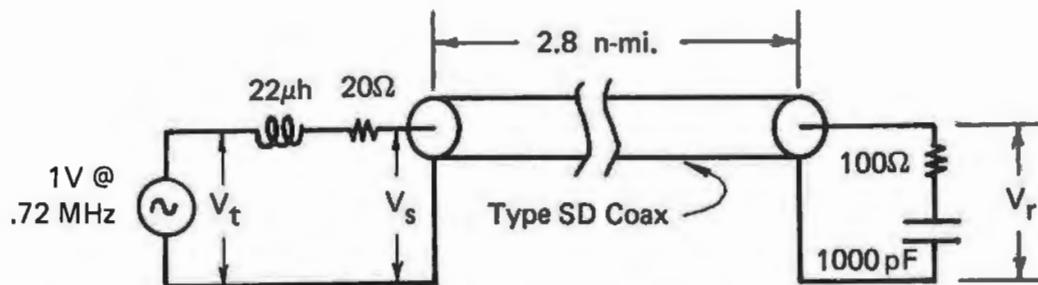


Figure 1-2.2 Doubly loaded coaxial cable for Ex. 1-2.1.

At 0.72 MHz, the characteristics of the SD coax cable are:

$$\begin{aligned}\alpha_{dB} &= 2.070 \text{ dB/n-mi.} \\ \beta &= 42.511 \text{ radians/n-mi.} \\ Z_0 &= 44.265 \Omega @ -0.315 \text{ degree}\end{aligned}$$

At the same frequency, the complex source and load impedances are:

$$\begin{aligned}Re Z_t &= 20 \text{ ohms} \\ Im Z_t &= j2\pi fL = j99.53 \text{ ohms} \\ Re Z_r &= 100 \text{ ohms} \\ Im Z_r &= -j/(2\pi fC) = -j221 \text{ ohms}\end{aligned}$$

Since this program is parasitic to Program 1-1, that program is run first with the line length required here (2.8 n-mi.). The printout from that program is included here for clarity.

HP-97 printout for Example 1-2.1

First, Program 1-1 is run to calculate and store Z_s and to load the registers.

```

2.070 ENT† load αdB in dB/n-mi.
42.511 ENT† load β in radians/n-mi.
.72+0j GSBA load frequency in hertz

44.265 ENT† load |Z0| in ohms
-.315 GSBB load ∠Z0 in degrees

100.000 ENT† load Re Zt in ohms
-221.000 GSBe load Im Zr in ohms

2.800 GSBE load line length in nautical miles

GSBd calculate Zs (will be automatically stored)
67.827 *** |Zs|, ohms
9.476 *** ∠Zs, degrees

```

Second, load and run this program.

```

20.00 ENT† load Re Zt
99.53 GSBe load Im Zt

1.00 GSBB load source voltage in volts

0.00 GSBE load line length to transmitting end and start
-6.54 *** 20 log |Vs|, dBV
-42.39 *** ∠Vs, degrees

2.80 GSBE load line length to receiving end and start
-0.54 *** 20 log |Vr|, dBV
-34.98 *** ∠Vr, degrees

1.00 GSBE load line length to 1 n-mi. from xmit end and start
-12.95 *** 20 log |V(x)|, dBV
22.15 *** ∠V(x), degrees

```

Derivation of Equations Used

A transmission line provides a conduit for the propagation of electrical power. If the transmission line is not terminated in the characteristic impedance of the line, Z_0 , then not all of the power that propagates down the line is absorbed in the termination, and thus some is reflected into the line and propagates back to the source. The "reflection coefficient," ρ , is a measure of the amount of power that is reflected. A reflection coefficient of zero ($\rho = 0$) implies no power is reflected, and all of it is absorbed by the load. When $\rho = \pm 1$, all the power is reflected. The reflection coefficient in terms of the characteristic impedance (Z_0) and the load impedance (Z_r) is given by Eq. (1-1.2).

If the transmission line is doubly terminated, then there will be a reflection coefficient for both ends, and Eq. (1-1.2) is used with Z_r replaced by Z_s , the cable input impedance at the transmitter end. This is the transmitter reflection coefficient and is designated ρ_t . The receiver reflection coefficient is left unsubscripted.

The power propagates along the transmission line as a voltage wave and a current wave. Considering both the voltage wave from the transmitter directly, and the reflected wave from the receiver, there exist points along the cable where these waves are in phase, and constructively add together; while there are other points where the waves are 180° out of phase and produce a voltage null.

Reference [43] (chapters 8 and 9) contains the solution to the wave equation for voltage and current waves traveling along a transmission line. The voltage and current along the transmission line can conveniently be expressed in terms of hyperbolic functions and a reference voltage and current taken at any point on the line. If x represents the distance from the transmitter (or source) to the point under observation, then the voltage and current ($V(x)$ and $I(x)$) at this point are:

$$\begin{bmatrix} V(x) \\ I(x) \end{bmatrix} = \begin{bmatrix} \{\cosh(\gamma x)\} & \{-Z_0 \sinh(\gamma x)\} \\ \{\frac{-1}{Z_0} \sinh(\gamma x)\} & \{\cosh(\gamma x)\} \end{bmatrix} \cdot \begin{bmatrix} V_s \\ I_s \end{bmatrix} \quad (1-2.4)$$

where the hyperbolic functions are defined by:

$$\text{Sinh } (\gamma x) = \frac{e^{\gamma x} - e^{-\gamma x}}{2} \quad (1-2.5)$$

$$\text{Cosh } (\gamma x) = \frac{e^{\gamma x} + e^{-\gamma x}}{2} \quad (1-2.6)$$

Remembering that $I_s = V_s/Z_s$, and using the transmitter reflection coefficient defined by:

$$\rho_t = \frac{Z_s/Z_0 - 1}{Z_s/Z_0 + 1} \quad (1-2.3)$$

Equation (1-2.4) may be solved for $V(x)$ yielding:

$$V(x) = \frac{V_s}{1 + \rho_t} \cdot \left[e^{-\gamma x} + \rho_t e^{\gamma x} \right] \quad (1-2.2)$$

Program Listing I

001	*LBL0	LOAD transmitter output Z
002	X#Y	in cartesian coordinates
003	+P	
004	X#Y	
005	*LBLA	LOAD transmitter output Z
006	P#S	in polar coordinates
007	ST07	
008	X#Y	
009	ST06	
010	P#S	
011	GT09	goto space and return subr
012	*LBLB	LOAD source voltage in volts
013	P#S	
014	ST09	
015	P#S	
016	GT09	goto space and return subr
017	*LBLE	LOAD distance, x, from
018	ST04	xmit and calculate $V(x)$
019	F2?	calculate ρ_t on the first
020	F2?	execution of label E
021	GT01	goto $V(x)$ calculation
022	P#S	ρ_t calculation routine
023	RCL8	Z_s
024	RCL1	Z_o
025	P#S	
026	-	
027	RCL8	$ Z_s $
028	RCL1	$ Z_o $
029	-	
030	+R	
031	STOA	$Re(Z_s/Z_o)$
032	EEX	
033	-	$Re(Z_s/Z_o - 1)$
034	X#Y	
035	STOB	$Im(Z_s/Z_o) = Im(Z_s/Z_o - 1)$
036	X#Y	
037	+P	
038	ST03	$ Z_s/Z_o - 1 $
039	X#Y	
040	ST06	$\Delta(Z_s/Z_o - 1)$
041	RCLB	$Im(Z_s/Z_o) = Im(Z_s/Z_o + 1)$
042	RCLA	$Re(Z_s/Z_o)$
043	EEX	
044	+	$Re(Z_s/Z_o + 1)$
045	+P	
046	ST-3	$ \rho_t $
047	X#Y	
048	ST-6	$\Delta \rho_t$
049	*LBL1	$V(x)$ calculation routine
050	RCL4	ℓ
051	RCL0	α_{dB}
052	X	
053	2	
054	0	
055	÷	$\alpha \ell / \ln 10$, nepers

REGISTERS

0	α_{dB}	1	$ Z_0 $	2	$ Z_r $	3	$ P_t $	4	ℓ	5	freq	6	$\lambda_p t$	7	scratch	8	$ Z_s $	9	scratch
S0	β	S1	$\frac{1}{4} Z_0$	S2	$\frac{1}{4} Z_r$	S3	$\frac{1}{4} \rho$	S4		S5	ω_m	S6	$ Z_t $	S7	$\frac{1}{4} Z_t$	S8	$\frac{1}{4} Z_s$	S9	V_t
A	scratchpad	B	scratchpad	C	scratchpad	D	20log e	E		F		G		H		I	index		

Program Listing II

NOTE FLAG SET STATUS

```

111      →R
112 RCLA
113      +
114 X#Y   Re(Zs + Zt)
115 RCLB
116      +
117 X#Y   Im(Zs + Zt)
118      →P
119 ST÷7  |Zs + Zt|
120 X#Y
121 ST-9  √(Zs + Zt)
122 P#S
123 RCL9  Vt
124 P#S
125 ST×7  complete |V(x)| calculation
126 RCL7
127 LOG
128      2
129      0
130      X
131 PRTX  20 log V(x)
132 RCL9
133 PRTX  √ V(x)
134 *LBL9  space and return subroutine
135 SPC
136 RTN

```

NOTE FLAG SET STATUS

LABELS					FLAGS		SET STATUS		
A	B source voltage	C	D	E calc V(x)	0		FLAGS	TRIG	DISP
$ Z_t \uparrow Z_t$	b	c	d	e	1		ON OFF	DEG ■	FIX ■
a $ReZ_t \uparrow ImZ_t$	b	c	d	e	1		0	GRAD	SCI
0	1 ρ calc jump	2	3	4	2 ρ calc ?		1	RAD	ENG
5	6	7	8	9 spc & rtn	3		2		n 2

PROGRAM 1-3 SECOND ORDER ACTIVE NETWORK TRANSMISSION FUNCTION.

Program Description and Equations Used

This program provides the coefficients of the numerator and denominator polynomials of the transmission function $T(s) = N(s)/D(s)$, of the generalized second order active network shown in Fig. 1-3.1. A second part of the program provides the polynomial roots. If a real (non-ideal) operational amplifier (op-amp) is used, the amplifier will have both finite gain and bandwidth. The compensation pole of the op-amp will introduce a parasitic pole causing $D(s)$ to become third order even though the RC network is set up to provide second order response. This program accepts the gain and 3 dB bandwidth of the amplifier and calculates the resulting third order transmission function.

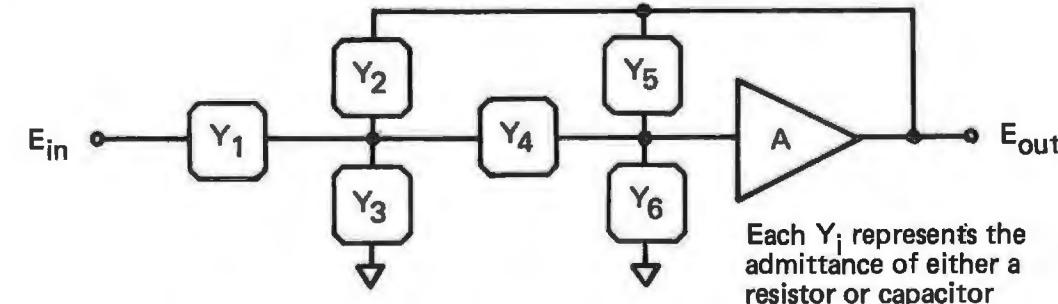


Figure 1-3.1 Generalized second order circuit.

If the natural frequencies of the response governed by the RC network alone are many decades removed from the amplifier unity gain crossover frequency, then the transmission function $T(s)$, will be practically equal to the transmission function of the second order network with an ideal infinite bandwidth amplifier. The component values dictated by many active filter references assume ideal operational amplifier characteristics.

When the natural frequencies are within a decade or two of the amplifier unity gain crossover frequency, then the parasitic pole will cause a noticeable shift in the natural frequencies governed by the RC network alone. The network can be predistorted so the natural frequencies shift to the desired positions (see Program 2-11).

The transmission function is determined by writing the nodal equations for the network, and solving for E_{out} in terms of E_{in} . This derivation is done later and provides:

$$E_{out} = \frac{A_0 Y_1 Y_4}{D(s)} \quad (1-3.1)$$

where

$$D(s) = (Y_1 + Y_2 + Y_3) [(Y_4 + Y_6)(1 + \tau s) + Y_5 (1 - A_0 + \tau s)] + \\ Y_4 [Y_6 + (1 + \tau s) + Y_5 (1 - A_0 + \tau s) - A_0 Y_2]$$

and where a one-pole model of the amplifier is assumed:

$$A = \frac{A_0}{1 + \tau s} \quad (1-3.2)$$

The sign of A_0 may be either positive or negative depending upon the amplifier characteristics (see examples). The first program uses Eq. (1-3.1) to form the numerator and denominator polynomials, and the second program finds the zeros of these polynomials (polynomial roots).

When the element values are loaded, capacitors are signified by a negative mantissa. The subroutine under label 8 tests the sign of the entry; if it is negative, the absolute value is stored; if it is positive, it is a resistor, and the reciprocal is taken to convert to conductance, and then multiplied by 10^{50} before storage.

The magnitude of the stored element value is used to signal whether the element is a resistor or a capacitor. Other programs use the sign of the stored value to differentiate between resistors and capacitors, but that indicator cannot be used in this program because algebraic operations are performed on the element values in the main program before the element type subroutine is entered and the resistor/capacitor test is done, i.e., the term $Y_5(1 - A_0)$ can have either sign depending upon the magnitude and sign of A_0 , and Y_5 can legitimately represent the admittance of either a resistor or a capacitor.

The magnitude test is done in the summing routine under label 0.

If the absolute value of the coefficient is greater than 10^{30} , it is assumed to be a conductance (s^0 term), the value is divided by 10^{50} to undo the original storage operation, and the summation is done in the stack. If the absolute value of the coefficient is less than 10^{30} , it is assumed to be a capacitance (s^1 term), and the summation is done in the designated i register.

Some terms in the denominator of Eq. (1-3.1) contain the factor τs . These terms generate s^1 and s^2 coefficients. Subroutine 3 is used to perform multiplication by τs and to append the s^1 and s^2 terms to the presently stored s^0 and s^1 terms to form the complete admittance sum set for the denominator segment being evaluated.

After each set of admittance sums (s^0 , s^1 , & s^2) are calculated and stored, polynomial multiplication is done to generate the coefficients of the various powers of s in the denominator polynomial. This multiplication is accomplished by the routine under label 6. If flag 0 is set, the polynomial coefficient registers are cleared before multiplication. This condition exists for the first product-of-sums. Flag 0 is cleared for the second product-of-sums to indicate continued summation into the polynomial coefficient registers.

After the denominator has been calculated, the polynomial coefficients are normalized by dividing by the s^0 polynomial coefficient. The numerator coefficient is likewise normalized, and the polynomial coefficients are provided as output. This normalization process can cause the program to halt displaying "ERROR" for certain classes of degenerate networks, e.g., a differentiator constructed with capacitors in locations 1 and 4, no elements in locations 2, 3, and 6, and feedback resistor in location 5. The series capacitors should be combined into a single capacitor in location 1 or 4 with the feedback resistor in location 2 or 5 and no elements in locations 3 and 6. The unspecified series elements can be 1 ohm resistors.

The second program finds the zeros of the denominator polynomial (poles of the transmission function). The numerator polynomial will be either a constant, a single zero at the origin, or a double zero at the origin depending on whether the filter is lowpass, bandpass, or highpass, respectively. The second program also indicates the degree of the zero, and the gain constant of the second order pair, K , after the third order root has been removed (if any), i.e.:


Lowpass: $T(s) = K \frac{1}{\frac{s^2}{\omega_n^2} + \frac{s}{\omega_n Q} + 1}$ (1-3.3)

Bandpass: $T(s) = K \frac{\frac{s}{\omega_n Q}}{\frac{s^2}{\omega_n^2} + \frac{s}{\omega_n Q} + 1}$ (1-3.4)

Highpass: $T(s) = K \frac{\frac{s^2}{\omega_n^2}}{\frac{s^2}{\omega_n^2} + \frac{s}{\omega_n Q} + 1}$ (1-3.5)

If the denominator polynomial is second order, the quadratic formula is used to find the zeros. If it is third order, a Newton-Raphson iterative technique is used to find the real third order zero (there will be at least one), then the third order polynomial is deflated to second order, and the quadratic formula is used to find the remaining zeros of the polynomial. If the zeros of the denominator polynomial are complex, the program will also calculate the natural frequency, $f_n = \omega_n / 2\pi$, and the Q, or quality factor of the complex pair (see the equation derivation part of this description for equations and details).

1-3 User Instructions

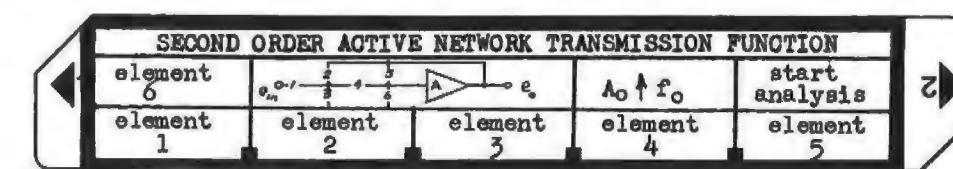

STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
1	Load both sides of program card			
2	Enter element 1 a) if resistor (value ≠ 0) b) if capacitor, enter negative value	R, ohms C, farad	A chs A	
3	Enter element 2 a) if resistor b) if capacitor c) if no element present	R, ohms C, farad zero	B chs B B	
4	Enter element 3 a) if resistor b) if capacitor c) if no element present	R, ohms C, farad zero	C chs C C	
5	Enter element 4 a) if resistor (value ≠ 0) b) if capacitor	R, ohms C, farad	D chs D	
6	Enter element 5 a) if resistor b) if capacitor c) if no element present	R, ohms C, farad zero	E chs E E	
7	Enter element 6 a) if resistor b) if capacitor c) if no element present	R, ohms C, farad zero	f A chs f A f A	
8	Enter operational amplifier parameters	A_o f_o , Hz	↑ f D	
9	Start analysis		f E	Den coeffs Num coeffs
10	Go back and change any element then rerun step 9, or load second card to find denominator pole locations, f_n , and Q			


User Instructions



STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
1	Load both sides of program card when display flashes, program execution begins unaided			
2	Program output			
2a	If three real roots, $(s+a)(s+b)(s+c)$			-a -b -c
2b	If one real root and a complex conjugate pair, $(s+a)(s+\alpha+j\beta)(s+\alpha-j\beta)$			-a β $-\alpha$ -B $-\alpha$ f _n (Hz) Q midband gain num zero locations
2c	If two real roots: $(s+a)(s+b)$			-a -b
2c	A complex conjugate pair, $(s+\alpha+j\beta)(s+\alpha-j\beta)$			β $-\alpha$ -B $-\alpha$ f _n (Hz) Q midband gain num zero locations

User Instructions


TI-59 TRANSLATION

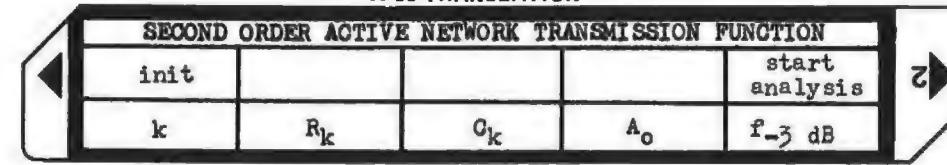

STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
1	Load both sides of program card one			
2	Initialize and clear registers		2nd [A]	0
3	Load elements			
	a) load element number (1 to 6)	k	A	k
	b) load element values:			
	if resistor	R _k , ohms	B	R _k
	if capacitor	C _k , F	C	C _k
	if no element present	0	C	0
	Repeat step 3 until all elements have been entered.			
4	Load amplifier dc gain (load negative gain for inverting op-amp)	A _o	D	A _o
5	Load -3 dB rolloff frequency of amplifier	f ₋₃ dB, Hz	E	f ₋₃ dB
6	Start analysis		2nd E	den coeffs
			R/S*	b ₃
			R/S*	b ₂
			R/S*	b ₁
			R/S*	1
				num coeffs
			R/S*	a ₂
			R/S*	a ₁
			R/S*	a ₀
	* "R/S" not necessary if the TI-59 is attached to the PC-100A printer. All results will be printed automatically after the program is started.			

User Instructions

TI-59 TRANSLATION

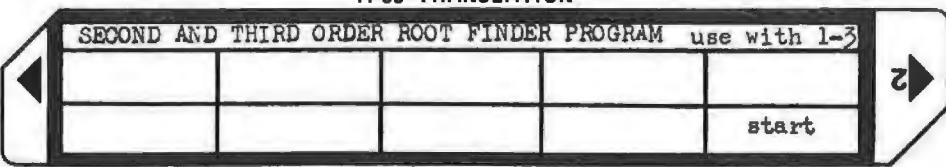

STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
7	Load both sides of program card 2			
8	Start second program		E	
a)	If three real roots: $(s+a)(s+b)(s+c)$		R/S*	-a -b -c
b)	If one real root and a complex conjugate pair: $(s+a)(s+\alpha+j\beta)(s+\alpha-j\beta)$		R/S*	-a
			R/S*	β
			R/S*	$-\alpha$
			R/S*	$-\beta$
			R/S*	$-\alpha$
			R/S*	$f_n, \text{ Hz}$
			R/S*	Q
			R/S*	midband gain
c)	If two real roots: $(s+a)(s+b)$		R/S*	-a
			R/S*	-b
d)	If a complex conjugate pair: $(s+\alpha+j\beta)(s+\alpha-j\beta)$		R/S*	β
			R/S*	$-\alpha$
			R/S*	$-\beta$
			R/S*	$-\alpha$
			R/S*	$f_n, \text{ Hz}$
			R/S*	Q
			R/S*	midband gain
*	"R/S" not necessary if the TI-59 is attached to the PC-100A printer. All results will be automatically printed after the program is started.			

Example 1-3.1

The schematic in Fig. 1-3.2 represents a second order active band-pass filter using the infinite gain, multiple feedback topology. The filter element values were designed assuming the op-amp to be ideal, i.e., having infinite gain and bandwidth. The type 741 op-amp is not ideal in that it has both finite gain and bandwidth. This example will use the program to show that the element values provide the desired specification when the op-amp has very large gain (-10^9) and infinite bandwidth ($\tau = 0$). The program will then be run with the gain and bandwidth values for the 741 type op-amp to show that both the pole natural frequency and "Q" have shifted away from the desired values. The 741 has a typical gain of -100,000, and open loop break frequency of 5 Hz.

The design specifications for the filter are:

center frequency: 10 kHz
midband gain: 10
quality factor, Q: 10
capacitor value: 1000 pF

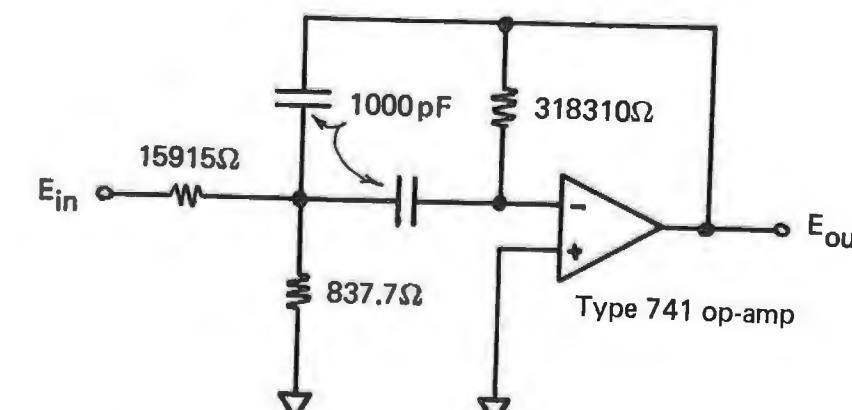


Figure 1-3.2 Second order bandpass active filter, infinite gain-multiple feedback topology.

HP-97 PRINTOUT FOR EXAMPLE 1-3.1

load first program and enter element values	
15915. GSBA element 1, resistor -1.-09 GSBB element 2, cap 837.7 GSBC element 3, resistor -1.-09 GSBD element 4, cap 318310. GSBE element 5, resistor 0. GSBo element 6, missing	
reload first card	
-1.09 ST06 enter infinite gain app 0. ST07 set T to zero (BW=∞)	
GSBe start analysis	
0.000+00 *** s ³ denominator coef 253.3-12 *** s ² " 1.592-06 *** s ¹ " 1.000+00 *** s ⁰ "	
0.000+00 *** s ² numerator coef -15.92-06 *** s ¹ " 0.000+00 *** s ⁰ "	
load second card & start analysis	
-4.400+06 *** real pole location	
62.75+03 *** imag } -3.142+03 *** real } complex conjugate poles -62.75+03 *** imag } -3.142+03 *** real }	
10.00+03 *** f _n } of second order pole pair 10.00+00 *** Q } of second order pole pair	
-10.00+00 *** midband gain	
0.000+00 *** numerator zero location	

TI-59 PRINTOUT FOR EXAMPLE 1-3.1

load first program and enter element values	
1. 15915. R element # resistor	
2. 1. -09 C element # capacitor	
3. 837.7 R element # resistor	
4. 1. -09 C element # capacitor	
5. 318310. R element # resistor	reload first card
-1. 09 A amplifier gain (ideal)	-100. 00 A 741 dc gain
1. 25 F amplifier BW (ideal)	5. 00 F 741 break freq
0.00 00 s ³ den coef	80.63-18 s ³ den coef
253.31-12 s ² "	355.14-12 s ² "
1.59-06 s ¹ "	1.91-06 s ¹ "
1.00 00 s ⁰ "	1.00 00 s ⁰ "
0.00 00 s ² num coef	0.00 00 s ² num coef
-15.92-06 s ¹ "	-15.92-06 s ¹ "
0.00 00 s ⁰ "	0.00 00 s ⁰ "
load second card	
-4.3997 06 real pole location	
62.75 03 imag } -3.14 03 real } complex conj. pole pair	53.03 03 -2.3760 03
-62.75 03 imag } -3.14 03 real }	-53.03 03 -2.3760 03
10.00 03 f _n	8.4499 03 11.17 00
10.00 00 Q	f _n
-10.00 00 midband gain	-9.4414 00 midband gain

Example 1-3.2

Figure 1-3.3 is the schematic of a second order highpass filter using the Sallen and Key controlled source topology. An operational amplifier is connected in the voltage follower configuration to provide the unity gain non-inverting buffer amplifier required. The design procedure assumes infinite bandwidth in this buffer, but physical op-amps, such as the 741 type have finite bandwidth (BW). This example will show how this finite bandwidth affects the filter performance. The design specifications are:

natural frequency, f_o :	10000 Hz
quality factor, Q:	$1/\sqrt{2} = 0.707$
capacitor value, C_1, C_4 :	1 nF
asymptotic high frequency gain:	unity

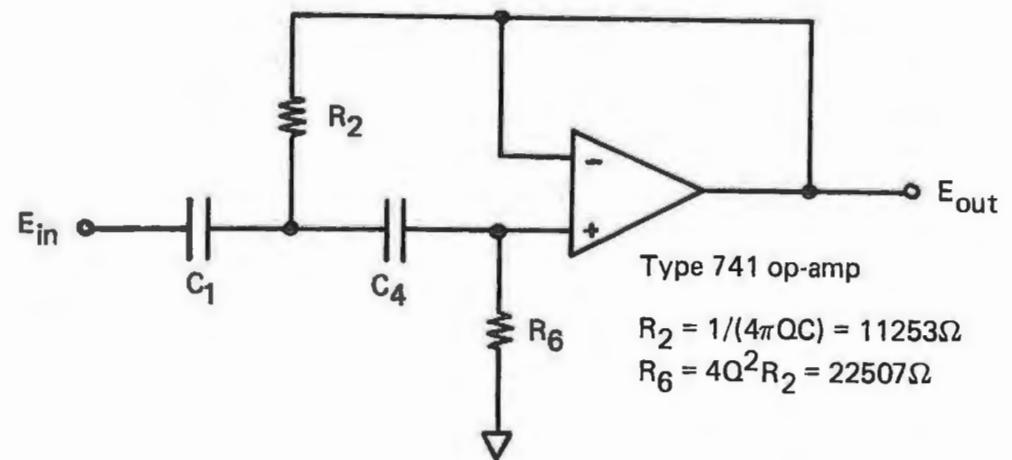


Figure 1-3.3 Sallen and Key type second order highpass filter.

The HP-97 printout is shown on the next page. Again, two runs were made; first the amplifier was assumed to be ideal, and the program output verifies the design specifications; second, the finite gain and bandwidth characteristics of the 741 operational amplifier were used. The program output for the second case shows the non-ideal (finite) characteristics of the 741 have caused the second order pole positions to shift away from the desired positions, and a real pole has also been introduced.

HP-97 PRINTOUT FOR EXAMPLE 1-3.2

load first program and enter element values	
-1.-09 GSBA element 1, capacitor 11253. GSBB element 2, resistor 0. GSBC element 3, missing -1.-09 GSBD element 4, capacitor 0. GSBE element 5, missing 22507. GSBo element 6, resistor	
 1. ST00 set $A_o = 1$ 0. ST07 set $\tau = \infty$ (BW = ∞)	
 GSBe start analysis 0.000+00 *** s^3 253.3-12 *** s^2 22.51-06 *** s^1 1.000+00 *** s^0	
 253.3-12 *** s^2 0.000+00 *** s^1 0.000+00 *** s^0	
 load second card & start analysis	
 -3.233+06 *** real pole location	
 44.43+03 *** imag -44.43+03 *** real } { complex conjugate poles	
 -44.43+03 *** imag } { complex conjugate poles -44.43+03 *** real } { of second order pole pair	
 10.00+03 *** f_n } { of second order pole pair 707.1-03 *** Q } { of second order pole pair	
 1.000+00 *** asymptotic gain	
 0.000+00 *** numerator zero locations	
 0.000+00 *** numerator zero locations	
 Reload first card and enter op-amp parameters	
 1. ENT1 gain 500000. GSBD bandwidth } type 741	
 GSBe start analysis 80.62-18 *** s^3 denominator coef 267.6-12 *** s^2 " " 22.82-06 *** s^1 " " 1.000+00 *** s^0 " "	
 253.3-12 *** s^2 numerator coef 0.000+00 *** s^1 " " 0.000+00 *** s^0 " "	
 load second card & start analysis	
 -3.233+06 *** real pole location	
 44.40+03 *** imag -43.19+03 *** real } { complex conjugate poles	
 -44.40+03 *** imag } { complex conjugate poles -43.19+03 *** real } { of second order pole pair	
 9.858+03 *** f_n } { of second order pole pair 717.0-03 *** Q } { of second order pole pair	
 971.7-03 *** asymptotic gain	
 0.000+00 *** numerator zero locations	
 0.000+00 *** numerator zero locations	

TI-59 PRINTOUT FOR EXAMPLE 1-3.2

load first program and enter element values	
1. -09 C element # capacitor	
2. 11253. R element # resistor	
4. 1. -09 C element # capacitor	
6. 22507. R element # resistor	
 1. A amplifier gain (ideal) 1. 00 A 741 gain	
 1. 25 F amplifier BW (ideal) 500. 03 F 741 BW	
 0.00 00 s^3 den coef 80.62-18 s^3 den coef	
253.27-12 s^2 " " 267.60-12 s^2 " "	
22.51-06 s^1 " " 22.82-06 s^1 " "	
1.00 00 s^0 " " 1.00 00 s^0 " "	
 253.27-12 s^2 num coef 253.27-12 s^2 num coef	
0.00 00 s^1 " " 0.00 00 s^1 " "	
0.00 00 s^0 " " 0.00 00 s^0 " "	
 load second card -3.23 06 real pole location	
 44.43 03 imag 44.40 03 imag	
-44.43 03 real } { complex conj. 43.19 03 real } { complex conj.	
 -44.43 03 imag pole pair 44.40 03 imag pole pair	
-44.43 03 real } { of second order pole pair 43.19 03 real } { of second order pole pair	
 10.00 03 f_n } { of second order pole pair 9.86 03 f_n } { of second order pole pair	
707.12-03 Q } { pole pair 717.04-03 Q } { pole pair	
 1.00 00 asymptotic gain 971.75-03 asymptotic gain	

Derivation of Equations and Algorithms Used

Active network transfer function: The schematic of the generalized second order active network is shown in Fig. 1-3.1. Let the junction of Y_1 , Y_2 , Y_3 , and Y_4 be designated node 1. Furthermore, let the junction of Y_4 , Y_5 , and Y_6 be designated as node 2. The nodal equations for this circuit may be written in matrix form in terms of the voltages at node 1 (E_1), and at node 2 (E_2):

$$\begin{bmatrix} \{Y_1 + Y_2 + Y_3 + Y_4\} & \{-Y_4\} \\ \{-Y_4\} & \{Y_4 + Y_5 + Y_6\} \end{bmatrix} \cdot \begin{bmatrix} E_1 \\ E_2 \end{bmatrix} = \begin{bmatrix} Y_1 & Y_2 \\ 0 & Y_5 \end{bmatrix} \cdot \begin{bmatrix} E_{in} \\ E_{out} \end{bmatrix} \quad (1-3.6)$$

Since $E_2 = E_{out}/A$, this expression is substituted into Eq. (1-3.6), and the dependent variables brought to the left hand side.

$$\begin{bmatrix} \{Y_1 + Y_2 + Y_3 + Y_4\} & \left\{ \frac{Y_4}{A} - Y_2 \right\} \\ \{-Y_4\} & \left\{ \frac{Y_4 + Y_5 + Y_6}{A} - Y_5 \right\} \end{bmatrix} \cdot \begin{bmatrix} E_1 \\ E_{out} \end{bmatrix} = \begin{bmatrix} Y_1 \\ 0 \end{bmatrix} \quad (E_{in}) \quad (1-3.7)$$

$T(s) = E_{out}/E_{in}$ may be obtained from Eq. (1-3.7) using Cramer's rule. To this end, the determinant of the coefficient matrix (Δ) is needed:

$$\Delta = (Y_1 + Y_2 + Y_3 + Y_4) \cdot \left[\frac{Y_4 + Y_5 + Y_6}{A} - Y_5 \right] - Y_4 \left[\frac{Y_4}{A} - Y_2 \right] \quad (1-3.8)$$

After clearing fractions and eliminating term subtraction,

$$A \cdot \Delta = (Y_1 + Y_2 + Y_3)[Y_4 + Y_6 + Y_5(1 - A)] + Y_4 [Y_5(1 - A) - AY_2 + Y_6] \quad (1-3.9)$$

Substituting $A = A_0/(1 + \tau s)$ as the amplifier gain, and clearing fractions, Eq. (1-3.9) becomes:

$$A_0 \cdot \Delta = (Y_1 + Y_2 + Y_3)[(Y_4 + Y_5)(1 + \tau s) + Y_5(1 - A_0 + \tau s)] + Y_4 [Y_6(1 + \tau s) + Y_5(1 - A_0 + \tau s) - A_0 \cdot Y_2] \quad (1-3.10)$$

Using Cramer's rule, the transmission function becomes:

$$T(s) = E_{out}/E_{in} = (Y_1 \cdot Y_4)/\Delta \quad (1-3.11)$$

Newton-Raphson solution for finding real zeros of third order polynomials:

The Newton-Raphson solution is an iterative procedure for finding the values of x where $f(x)$ becomes zero, hence, these values of x are called the zeros of $f(x)$. If the mathematical operations are restricted to real numbers, then the procedure will only find the real zeros of the function, $f(x)$. All odd ordered polynomials with real coefficients have at least one real zero. The third order polynomial generated by this program falls into this class, therefore real arithmetic is used to extract the real zero.

Given the function $f(x) = 0$, the Newton-Raphson solution provides a new estimate, x_{i+1} , based on the present estimate, x_i , and the tangent to $f(x_i)$. The value of x_{i+1} is determined by calculating the intercept of the tangent, $f'(x_i)$ on the x axis as shown in Fig. 1-3.2.

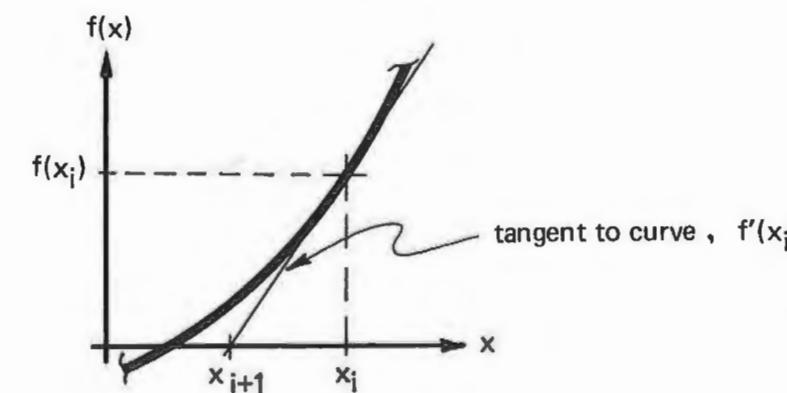


Figure 1-3.2 Newton-Raphson solution method.

$$f'(x_i) = \Delta f(x_i)/\Delta x_i = (f(x_i) - 0)/(x_i - x_{i+1})$$

Solving for x_{i+1} :

$$x_{i+1} = x_i - f(x_i)/f'(x_i)$$

The iteration is stopped when the absolute value of the correction term, $f(x_i)/f'(x_i)$ becomes smaller than the desired error limit, $x_i \cdot 10^{-8}$.

Once the real zero of the third order polynomial has been found, a polynomial division is done to deflate the polynomial to second order. The quadratic equation is used to obtain the zeros of the second order

polynomial, and these zeros may be complex. If $s = a$ is a zero of $f(s)$, then $s-a$ must be a factor of $f(s)$, and can be removed:

$$\begin{aligned} & \frac{b_3s^2 + (ab_3 + b_2)s + (a(ab_3 + b_2) + b_1)}{s-a} \\ & \frac{-b_3s^3 + b_2s^2 + b_1s + 1}{-(b_3s^3 - ab_3s^2)} \\ & \frac{(ab_3 + b_2)s^2 + b_1s + 1}{(ab_3 + b_2)s^2 + b_1s + 1} \\ & \frac{-[(ab_3 + b_2)s^2 - a(ab_3 + b_2)s]}{a(ab_3 + b_2)s + b_1s + 1} \\ & \frac{-[a(ab_3 + b_2)s + b_1s - a[a(ab_3 + b_2) + b_1]]}{0*} \end{aligned} \quad (1-3.14)$$

The third order polynomial is evaluated in nested form, i.e.:

$$D(s) = ((b_3)s + b_2)s + b_1s + 1 \quad (1-3.15)$$

When $s = a$, the intermediate products in $D(s)$ are the same as the second order polynomial coefficients in Eq. (1-3.14). These intermediate products are stored at lines 027 and 031 of the program on the second card. The numbers stored only have value in the last iteration loop before loop exit, at which time $s = a$, and $f(s) = 0$, the desired result.

The second order polynomial is normalized so $c_0 = 1$ (lines 064 to 066). This normalization places the second order polynomial in the same form as the third order polynomial was originally. The quadratic formula is now used to find the zeros of the second order polynomial, $c_2s^2 + c_1s + 1$.

$$s_{1,2} = -c_1/(2c_2) \pm \sqrt{(c_1/(2c_2))^2 - 1/c_2} \quad (1-3.16)$$

If the discriminant, $(c_1/(2c_2))^2 - 1/c_2$, is positive, then two real zeros exist, if it is zero, a double zero exists, and if it is negative, a complex conjugate pair of zeros exist. Steps 067 through 102 find the zeros of the second order polynomial.

If the zeros of the second order polynomial are complex conjugates, then the poles of the transmission function are also complex conjugates, and a natural frequency, f_n , and quality factor, Q , may be calculated:

$$f_n = 1/(2\pi\sqrt{c_2}) \quad (1-3.17)$$

$$Q = \sqrt{c_2}/c_1 \quad (1-3.18)$$

These calculations are performed by steps 103 through 113 of the program. Assuming the third order real pole of the transmission function (parasitic pole caused by the op-amp characteristics) to be large compared to the other poles, then the gain term, K , can be defined in terms of the numerator and denominator coefficients:

$$T(s) = \frac{a_2s^2 + a_1s + a_0}{(s/a + 1)(c_2s^2 + c_1s + 1)} \quad (1-3.19)$$

$$\text{lowpass case: } K = a_0 \quad (1-3.20)$$

$$\text{bandpass case: } K = a_1/c_1 \quad (1-3.21)$$

$$\text{highpass case: } K = a_2/c_2 \quad (1-3.22)$$

The gain term is calculated by steps 114 through 137 of the program.

* By definition since $s = a$ is a zero of the polynomial.

Program Listing I

```

001 *LBLF LOAD ELEMENT 1
002 EEX
003 GT0E
004 *LBLF LOAD ELEMENT 2
005 2
006 GT09
007 *LBLC LOAD ELEMENT 3
008 3
009 GT09
010 *LBLD LOAD ELEMENT 4
011 4
012 GT09
013 *LBLF LOAD ELEMENT 5
014 5
015 GT09
016 *LBLA LOAD ELEMENT 6
017 6
018 *LBL8 element load subroutine
019 STOI store register index
020 R4 recover and store
021 ST03 element value
022 X>0? test for resistor
023 GT0P
024 CHS
025 GT0I store capacitor value
026 *LBL8
027 1/X calculate conductance,
028 EEX multiply by 1050, and store
029 5
030 0
031 ST08 store 1050 for later use
032 X
033 *LBL7
034 STOI store modified element value
035 RCL9 recall original element to
036 RTN display and return to keybd
037 *LBLW LOAD A0 AND f0 OF AMPLIFIER
038 PI
039 X
040 ENT↑ calculate and store
041 + τ = 1/(2πf0)
042 1/X
043 ST07
044 R↓ recover and store A0
045 ST08
046 RTN return control to keyboard
047 *LBLF START ANALYSIS
048 GSB1
049 RCL1 calculate s0 and s1 terms
050 GSB0
051 RCL2 of Y1 + Y2 + Y3
052 GSB6
053 RCL3
054 GSB2
055 RCL4
056 GSB8

```

REGISTERS

0 A ₀	1 Y ₁	2 Y ₂	3 Y ₃	4 Y ₄	5 Y ₅	6 Y ₆	7 τ	8 10 ⁵⁰	9 scratch
S0 Σ s ⁰ terms	S1 Σ s ¹ terms	S2 Σ s ² terms	S3 Σ s ³ terms	S4	S5 s ₁ ²	S6 s ₁ ⁰	S7 s ₁ ¹	S8 s ₂ ⁰	S9 s ₂ ¹
A b ₀	B D ₁	C D ₂	D D ₃	E scratchpad	F index				

```

057 RCL6
058 GSB0
059 RCL5 calculate and store s0 and
060 EEX s1 terms of:
061 RCL9
062 X Y4 + Y6 + Y5(1 - A0)
063 ST09
064 GSB2
065 RCL4
066 GSB0 calculate and store s1 and
067 RCL5
068 GSB0 s2 terms of:
069 RCL6
070 GSB0 τs(Y4 + Y5 + Y6)
071 GSB3
072 SPC calculate and store:
073 GSB6 (Y4 + Y5 + Y6)(1 + τs) + Y6(1 - A0 + τs)
074 GSB1 initialize index counter
075 RCL4
076 GSB2 calculate and store Y4
077 RCL6 calculate s0 and s1 terms
078 GSB0 of:
079 RCL9
080 GSB8 Y6 + Y5(1 - A0) - A0Y2
081 RCL2
082 RCL0
083 RCL8
084 X
085 CHS
086 GSB2
087 RCL6
088 GSB0 calculate and store s1 and
089 RCL5
090 GSB0 s2 terms of τs(Y5 + Y6)
091 GSB3
092 CF0 clear flag 0 to indicate
093 GSB6 additional summing and
094 P+S calculate and store:
095 RCL0 \ Y4{Y6(1 + τs) + Y5(1 - A0 + τs) - A0Y2}
096 STOA normalize denominator terms:
097 ST=1
098 ST=2 a2 s3 + a2 s2 + a1 s + 1
099 ST=3
100 RCL3 recall, store, and print
101 PRTX normalized denominator terms
102 ST0D
103 RCL2
104 PRTX a3/a0 → RD
105 ST0C
106 RCL1 a2/a0 → RC
107 P+S
108 PRTX a1/a0 → RB
109 ST0B
110 EEX
111 ENT↑
112 PRTX

```

Program Listing II

```

113 SPC
114 SF0 indicate summing register clr
115 GSB1 initialize registers and index
116 RCL1 calculate and store Y1
117 GSB2
118 RCL4 calculate and store Y4
119 GSB2
120 CLX
121 ST0I set s2 term of Y4 to zero
122 GSB6 calculate and store Y1 · Y4
123 RCL8
124 P+S normalize numerator terms
125 RCLA ÷
126 STX2
127 STX1
128 STX0
129 STX0
130 RCL2
131 PRTX
132 RCL1 recall and print
133 PRTX numerator terms
134 RCL0
135 P+S
136 PRTX
137 SPC
138 *LBL6 wait loop for 2nd card read
139 PSE
140 GT0b
141 *LBL0 subroutine to determine
142 ENT↑ whether recalled Y element
143 ABS is a conductance or a
144 EEX capacitance
145 3 If a conductance, perform
146 0 summation in the stack,
147 X>Y? otherwise, element is a
148 GT09 susceptibility, and summation is
149 R↓ done in the designated
150 R↓ i register.
151 RCL8
152 ÷
153 +
154 RTN
155 *LBL9 susceptance summation in R(i)
156 R↓
157 R↓
158 ST+i
159 R↓
160 RTN
161 *LBL1 register and index
162 1 initialization
163 9
164 STOI 19 → RI
165 CLX
166 STOI 0 → R19
167 RTN

```

LABELS					FLAGS		SET STATUS	
A Load Y ₁	B Load Y ₂	C Load Y ₃	D Load Y ₄	E Load Y ₅	0 continued summation	FLAGS	TRIG	DISP
a Load Y ₆	b second card wait loop	c	d Load A ₀ & f ₀	e start analysis	1	0 ON OFF	0 DEG	0 USERS CHOICE
0 sum R ≠ sc	1 initialize	2 loop terminate	3 calculate s ⁰ & s ¹	4 summation subroutine	2	1 1	1 GRAD	1 SCI
5 summation initialize	6 polynomial multiplication	7 input routine	8 input routine	9 recall subroutine	3	2 2	2 RAD	2 ENG
						3 3		n

Program Listing I

```

001 *LBL1 START ANALYSIS
002 SPC
003 P2S
004 RCLD if  $s^3$  coefficient is not
005 zero go to 3rd order soln
006 otherwise store remaining
007 second order coefficients
008 ST09 and go to second order
009 RCLB solution
010 ST08
011 GT02
012 *LBL0 third order solution
013 RCLC
014 X $\neq$ Y calculate initial guess
015 = for real 3rd order root
016 CHS
017 ST06
018 *LBL1 Newton-Raphson start
019 RCL6
020 ENT↑
021 ENT↑
022 ENT↑
023 RCLD
024 X
025 RCLC
026 +
027 ST08
028 X
029 RCLB calculate  $f(x_1)$ 
030 +
031 ST07
032 X
033 EEX
034 +
035 ST05
036 CLX
037 RCLD
038 3
039 X
040 X
041 RCLC
042 ENT↑ calculate  $f'(x_1)$ 
043 +
044 +
045 X
046 RCLB
047 +
048 X $\neq$ 0?  $f'(x_1) = 0$  escape
049 ST=5 calc  $f(x_1)/f'(x_1)$ 
050 RCL5 apply correction to  $x_1$ 
051 ST-6
052 ABS
053 RCL6
054 EEX
055 8
056 ÷ test for loop exit
057 ABS
058 X $\leq$ Y?
059 GT01
060 RCL6 print real root
061 GSB9
062 RCLD
063 ST09 normalize remaining
064 RCL7 second order coefficients
065 ST=8
066 ST=9

```

REGISTERS

0 A ₀	1 Y ₁	2 Y ₂	3 Y ₃	4 Y ₄	5 Y ₅	6 Y ₆	7 γ	8 scratch	9 scratch
S ₀ 0 $\sum s_n$	S ₁ 1 $\sum s_n$	S ₂ 2 $\sum s_n$	S ₃	S ₄	S ₅ scratch	S ₆ σ	S ₇ $c_0, 1/c_2$	S ₈ $c_1, c_1/2c_2$	S ₉ c_2
A b ₀	B D ₁	C D ₂	D D ₃	E	F	G	H	I	J

Program Listing II

```

067 *LBL2 second order solution
068 RCL9  $c_2$ 
069 ENT↑
070 +  $2*c_2$ 
071 ST=8 }  $c_1/(2c_2)$ 
072 RCL8 }
073 X2
074 RCL9
075 1/X
076 ST07
077 -  $(c_1/(2c_2))^2 - 1/c_2$ 
078 X $\neq$ 0? if discriminant is negative,
079 GT03 go to imaginary solution
080 JX
081 ST05
082 RCL8 calculate and print
083 - one real root
084 GSB9
085 RCL5
086 RCL8 calculate and print
087 + other real root
088 CHS
089 GT00
090 *LBL3 imaginary solution routine
091 CHS
092 JX
093 ST05
094 PRTX calculate and print
095 RCL8 one imaginary root
096 CHS
097 GSB9
098 RCL5
099 CHS calculate and print
100 PRTX other imaginary root
101 X $\neq$ Y
102 GSB9
103 RCL7  $\omega_n^2$ 
104 JX
105 2
106 =
107 ST05  $\omega_n/2$ 
108 PI
109 =
110 PRTX  $f_n$ , the natural frequency
111 RCL5
112 RCL8
113 = Q, the quality factor

```

LABELS					FLAGS		SET STATUS		
A	B	C	D	E start analysis	0	FLAGS	TRIG	DISP	
a	b	c	d	e	1	0	ON OFF	DEG ■ FIX SCI ENG n	
0 local label	1 local label	2 2nd order solution	3 imag roots	4	2	1	GRAD RAD	SCI ENG ■	
5	6	7	8 P2S, prt & space	9 print & space	3	2	3	n 3	

Suggested program changes for the HP-67: Program space does not allow the inclusion of a print, R/S toggle and associated output routine.

To cause the program execution to stop at the data output points, replace the "print" statements with "R/S" statements at the following line numbers: 101, 104, 108, 112, 131, 133, and 136 in program one, and at lines 094, 100, 110, 139, and 143 in program two.

If these changes are made, the program will stop at each output point. To continue program execution, key a "R/S" command from the keyboard.

TI-59 PROGRAM LISTING 1-3 card 1

000	76	LBL	subroutine to sum	050	05	05
001	44	SUM	conductance & susceptance	051	00	0
002	42	STO	store entry in scratchpad	052	72	ST* clear next set of storage
003	09	09		053	04	04 registers
004	50	I _X I	test for conductance	054	72	ST*
005	32	X _{IT}	If entry is smaller than	055	05	05
006	01	1	10 ⁵⁰ , then it is a	056	92	RTN return to main program
007	52	EE	susceptance and program	057	76	LBL LOAD ELEMENT INDEX
008	03	3	execution jumps to	058	11	A
009	00	0	step 24.	059	98	ADV space paper in printer
010	77	GE		060	22	INV
011	00	00		061	52	EE set fix 0 format
012	24	24		062	22	INV
013	43	RCL		063	57	ENG
014	09	09	recover entry	064	99	PRT print element index
015	55	÷		065	85	+
016	01	1	remove conductance	066	32	X _{IT} save index entry
017	52	EE	scaling	067	01	1
018	05	5		068	00	0 calculate storage
019	00	0		069	95	= register location
020	95	=		070	42	STO
021	74	SM*	sum conductance	071	04	04
022	05	05		072	32	X _{IT} recover index to display
023	92	RTN	return to main program	073	91	R/S stop program execution
024	43	RCL	recover entry	074	76	LBL LOAD RESISTOR VALUE
025	09	09		075	12	B
026	74	SM*	sum susceptance	076	35	I _X X form conductance
027	04	04		077	65	×
028	92	RTN	return to main program	078	32	X _{IT} save conductance
029	76	LBL	initialization	079	01	1
030	59	INT	subroutine	080	52	EE multiply conductance by
031	02	2		081	05	10 ⁵⁰ and indirectly store
032	00	0	initialize susceptance	082	00	0
033	42	STO	storage register index	083	95	=
034	04	04		084	72	ST*
035	02	2		085	04	04
036	01	1	initialize conductance	086	03	3 setup to print "R" as
037	42	STO	storage register index	087	05	annotation on right
038	05	05		088	69	DP hand edge of printout
039	61	GTO	jump to step 51 and	089	04	04
040	00	00	continue program	090	32	X _{IT}
041	51	51	execution	091	35	I _X X
042	76	LBL	subroutine to complete	092	22	INV recover resistor entry
043	85	+	summation	093	52	EE and print annotated
044	71	SBR	gosub subroutine "sum"	094	69	DP value
045	44	SUM		095	06	06
046	02	2		096	91	R/S stop program execution
047	44	SUM	increment storage	097	76	LBL LOAD CAPACITOR VALUE
048	04	04	register indices	098	13	C
049	44	SUM		099	72	ST*

Note: This translation was provided by Mr. Roger Junk.

TI-59 PROGRAM LISTING 1-3 card 1

100	04	04	indirectly store cap	-
101	32	XIT	save entry	-
102	01	1		
103	05	5	setup to print "C" on	
104	69	OP	right hand edge of paper	
105	04	04		
106	32	XIT		
107	57	ENG	print capacitor value in	
108	69	OP	engineering format along	
109	06	06	with annotation	
110	91	R/S	stop program execution	
111	76	LBL	LOAD OP-AMP DC GAIN, A_o	
112	14	E		
113	42	STD		
114	10	10	store A_o	
115	32	XIT	save entry	-
116	01	1		
117	03	3	setup to print "A" on	
118	69	OP	right hand edge of paper	
119	04	04		
120	32	XIT	recover entry,	
121	98	ADV	space paper, and	
122	69	OP	print entry and notation	
123	06	06		
124	91	R/S	stop program execution	
125	76	LBL	LOAD OP-AMP BREAK	
126	15	E	FREQUENCY (-3 dB point)	
127	65	X		
128	32	XIT	save entry	-
129	02	2		
130	65	X		
131	89	#	form and store:	
132	95	=	$\gamma = \frac{1}{2\pi f - 3 \text{ dB}}$	
133	35	1/X		
134	42	STD		
135	17	17		
136	01	1		
137	52	EE	if entry is larger than	
138	02	2	10^{20} set γ to zero	
139	00	0		
140	77	GE		
141	01	01		
142	46	46		
143	00	0		
144	42	STD		
145	17	17		
146	02	2		
147	01	1	setup to print "F" on	
148	69	OP	right hand edge of paper	
149	04	04		
150	32	XIT	recover entry	-
151	98	ADV	space paper and	
152	69	OP	print annotated entry	
153	06	06		
154	91	R/S	stop program execution	
155	76	LBL	INITIALIZE	
156	16	H*		
157	00	0		
158	42	STD	zero elements 2, 3, 5, & 6	
159	12	12		
160	42	STD		
161	13	13		
162	42	STD		
163	15	15		
164	42	STD		
165	16	16		
166	91	R/S	stop program execution	
167	76	LBL	START ANALYSIS	
168	10	E*		
169	71	SBR	test for printer attached	
170	04	04	to calculator	
171	75	75		
172	71	SBR	initialize counters and	
173	59	INT	registers	
174	43	RCL		
175	11	11		
176	71	SBR		
177	44	SUM		
178	43	RCL	calculate and store	
179	12	12	s^0 and s^1 terms of:	
180	71	SBR		
181	44	SUM	$Y_1 + Y_2 + Y_3$	
182	43	RCL		
183	13	13		
184	71	SBR		
185	85	+		
186	43	RCL		
187	14	14		
188	71	SBR		
189	44	SUM		
190	43	RCL	calculate and store	
191	16	16	s^0 and s^1 terms of:	
192	71	SBR	$Y_4 + Y_6 + Y_5(1 - A_o)$	
193	44	SUM		
194	01	1		
195	75	-		
196	43	RCL		
197	10	10		
198	95	=		
199	65	X		

TI-59 PROGRAM LISTING 1-3 card 1

200	43	RCL		
201	15	15		
202	95	=		
203	42	STD		
204	19	19		
205	71	SBR		
206	85	+		
207	43	RCL		
208	14	14		
209	71	SBR		
210	44	SUM		
211	43	RCL	calculate and store	
212	15	15	s^1 and s^2 terms of:	
213	71	SBR	$\tau_s(Y_4 + Y_5 + Y_6)$	
214	44	SUM		
215	43	RCL		
216	16	16		
217	71	SBR		
218	44	SUM		
219	71	SBR		
220	49	PRD		
221	86	STF	calculate and store:	
222	00	00	$(Y_1 + Y_2 + Y_3) \{ (Y_4 + Y_6)(1 + \tau_s) + Y_5(1 - A_o + \tau_s) \}$	
223	71	SBR	$= D_1$	
224	65	X		
225	71	SBR		
226	59	INT	initialize indices	
227	43	RCL		
228	14	14	calculate and store	
229	71	SBR	s^0 and s^1 terms of	
230	85	+	Y_4	
231	43	RCL		
232	16	16		
233	71	SBR		
234	44	SUM		
235	43	RCL	calculate and store	
236	19	19	s^0 and s^1 terms of:	
237	71	SBR	$Y_6 + Y_5(1 - A_o) + A_o Y_2$	
238	44	SUM		
239	43	RCL		
240	12	12		
241	65	X		
242	43	RCL		
243	10	10		
244	95	=		
245	94	+/-		
246	71	SBR		
247	85	+		
248	43	RCL		
249	16	16		
250	71	SBR		
251	44	SUM	calculate and store	
252	43	RCL	s^1 and s^2 terms of:	
253	15	15	$\tau_s(Y_5 + Y_6)$	
254	71	SBR		
255	44	SUM		
256	71	SBR		
257	49	PRD		
258	22	INV	calculate and store:	
259	86	STF	$D_1 + Y_4 \{ Y_6(1 + \tau_s) + Y_5(1 - A_o + \tau_s) - A_o Y_2 \}$	
260	00	00		
261	71	SBR		
262	65	X	test for non-zero denominator coeffs	
263	29	CP		
264	43	RCL	non-zero test continued	
265	00	00		
266	22	INV		
267	67	EQ		
268	02	02	non-zero test concluded	
269	78	78		
270	43	RCL		
271	01	01		
272	22	INV		
273	67	EQ		
274	02	02		
275	78	78		
276	43	RCL	normalize denominator terms	
277	02	02		
278	42	STD		
279	18	18		
280	35	1/X		
281	49	PRD		
282	00	00		
283	49	PRD		
284	01	01		
285	49	PRD		
286	02	02		
287	49	PRD		
288	03	03		
289	43	RCL	recall and print s^3	
290	03	03	denominator coefficient	
291	71	SBR	(program will stop if	
292	98	ADV	printer is not attached)	
293	42	STD		

TI-59 PROGRAM LISTING

1-3 card 1

300	42	STD	350	04	04
301	28	28	351	64	64
302	43	RCL	352	43	RCL
303	01	01	353	00	00, recall and print s^0
304	71	SBR	354	71	SBR numerator coefficient
305	99	PRT	355	04	04
306	42	STD	356	64	64
307	27	27	357	91	R/S stop program execution
308	43	RCL	358	00	0
309	00	00	359	00	0 unused program memory
310	71	SBR	360	00	0 denominator coefficient
311	99	PRT	361	00	0
312	42	STD	362	00	0
313	26	26	363	00	0
314	86	STF	364	00	0 indicate first product
315	00	00	365	00	0 of sums
316	71	SBR	366	00	0 initialize indices
317	59	INT	367	00	0
318	43	RCL	368	76	LBL subroutine to multiply
319	11	11	369	49	PRD by γ s to form s^2 and
320	71	SBR	370	43	RCL additional s^1 terms, and
321	85	+	371	17	add to presently stored
322	43	RCL	372	49	PRD terms
323	14	14	373	24	24
324	71	SBR	374	65	x
325	85	+	375	43	RCL
326	00	0	376	25	25
327	72	ST*	377	95	=
328	04	04	378	44	SUM
329	71	SBR	379	22	22
330	65	x	380	92	RTN
331	43	RCL	381	76	LBL polynomial multiplication
332	10	10	382	65	x subroutine
333	55	÷	383	00	0 normalize numerator
			384	71	SBR coefficients
334	43	RCL	385	04	04
335	18	18	386	49	48
336	95	=	387	43	RCL
337	49	PRD	388	23	23
338	02	02	389	65	x s^0 term calculation
339	49	PRD	390	43	RCL
340	01	01	391	21	21
341	49	PRD	392	95	=
342	00	00	393	74	SM*
343	43	RCL	394	05	05
344	02	02	395	01	1 recall and print s^2
345	71	SBR	396	71	SBR numerator coefficient
346	98	ADV	397	04	04 s^1 term calculation
347	43	RCL	398	48	48
348	01	01	399	43	RCL numerator coefficient
349	71	SBR			

TI-59 PROGRAM LISTING

1-3 card 1

400	22	22	450	22	INV
401	65	x	451	87	IFF
402	43	RCL	452	00	00
403	21	21	453	04	04
404	95	=	454	58	58
405	74	SM*	455	00	0
406	05	05	456	72	ST*
407	43	RCL	457	05	05
408	23	23	458	92	RTN
409	65	x	459	76	LBL subroutine to print
410	43	RCL	460	98	ADV and continue if
411	20	20	461	98	ADV calculator attached to
412	95	=	462	76	LBL PC-100A printer, or else
413	74	SM*	463	99	PRT to stop program execution
414	05	05	464	57	ENG and display answer
415	02	2	465	99	PRT
416	71	SBR	466	22	INV
417	04	04	467	87	IFF
418	48	48	468	01	01
419	43	RCL	469	04	04
420	22	22	470	74	74
421	65	x	471	91	R/S
422	43	RCL	472	22	INV
423	20	20	473	57	ENG
424	95	=	474	92	RTN
425	74	SM*	475	69	DP subroutine to sense
426	05	05	476	08	08 PC-100A printer is
427	43	RCL	477	86	STF attached to calculator
428	24	24	478	01	01
429	65	x	479	92	RTN
430	43	RCL			
431	21	21			
432	95	=			
433	74	SM*			
434	05	05			
435	03	3			
436	71	SBR			
437	04	04			
438	48	48			
439	43	RCL			
440	24	24			
441	65	x	441	65	s^3 term calculation
442	43	RCL	442	43	RCL
443	20	20	443	20	20
444	95	=	444	95	=
445	74	SM*	445	74	SM*
446	05	05	446	05	05
447	92	RTN	447	92	RTN
448	42	STD polynomial multiplication	448	42	STD polynomial multiplication
449	05	05 storage subroutine	449	05	05 storage subroutine

REGISTER ALLOCATIONS FOR TI-59 1-3 card 1

register number	contents
0	sum of s^0 terms
1	sum of s^1 terms
2	sum of s^2 terms
3	sum of s^3 terms
4	indirect storage register index
5	indirect storage register index
6	
7	
8	
9	
10	A_0 , the op-amp dc gain
11	Y_1
12	Y_2
13	Y_3
14	Y_4
15	Y_5
16	Y_6
17	τ
18	b_0
19	$Y_5(1-A_0)$
20	$\frac{-----}{s_2^1}$
21	$\frac{-----}{s_2^0}$
22	$\frac{-----}{s_1^1}$
23	$\frac{-----}{s_1^0}$
24	$\frac{-----}{s_1^2}$
25	
26	D_0
27	D_1
28	D_2
29	D_3
30	

TI-59 PROGRAM LISTING 1-3 card 2

000	76	LBL	START		050	43	RCL	
001	15	E			051	29	29	
002	71	SBR		test for PG-100A printer	052	65	x	
003	04	04		attached to calculator	053	43	RCL	
004	75	75			054	23	23	
005	43	RCL			055	85	+	
006	29	29		if s^3 coefficient is zero,	056	02	2	calculate $f'(x_i)$
007	29	CP		go to second order	057	65	x	
008	67	E0		solution routine	058	43	RCL	
009	01	01			059	28	28	
010	19	19			060	95	=	
011	55	÷			061	65	x	
012	43	RCL		calculate initial guess	062	43	RCL	
013	28	28		for real third order root	063	23	23	
014	95	=			064	85	+	
015	35	1/X		$x_0 = D_2/D_3$	065	43	RCL	
016	94	+/-			066	27	27	
017	42	STD			067	95	=	
018	23	23			068	29	CP	
019	43	RCL		Newton-Raphson start	069	67	E0	$f'(x_i) = 0$ escape
020	23	23			070	00	00	
021	65	x			071	75	75	
022	43	RCL			072	35	1/X	
023	29	29			073	49	PRD	calc $f(x_i)/f'(x_i)$
024	85	+			074	25	25	
025	43	RCL			075	43	RCL	
026	28	28			076	25	25	
027	95	=			077	94	+/-	apply correction to x_i
028	42	STD			078	44	SUM	
029	21	21			079	23	23	
030	65	x			080	50	I _X I	
031	43	RCL			081	32	X _T T	
032	23	23			082	43	RCL	
033	85	+		calculate $f(x_i)$	083	23	23	
034	43	RCL			084	55	÷	
035	27	27			085	01	1	
036	95	=			086	52	EE	test for loop exit
037	42	STD			087	08	8	
038	22	22			088	95	=	
039	65	x			089	50	I _X I	
040	43	RCL			090	22	INV	
041	23	23			091	77	GE	
042	85	+			092	00	00	
043	43	RCL			093	19	19	
044	26	26			094	43	RCL	
045	95	=			095	23	23	
046	42	STD			096	71	SBR	print real root
047	25	25			097	04	04	
048	03	3			098	65	65	
049	65	x			099	43	RCL	

TI-59 PROGRAM LISTING 1-3 card 2

100	29	29	
101	42	STD	
102	20	20	
103	43	RCL	
104	22	22	
105	29	CP	
106	67	EQ	normalize second order coefficients
107	01	01	
108	31	31	
109	35	1/X	
110	49	PRD	
111	20	20	
112	49	PRD	
113	21	21	
114	49	PRD	
115	22	22	
116	61	STD	
117	01	01	
118	31	31	
119	43	RCL	
120	28	28	
121	42	STD	store second order coefficients
122	20	20	
123	43	RCL	
124	27	27	
125	42	STD	
126	21	21	
127	43	RCL	
128	26	26	
129	42	STD	
130	22	22	
131	43	RCL	second order solution:
132	20	20	
133	35	1/X	
134	49	PRD	
135	22	22	
136	55	÷	
137	02	2	
138	95	=	calculate discriminant,
139	49	PRD	$b^2 - 4ac$
140	21	21	
141	43	RCL	
142	21	21	
143	33	X ²	
144	75	-	
145	43	RCL	
146	22	22	
147	95	=	
148	29	CP	test for negative
149	22	INV	discriminant

TI-59 PROGRAM LISTING 1-3 card 2

150	77	GE	
151	01	01	
152	75	75	
153	34	FX	
154	42	STD	
155	25	25	
156	75	-	
157	43	RCL	calculate and print one real root
158	21	21	
159	95	=	
160	71	SBR	
161	04	04	
162	65	65	
163	43	RCL	
164	25	25	
165	85	+	
166	43	RCL	
167	08	08	calculate and print other real root
168	94	+/-	
169	71	SBR	
170	04	04	
171	65	65	
172	61	GTO	
173	02	02	
174	25	25	
175	94	+/-	imaginary solution:
176	34	FX	
177	42	STD	
178	25	25	
179	71	SBR	
180	04	04	
181	65	65	calculate and print one complex root
182	43	RCL	
183	21	21	
184	94	+/-	
185	71	SBR	
186	04	04	
187	66	66	
188	43	RCL	
189	25	25	
190	94	+/-	
191	71	SBR	
192	04	04	
193	65	65	
194	43	RCL	calculate and print the other complex root
195	21	21	
196	94	+/-	
197	71	SBR	
198	04	04	
199	66	66	
200	68	NOP	
201	68	NOP	
202	43	RCL	
203	22	22	
204	34	FX	
205	55	÷	
206	02	2	
207	95	=	
208	42	STD	calculate and print fn, the natural frequency
209	25	25	
210	55	÷	
211	89	π	
212	95	=	
213	71	SBR	
214	04	04	
215	65	65	
216	43	RCL	
217	25	25	
218	55	÷	
219	43	RCL	
220	21	21	calculate and print Q
221	95	=	
222	71	SBR	
223	04	04	
224	66	66	
225	43	RCL	
226	20	20	
227	49	PRD	
228	22	22	restore second order coefficients
229	65	×	
230	02	2	
231	95	=	
232	49	PRD	
233	21	21	
234	43	RCL	
235	02	02	
236	22	INV	
237	67	EQ	is numerator second order
238	02	02	
239	55	55	
240	43	RCL	
241	00	00	
242	22	INV	
243	67	EQ	is numerator a constant?
244	02	02	
245	59	59	
246	43	RCL	
247	01	01	
248	55	÷	
249	43	RCL	
250	21	21	
251	95	=	
252	61	GTO	
253	02	02	
254	59	59	
255	55	÷	calculate and print the gain term, K
256	43	RCL	
257	20	20	
258	95	=	
259	71	SBR	
260	04	04	
261	65	65	
262	61	GTO	
263	91	R/S	
264	00	0	
265	00	0	
266	00	0	
267	00	0	
268	00	0	
269	00	0	
270	00	0	
457	00	0	
458	00	0	
459	00	0	
460	76	LBL	subroutine to lock up
461	91	R/S	"R/S" command-prevents
462	61	GTO	further program execution
463	04	04	via the "R/S" command
464	61	61	
465	98	ADV	
466	99	PRT	
467	68	NOP	print or display subroutine
468	22	INV	
469	87	IFF	
470	01	01	
471	04	04	
472	74	74	
473	91	R/S	
474	92	RTN	
475	69	DP	
476	08	08	PC-100A sense routine
477	86	STF	
478	01	01	
479	92	RTN	

REGISTER ALLOCATIONS FOR TI-59 1-3 card 2

register number	contents
0	N_0
1	N_1
2	N_2
3	
4	
5	
6	
7	
8	
9	
10	A_0
11	Y_1
12	Y_2
13	Y_3
14	Y_4
15	Y_5
16	Y_6
17	τ
18	b_0
19	
20	c_2
21	$c_1, c_1/2c_2$
22	$c_0, 1/c_2$
23	x_i
24	
25	$f(x_i)/f'(x_i)$
26	D_0
27	D_1
28	D_2
29	D_3

PROGRAM 1-4 L N A P, LADDER NETWORK ANALYSIS PROGRAM.Program Description and Equations Used

This program evaluates the frequency response and input impedance of a RLC ladder network containing up to 4 nodes and 8 branches using a sweep of discrete evaluation frequencies. The frequency response is provided as magnitude (dB) and phase (degrees, radians, or grads), and the input impedance is provided as real and imaginary parts (ohms). The evaluation frequency may be incremented in a linear manner using an additive increment or in a logarithmic manner using a multiplicative increment.

Each branch of the ladder may contain a resistor (R), a capacitor (C), an inductor (L), a series RC, a parallel RC, a series RL, or a parallel RL network. All element values are stored, and may be reviewed at any time to check or correct the component values and interconnection.

Because of the number of available storage registers in the HP-67/97, the number of nodes cannot exceed four, while the TI-59 can accommodate the data for ten nodes. Elements that inhibit signal flow through the network are not allowed, and will cause the program execution to halt displaying "Error." Examples of these inhibiting elements are a shunt resistor or a shunt inductor having zero value, or series capacitors in series branches having zero values.

The algorithm used by this program assumes 1 volt at the output of the ladder network (see Fig. 1-4.1). From the knowledge of the last branch admittance, the complex branch current may be determined. Since no current flows out of the last node, the last shunt branch current must also flow through the preceding series branch. The complex voltage drop across this branch may be determined by multiplying the branch impedance and the branch current. By adding the series branch voltage to the last node voltage, the next lower node voltage may be obtained. This node voltage times the shunt node admittance will yield the shunt node current. Adding this shunt node current to the previous series

branch current will yield the next lower series branch current.

This loop is repeated until the input voltage source is reached (node 0). The frequency response is found from Eq. (1-4.1) and the input impedance from Eq. (1-4.2), i.e.:

$$T(j\omega) = E_{out}/E_{in} = 1/E_0 \quad (1-4.1)$$

$$Z_{in}(j\omega) = E_0/I_0 \quad (1-4.2)$$

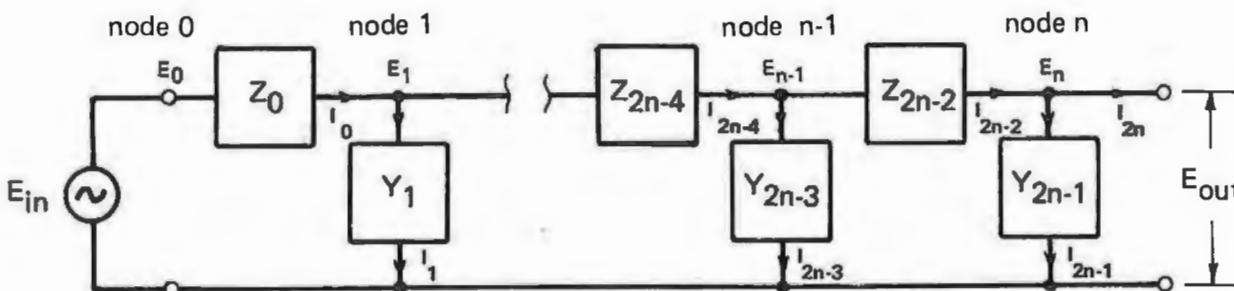


Figure 1-4.1 General ladder network topology.

The preceding algorithm may be expressed in mathematical shorthand using indices:

$$I_{2k-2} = (E_k)(Y_{2k-1}) + I_{2k} \quad (1-4.3)$$

$$E_{k-1} = (I_{2k-2})(Z_{2k-2}) + E_k \quad (1-4.4)$$

where $k = n, n-1, n-2, \dots, 1$, and n is the highest numbered node. The initial conditions for the n -th node are given by:

$$I_{2n} = 0 \quad (1-4.5)$$

$$E_n = 1 + j0 \quad (1-4.6)$$


Equation (1-4.3) is evaluated for I_{2k-2} and substituted into Eq. (1-4.4) to obtain the next lower numbered node voltage. The index, k , is decremented by one, and Eqs. (1-4.3) and (1-4.4) are again evaluated. This process is continued until the voltage at node 0 is obtained. Equation (1-4.1) is used to find the frequency response, $T(j\omega)$, from the node 0 voltage, and Eq. (1-4.2) is used to find the input impedance.

User Instructions

L N A P, LADDER NETWORK ANALYSIS PROGRAM				
# of nodes	linear sweep	log sweep	data review	start analysis
load R	load L	load O	load start freq	load freq increment

STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
1	Load both sides of the magnetic card			
2	Load the number of nodes in the network The number of nodes cannot exceed four	# nodes	f A	# branches
3	Enter data starting with the highest numbered node: a) If parallel RC or RL: key in resistance and change sign* R, ohms key in inductance L, henry OR key in capacitance C, farad	chs* A B C	branch # br # - 1 br # - 1	branch # br # - 1 br # - 1
	b) If series RC or RL: key in resistance R, ohms key in inductance L, henry OR key in capacitance C, farad	A B C	branch # br # - 1 br # - 1	branch # br # - 1 br # - 1
	For resistance, inductance, or capacitance alone in one branch, use step 3b with zero resistance for L or 0 entry, or use zero inductance for resistance entry. A zero or positive resistance is interpreted as a series branch indication.			
	Alternately, step 3a may be used to enter single inductors or capacitors by entering a very large negative resistance like -10^{20} ohms.			
	Fastest program execution will result if the zero resistance method with step 3b is used for series branches, and the large negative resistance method with step 3a is used for shunt branches. By observing this convention, the program will not use the series to parallel conversion subroutine which requires about 2 seconds to execute each time it is called.			
	Repeat step 3 until all branches including branch 0 have been entered.			
	* The sign change must affect the mantissa and not the exponent on numbers entered using scientific notation.			

User Instructions

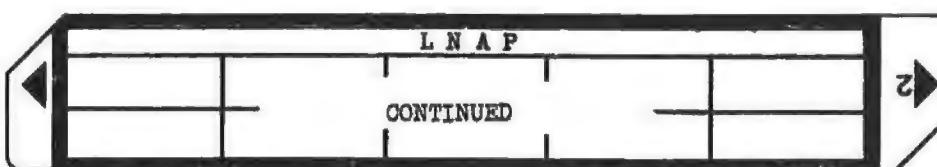

STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
4	To review stored element values		f D	branch # R _n * L _n or C _n ** space R _{n-1} * L ₀ ** : R ₀ * L ₀ or C ₀ **
	* A negative resistance value indicates a parallel connection of elements			
	** A negative value for the reactive element indicates the element is a capacitor. The capacitance value is the absolute value of the number given.			
5	To change the value of a stored element:	branch #	STO I	
a)	Key in branch number to be changed	R	A	
b)	Key in correct resistance	L OR	B OR	
c)	Key in correct reactive element value	C	C	
	Repeat step 4 or 5 if desired.			
6	To run analysis:		D	
a)	Load start frequency in hertz	f start	E	
b)	Load frequency increment (for linear sweep, the new frequency will be the old frequency plus the increment, and for log sweep, the new frequency will be the old frequency times the increment)	fincr		
c)	Select linear or logarithmic sweep For linear sweep For logarithmic sweep	f B f C		NOH N1"
	Steps 6a, 6b, and 6c may be executed in any order.			
d)	Start analysis run	f E		see Ex. (1-4.1)

User Instructions



STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
7	To stop the analysis: Wait until the pause that occurs after the imaginary Z _{in} is printed, then key R/S		R/S	
	If the program execution is halted without waiting for the pause, the primary and secondary registers may be left interchanged.			
	If a register interchange is suspected, recall register 0 and check to see that branch 0 resistance is stored there.			
	If the branch 0 reactive element is found in register 0, an interchange has occurred, and a P>S operation is required.		P>S	

Example 1-4.1

Figure 1-4.2 is the schematic of a predistorted 8th order Butterworth lowpass filter with a -3 dB cutoff frequency of 1000 Hz, and a design impedance level of 1000 ohms. Determine the frequency response and input impedance of this filter over a frequency range of 100 Hz to 10 kHz using a logarithmic sweep with 10 points per decade.

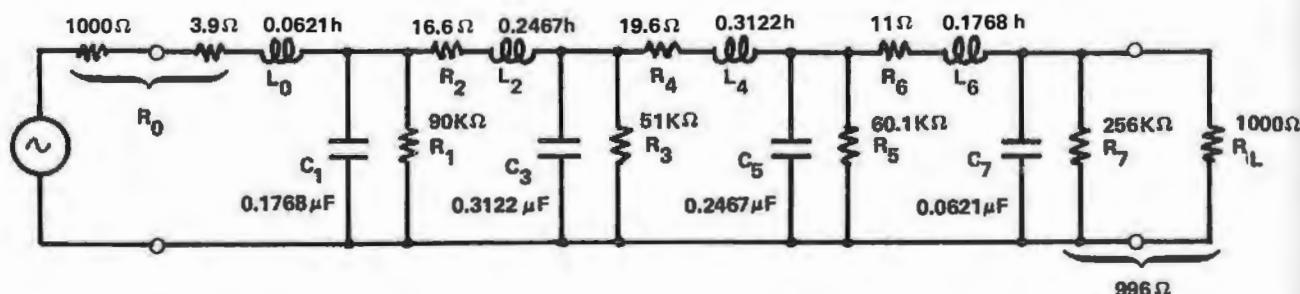


Figure 1-4.2 Predistorted 8th order Butterworth LP filter.

HP-97 PRINTOUT FOR EXAMPLE 1-4.1

PROGRAM INPUT		DATA REVIEW	
4.00 GSBA	load # of nodes		
-996. GSBA	R7*	7.000+00	*** branch number
.0621-06 GSBC	C7	-996.0+00	*** resistive part*
11. GSBA	R6	-62.10-09	*** reactive part**
.1768 GSBB	L6	6.000+00	
-60100. GSBA	R5	11.00+00	
.2647-06 GSBC	C5	176.8-03	
19.6 GSBA	R4	5.000+00	***
.3122 GSBB	L4	-60.10+03	***
-51000. GSBA	R3	-264.7-09	***
.3122-06 GSBC	C3	4.000+00	***
16.6 GSBA	R2	19.60+00	***
.2647 GSBB	L2	312.2-03	***
-90000. GSBA	R1	3.000+00	***
.1768-06 GSBC	C1	-51.00+03	***
1003.5 GSBA	R0	-312.2-09	***
.0621 GSBB	C0	2.000+00	***
		16.60+00	***
		264.7-03	***
		1.000+00	***
		-90.00+03	***
		-176.8-09	***
		0.000+00	***
		1.004+03	***
		62.10-03	***

* A negative sign indicates a parallel connection of elements.

** A negative sign indicates a capacitor as the reactive element.

HP-97 PRINTOUT FOR EXAMPLE 1-4.1

```

GSBc select log sweep
100. GSBD load start frequency
    .1 10x calculate freq increment for 10 points per decade
1.259+00 *** multiplicative increment (manual print command)
GSBE load multiplicative increment
GSBe start analysis

```

PROGRAM OUTPUT

100.0+00 freq, Hz	316.2+00	1.000+03	3.162+03
-6.467+00 gain, dB	-6.482+00	-9.816+00	-86.07+00
-29.40+00 phase, °	-94.00+00	2.263+00	95.46+00
2.000+03 Re Z _{in} , Ω	2.000+03	5.622+03	1.005+03
208.2-03 Im Z _{in} , Ω	115.0-03	-415.8+00	932.4+00
125.9+00	398.1+00	1.259+03	3.981+03
-6.468+00	-6.493+00	-22.54+00	-102.0+00
-37.04+00	-119.2+00	-98.07+00	75.48+00
2.000+03	2.000+03	1.049+03	1.005+03
250.4-03	-723.8-03	-813.0+00	1.319+03
158.5+00	501.2+00	1.585+03	5.012+03
-6.470+00	-6.513+00	-38.24+00	-118.0+00
-46.68+00	-152.0+00	-161.3+00	59.79+00
2.000+03	1.993+03	1.013+03	1.004+03
292.3-03	-2.388+00	-139.0+00	1.772+03
199.5+00	631.0+00	1.995+03	6.310+03
-6.472+00	-6.557+00	-54.14+00	-134.0+00
-58.87+00	164.2+00	154.3+00	47.41+00
2.000+03	1.957+03	1.008+03	1.004+03
322.3-03	17.75+00	248.9+00	2.317+03
251.2+00	794.3+00	2.512+03	7.943+03
-6.476+00	-6.770+00	-70.03+00	-150.0+00
-74.33+00	101.8+00	121.1+00	37.62+00
2.000+03	1.931+03	1.006+03	1.004+03
305.9-03	275.6+00	586.1+00	2.985+03
			10.00+03
			-166.0+00
			29.86+00
			1.004+03
			3.811+03

Example 1-4.2

Over a frequency range of 8 Hz to 12 Hz using a linear sweep with 0.2 Hz steps, evaluate the transmission function and input impedance of the network shown in Fig. 1-4.3.

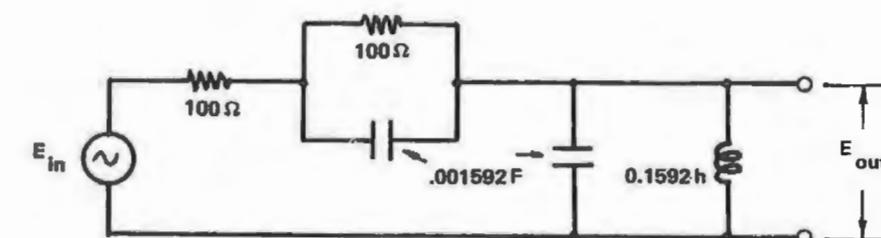


Figure 1-4.3 Network for Example 1-4.2.

The network must be redrawn with the insertion of dummy elements to place it in the ladder format meeting the program input requirements, i.e., only parallel RC or RL networks can be accommodated, not parallel LC networks. The redrawn network is shown in Fig. 1-4.4.

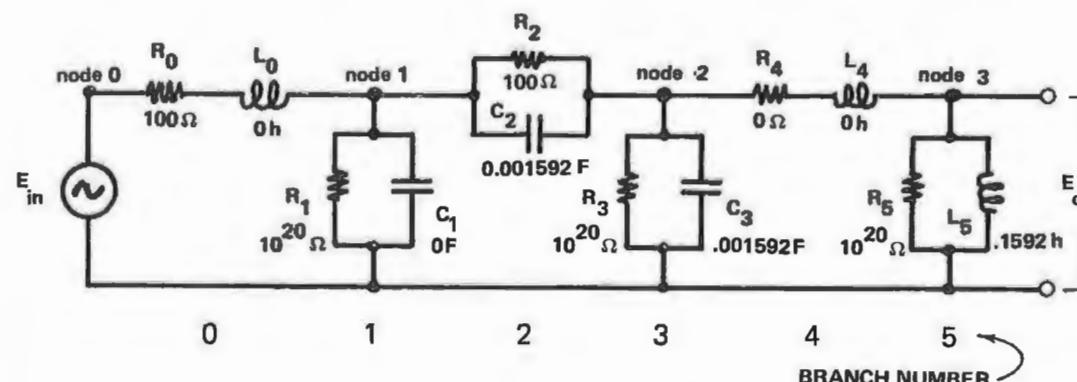


Figure 1-4.4 Network of Fig. 1-4.3 redrawn with dummy elements.

HP-97 PRINTOUT FOR EXAMPLE 1-4.2

8. GSBD start frequency
 .2 GSBE frequency increment
 GSBB select linear sweep
 GSBe start analysis } Analysis Particulars

PROGRAM INPUT	DATA REVIEW
3.00 GSBA enter # of nodes	
-1.+20 GSBA R5 *	GSBD start data review
.159155 GSBB L5	5.000+00 *** branch number
0. GSBA R4	-100.0+18 *** resistive part *
0. GSBB L4	159.2-63 *** reactive part **
	4.000+00 ***
-1.+20 GSBA R3	0.000+00 ***
1.59155-03 GSBC O3	0.000+00 ***
-100. GSBA R2	3.000+00 ***
1.59155-03 GSBC O2	-100.0+18 ***
	-1.592-03 ***
-1.+20 GSBA R1	8.400+00
0. GSBC O1	2.000+00 ***
	-11.13+00
100. GSBA R0	-100.0+00 ***
0. GSBB L0	-1.592-03 ***
	1.000+00 ***
	-100.0+18 ***
	0.000+00 ***
	0.000+00 ***
	100.0+00 ***
	0.000+00 ***

* A negative sign indicates parallel connection of elements.

** A negative sign indicates a capacitor.

8.000+00 freq, Hz	9.000+00	10.00+00	11.00+00
-13.24+00 gain, dB	-7.123+00	-6.158-06	-7.057+00
84.42+00 phase, °	70.22+00	-414.3-06	-58.65+00
101.5+00 Re Z _{in} , Ω	101.2+00	101.0+00	100.8+00
9.915+00 Im Z _{in} , Ω	36.39+00	-13.97+06	-61.40+00
8.200+00	9.200+00	10.20+00	11.20+00
-12.23+00	-5.473+00	-928.2-03	-8.251+00
82.69+00	64.09+00	-21.06+00	-62.31+00
101.5+00	101.2+00	101.0+00	100.8+00
13.01+00	49.15+00	-262.2+00	-52.88+00
8.400+00	9.400+00	10.40+00	11.40+00
-11.13+00	-3.663+00	-2.509+00	-9.306+00
80.60+00	55.32+00	-36.38+00	-65.11+00
101.4+00	101.1+00	100.9+00	100.8+00
16.79+00	70.24+00	-137.0+00	-46.76+00
8.600+00	9.600+00	10.60+00	11.60+00
-9.930+00	-1.819+00	-4.173+00	-10.25+00
77.99+00	42.03+00	-46.69+00	-67.31+00
101.3+00	101.1+00	100.9+00	100.7+00
21.55+00	112.1+00	-95.11+00	-42.12+00
8.800+00	9.800+00	10.80+00	11.80+00
-8.602+00	-361.1-03	-5.702+00	-11.09+00
74.66+00	23.05+00	-53.70+00	-69.09+00
101.3+00	101.0+00	100.9+00	100.7+00
27.79+00	237.4+00	-74.08+00	-38.49+00
		12.00+00	
		-11.86+00	
		-70.55+00	
		100.7+00	
		-35.55+00	

TI-59 PRINTOUT FOR EXAMPLE 1-4.2

DATA REVIEW	PROGRAM OUTPUT
5. branch #	0.10 freq, Hz
-1. 20 resistive part *	-267.18 phase, °
0.159155 reactive part **	-65.99 gain, dB
	199.01 Re Z _{in} , Ω
	-9.80 Im Z _{in} , Ω
4.	
0.	
0.	0.13
	-266.46
3.	-63.97
-1. 20	198.44
-0.00159155	-12.27
2.	
-100.	0.16
-0.00159155	-265.57
	-61.94
1.	197.55
-1. 20	-15.30
0.	
0.	0.20
100.	-264.47
0.	-59.89
	196.17
	-18.99
	0.25
	-263.13
	-57.82
	194.06
	-23.38
	0.32
	-261.53
	-55.70
	190.91
	-28.43

References and Equation Derivation

The algorithm is completely described in the program description section. This particular analysis method is widely referenced. The earliest reference known to the author is T.R. Bashkow [4].

Program Listing I

```

001 *LBLA LOAD RESISTOR VALUE
002 GSB5 odd or even branch?
003 F0? if odd numbered branch,
004 1/X form G = -1/R
005 F0? form G = -1/R
006 CHS
007 STO1 store value
008 RCLI recall branch # to display
009 RTN return control to keyboard
010 *LBLC LOAD CAPACITOR VALUE
011 CHS change sign of entry
012 *LBLD LOAD INDUCTOR VALUE
013 GSB5 odd numbered branch?
014 F0? change sign of entry if
015 CHS branch number is odd
016 P2S indirectly store reactive
017 STO1 element values
018 P2S
019 DSZI decrement branch number
020 CF3 clr flag 3 (a NOP statement)
021 RCLI recall branch number
022 GT07 goto space and return
023 *LBLD LOAD START FREQUENCY
024 ST08
025 GT07
026 *LBLD LOAD FREQUENCY INCREMENT
027 ST09
028 GT07
029 *LBLA LOAD NUMBER OF NODES
030 ST0E store number of nodes
031 *LBL4 initialization routine
032 EEX
033 STOA  $E_n = 1 + j0$ 
034 CLX
035 STOB
036 STOC
037 STOD  $I_{2n} = 0 + j0$ 
038 RCLE
039 ENT1 calculate and store
040 + highest branch number
041 EEX
042 - Br# = 2(# nodes) - 1
043 STOI
044 CF3 clear data entry flag and
045 GT07 goto space and return
046 *LBLB SET LINEAR SWEEP
047 CF1
048 CLX place "zero" in display
049 GT07 goto space and return
050 *LBLc SET LOGARITHMIC SWEEP
051 SF1
052 EEX
053 *LBL7 space and return subroutine
054 SPC
055 RTN
056 *LBLd INPUT DATA REVIEW
057 GSB4 initialize
058 *LBL8 review loop start
059 GSB5 odd numbered branch?
060 RCLI recall and print branch #
061 PRTX
062 RCLI recall branch R or G
063 F0? if odd branch (flag 0 set)
064 1/X form -1/R(1)
065 CHS
066 CHS
067 PRTX print branch resistance
068 P2S
069 RCLI recall branch L or C
070 P2S
071 F0? change sign if branch odd
072 CHS
073 PRTX print L or -C
074 SPC
075 F3? test for loop exit
076 RTN
077 SF3 decrement index register
078 DSZI and SF3 if index is zero
079 CF3
080 GT08
081 *LBLd LNAP ANALYSIS START
082 GSB4 goto initialization
083 *LBL9 analysis loop start
084 GSB3 recall shunt branch elements
085 RCLB recall complex node voltages
086 RCLA and execute complex multiply
087 GSB1
088 RCLD recall previous complex
089 RCLC branch current and perform
090 GSB2 complex addition
091 STOC
092 X2Y store complex branch
093 STOD currents for present branch
094 X2Y
095 CF0 decrement index register
096 DSZI & SF0 if index is zero
097 SF0
098 GSB3 recall series branch elts
099 GSB1 execute complex multiply
100 RCLB recall complex node voltage
101 RCLA and add to branch voltage
102 GSB2
103 X2Y store new complex node
104 STOB voltage
105 X2Y
106 STOA
107 DSZI decrement branch number and
108 F0? test for loop exit
109 GT09
110 +P convert to magnitude & angle

```

REGISTERS

0 R0	1 G1	2 R2	3 G3	4 R4	5 G5	6 R6	7 G7	8 start freq	9 freq increment
S0 -C0 or L0	S1 C1 or -L1	S2 C2 or L2	S3 C3 or -L3	S4 C4 or L4	S5 C5 or -L5	S6 C6 or L6	S7 C7 or -L7	S8 cmplx	S9 cmplx
-C0 or L0	C1 or -L1	C2 or L2	C3 or -L3	C4 or L4	C5 or -L5	C6 or L6	C7 or -L7	multiply	multiply

A Re Ek

B Im Ek

C Re Ik

D Im Ik

E number of nodes

F index

Program Listing II

```

111 STOA temporarily store |Ein|_
112 LOG convert to dB
113 2
114 0
115 X
116 RCL8
117 RND recall and print present
118 PRTX analysis frequency
119 R↓
120 CHS recover and print -dB
121 RND
122 PRTX
123 R↓ recover phase angle
124 STOB temporarily store |Ein|_
125 CHS
126 RND print -(phase angle)
127 PRTX
128 RCLD recall I0
129 RCLC
130 +P
131 RCLA
132 X2Y
133 =
134 X2Y perform complex division:
135 RCLB
136 X2Y  $Z_{in} = E_{in}/I_0$ 
137 -
138 X2Y
139 +R
140 PRTX print Re Zin
141 X2Y
142 PRTX print Im Zin
143 PSE
144 RCL9 recall frequency increment
145 F1?
146 STx8 use multiplicative increment
147 F1? if logarithmic sweep selected
148 GT0e
149 ST+8 use additive increment if
150 GT0e linear sweep selected
151 *LBL1 complex multiplication
152 P2S  $(a+jb)(c+jd) = e+jf$ 
153 ST08 a
154 ST09 a
155 R↓
156 ENT↑
157 R↓
158 R↓ c
159 STx8 ac in register 8
160 R↓ d
161 STx9 ad in register 9
162 X bd in stack
163 ST-8 ac - bd in register 8
164 R↓
165 X bc in stack
166 ST+9 ad + bc in register 9
167 RCL9 rcl f = ac + bc
168 RCL8 rcl e, ac - bd - e
169 P2S restore register order
170 RTN return to main program
171 *LBL2 complex add subroutine
172 X2Y
173 R↓
174 +
175 R↓
176 +
177 R↓
178 RTN return to main program
179 *LBL3 complex recall subroutine
180 RCL8 calculate  $\omega = 2\pi f$ 
181 Pi
182 X
183 ENT↑
184 +
185 P2S
186 RCLI recall resistive element
187 P2S element, b_x, and form
188 X  $2\pi f b_x$ 
189 X0?
190 1/X form reciprocal if b_x < 0
191 RCLI recall resistive element
192 X0? if < 0, perform parallel
193 GT03 series conversion
194 RTN return to main program
195 *LBL3 parallel series conversion
196 ABS conductance = resistance
197 1/X
198 X2Y
199 1/X susceptance = reactance
200 X2Y
201 +P
202 1/X calculate complex inverse
203 +R
204 RTN return to main program
205 *LBL5 odd or even branch subr
206 RCLI
207 2 form 0 if branch even
208 = or 0.5 if branch odd
209 FRC
210 SF0
211 X=0? set flag 0 if branch is odd
212 CF0
213 R↓ restore x register in stack
214 RTN return to main program

```

LABELS					FLAGS	SET STATUS		
A load R	B load L	C load C	D load start freq increment	E load freq increment	odd branch	FLAGS	TRIG	DISP
a load # of nodes	b set linear sweep	c set log sweep	d start data revu	e start analysis	1 log/lin	0 ON	DEG	FIX
0	1 complex multiply	2 complex add	3 complex recall	4 initialize	2	1 OFF	GRAD	SCI
5 odd/even branch	6 series parallel	7 log sweep	8	9	3 data entry	2 RAD	RAD	ENG n-3

1-4 TI-59 PROGRAM LISTING

000	76	LBL	LOAD RESISTOR VALUE	050	44	SUM	
001	11	R		051	56	56	
002	42	STO	temporarily store	052	43	RCL	recall reactive
003	57	57		053	58	58	element to display
004	71	SBR	set flag 0 if branch number is odd	054	92	RTN	
005	04	04		055	76	LBL	LOAD SWEEP STARTING FREQ
006	18	18		056	14	D	
007	43	RCL	recall entry	057	42	STO	
008	57	57		058	55	55	
009	87	IFF	if odd branch, form G = -1/R	059	92	RTN	
010	00	00		060	76	LBL	LOAD FREQ INCREMENT
011	00	00		061	15	E	
012	18	18		062	42	STO	
013	72	ST*	store R or G	063	54	54	
014	59	59		064	92	RTN	
015	43	RCL	recall resistor value to display	065	76	LBL	SELECT LINEAR SWEEP
016	57	57		066	17	B'	
017	92	RTN		067	22	INV	
018	94	+/-	routine for G = -1/R	068	86	STF	
019	35	1/X		069	01	01	
020	61	GTO		070	00	0	display 0
021	00	00		071	92	RTN	
022	13	13		072	76	LBL	SELECT LOG SWEEP
023	76	LBL	LOAD CAPACITOR VALUE	073	18	C'	
024	13	C		074	86	STF	
025	54	>		075	01	01	
026	94	+/-	change sign and temporarily store	076	01	1	display 1
027	42	STO		077	92	RTN	
028	58	58		078	76	LBL	INPUT DATA REVIEW
029	76	LBL	LOAD INDUCTOR VALUE	079	19	D'	
030	12	B		080	71	SBR	
031	42	STO		081	03	03	initialize
032	58	58		082	80	80	
033	71	SBR	set flag 0 if branch number is odd	083	71	SBR	
034	04	04		084	04	04	set flag 0 if branch number is odd
035	18	18		085	18	18	
036	43	RCL	recall entry	086	53	<	
037	58	58		087	43	RCL	recall branch number
038	22	INV	if branch number is odd, change the sign of the entry	088	59	59	
039	87	IFF		089	75	-	
040	00	00		090	01	1*	
041	00	00		091	00	0	
042	44	44		092	54	>	
043	94	+/-		093	98	ADV	
044	72	ST*	store reactive element	094	71	SBR	
045	56	56		095	04	04	print or display branch number
046	01	1	decrement index of resistive and reactive storage registers	096	66	66	
047	94	+/-		097	73	RC*	recall resistive element
048	44	SUM		098	59	59	
049	59	59		099	22	INV	

This translation was provided by Mr. Walter Ware

1-4 TI-59 PROGRAM LISTING

100	87	IFF	if odd branch, form R = -1/G	150	03	03	
101	00	00		151	68	NOP	
102	01	01		152	68	NOP	
103	06	06		153	68	NOP	
104	35	1/X		154	61	GTO	
105	94	+/-		155	00	00	goto loop start
106	71	SBR		156	83	83	
107	04	04	display or print resistance	157	29	CP	complex recall subr
108	66	66		158	53	(
109	73	RC*	recall reactive element	159	43	RCL	
110	56	56		160	55	55	calculate w=2πf
111	22	INV	if odd branch, change sign	161	65	X	
112	87	IFF		162	89	†	
113	00	00		163	65	X	
114	01	01		164	02	2	
115	17	17		165	65	X	recall reactive branch
116	94	+/-		166	73	RC*	element value and
117	71	SBR		167	56	56	form branch impedance
118	04	04	print or display L or C	168	54)	
119	66	66		169	77	GE	
120	87	IFF		170	01	01	if impedance is negative, form reciprocal
121	03	03	test for loop exit	171	73	73	
122	01	01		172	35	1/X	
123	47	47		173	42	STO	store impedance
124	86	STF		174	58	58	
125	03	03	decrement indirect storage register indices	175	73	RC*	
126	01	1		176	59	59	recall branch resistance and store
127	94	+/-		177	42	STO	
128	44	SUM		178	57	57	
129	56	56		179	22	INV	
130	44	SUM		180	77	GE	if resistance negative, perform series=parallel conversion
131	59	59		181	01	01	
132	43	RCL		182	84	84	
133	09	09		183	92	RTN	
134	85	+	set t = 10	184	43	RCL	series=parallel conversion subroutine
135	01	1		185	57	57	
136	95	=		186	50	I×I	
137	32	X*T		187	35	1/X	conductance=Resistance
138	43	RCL		188	32	X*T	
139	59	59	recall register index	189	43	RCL	
140	22	INV		190	58	58	
141	67	E0	if index = 10, execute one more loop	191	35	1/X	susceptance=reactance
142	01	01		192	94	+/-	
143	48	48		193	22	INV	
144	61	GTO		194	37	P/R	
145	00	00		195	94	+/-	calculate complex inverse
146	83	83		196	32	X*T	
147	92	RTN		197	35	1/X	
148	22	INV	clear flag 3	198	32	X*T	
149	86	STF		199	37	P/R	

1-4

TI-59 PROGRAM LISTING

200	42	STD	temporarily store immittance	250	59	59
201	58	58		251	71	SBR
202	32	XIT		252	01	01
203	42	STD	temporarily store resistance or cond	253	57	57
204	57	57		254	43	RCL
205	92	RTN	return to main program	255	57	57
206	76	LBL	LNAP ANALYSIS START	256	42	STD
207	10	E ¹		257	01	01
208	58	FIX		258	43	RCL
209	02	02	set display mode	259	58	58
210	98	ADV	advance paper	260	42	STD
211	98	ADV		261	02	02
212	71	SBR		262	43	RCL
213	03	03	initialize	263	51	51
214	83	83		264	42	STD
215	71	SBR		265	03	03
216	01	01	recall shunt branch	266	43	RCL
217	57	57		267	52	52
218	43	RCL		268	42	STD
219	57	57	recall complex node voltage and execute complex multiply to obtain complex branch current	269	04	04
220	42	STD		270	36	PGM
221	01	01		271	04	04
222	43	RCL		272	13	C
223	58	58		273	43	RCL
224	42	STD		274	01	01
225	02	02		275	44	SUM
226	43	RCL		276	49	49
227	49	49		277	43	RCL
228	42	STD		278	02	02
229	03	03		279	44	SUM
230	43	RCL		280	50	50
231	50	50		281	01	1
232	42	STD		282	94	+/-
233	04	04		283	44	SUM
234	36	PGM		284	56	56
235	04	04		285	44	SUM
236	13	C		286	59	59
237	43	RCL		287	43	RCL
238	01	01	recall previous complex branch current, perform complex add and store result	288	09	09
239	44	SUM		289	32	XIT
240	51	51		290	43	RCL
241	43	RCL		291	59	59
242	02	02		292	67	EQ
243	44	SUM		293	02	02
244	52	52		294	98	98
245	01	1		295	61	GTO
246	94	+/-	decrement indirect recall indices	296	02	02
247	44	SUM		297	15	15
248	56	56		298	43	RCL
249	44	SUM		299	55	55

1-4

TI-59 PROGRAM LISTING

300	71	SBR	print or display frequency	350	04	04
301	04	04		351	66	66
302	66	66		352	43	RCL
303	43	RCL		353	02	02
304	49	49	recall complex input voltage	354	71	SBR
305	32	XIT		355	04	04
306	43	RCL		356	66	66
307	50	50		357	43	RCL
308	22	INV		358	54	54
309	37	P/R	convert to polar	359	97	IFF
310	94	+/-		360	01	01
311	42	STD	change sign of angle and store	361	03	03
312	05	05		362	68	68
313	71	SBR	print or display angle of network transmission function	363	44	SUM
314	04	04		364	55	55
315	66	66		365	61	GTO
316	32	XIT	calculate 20 log of network transmission function magnitude	366	02	02
317	28	LNG		367	06	06
318	94	+/-		368	49	PRD
319	65	X		369	55	55
320	02	2		370	61	GTO
321	00	0		371	02	02
322	95	=		372	06	06
323	42	STD		373	76	LBL
324	06	06	LOAD NUMBER OF NODES	374	16	A ¹
325	71	SBR		375	71	SBR
326	04	04	print or display dB response	376	04	04
327	66	66		377	75	75
328	43	RCL		378	42	STD
329	49	49		379	53	53
330	42	STD	recall complex network input voltage	380	09	9
331	01	01		381	42	STD
332	43	RCL		382	09	09
333	50	50		383	53	C
334	42	STD		384	43	RCL
335	02	02		385	53	53
336	43	RCL		386	65	X
337	51	51		387	02	2
338	42	STD	recall complex network input current	388	75	-
339	03	03		389	01	1
340	43	RCL		390	85	+
341	52	52		391	01	t
342	42	STD		392	00	0
343	04	04		393	54)
344	36	PGM		394	42	STD
345	04	04	perform complex division	395	59	59
346	18	C*		396	85	+
347	43	RCL		397	01	1
348	01	01	print or display Re Z _{in}	398	00	0
349	71	SBR		399	54)

1-4

TI-59 PROGRAM LISTING

400	42	STO	450	00	0
401	56	56	451	00	0
402	01	1	452	00	0
403	42	STO	453	00	0
404	49	49	454	00	0
405	00	0	455	00	0
406	42	STO	456	00	0
		$E_n = 1 + j0$	457	00	0
407	50	50	458	00	0
408	42	STO	459	00	0
409	51	51	460	00	0
410	42	STO	461	00	0
411	52	52	462	00	0
412	22	INV	463	00	0
413	86	STF	464	00	0
414	03	03	465	00	0
415	43	RCL	466	22	INV
416	53	53	467	87	IFF
417	92	RTN			print or R/S routine
418	29	CP	468	05	05
		odd or even branch subr	469	04	04
419	22	INV	470	73	73
420	86	STF	471	91	R/S
421	00	00	472	92	RTN
422	43	RCL	473	99	PRT
423	59	59	474	92	RTN
424	55	+	475	69	OP
425	02	2	476	08	08
426	54)			printer sense routine
427	22	INV	477	86	STF
428	59	INT	478	05	05
429	67	EQ	479	92	RTN
430	04	04			
431	34	34			
432	86	STF			
433	00	00			
434	92	RTN			
435	00	0			
436	00	0			unused program memory
437	00	0			
438	00	0			
439	00	0			
440	00	0			
441	00	0			
442	00	0			
443	00	0			
444	00	0			
445	00	0			
446	00	0			
447	00	0			
448	00	0			
449	00	0			

REGISTER ALLOCATIONS FOR TI-59

register number	contents
0	
1	Re
2	Im
3	Re
4	Im
5	xmsn fcn magnitude
6	
7	
8	
9	loop counter
10	
11	
12	
13	
14	real immittance storage
15	
16	
17	
18	
19	
20	
21	
22	
23	
24	
25	
26	
27	
28	
29	
30	
31	
32	
33	
34	
35	
36	
37	
38	
39	
40	

PROGRAM 1-5 LC-LNAP, LC LADDER NETWORK ANALYSIS PROGRAM.

Program Description and Equations Used

This program evaluates the frequency response and input impedance of a resistively terminated lossless (LC) ladder network having up to seven branches. The frequency response is provided as magnitude (dB) and phase (degrees, radians, or grads), and the input impedance is provided as real and imaginary parts.

The input impedance is the impedance seen by the voltage generator in the source. It is more common to calculate the input impedance at the input terminals of the lossless ladder network, but this way was not implemented because program steps are not available for the coding to recall the source resistor value and subtract it from the real part of the input impedance. If the program feature of allowing the number of branches to be entered via a user definable key (key "a") is sacrificed, and the number of branches is stored into register E, then the additional coding for calculating the network input impedance can be added to the program by deleting steps 028 and 029 and adding "RCL0," "-" after step 097 (099 before deletions).


The frequency response and input impedance evaluation frequency can be incremented in either a linear manner using an additive increment, or a logarithmic manner using a multiplicative increment. Each branch of the network may contain an inductor (L), a capacitor (C), a series LC network, or a parallel LC network. All element values and interconnection topology are stored, and can be reviewed at any time to check or correct the component values or interconnection.

Because of the available number of HP-67/97 registers, the number of branches cannot exceed seven. The TI-59 can accommodate data for 20 branches. Elements that inhibit signal flow through the network are not allowed, and will cause the program execution to halt displaying "Error." Examples of elements that inhibit signal flow are single shunt resistors or inductors that have zero value, or series capacitors in series

User Instructions


branches that have zero value.

The algorithm used by this program is the same as used in Program 1-4 where 1 volt is assumed at the network output, and the required input voltage is calculated. In this program, the branch immittances (impedances or admittances) are purely imaginary, and the branch numbers start with branch #1 instead of branch #0. This changes all indices by +1. The difference is necessary to let the DSZ instruction operation allow the source resistance to be added to branch #1 with minimum coding. The load resistance is combined with the last branch immittance. If the number of branches is odd, the last branch consists of the load resistor alone.

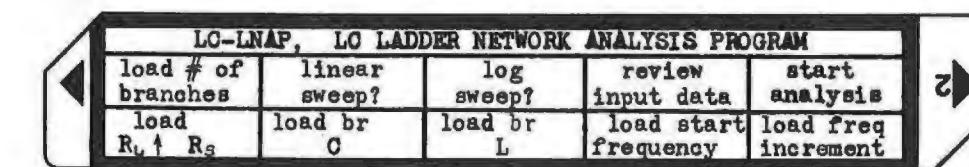

STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
1	Load both sides of magnetic card			
2	Load the number of branches in the network	# branches	f A	
3	Enter the load and source resistances in ohms	R _L R _S	ENT↑ A	
4	Load branch capacitance: If a parallel tank in a series branch, or a series tank in a shunt branch, change the sign of the mantissa in the capacitor value	$\pm C_{branch}$ (farads)	B	
	Start loading network capacitors (and inductors) from the highest numbered branch (load resistor end)			
5	Load branch inductance: If a parallel tank in a series branch, or a series tank in a shunt branch, change the sign of the mantissa in the inductor value	$\pm L_{branch}$ (henries)	C	
6	Input data review (optional) Negative element values indicate series tanks in shunt branches, or parallel tanks in series branches		f D	R _{load} space highest branch # $\pm C$ $\pm L$ space :
7	Select frequency sweep mode: a) linear sweep b) logarithmic sweep		f B f C	R _{source}
8	Load start frequency for sweep in hertz	f _{start}	D	

User Instructions

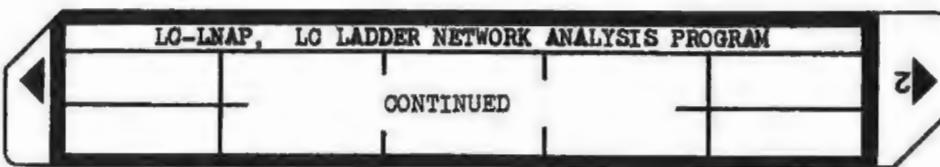

STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
9	Load frequency increment If linear sweep, the increment is added to the present frequency to obtain the next frequency. If logarithmic sweep, the increment is multiplied by the present frequency to obtain the next frequency.	fincr	E	
10	Start analysis * The phase units will be in whatever trig mode the calculator is set. The trig mode is at the discretion of the user.		f E	freq (Hz) gain (dB) phase*() Re Zin, Ω Im Zin, Ω space ⋮ ⋮
11	Stop analysis: Press R/S when the printer starts to print. Pressing R/S at other times may leave the registers interchanged. To determine if an interchange has occurred, goto step 6 and review input data. If L and C values are reversed, execute a P=S instruction from the keyboard.			

Example 1-5.1

Bartlett's bisection theorem [53], [56], [57] has been applied to an equally terminated (1000 ohm) third order Butterworth bandpass filter with 10 kHz center frequency and 1 kHz bandwidth to produce the unequally terminated LC filter shown in Fig. 1-5.1. The source resistance is 1000 ohms and the load resistance is 10000 ohms. Determine the frequency response and input impedance of this LC network over a frequency range of 9000 Hz to 10900 Hz using a linear sweep with 100 Hz steps.

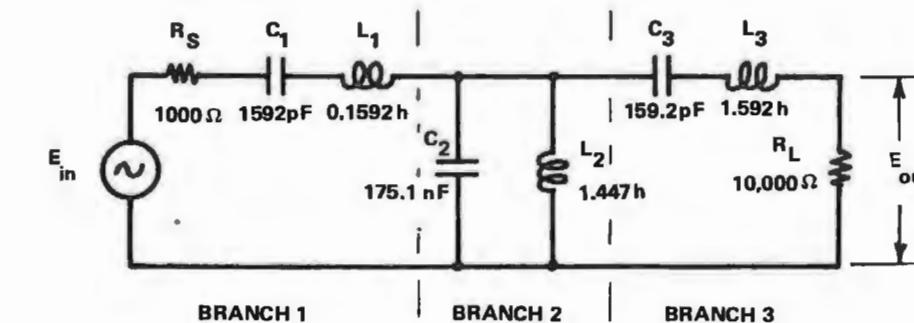


Figure 1-5.2 Network for Example 1-5.1.

PROGRAM INPUT	DATA REVIEW
3.00 GSBa number of branches	GSBd start review
10000. ENTT RL	10.00+03 *** load resistance
1000. GSBA RS	3.000+00 *** branch number
159.2-12 GSBB C3	159.2-12 *** C
1.592 GSBC L3	1.592+00 *** L
.1751-06 GSBB C2	2.000+06 *** branch number
1.447-03 GSBC L2	175.1-09 *** C
1.447-03 GSBC L2	1.447-03 *** L
1592.-12 GSBB C1	1.000+00 *** branch number
.1592 GSBC L1	1.592-09 *** C
.1592 GSBC L1	159.2-05 *** L
GSBb linear sweep	1.000+03 *** source resistance
9000.00 GSBD start freq, Hz	
100.00 GSBE freq incr, Hz	

HP-97 PRINTOUT FOR EXAMPLE 1-5.1

GSBe start analysis

PROGRAM OUTPUT

9000.00	freq, Hz	9500.00	10000.00	10500.00
-20.29	gain, dB	-4.14	-0.83	-3.58
-146.92	phase, °	138.09	-0.48	-132.20
1003.54	Re Z _{in} , Ω	1042.21	10994.89	1048.18
-1666.97	Im Z _{in} , Ω	-93.28	-227.42	10.31
9100.00		9600.00	10100.00	10600.00
-17.44		-1.93	-0.83	-6.35
-154.43		106.39	-23.45	-157.06
1005.32		1083.75	2916.29	1027.54
-1391.66		364.31	-3831.85	363.73
9200.00		9700.00	10200.00	10700.00
-14.32		-1.04	-0.84	-9.45
-164.23		74.86	-47.28	-175.59
1008.28		1186.21	1504.60	1016.80
-1105.20		979.39	-1965.91	668.18
9300.00		9800.00	10300.00	10800.00
-10.93		-0.85	-1.01	-12.47
-177.51		47.27	-73.45	170.95
1013.48		1498.05	1195.73	1010.80
-801.44		1951.68	-1020.61	941.35
9400.00		9900.00	10400.00	10900.00
-7.40		-0.83	-1.76	-15.27
163.89		22.71	-102.68	160.95
1023.10		2964.18	1091.62	1007.25
-470.17		3870.77	-426.27	1192.23

Example 1-5.2

The filter shown in Fig. 1-5.3 is a 5th order, 30° modular angle, 50% reflection coefficient elliptic filter designed for 10 kHz cutoff frequency and 1000 ohm impedance level. This example shows how dummy elements are inserted to place the filter in proper ladder format for this program. The frequency response and input impedance are calculated with the analysis frequency being logarithmically swept from 1 kHz to 100 kHz using 10 points per decade.

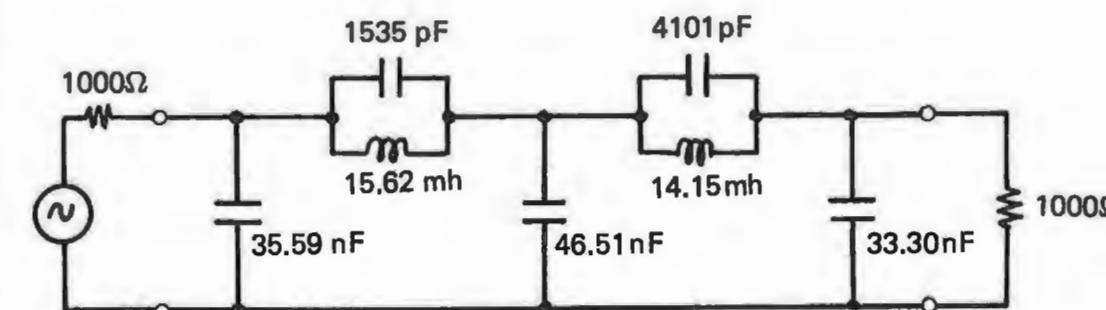


Figure 1-5.3 Elliptic filter for Example 1-5.2.

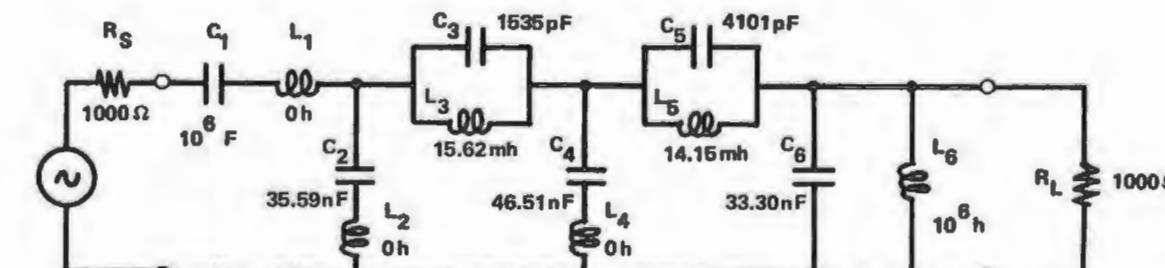


Figure 1-5.4 Network of Fig. 1-5.3 redrawn with dummy elements to place in proper ladder format for program input.

HP-97 PRINTOUT FOR EXAMPLE 1-5.2

PROGRAM INPUT	DATA REVIEW
6.00 GSBo # of branches	GSBo start review
1000. ENT† enter load R	1.000+03 *** load resistance
GSBA enter source R	
.03330-06 GSBB 06	6.000+00 *** branch number
1.+06 GSBC L6 (dummy)	33.30-09 *** C
	1.000+06 *** L
-4101.-12 GSBB 05 (note minus)	5.000+00 *** branch number
-14.15-03 GSBC L5	-4.101-09 *** C
	-14.15-03 *** L
-.04651-06 GSBB 04	4.000+00 *** branch number
0. GSBC L4 (dummy)	-46.51-09 *** C
	0.000+00 *** L
-1535.-12 GSBB 03 (note minus)	
-15.62-03 GSBC L3	3.000+00 *** branch number
" "	-1.535-09 *** C
	-15.62-03 *** L
-.03559-06 GSBB 02	
0. GSBC L2 (dummy)	2.000+00 *** branch number
	-35.59-09 *** C
1.+06 GSBB 01 (dummy)	0.000+00 *** L
0. GSBC L1 (dummy)	
	1.000+00 *** branch number
	1.000+06 *** C
GSBo log sweep	0.000+00 *** L
1000. GSBD start freq	1.000+03 *** source resistance
.10 10 ^x increment for	
GSBE 10 points per decade	

HP-97 PRINTOUT FOR EXAMPLE 1-5.2

DSP3 set display format
 GSBe start analysis

PROGRAM OUTPUT
1000.000 freq, Hz 3162.278
-6.304 gain, dB -7.265
-25.492 phase, ° -71.409
1731.945 Re Z _{in} , Ω 1341.972
-354.815 Im Z _{in} , Ω -144.944
1258.925 3981.072
-6.445 -7.140
-31.679 -87.812
1641.443 1354.476
-367.449 -16.643
1584.893 5011.872
-6.636 -6.543
-39.149 -111.901
1545.329 1510.069
-354.383 144.638
1995.262 6309.573
-6.872 -6.035
-48.061 -151.933
1455.184 2050.032
-312.318 -105.785
2511.886 7943.282
-7.114 -7.176
-58.642 154.808
1383.210 1466.092
-242.073 -532.050
100000.000
-78.338
-85.064
1000.000
-43.101

Program Listing I

```

001 *LBLP LOAD RL+Rs
002 ST00 store Rs
003 R↓
004 P+S
005 ST00 store RL
006 P+S
007 GT07 goto space and return
008 *LBLC LOAD BRANCH INDUCTANCE
009 CHS indicate inductance by chs
010 P+S
011 GSBE interchange registers and
012 P+S goto capacitor load routine
013 DSZI decrement branch number
014 RCLI decrement and recall branch
015 ST07 goto space and return
016 *LBLB LOAD BRANCH CAPACITANCE
017 GSBS odd/even branch?
018 F0? change sign of entry if
019 CHS branch number is odd
020 ST01 store entry
021 RTN return control to keyboard
022 *LBLD LOAD START FREQUENCY
023 ST08
024 GT07
025 *LBLB LOAD FREQUENCY INCREMENT
026 ST09
027 GT07
028 *LBLa LOAD NUMBER OF BRANCHES
029 ST0E
030 *LBL4 initialization routine
031 EEX
032 ST0A  $E_n = 1 + j0$ 
033 CLX
034 ST0B
035 ST0C
036 ST0D  $I_{2n+1} = 0 + j0$ 
037 RCLC set index to
038 ST0I highest branch number
039 SF2 initialize flags
040 CF3
041 GT07 goto space and return
042 *LBL6 SELECT LINEAR SWEEP
043 CF1
044 GT07
045 *LBLc SELECT LOGARITHMIC SWEEP
046 SF1
047 GT07
048 *LBLd START ANALYSIS
049 GSB4 initialize
050 *LBL9 analysis loop start
051 GSB3 recall shunt branch y
052 RCLB recall complex node voltage
053 RCLA
054 GSB1 calculate shunt branch I
055 RCLC recall next higher (series)
056 RCLD branch current

```

REGISTERS

⁰ R _s	¹ C ₁	² C ₂	³ C ₃	⁴ C ₄	⁵ C ₅	⁶ C ₆	⁷ C ₇	spresent	freq
SO R _L	S ₁ L ₁	S ₂ L ₂	S ₃ L ₃	S ₄ L ₄	S ₅ L ₅	S ₆ L ₆	S ₇ L ₇	frequency	increment
A Re E _k	B Im E _k	C Re I _j	D Im I _j	E number of branches	F index				

```

057 GSB2 add complex branch currents
058 ST0C store next lower branch
059 XZY current (complex)
060 ST0D
061 DSZI decrement branch number
062 GSB3 recall series branch Z
063 CLX
064 RCL0
065 CF0
066 DSZI If branch 1, add
067 SF0 source resistance to
068 F0? branch impedance
069 CLX
070 ENT↑
071 RCLD recall present
072 RCLC branch current
073 GSB1 calculate branch voltage
074 RCLA recall next higher
075 RCLB branch voltage
076 GSB2 add branch voltages
077 ST0A
078 XZY store next lower
079 ST0B node voltage
080 F0? test for loop exit
081 GT09
082 XZY
083 +P convert to magnitude & angle
084 LOG
085 2
086 0 calculate magnitude in dB
087 X
088 RCL0 recall present frequency
089 SF0 indicate sign change in p/o
090 GSB0 go sub printout (p/o) routine
091 RCLD
092 CHS
093 RCLC recall branch 1 current ( $I_0$ )
094 +P and form complex inverse
095 1/X
096 +R
097 RCLB recall node 0 voltage ( $E_{in}$ )
098 RCLA
099 GSB1 perform complex multiply
100 PRTX print Re  $Z_{in}$ 
101 XZY
102 PRTX print Im  $Z_{in}$ 
103 RCL9 recall frequency increment
104 F1?
105 STx8 multiply present frequency
106 F1? by increment if log sweep
107 GT0e
108 ST+8 add increment to present
109 GT0e frequency if linear sweep
110 *LBLd INPUT DATA REVIEW
111 GSB4 initialize registers & flags
112 P+S

```

Program Listing II

```

113 RCL0
114 P+S
115 PRTX
116 *LBL8 data review loop start
117 GSB5 odd/even branch?
118 P+S
119 RCLi recall branch inductance
120 P+S
121 CHS
122 RCLi recall branch capacitance
123 PCLi recall branch number
124 SPC
125 GSB0 go sub printout routine
126 DSZI decrement branch number
127 GT08 and exit at branch 0
128 RCL0
129 SPC
130 PRTX source resistance
131 *LBL7 space and return subroutine
132 SPC
133 RTN
134 *LBL0 output subroutine
135 PRTX print x register contents
136 GSB0 print y register contents
137 *LBL0 print z register contents
138 R↓
139 F0?
140 CHS if odd branch, change sign
141 PRTX
142 RTN return to subroutine call
143 *LBL1 complex multiplication
144 P+S  $(a+jb)(c+jd) = e+jf$ 
145 ST08 a
146 ST09 a
147 R↓ b
148 ENT↑ b
149 R↓ b
150 R↓ c
151 STx8 ac
152 R↓ d
153 STx9 ad
154 x bd
155 ST-8 ac - bd = e
156 R↓ b
157 x bc
158 ST+9 ad + bd = f
159 RCL9 recall f
160 RCL8 recall e
161 P+S
162 RTN return to subroutine call
163 *LBL2 complex add:  $(bt+ctd) + (a+jb) + (c+jd) = e+jf$ 
164 R↓  $(a+jb) + (c+jd) = e+jf$ 
165 + a + c = e
166 R↓
167 + b + d = f
168 R↓

```

LABELS

A Load RL+Rs	B load C _i	C load L _i	D load start freq	E load freq incr	F odd br
# of branches	b linear sweep	c log sweep	d data review	e start analysis	1 log swp
0 multiple uses	2 complex multiply	3 complex add	4 complex recall	2 first time thru loop	3 initialize thru loop
5 odd/even branch	6 space & return	7 input data loop	8 input analysis loop	9	10

FLAGS

FLAGS	TRIG	DISP
ON OFF	DEG GRAD RAD	FIX SCI ENG
0	■ ■ ■	■ ■ ■
2	■ ■ ■	■ ■ ■
3	■ ■ ■	■ ■ ■

SET STATUS

**PROGRAM 1-6 EQUIVALENT INPUT NOISE OF AN AMPLIFIER WITH
GENERALIZED INPUT COUPLING NETWORK**

Program Description and Equations Used

When low noise amplifiers are designed, the amplifier equivalent current and voltage noise densities (noise in a 1 Hz band), and the coupling network noise sources, response, and impedance behavior must be considered. This program calculates the total noise voltage density that is reflected to the amplifier input which is coupled to a sensor by means of a transformer (Fig. 1-6.1).

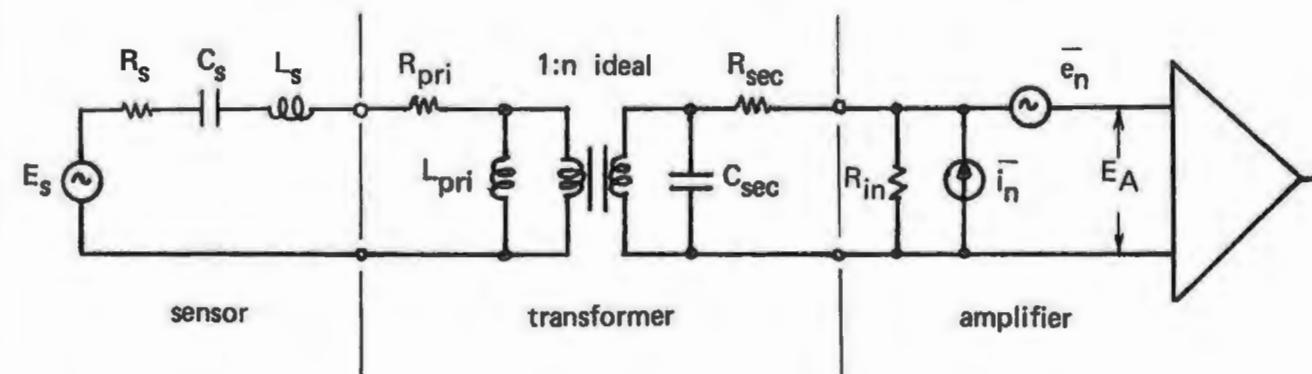


Figure 1-6.1 Generalized input coupling network.

The transformer model includes the turns ratio (1:n), the primary and secondary resistances (R_{pri} and R_{sec}), the primary inductance (L_{pri}), and the secondary capacitance (C_{sec}). The coupling network noise sources include: the thermal noise densities (Johnson noise) of the transformer primary and secondary resistances and of the source resistance, the amplifier equivalent voltage noise density (\bar{e}_n), and the equivalent noise voltage density generated by the amplifier current noise density (\bar{i}_n) flowing through the coupling network impedance presented to the amplifier input.

User Instructions


The noise voltage density of each noise source is reflected to the amplifier input through the network gain (at the analysis frequency) from the noise source location to the amplifier input. The total noise reflected to the amplifier input is calculated from the root-sum-squared (RSS) values of the individual contributions.

The sensor is represented by a voltage source (E_s) and a series LRC network (L_s , R_s , and C_s). The inductance may be set to zero if not needed, and the capacitor may be set to 10^{50} farads to remove its contribution. The sensor resistance may be zero if the transformer primary resistance is not zero and vice-versa.

The equivalent circuit can be modified to reflect the transformer secondary capacitance to the primary if desired by deleting steps 059, 060, and 061 in the program. The primary capacitance is now loaded in step 2f of the users' instructions. This modification allows piezoelectric transducer elements to be modeled as the source. R_{pri} is set to zero, and the transformer primary capacitance is used to represent the clamped capacity of the piezoelectric element.

If the transformer is not wanted in the circuit, the turns ratio should be set to one.

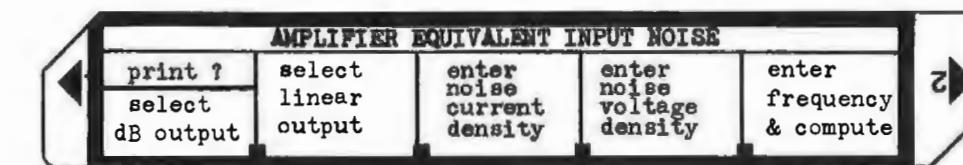The equations are derived using nodal analysis, and the user is referred to the section following Example 1-6.2 for details.



STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
1	Load both sides of the program card			
2	Load network element values a) sensor resistance, ohms b) sensor capacitance, farads c) sensor inductance, henries d) transformer primary resistance, Ω e) transformer primary inductance, h f) xfmr secondary capacitance, farads g) xfmr secondary resistance, ohms h) amplifier input resistance, ohms i) transformer turns ratio	R_s C_s L_s R_{pri} L_{pri} C_{sec} R_{sec} R_{in} n	<input type="button" value="STO 0"/> <input type="button" value="STO 1"/> <input type="button" value="STO 2"/> <input type="button" value="STO 3"/> <input type="button" value="STO 4"/> <input type="button" value="STO 5"/> <input type="button" value="STO 6"/> <input type="button" value="STO 7"/> <input type="button" value="STO 8"/>	
3	Select output mode a) for voltages in dBV and network gain in dB b) for voltages in volts, and network gain as a voltage ratio		<input type="checkbox"/> A <input type="checkbox"/> B	
4	Select print(1) / run-stop (0) option		<input type="checkbox"/> f <input type="checkbox"/> A	0,1
5	Enter amplifier input noise current density $\bar{i}_n, A/\sqrt{Hz}$		<input type="checkbox"/> C	
6	Enter amplifier input noise voltage density $\bar{e}_n, V/\sqrt{Hz}$		<input type="checkbox"/> D	
7	Enter analysis frequency and compute output f, Hz		<input type="checkbox"/> E	gain space \bar{e}_1 \bar{e}_2 \bar{e}_3 \bar{e}_n, amp $\bar{i}_n \cdot Z, amp$ space RSS noise space space
8	Note: All noise voltages are reflected to the amplifier input, i.e., the gain of the network from the noise voltage source to the amplifier input is taken into account.			
	For another case, go back to steps 2 thru 6 as required			

Example 1-6.1

A type 2N4867A low-noise field effect transistor (FET) is to be used as a preamplifier for a piezoelectric hydrophone. A frequency range of 10 Hz to 1000 Hz is to be covered. The hydrophone is operating well below its self-resonant frequency, hence, its equivalent circuit is accurately represented by a 4000 pF capacitor in series with a 10 ohm resistor. To avoid preamplifier overload problems from cable flutter and other subsonic signals, the input resistance of the preamplifier is chosen to provide a 50 Hz low frequency break with the hydrophone capacity. The hydrophone will be coupled to the preamp without using a transformer, therefore a dummy turns ratio of 1:1 will be used in the program. The current and voltage noise densities for the 2N4867A are listed in Table 1-6.1.

Table 1-6.1 Current and voltage noise densities of 2N4867A operating at drain current I_{dss} .

Frequency, Hz	\bar{i}_n , noise A/ $\sqrt{\text{Hz}}$	\bar{e}_n , noise V/ $\sqrt{\text{Hz}}$
10	6×10^{-16}	7.0×10^{-9}
20	6×10^{-16}	5.3×10^{-9}
50	6×10^{-16}	4.1×10^{-9}
100	6×10^{-16}	3.6×10^{-9}
200	6.1×10^{-16}	3.2×10^{-9}
500	6.2×10^{-16}	2.8×10^{-9}
1000	6.3×10^{-16}	2.7×10^{-9}

The HP-97 printout is shown on the next page. Dummy values have been entered for unused components to remove their contribution.

HP-97 PRINTOUT FOR EXAMPLE 1-6.1

PROGRAM INPUT

```

10.0 ST00 sensor resistance
4.09 ST01 sensor capacitance
0.0 ST02 sensor inductance
0.0 ST03 primary resistance
1.+50 ST04 primary inductance
0.0 ST05 secondary capacitance
1.0 ST06 secondary resistance
RCL1
50.0 X
Pi
2.0 X } calculate and store
        } amplifier input
        } resistance for
        } 50 Hz breakpoint
795774.7 *** ST07
1.0 ST08 n, xfmr turns ratio
GSBA select dB/dBV output

```

3.6-09 GSBD \bar{e}_n @ 100 Hz.
100.0 GSBE frequency

-1.0 ***

-188.9 ***

-198.9 ***

-145.9 ***

-168.9 ***

-193.4 ***

-145.9 *** total noise at 100 Hz

6.1-16 GSBC \bar{i}_n @ 200 Hz
3.2-05 GSBD \bar{e}_n @ 200 Hz
200.0 GSBE frequency

-0.3 ***

-168.2 ***

-198.2 ***

-151.2 ***

-169.9 ***

-198.6 ***

-151.1 *** total noise at 200 Hz

6.2-16 GSBC \bar{i}_n @ 500 Hz
2.8-09 GSBD \bar{e}_n @ 500 Hz
500.0 GSBE frequency

0.0 ***

-188.6 ***

-198.0 ***

-158.9 ***

-171.1 ***

-206.2 ***

-158.7 *** total noise at 500 Hz

6.3-16 GSBC \bar{i}_n @ 1000 Hz
2.7-09 GSBD \bar{e}_n @ 1000 Hz
1000.0 GSBE frequency

0.0 ***

-187.9 ***

-197.9 ***

-164.9 ***

-171.4 ***

-212.0 ***

-164.0 *** total noise at 1000 Hz

PROGRAM OUTPUT

```

6.1-16 GSBC  $\bar{i}_n$  @ 10 Hz
7.-09 GSBD  $\bar{e}_n$  @ 10 Hz
10.0 GSBE frequency
-14.1 ***  $A_v$ , network gain, dB
-202.1 ***  $R_s+R_{pri}$  thermal noise, dBV
-212.1 ***  $R_{sec}$  thermal noise, dBV
-139.1 ***  $R_{dn}$  thermal noise, dBV
-163.1 ***  $\bar{e}_n$ , transistor
-186.6 ***  $\bar{i}_n*Z$  equiv noise, dBV
-139.1 *** total noise (RSS), dBV

```

```

5.3-09 GSBD  $\bar{e}_n$  @ 20 Hz *
20.0 GSBE frequency
-8.6 ***
-196.5 *** *  $\bar{i}_n$  is unchanged
from the previous
entry.
-206.5 ***
-139.5 ***
-165.5 ***
-187.1 ***
-139.5 *** total noise at 20 Hz

```

4.1-09 GSBD \bar{e}_n @ 50 Hz
50.0 GSBE frequency

```

-3.0 ***
-198.9 ***
-200.9 ***
-141.9 ***
-167.7 ***
-189.4 ***
-141.9 *** total noise at 50 Hz

```

Example 1-6.1 continued

This example points up one of the problems associated with using the characteristics of the sensor impedance along with the amplifier input resistance to effect frequency shaping. It will be noticed that the dominant source of noise comes from the thermal noise of the input resistor. The low noise characteristics of the input transistor are buried by the input resistor noise contribution.

If the input resistor is made larger, the noise contribution of the input resistor will be less. Although this statement may seem backwards, the logic may be seen by looking at the input resistor and its noise generator as a Norton equivalent source instead of a Thevenin equivalent as is presently used. In this light, one can see that the injected noise current is proportional to $1/\sqrt{R}$. Since other circuit impedances are unchanged, lower injected noise current means lower input resistor noise contribution.

The input resistor noise contribution may also be reduced by lowering the sensor impedance to lower the noise voltage resulting from the input resistor noise current.

To illustrate the above point, the example is rerun using a larger input resistor; 100 megohms is used instead of 796 kilohms. The HP-97 printout for this case is shown on the next page. The noise contribution of the input resistor loses dominance above 500 Hz in this case.

Fortunately, the ocean self noise is greatest at low frequencies, and low noise performance is less critical here.

EXAMPLE 1-6.1 CONTINUED

PROGRAM INPUT

```
100.+06 ST07 store new Rin
PREG print registers to show
               currently stored values
10.00+00 0 sensor resistance
4.000-09 1 sensor capacitance
0.000+00 2 sensor inductance
0.000+00 3 primary resistance
100.0+48 4 primary inductance
0.000+00 5 secondary capacitance
1.000+00 6 secondary resistance
100.0+06 7 input resistance
1.000+00 8 xfmr turns ratio
```

3.6-09 GSBD \bar{e}_n @ 100 Hz
 100.0 GSBE frequency

0.0 ***

-187.9 ***
 -197.9 ***
 -165.9 ***
 -168.9 ***
 -192.4 ***

-164.1 *** total noise at 100 Hz

PROGRAM OUTPUT

```
6.-16 GSBC  $\bar{i}_n$  @ 10 Hz
7.-09 GSBD  $\bar{e}_n$  @ 10 Hz
10. GSBE frequency
0.0 ***  $A_v$ , network gain, dB
-187.9 ***  $R_s + R_{pri}$  thermal noise, dBV
-197.9 ***  $R_{sec}$  thermal noise, dBV
-145.9 ***  $R_{in}$  thermal noise, dBV
-163.1 ***  $\bar{e}_n$ , transistor, dBV
-172.4 ***  $\bar{i}_{n+Z}$  equiv. noise, dBV
-145.6 *** total noise (RSS), dBV
```

6.1-16 GSBC \bar{i}_n @ 200 Hz
 3.2-09 GSBD \bar{e}_n @ 200 Hz
 200.0 GSBE frequency

0.0 ***

-187.9 ***
 -197.9 ***
 -171.9 ***
 -169.9 ***
 -198.3 ***

-167.7 *** total noise at 200 Hz

```
5.3-09 GSBD  $\bar{e}_n$  @ 20 Hz *
20.0 GSBE frequency
0.0 ***
* $\bar{i}_n$  is unchanged
from the last
entry.
-187.9 ***
-197.9 ***
-151.9 ***
-165.5 ***
-178.5 ***
-151.7 *** total noise at 20 Hz
```

6.2-16 GSBC \bar{i}_n @ 500 Hz
 2.3-09 GSBD \bar{e}_n @ 500 Hz
 500.0 GSBE frequency

0.0 ***

-187.9 ***
 -197.9 ***
 -179.9 ***
 -171.1 ***
 -206.1 ***

-170.4 *** total noise at 500 Hz

```
4.1-09 GSBD  $\bar{e}_n$  @ 50 Hz
50.0 GSBE frequency
0.0 ***
-187.9 ***
-137.3 ***
-159.5 ***
-167.7 ***
-186.4 ***
-159.2 *** total noise at 50 Hz
```

6.3-16 GSBC \bar{i}_n @ 1000 Hz
 2.7-09 GSBD \bar{e}_n @ 1000 Hz
 1000.0 GSBE frequency

0.0 ***

-187.9 ***
 -197.9 ***
 -185.9 ***
 -171.4 ***
 -212.0 ***

-171.1 *** total noise at 1000 Hz

Example 1-6.2

A small hydrophone is to be matched to a low-noise preamplifier for optimum noise performance at 30 kHz. The hydrophone equivalent circuit is shown in Fig. 1-6.2. The amplifier input transistor will be a 2N4867A FET operating at a drain current of I_{dss} .

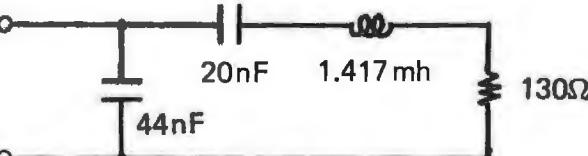


Figure 1-6.2 Hydrophone equivalent circuit.

Table 1-6.2 Current and voltage noise densities of 2N4867A operating at I_{dss} .

Frequency, kHz	$\overline{i_n}$, A/\sqrt{Hz}	$\overline{e_n}$, V/\sqrt{Hz}
10	8.0×10^{-16}	2.3×10^{-9}
15	1.0×10^{-15}	
20	1.2×10^{-15}	
25	1.4×10^{-15}	
30	1.6×10^{-15}	2.3×10^{-9}
35	1.75×10^{-15}	2.2×10^{-9}
40	1.9×10^{-15}	
45	2.15×10^{-15}	
50	2.4×10^{-15}	
55	2.7×10^{-15}	
60	3.0×10^{-15}	2.2×10^{-9}

Before the analysis is started, the transformer turns ratio, primary inductance, and amplifier input resistance must be chosen. The transformer ratio should be kept low to minimize the current noise contribution of the input transistor.

The parallel equivalent circuit of the hydrophone at 30 kHz is required. The capacitive part will be resonated by the transformer

primary inductance, leaving only the resistive part. Figure 1-6.3 shows the parallel equivalent circuit before resonating, and Fig. 1-6.4 shows the HP-97 calculations used to obtain the parallel equivalent circuit.

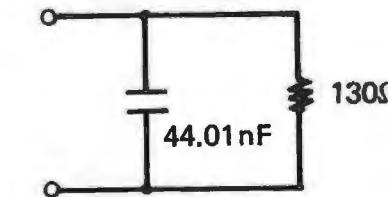


Figure 1-6.3 Parallel equivalent circuit of hydrophone at 30 kHz.

30000. P:	enter frequency and calculate and store
x	$\omega = 2\pi f \rightarrow R_E$
2. x	form ωL
STOE	
1.407-03 x	form $1/(\omega C)$
RCLE	
20000.-12 x	form and print
1/X	$\omega L - 1/(\omega C) = Im Z$
-44.99-03 ***	load $Re Z$
130. +P	
1/X	X \Rightarrow Y convert impedance
X \Rightarrow Y	CHS to admittance
+R	X \Rightarrow Y
130.0+00 ***	Re Y in ohms
1/X	Re Y back in mhos
X \Rightarrow Y	Im Y
44000.-12 RCLE	add clamp capacity
x	susceptance
+	RCLE convert total
	\div susceptance to
44.01-09 ***	capacitance & print

Figure 1-6.4 HP-97 printout showing calculations used to find the parallel equivalent circuit at 30 kHz.

The thermal noise of the equivalent parallel resistor in a one Hz band is:

$$\overline{e_n}(130 \Omega) = \sqrt{4KT(130)} = 1.45 \times 10^{-9} V/\sqrt{Hz}$$

If the transformer raises this noise to 6 dB above the transistor noise, the RSS sum of both resistor and transistor noises will be 1 dB higher

than the resistor noise alone. The transformer turns-ratio necessary to meet this condition is:

$$n = \frac{2(2.2 \times 10^{-9})}{1.45 \times 10^{-9}} = 3.03$$

The noise current contribution to the total noise voltage also may be calculated (only $\text{Re } Z_{\text{in}}$ is used as $\text{Im } Z_{\text{in}}$ is resonated out):

$$\overline{e_n} = \overline{i_n} \cdot n^2 \cdot |Z_{\text{in}}| = (1.6 \times 10^{-15})(10^2)(130) = 20.8 \times 10^{-12} \text{ V}/\sqrt{\text{Hz}}$$

This contribution is insignificant compared to the voltage noise term, and the transformer ratio may be raised to make the dominant noise source that of the hydrophone resistance only. This will be the best noise performance obtainable.

With a transformer ratio of 10:1, the equivalent hydrophone resistor noise is $1.45 \times 10^{-8} \text{ V}/\sqrt{\text{Hz}}$ at the transistor input, and the RSS of both the transistor and resistor noises is 1.467×10^{-8} . This RSS voltage is only 0.1 dB above the resistor noise alone!

To represent the equivalent hydrophone shunt capacity (44.01 nF), the transformer secondary capacitance term, C_{sec} is used. This equivalent secondary capacity is the primary capacity (hydrophone capacity) divided by the square of the turns ratio:

$$C_{\text{sec}} = (44.01 \text{ nF})/(10^2) = 440 \text{ pF}$$

The primary inductance is chosen to parallel resonate with the equivalent hydrophone capacity, 44.01 nF, at the design frequency of 30 kHz. This primary inductance is:

$$L_{\text{pri}} = 1/((2\pi f)^2 C) = 1/((2\pi 30000)^2 \cdot 44.01 \times 10^{-9})$$

$$L_{\text{pri}} = 639.5 \mu\text{H}$$

The "Q" of the network is $R/(2\pi f L) = 1.078$, which means the approximate bandwidth of the network is $30000/1.078 = 27829 \text{ Hz}$. Additional broadbanding using the shunting effect of an amplifier input resistor is not necessary. This input resistor may be removed altogether as the transformer secondary provides the dc return for the transistor gate connection. The input resistor will be omitted by making its value 10^{50} ohms .

The HP-97 printout for this example is shown on the next page, and the equivalent circuit is shown in Fig. 1-6.5.

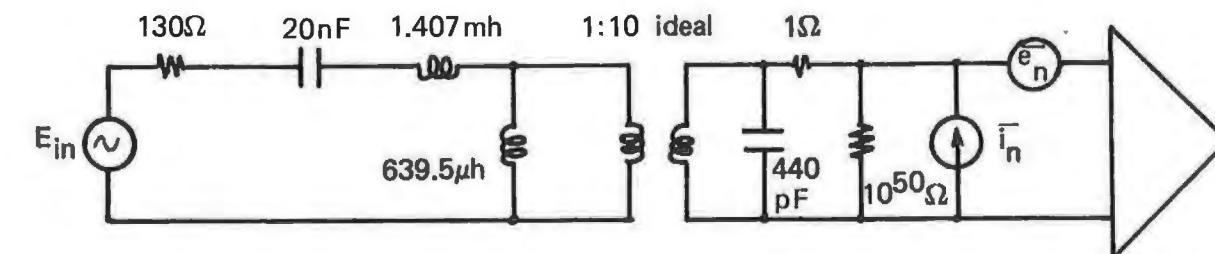


Figure 1-6.5 Equivalent circuit for hydrophone and amplifier.

HP-97 PRINTOUT FOR EXAMPLE 1-6.2

130.0 ST00 R _s 20000.-12 ST01 C _s 1.407.-03 ST02 L _s 0.0 ST03 R _{pri} 639.5-06 ST04 L _{pri} 440.-12 ST05 C _{sec} 1.0 ST06 R _{sec} 1.+50 ST07 R _{in} 10.0 ST08 ntransformer GSBA select dB mode for p/d	1.4-15 GSBC I _n @ 25 kHz 25000.0 GSBE freq & start 21.9 *** -154.9 *** -197.9 *** -611.8 *** -172.8 *** -211.0 *** -154.8 *** \bar{e}_n tot @ 25kHz	2.15-15 GSBC I _n @ 45 kHz 45000.0 GSBE freq & start 19.6 *** -157.1 *** -197.9 *** -610.1 *** -173.2 *** -205.5 *** -157.0 *** \bar{e}_n tot @ 45kHz
PROGRAM OUTPUT		
8.-16 GSBC load I _n @10kHz 2.3-09 GSBD load e _n @ " 10000.0 GSBE load freq & start -3.5 *** A _y dB	1.6-15 GSBC I _n @ 30 kHz 30000.0 GSBE freq & start 28.6 *** -156.8 *** -197.9 *** -615.6 *** -172.8 *** -213.6 *** -156.7 *** \bar{e}_n tot @ 30kHz	2.4-15 GSBC I _n @ 50 kHz 50000.0 GSBE freq & start 14.5 *** -162.3 *** -197.9 *** -613.6 *** -173.2 *** -208.1 *** -162.0 *** \bar{e}_n tot @ 50kHz
1.-15 GSBC I _n @ 15 kHz * 15000.0 GSBE freq & start (* \bar{e}_n unchanged) 7.4 ***	1.75-15 GSBC I _n @ 35 kHz 2.2-09 GSBD e _n @ " 35000.0 GSBE freq & start 21.3 *** -155.4 *** -197.9 *** -612.8 *** -173.2 *** -210.1 *** -167.7 *** \bar{e}_n tot @ 15kHz	2.7-15 GSBC I _n @ 55 kHz 55000.0 GSBE freq & start 10.5 *** -166.3 *** -197.9 *** -616.2 *** -173.2 *** -209.6 *** -165.5 *** \bar{e}_n tot @ 55kHz
1.2-15 GSBC I _n @ 20 kHz 20000.0 GSBE freq & start 19.6 ***	1.9-15 GSBC I _n @ 40 kHz 40000.0 GSBE freq & start 23.4 *** -153.4 *** -197.9 *** -608.4 *** -173.2 *** -204.9 *** -157.0 *** \bar{e}_n tot @ 20kHz	3.-15 GSBC I _n @ 60 kHz 60000.0 GSBE freq & start 7.4 *** -169.4 *** -197.9 *** -618.1 *** -173.2 *** -210.6 *** -167.8 *** \bar{e}_n tot @ 60kHz

Example 1-6.2 is meant to illustrate both the program functioning and to give some insight on hydrophone matching. The gain versus frequency response has two peaks, which is characteristic of doubly tuned networks.

The whole subject of optimum hydrophone matching is beyond the scope of this program and discussion. Equiripple passband response and optimum noise performance may be simultaneously obtained with higher order matching networks which represent bandpass filter like structures and include the hydrophone equivalent circuit in the filter structure. Typical broadbanding networks are fifth order and have Chebyshev responses. These networks are an extension of the work of Fano [23] and Matthaei [37].

Derivation of Equations Used

The network shown in Fig. 1-6.1 is redrawn with the components on the secondary side of the transformer reflected to the primary side, and the thermal noise sources of the resistors added. This new network is shown in Fig. 1-6.6.

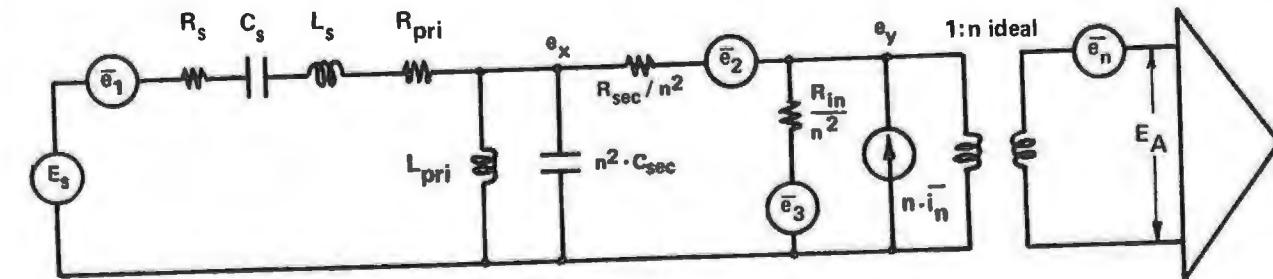


Fig. 1-6.6 Network of Fig. 1-6.1 redrawn with the transformer moved to the right side.

The network of Fig. 1-6.6 is shown in Fig. 1-6.7 with the individual element groups replaced by generalized admittance blocks. The noise voltage densities of the noise generators are defined by Eqs. (1-6.1) through (1-6.3), and the admittance blocks are defined by Eqs. (1-6.4) through (1-6.7).

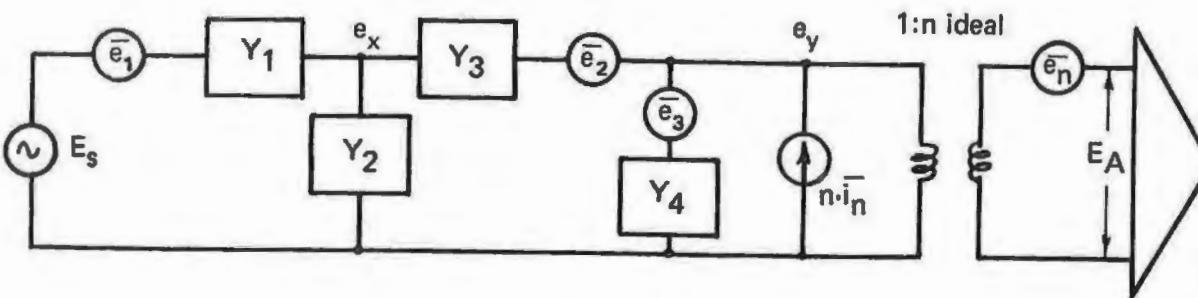


Figure 1-6.7 Network of Fig. 1-6.6 redrawn with generalized admittance blocks.

$$\bar{e}_1 = \sqrt{4KT(R_s + R_{pri})} \quad (1-6.1)$$

$$\bar{e}_2 = (1/n) \sqrt{4KTR_{sec}} \quad (1-6.2)$$

$$\bar{e}_3 = (1/n) \sqrt{4KTR_{in}} \quad (1-6.3)$$

$$Y_1 = \frac{1}{R_s + R_{pri} + sL_s + 1/(sC_s)} = \frac{1}{R_s + R_{pri} + j(\omega L_s - 1/(\omega C_s))} \quad (1-6.4)$$

$$Y_2 = s(n^2 \cdot C_{sec}) + 1/(sL_{pri}) = j(n^2 \omega C_{sec} - 1/(\omega L_{pri})) \quad (1-6.5)$$

$$Y_3 = n^2/R_{sec} \quad s = j\omega \quad (1-6.6)$$

$$Y_4 = n^2/R_{in}$$

Where K is Boltzmann's constant (1.380×10^{-23} Joules/K), and T is the temperature in Kelvin (290 K at room temperature).

The nodal equations are written from Fig. 1-6.7:

$$\begin{bmatrix} (Y_1 + Y_2 + Y_3) & (-Y_3) \\ (-Y_3) & (Y_3 + Y_4) \end{bmatrix} \cdot \begin{bmatrix} e_x \\ e_y \end{bmatrix} = \begin{bmatrix} Y_1(\bar{e}_1 + E_s) - Y_3\bar{e}_2 \\ Y_3\bar{e}_2 + Y_4\bar{e}_3 + n\bar{i}_n \end{bmatrix} \quad (1-6.8)$$

The variable, e_y , is obtained using Cramer's rule. The determinant of the coefficient matrix is designated Δ .

$$\Delta = (Y_1 + Y_2 + Y_3)(Y_3 + Y_4) - Y_3^2$$

which upon rearranging yields:

$$\Delta = (Y_1 + Y_2 + Y_3)(Y_4) + (Y_1 + Y_2)(Y_3) \quad (1-6.9)$$

Substituting the constant matrix (right hand side) into the second column of the coefficient matrix, and evaluating the determinant yields the following:

$$n \cdot e_y = (n/\Delta) [(Y_1 + Y_2 + Y_3)(Y_3\bar{e}_2 + Y_4\bar{e}_3 + n\bar{i}_n) + (Y_1 Y_3)(\bar{e}_1 + E_s) - (Y_3^2)(\bar{e}_2)] \quad (1-6.10)$$

Simplifying and removing term subtraction yields:

$$n \cdot e_y = (n/\Delta) [(Y_1 + Y_2 + Y_3)(Y_4\bar{e}_3 + n\bar{i}_n) + (Y_1 Y_3)(\bar{e}_1 + E_s) + (Y_1 - Y_2)(Y_3\bar{e}_2)] \quad (1-6.11)$$

$$\text{The voltage gain of the network is: } n \frac{\partial e_y}{\partial E_s} = \frac{\partial e_A}{\partial E_s} = A_v, \text{ or:} \quad (1-6.12)$$

$$A_v = (n Y_1 Y_3) / (\Delta), \quad (1-6.13)$$

In terms of magnitude only:

$$A_v = n \cdot |Y_1| \cdot |Y_3| / |\Delta| \quad (1-6.14)$$

Since the noise voltages \bar{e}_2 , \bar{e}_3 , and \bar{e}_n , and the current \bar{i}_n are random in nature, their addition must be done in RSS fashion to obtain the overall RMS noise voltage at the amplifier input, e_A , i.e.,

$$\bar{e}_A^2 = \bar{e}_n^2 + n^2 \cdot \bar{e}_y^2 \quad (1-6.15)$$

Upon expanding:

$$\bar{e}_A^2 = \bar{e}_n^2 + \frac{n^2}{|\Delta|^2} (|Y_1 + Y_2 + Y_3|^2 \cdot (\bar{e}_3^2 |Y_4|^2 + n^2 \bar{i}_n^2) + |Y_1 Y_3|^2 \cdot \bar{e}_1^2 + |Y_1 + Y_2|^2 Y_3^2 \bar{e}_2^2) \quad (1-6.16)$$

This program uses Eqs. (1-6.14) and (1-6.16) to calculate the overall noise voltage density.

Program Listing I

```

001 #LBLA SELECT OUTPUT IN dB & dBV
002 CF1
003 RTN
004 #LBLB SELECT OUTPUT IN RATIO
005 SF1 AND VOLTS
006 RTN
007 #LBLC LOAD AMPLIFIER INPUT CURRENT
008 PSS NOISE DENSITY IN A/VHz
009 F3? if numeric entry, jump to
010 GT00 storage routine
011 RCL8 recall presently stored value
012 PSS jump to print and space
013 GT02 routine
014 #LBLB store entered value of  $\bar{I}_n$ , and return control to keyboard
015 ST00 form and store  $Im(Y_1 + Y_2)$ 
016 PSS
017 RTN
018 #LBBD LOAD AMPLIFIER INPUT VOLTAGE
019 F3? NOISE DENSITY IN V/ $\sqrt{\text{Hz}}$ 
020 GT00 if numeric entry, jump
021 RCL9 recall presently stored value
022 #LBL2 print and space routine
023 PRTX
024 SPC
025 RTN return control to keyboard
026 #LBLB store entered value of  $\bar{e}_n$ 
027 ST09
028 RTN return control to keyboard
029 #LBLE LOAD ANALYSIS FREQ & START
030 F3? if numeric entry, store it
031 ST01
032 RCLI recall present stored freq
033 GSB3 if flag 0, space
034 ENT†
035 + form and store  $\omega = 2\pi f$ 
036 PI
037 X
038 ST0E
039 RCL2 form  $\omega L_{\text{sens}}$ 
040 X
041 RCLE
042 RCL1
043 X form  $1/(w_0 \text{sens})$ 
044 1/X
045 - Im  $Z_1 = \omega L_s - 1/(w C_s)$ 
046 RCL0
047 RCL3 Re  $Z_1 = R_s + R_{\text{pri}}$ 
048 +
049 +P convert rectangular to polar
050 1/X
051 ST0D form and store  $|Y_1|$ 
052 X:Y
053 CHS finish complex inverse, and return output in
054 X:Y rectangular co-ordinates
055 +R

```

REGISTERS

⁰ R_s	¹ \bar{I}_n	² L_s	³ R_{pri}	⁴ L_{pri}	⁵ C_{sec}	⁶ R_{sec}	⁷ R_{in}	⁸ n	⁹ $\bar{e}_n \text{amp}$
S0 $\bar{I}_n \text{amp}$	S1 $\sum V^2$	S2 $ Y_3(Y_1 + Y_2) $	S3	S4	S5	S6	S7	S8	S9
^A $Re Y_1, \frac{n}{ \Delta }$	^B $Im(Y_1 + Y_2), 4KT$	^C $ Y_3 , Y_1 Y_3 $	^D $ Y_1 , A_v $	^E $2\pi f, Y_1 + Y_2 + Y_3 $	f, the freq for analysis				

```

056 ST0A store  $Re(Y_1 + Y_2), Re Y_1$ 
057 X:Y calculate and store
058 RCL5  $Im(Y_1 + Y_2)$ 
059 RCL8
060 X2 calculate  $n^2 w C_{\text{sec}}$ 
061 X
062 RCLE
063 X
064 +
065 RCL8 calculate  $1/(w L_{\text{pri}})$ 
066 RCL4
067 X
068 1/X
069 -
070 ST0B form and store  $Im(Y_1 + Y_2)$ 
071 RCLA take  $Y_1 + Y_2$  to polar
072 +P
073 RCL8 calculate and store
074 X2  $Y_3 = n^2 / R_{\text{sec}}$ 
075 RCL6
076 =
077 ST0C
078 X form and store  $|Y_3| \cdot |Y_1 + Y_2|$ 
079 PSS
080 ST02
081 PSS
082 RCLB  $Im(Y_1 + Y_2 + Y_3) / Im(Y_1 + Y_2)$ 
083 RCLA calculate  $Re(Y_1 + Y_2 + Y_3)$ 
084 RCLC
085 +
086 +P
087 ST0E form and store  $Y_1 + Y_2 + Y_3$ 
088 RCL8 form  $|Y_4| \cdot |Y_1 + Y_2 + Y_3|$ 
089 X2
090 X
091 RCL7
092 =
093 +R form  $Re Im(Y_4(Y_1 + Y_2 + Y_3))$ 
094 RCLA form  $Re(Y_3(Y_1 + Y_2))$ 
095 RCLC
096 X
097 +
098 X:Y form  $Im(Y_3(Y_1 + Y_2))$ 
099 RCLB
100 RCLC
101 X
102 +
103 +P form  $|\Delta|$ 
104 RCL8 form and store  $n/|\Delta|$ 
105 =
106 1/X
107 ST0A
108 RCLD form  $|Y_1 Y_3|$ 
109 RCLC
110 X

```

Program Listing II

```

1-6
111 ST0C calculate and store:
112 X
113 ST0D  $|A_v| = n \cdot |Y_1 Y_3| / |\Delta|$ 
114 GSB1 print  $A_v$  or  $20 \cdot \log A_v$ 
115 0 initialize  $\Sigma V^2$  register
116 PSS
117 ST01
118 PSS
119 GSB3 space if flag 0 is set
120 1 form and store 4KT
121 .
122 6
123 1
124 7
125 3
126 6
127 EEX
128 CHS
129 2
130 0
131 ST0B
132 RCL8 calculate and output:
133 RCL3  $A_v \cdot \sqrt{4KT(R_s + R_{\text{pri}})}$ 
134 +
135 X which is the transformer primary resistance and
136 JX sensor resistance thermal
137 RCLD voltage noise density
138 X
139 GSB1
140 RCLB calculate and output:
141 RCL6  $|Y_3(Y_1 + Y_2)/\Delta| \cdot \sqrt{4KT R_{\text{sec}}}$ 
142 X which is the transformer secondary resistance thermal
143 JX voltage noise density
144 RCL8
145 =
146 PSS
147 RCL2
148 PSS
149 X
150 RCLA
151 X
152 GSB1
153 RCLB calculate and output:
154 RCL7
155 =
156 JX  $\frac{n}{|\Delta|} |Y_4(Y_1 + Y_2 + Y_3)| \cdot \sqrt{4KT R_{\text{in}}}$ 
157 RCL8 which is the thermal noise
158 X voltage density due to the
159 RCLA amplifier input resistance
160 RCLC
161 X
162 ST0E
163 X
164 GSB1
165 RCL9 recall and output the
amplifier noise voltage dens

```

LABELS					FLAGS		SET STATUS		
^A select dB	^B select linear	^C load \bar{I}_n	^D load \bar{e}_n	^E input freq & go	⁰ R/S, prt	FLAGS	TRIG	DISP	
a	b	c	d	e	'dB/ linear	ON OFF	DEG ■	FIX	
⁰ local lbl	¹ output	² print R/S	³ spc if FO	⁴	2	1	GRAD ■	SCI	
5	6	7	8	9	3 data entry	2	RAD	ENG	

Part 2
FILTER DESIGN

PROGRAM 2-1 BUTTERWORTH AND CHEBYSHEV FILTER ORDER CALCULATION.

Program Description and Equations Used

This program calculates the minimum filter order required to meet specifications for maximum passband attenuation (A_p _{dB}) and minimum stopband attenuation (A_s _{dB}) for the Butterworth or Chebyshev filter approximations. A second part of the program calculates the stopband-to-passband frequency ratio, λ , if the filter order and type are given. Furthermore, a third part of the program predicts the stopband attenuation if n , λ , A_p _{dB}, and the filter order are provided.

Figures 2-1.1 and 2-1.2 are nomographs adapted from Kawakami [34], and can prove useful to rough out the problem and provide tradeoffs. Once the desired parameters have been estimated, this program may be used to fine-tune the results.

Equation (2.1.1) is the analytic expression for the Butterworth amplitude response characteristic.

$$A_s^2 - 1 = (A_p^2 - 1) \lambda^{2n} \quad (2-1.1)$$

where

$$A_s^2 = 10^{0.1 A_s \text{ dB}} \quad (2-1.2)$$

and

$$A_p^2 = 10^{0.1 A_p \text{ dB}} \quad (2-1.3)$$

The quantities A_s and A_p are ratios greater than one (it is the convention to express attenuation as positive decibels).

Equations (2-1.1), (2-1.2), and (2-1.3) can be used to find expressions for A_s _{dB}, λ , or n :

$$A_s \text{dB} = 10 \cdot \log \left[(A_p^2 - 1) \lambda^{2n} + 1 \right] \quad (2-1-4)$$

$$\lambda = \left[\frac{A_s^2 - 1}{A_p^2 - 1} \right]^{\frac{1}{2n}} = \left[\sqrt{\frac{A_s^2 - 1}{A_p^2 - 1}} \right]^{\frac{1}{n}} \quad (2-1-5)$$

$$n = \frac{\ln \sqrt{\frac{A_s^2 - 1}{A_p^2 - 1}}}{\ln \lambda} \quad (2-1-6)$$

Equation (2-1.7) is the analytic expression for the Chebyshev amplitude characteristic where A_s^2 and A_p^2 are defined by Eqs. (2-1.2) and (2-1.3). Equation (2-1.7) can also yield expressions for $A_s \text{dB}$, λ , or n :

$$A_s^2 - 1 = (A_p^2 - 1) [\cosh(n \cosh^{-1} \lambda)]^2 \quad (2-1-7)$$

$$A_s \text{dB} = 10 \cdot \log [(A_p^2 - 1) (\cosh(n \cosh^{-1} \lambda)^2 + 1)]^2 \quad (2-1-8)$$

$$\lambda = \cosh \left(\frac{1}{n} \cosh^{-1} \sqrt{\frac{A_s^2 - 1}{A_p^2 - 1}} \right) \quad (2-1-9)$$

$$n = \frac{\cosh^{-1} \sqrt{\frac{A_s^2 - 1}{A_p^2 - 1}}}{\cosh^{-1} \lambda} \quad (2-1-10)$$

A certain degree of similarity can be noticed between the Butterworth and Chebyshev equations. Keeping in mind that \ln and \exp are complementary operations as are \cosh and \cosh^{-1} , and noticing that y^x can be expressed as $\exp(x \cdot \ln y)$, then replacing \ln with \cosh and \exp with \cosh^{-1} will convert the Butterworth formulas to the Chebyshev

formulas. This technique is used by this program where flag 1 indicates the function to be used (set for Butterworth).

A separate subprogram is also included to aid in the specification of bandpass or bandstop filters. The characteristics of these filters are symmetrical when plotted on logarithmic frequency scales (log paper). This characteristic implies geometric symmetry of the various defining frequencies (-3dB, etc.) about the filter center frequency, i.e., the center frequency is the square root of the product of similar response frequencies located above and below the center frequency.

To use the bandstop and bandpass programs in this section, the filter center frequency (f_o) and bandwidth (BW) are needed, however, when specifying the filter initially, the bandedge frequencies may be of greater interest. The separate subprogram provides the conversion between center frequency and bandwidth, and upper and lower bandedge frequencies (f_{upr} and f_{lwr}), and vice-versa. The definition of "bandedge frequencies" in the present context means a pair of frequencies (one on either side of the center frequency) where the filter attenuation is the same, i.e., -0.01 dB, -3 dB, -60 dB, etc.

To convert from center frequency and bandwidth to upper and lower bandedge frequencies, Eqs. (2-1.11) and (2-1.12) apply.

$$f_{upr} = (BW/2) + \sqrt{(BW/2)^2 + f_o^2} \quad (2-1-11)$$

$$f_{lwr} = (f_o^2)/f_{upr} \quad (2-1-12)$$

To do the reverse conversion, i.e., to go from upper and lower bandedge frequencies to center frequency and bandwidth, Eqs. (2-1.13) and (2-1.14) apply.

$$f_o = \sqrt{(f_{upr})(f_{lwr})} \quad (2-1-13)$$

$$BW = f_{upr} - f_{lwr} \quad (2-1-14)$$

In the case of a bandpass or bandstop filter, the stopband-to-passband frequency ratio, λ , still holds. The user should remember to use bandwidths, and not bandedge frequencies. This is an easy trap to fall into since bandedge frequencies and bandwidths can be one and the same for lowpass filters.

User Instructions

BUTTERWORTH AND CHEBYSHEV FILTER ORDER CALCULATION				
Butterworth	Chebyshev	print, R/S	BW↑f _o → f _{upr} , f _{lwr}	f _{upr} ↑f _{lwr} → f _o , BW
A _p dB	A _s dB	n → λ	λ → n	λ → A _s dB
1 Load program card (either side)				
2 Select print (HP-97), or R/S (HP-67) option			<input type="button" value="f"/> <input type="button" value="C"/> <input type="button" value="f"/> <input type="button" value="C"/> <input type="button" value="f"/> <input type="button" value="C"/>	1 (print) 0 (R/S) 1 ⋮
3 Select filter type:				
Butterworth			<input type="button" value="f"/> <input type="button" value="A"/> <input type="button" value="f"/> <input type="button" value="B"/>	
Chebyshev				
4 Load the maximum passband attenuation in dB	A _p dB		<input type="button" value="A"/>	
5 Load the minimum stopband attenuation in dB	A _s dB		<input type="button" value="B"/>	
6 To find filter order, n, given the frequency ratio, λ, load λ	λ		<input type="button" value="D"/>	n
7 To find the frequency ratio, λ, given the filter order, n: load n (n must be integer)	n		<input type="button" value="C"/>	λ
8 After finding n, to find A _s (dB) given λ				
a) perform step 7 to store n				
b) load λ	λ		<input type="button" value="E"/>	A _s dB
Step 8b may be repeated with other values of λ without having to repeat step 8a.				
9 A separate program section to aid with bandpass filter selection, enter bandwidth and center frequency and calculate the upper and lower bandedge frequencies, or vice-versa				
load bandwidth (for any dB down points)	BW, Hz		<input style="vertical-align: middle; margin-right: 5px;" type="button" value="ENT"/> ↑ <input type="button" value="f"/> <input type="button" value="D"/>	f _{upr} , Hz f _{lwr} , Hz
load center frequency	f _o , Hz		<input style="vertical-align: middle; margin-right: 5px;" type="button" value="ENT"/> ↓ <input type="button" value="f"/> <input type="button" value="E"/>	f _o , Hz BW, Hz
load upper bandedge frequency	f _{upr} , Hz			
load lower bandedge frequency	f _{lwr} , Hz			

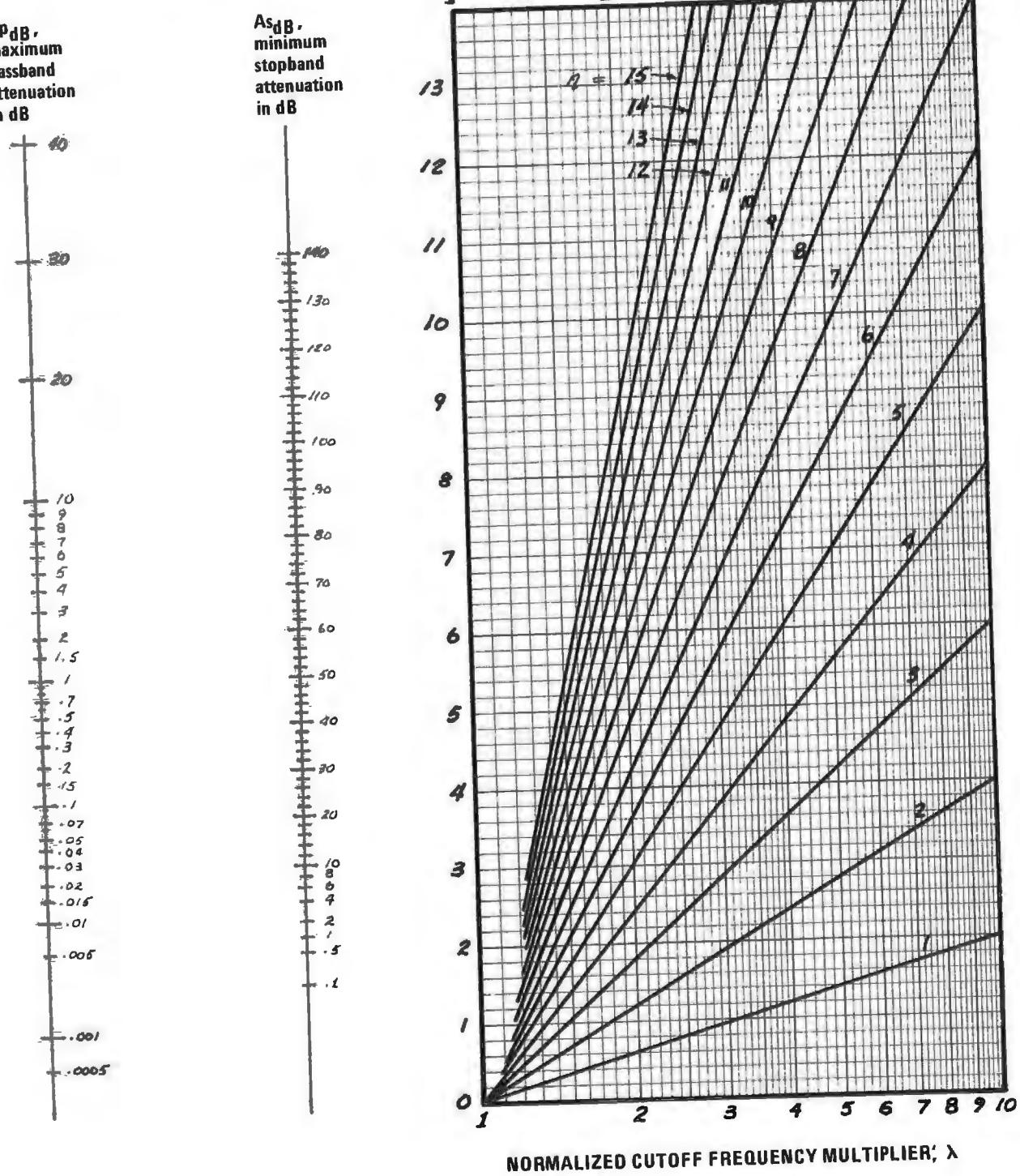


Figure 2-1.1 Butterworth filter nomograph.

$$A_s^2 - 1 = (A_p^2 - 1)\lambda^{2n}$$

Adapted from Kawakami [34]

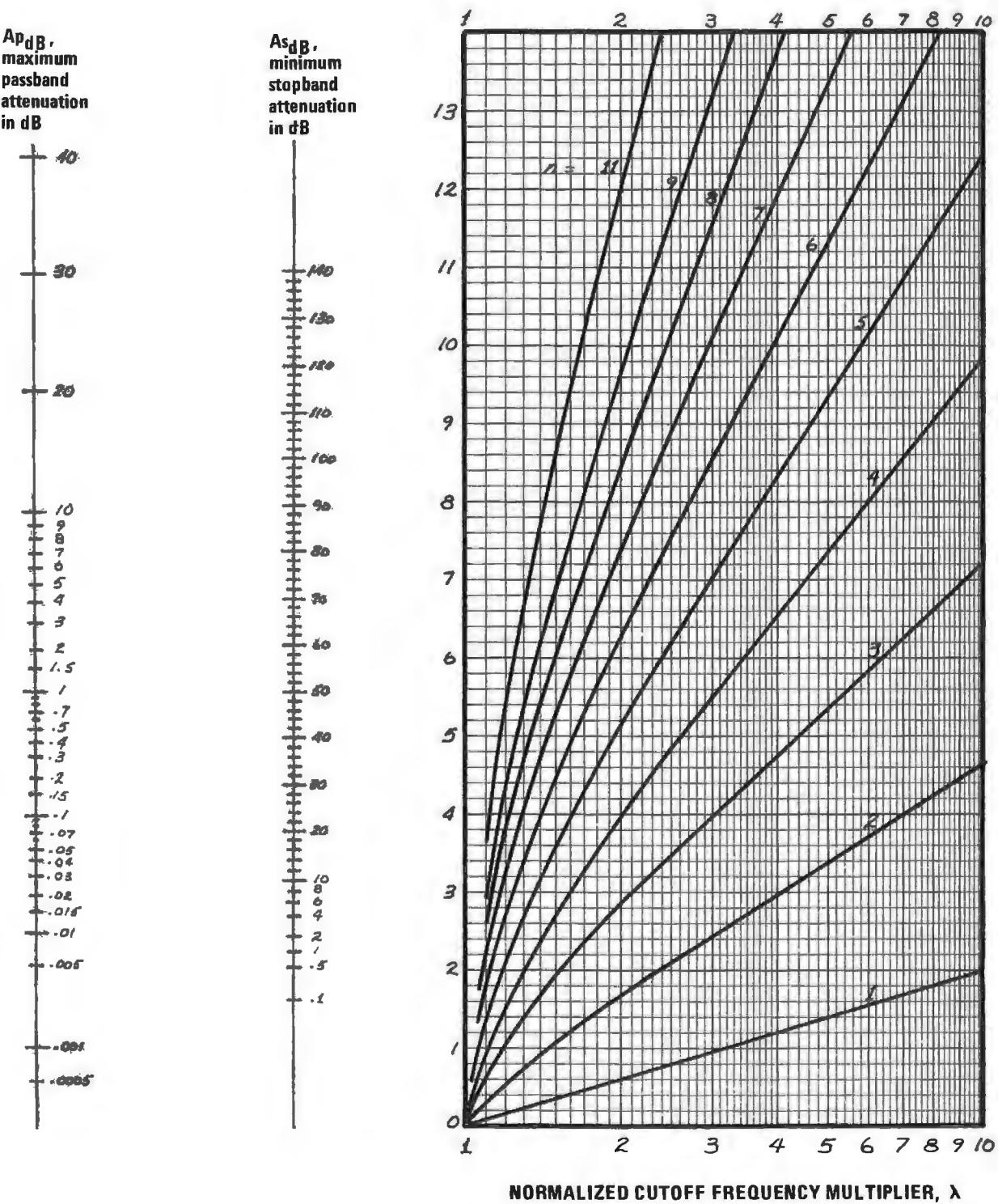


Figure 2-1.2 Chebyshev filter nomograph.

$$A_s^2 - 1 = (A_p^2 - 1) \{ \cosh(n \cdot \cosh^{-1} \lambda) \}$$

Adapted from Kawakami [34]

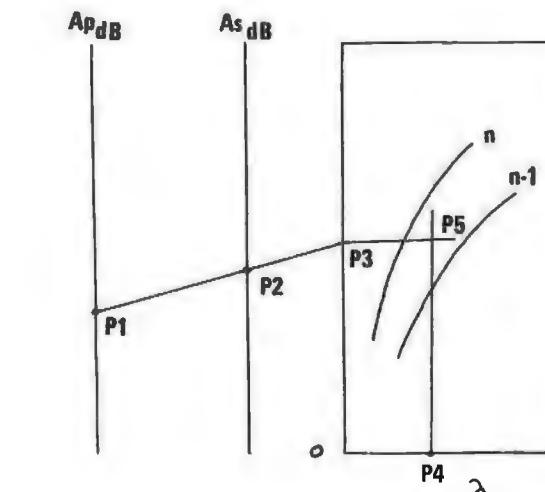
How to Use the Nomographs

Figure 2-1.3 Nomograph use.

P_1 and P_2 are the required passband and stopband attenuation, P_3 is a turning point, P_4 represents the ratio between the frequencies where the stopband attenuation and the passband attenuation are specified, and P_5 represents the required filter order, n .

Since n must be an integer, and P_5 will generally lie between two integral numbers, always choose the larger of the two integers. Furthermore, if any of the narrowband approximations to bandpass filters are going to be generated, and Chebyshev response is specified, n must be an odd integer. This requirement occurs as even ordered Chebyshev filters have unequal termination resistances, and the narrowband bandpass approximations require equal termination resistances.

These nomographs are also contained in Zverev, however, the two vertical scales appear to be misregistered slightly, and in some applications will give inaccurate results.

These nomographs may also be used in other ways. If the filter order is known, then the filter response may be predicted. In this case, P_5 would lie directly on one of the filter order lines, λ and P_1 , or P_2 are the input variables, with P_2 , or P_1 being the output quantity.

Example 2-1.1 Highpass filter

A Butterworth filter is to pass 20 kHz and higher with 3 dB or less attenuation, and reject 10 kHz and lower with at least 40 dB of attenuation. Find the minimum filter order to meet these specifications.

```

GSE0 select Butterworth
3.00 GSE1 load ApdB
40.00 GSE2 load AsdB
2.00 GSE3 load λ = (20 kHz)/(10 kHz) = 2, & calculate n
0.65 *** filter order, n (use n = 7)

```

Example 2-1.2 Bandpass filter

A Chebyshev bandpass filter is centered at 100 kHz (center frequency is not a parameter of the filter order calculation). Frequencies in a 20 kHz passband (geometrically centered about the center frequency) must be passed with 0.5 dB attenuation or less, and frequencies outside a 40 kHz bandwidth (again geometrically centered) must be rejected with at least 40 dB attenuation. Find the minimum filter order to meet these requirements.

```

GCE0 select Chebyshev
.50 GCB1 load passband ripple in dB (ApdB)
40.00 GCB2 load minimum stopband attenuation in dB (AsdB)
2.00 GCB3 load λ = (40 kHz)/(20 kHz) = 2, and calculate n
4.82 *** filter order, n (use n = 5 as smallest integer
value to meet specs)

```

Example 2-1.3 Bandstop example

A maximally flat (Butterworth) bandstop filter is centered at 20 kHz. Frequencies lying outside a 10 kHz band geometrically centered on the center frequency should be attenuated by 3 dB or less. Frequencies inside a band of 1 kHz geometrically centered on the center frequency should be attenuated by at least 60 dB. Find the minimum filter order meeting these specifications.

```

GSE0 select Butterworth
3.00 GSE1 load ApdB
60.00 GSE2 load AsdB
10.00 GSE3 load λ = (10 kHz)/(1 kHz) = 10 & calculate n
3.00 *** filter order required

```

```

GSP4 display 4 figures past the decimal point
3.0010 *** the filter order required is greater than 3

```

```

3.0000 GSBC enter filter order of exactly three & calc. λ
10.0079 *** λ where filter is 60 dB down

```

```

10.0000 GSBE enter λ and calculate AsdB
55.9794 *** AsdB at λ = 10

```

This bandstop example shows other features of this program. Given n, the ratio, λ , where A_s is met is calculated, and alternately, given λ , A_s for this ratio is calculated.

As an aside, Butterworth filters are not exactly three dB down at the bandedge, but are $10 \cdot \log_{10} 2 = 3.010299957$ dB. If this number had been entered for A_p , the calculated filter order would have been three (to seven significant figures).

Example 2-1.4 Lowpass filter

Find the frequency where a 2 dB ripple, 7th order Chebyshev lowpass filter will be 60 dB down when the cutoff (-2dB) frequency is 1000 Hz.

```

GSE0 select Chebyshev
2.00 GSE1 load ApdB, the passband ripple
60.00 GSE2 load AsdB, the minimum stopband rejection
7.00 GSE3 load the filter order, n, and calculate λ
1.70 *** λ to meet above requirements

```

```

1000.00   cutoff frequency of filter times λ
1701.27 *** frequency where the filter is 60 dB down

```

Program Listing I

```

001 *LBLA LOAD ApdB
002 GSB0
003 ST01 store Ap2 - 1
004 RTN
005 *LBLB LOAD AsdB
006 GSB0
007 ST02 store As2 - 1
008 RTN
009 *LBL0 subroutine to convert dB to
010 EEX (magnitude)2 - 1
011 1
012 ÷
013 10X
014 EEX
015 -
016 RTN
017 *LBLC LOAD n, THE FILTER ORDER
018 ST03 AND CALCULATE λ
019 RCL2
020 RCL1 calculate k = √(As2 - 1) / √(Ap2 - 1)
021 ÷
022 JX
023 F1? jump if Butterworth
024 GT03
025 GSB2 calculate cosh k
026 RCL3
027 ÷
028 GSB1 calc λ = cosh-1(1/n cosh k)
029 ST04
030 GT08 goto the print/stop routine
031 *LBL3 calculate λ for Butterworth
032 RCL3
033 1/X
034 YX λ = (k)n
035 ST04
036 GT08
037 *LBLD LOAD λ AND CALCULATE n
038 ST04
039 RCL2
040 RCL1 calculate k
041 ÷
042 JX
043 F1? jump if Butterworth
044 GT03
045 GSB2
046 RCL4 for Chebyshev:
047 GSB2
048 ÷ n = cosh-1 k / cosh-1 λ
049 ST03
050 GT08
051 *LBL3
052 LN for Butterworth:
053 RCL4
054 LN n = ln k / ln λ
055 ÷
056 ST03
057 GT08
058 *LBLE LOAD λ AND CALCULATE AsdB
059 F1? jump if Butterworth
060 GT03
061 GSB2
062 RCL3 for Chebyshev:
063 X
064 GSB1 q = cosh(n·cosh-1 λ)
065 GT04
066 *LBL3 for Butterworth:
067 RCL3
068 YX q = (λ)n
069 *LBL4 common part for Buttr & Cheb
070 X2
071 RCL1
072 X
073 EEX AsdB = 10·log((Ap2-1)q2+1)
074 +
075 LOG
076 EEX
077 1
078 X
079 GT08

```

REGISTERS

0	1 A _p ² - 1	2 A _s ² - 1	3 n	4 λ	5	6	7	8	9
S0	S1	S2	S3	S4	S5	S6	S7	S8	S9
A	B	C	D	E	I				

Program Listing II

```

080 *LBL1 cosh x subroutine
081 eX
082 ENT↑
083 1/X cosh x = eX + e-X
084 +
085 2
086 ÷
087 RTN
088 *LBL2 cosh-1 x subroutine
089 ENT↑
090 X2
091 EEX
092 -
093 JX cosh-1 x = ln(x + √(x2 - 1))
094 +
095 LN
096 RTN
097 *LBLa SELECT BUTTERWORTH
098 SF1
099 RTN
100 *LBLb SELECT CHEBYSHEV
101 CF1
102 RTN
103 *LBLc SELECT PRINT OR R/S
104 F0? jump if flag 0 is set
105 GT03
106 SF0
107 1 set flag 0 to indicate print
108 RTN
109 *LBL3
110 CF0 clear flag 1 to indicate R/S
111 0
112 RTN
131 *LBLe BANDPASS: enter fupr & flwr
132 ST05 calculate fo and BW
133 X2
134 ST06
135 X
136 JX
137 GSB9
138 RCL6
139 RCL5 BW = fupr - flwr
140 -
141 *LBL8 print or R/S subroutine
142 GSB9
143 F0? if flag 0, space
144 SPC
145 RTN
146 *LBL9
147 F0? if flag 0, go to print
148 GT09
149 R/S flag 0 not set, R/S
150 RTN
151 *LBL9
152 PRTX
153 RTN

```

LABELS					FLAGS	SET STATUS		
A Ap dB	B As dB	C n → λ	D λ → n	E λ → As dB	0 print?	FLAGS	TRIG	DISP
a set Buttr	b set Chebyshev	c print, no-print	d f _o + BW → f _u , f _l	e	1 Buttr	--USERS CHOICE--		
0 dB → ² - 1	1 cosh x	2 cosh ⁻¹ x	3	4	2	0 DEG	FIX	
5	6	7	8 print & space	9 print	3	1 GRAD	SCI	
						2 RAD	ENG	
						3	n	

**PROGRAM 2-2 BUTTERWORTH AND CHEBYSHEV FILTER
FREQUENCY RESPONSE AND GROUP DELAY.**

Program Description and Equations Used

This program calculates the frequency response (magnitude in dB and phase in degrees) and the un-normalized group delay in seconds for the Butterworth or Chebyshev all pole filter approximations. The response may be in lowpass, highpass, bandpass, or bandstop form (the lowpass and highpass responses are special cases of the bandpass and bandstop responses respectively in that the center frequency is zero). Both single frequency analysis and frequency sweeps may be done. The sweep can be linear using an additive increment, or logarithmic using a multiplicative increment.

The actual analysis routine that is buried within the program analyzes a normalized lowpass filter. The input data is normalized and transformed as required to place it in normalized lowpass form. The phase and gain response (frequency response) of the normalized lowpass filter is the same as the original filter type before transformation; hence, no reverse transformation is necessary for output. The group delay is the rate of change of phase with respect to frequency (derivative of the phase function) and is affected by the transformation to normalized lowpass form, therefore, an output transformation from the normalized lowpass group delay is required.

The logarithm of the normalized lowpass filter transmission function, $T(j\Omega)$ is composed of two components, the attenuation, a , and the phase, b . As a complex number, these two components represent the constant, g :

$$T(j\Omega) = \prod_k \frac{K}{\sigma_k + j(\omega_k - \Omega)} \quad (2.2.1)$$

$$g = \ln(T(j\Omega)) = a + jb \quad (2-2.2)$$

$$\Omega = F(\omega) \quad (2-2.3)$$

$$\omega = 2\pi f \quad (2-2.4)$$

where $F(\omega)$ represents the transformation to normalized lowpass, and σ_k and ω_k are the pole locations of the Butterworth or Chebyshev normalized lowpass transfer function (see the equation derivation section following the examples for pole location details).

The group delay of the normalized lowpass filter is the derivative of the phase function, b , taken with respect to radian frequency:

$$b = \sum_{k=1}^n \tan^{-1} \left\{ \frac{\omega_k - \Omega}{\sigma_k} \right\} \quad (2-2.5)$$

$$\tau_{g_{nor}} = \frac{db}{d\Omega} = \sum_{k=1}^n \frac{|\sigma_k|}{\sigma_k^2 + (\omega_k - \Omega)^2} \quad (2-2.6)$$

The group delay is denormalized by multiplying the normalized group delay, Eq. (2-2.6), by the derivative of the transformation function, Eq. (2-2.3), taken with respect to the un-normalized radian frequency, ω .

$$\tau_g = \tau_{g_{nor}} \cdot \frac{d\Omega}{d\omega} \quad (2-2.7)$$

The transform functions for the bandpass and lowpass cases are:

$$\Omega_{BP} = \left| \frac{1}{BW} \left\{ f - \frac{f_o^2}{f} \right\} \right| \quad (2-2.8)$$

$$\frac{d\Omega_{BP}}{d\omega} = \frac{1}{2\pi BW} \left\{ 1 + \frac{f_o^2}{f^2} \right\} \quad (2-2.9)$$

where "BW" and "f_o" are the bandwidth and center frequency of the bandpass filter in hertz, and "f" is the frequency to be transformed (in hertz). The center frequency is zero for the lowpass case.

The transform functions for the bandstop and highpass cases are:


$$\Omega_{BS} = \frac{1}{\Omega_{BP}} = \left| \frac{\frac{BW}{f^2}}{f - \frac{f_o^2}{f}} \right| \quad (2.2.10)$$

$$\frac{d\Omega_{BS}}{d\omega} = \frac{BW}{2\pi} \left\{ \frac{f^2 + f_o^2}{(f^2 - f_o^2)^2} \right\} \quad (2-2.11)$$

The definitions of the terms are the same as above, and the highpass case has zero center frequency also.

The program uses Eqs. (2-2.8) and (2-2.10) to transform the input data to normalized lowpass, and then evaluates Eqs. (2-2.1) and (2-2.6) to obtain the frequency response and normalized lowpass group delay. The group delay is denormalized using Eqs. (2-2.9) or (2-2.11), and the frequency response and group delay are printed (HP-97 only) and displayed.

User Instructions

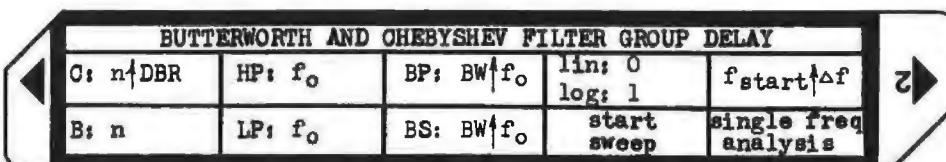

STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
1	Load both sides of magnetic card			
2	a) if Butterworth, enter filter order b) if Chebyshev: enter passband ripple in dB enter filter order	n DBR n	A ENT↑ f A	
3	Select filter type and enter characteristics a) if lowpass: enter cutoff frequency* b) if highpass: enter cutoff frequency* c) if bandstop: enter bandwidth** enter center frequency d) if bandpass: enter bandwidth** enter center frequency	BW, Hz BW, Hz BW, Hz BW, Hz f _o , Hz BW, Hz f _o , Hz	B f B ENT↑ C ENT↑ f C	
4	If sweep of frequencies is desired: a) select linear or logarithmic sweep (toggle) b) enter sweep starting frequency in hertz c) enter frequency increment: if linear sweep, the increment is additive; if logarithmic, the increment is multiplicative. d) start sweep	f start f	f D f D f D ENT↑ f E D	0 1 0 : f, Hz loss, dB phase, deg group delay sec
5	for analysis at a single frequency	f, Hz	E	analysis above
	NOTE (* & **). The LP & HP cutoff frequency and the BP & BS bandwidth are defined as the -3dB point for Butterworth, and the -DBR point for Chebyshev.			

Example 2-2.1

Calculate the amplitude, phase, and group delay characteristics of a third order, 1 dB ripple Chebyshev bandpass filter with 1000 Hz bandwidth and 10000 Hz center frequency. Calculate these characteristics from 8000 Hz to 12000 Hz in linear increments of 100 Hz.

PROGRAM INPUT	PROGRAM OUTPUT
3. ENT↑ n 1. GSBa DBR	8.000+03 9.000+03 10.00+03 11.00+03 12.00+03 -45.04+00 -24.06+00 0.000+00 -21.06+00 -39.53+00 -257.1+00 -240.1+00 0.000+00 -235.9+00 -254.0+00 21.23-06 110.6-06 802.3-06 121.1-06 21.89-06
1000. ENT↑ BW 10000. GSBc fo Z bandpass GSBD } linear 0.000+00 *** } sweep	8.100+03 9.100+03 10.10+03 11.10+03 frequency -43.48+00 -20.73+00 -345.5-03 -23.78+00 20 log H(jω) -256.3+00 -235.4+00 -27.82+00 -239.7+00 H(jω), deg 23.69-06 151.2-06 723.6-06 92.14-06 Tg, sec
8000. ENT↑ fstart 100. GSBe Δf	8.200+03 9.200+03 10.20+03 11.20+03 -41.85+00 -16.90+00 -894.2-03 -26.20+00 -255.4+00 -228.8+00 -51.87+00 -242.6+00 26.62-06 223.1-06 624.7-06 72.90-06
GSBD start analysis	8.300+03 9.300+03 10.30+03 11.30+03 -40.13+00 -12.35+00 -906.8-03 -28.38+00 -254.4+00 -218.5+00 -74.49+00 -245.0+00 30.17-06 371.0-06 667.2-06 59.38-06
	8.400+03 9.400+03 10.40+03 11.40+03 -38.31+00 -6.901+00 -195.5-03 -30.36+00 -253.3+00 -199.6+00 -103.5+00 -247.0+00 34.53-06 731.4-06 1.006-03 49.47-06
	8.500+03 9.500+03 10.50+03 11.50+03 -36.37+00 -1.466+00 -654.3-03 -32.17+00 -251.9+00 -160.9+00 -148.3+00 -248.6+00 39.96-06 1.430-03 1.371-03 41.94-06
	8.600+03 9.600+03 10.60+03 11.60+03 -34.30+00 -82.00-03 -4.904+00 -33.85+00 -250.4+00 -109.8+00 -189.4+00 -250.0+00 46.88-06 1.189-03 844.2-06 36.08-06
	8.700+03 9.700+03 10.70+03 11.70+03 -32.07+00 -865.9-03 -9.967+00 -35.42+00 -248.5+00 -76.75+00 -211.4+00 -251.2+00 55.92-06 726.3-06 432.4-06 31.41-06
	8.800+03 9.800+03 10.80+03 11.80+03 -29.66+00 -909.1-03 -14.30+00 -36.87+00 -246.3+00 -52.79+00 -223.3+00 -252.3+00 68.11-06 648.4-06 253.9-06 27.62-06
	8.900+03 9.900+03 10.90+03 11.90+03 -27.01+00 -351.4-03 -17.94+00 -38.24+00 -243.6+00 -28.08+00 -230.8+00 -253.2+00 85.24-06 737.1-06 168.4-06 24.50-06

Equations Used and Pole Locations

Butterworth pole locations: The pole locations of a normalized lowpass Butterworth filter lie on a circle in the complex plane. Odd ordered filters have a real pole plus complex conjugate pairs. Even order filters have only complex conjugate pairs. No poles ever lie directly on the $j\omega$ axis. Figure 2-2.1 shows the pole locations for a 5th order normalized Butterworth lowpass filter, and Eqs. (2-2.12) and (2-2.13) show the generalized pole locations.

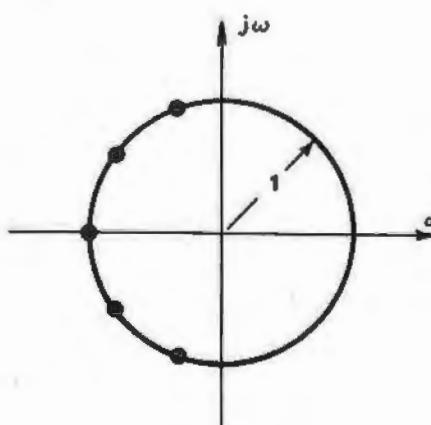


Figure 2-2.1 Butterworth pole locations.

Pole locations:

$$\text{Real part, } \sigma_k = -\sin\left(\frac{2k-1}{2n}\pi\right) \quad (2-2.12)$$

$$\text{Imag part, } \omega_k = \cos\left(\frac{2k-1}{2n}\pi\right) \quad (2-2.13)$$

$$k = 1, 2, \dots, n$$

(trig argument is in radians)

The attenuation of the normalized Butterworth lowpass filter is 3 dB at $\omega = 1$. At other frequencies, the attenuation in dB is expressed by:

$$A_{dB} = 10 \log(1 + \omega^{2n}) \quad (2-2.14)$$

As shown by this equation, the attenuation monotonically increases as frequency increases. Figure 2-2.2 shows the general shape of the Butterworth response.

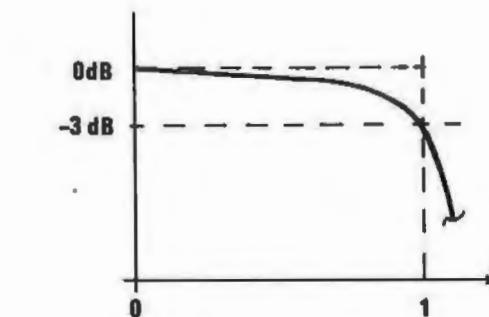


Figure 2-2.2 Normalized Butterworth amplitude response.

Chebyshev pole locations: The normalized lowpass pole locations of a Chebyshev lowpass filter lie on an ellipse with major axis dimension $\cosh a$, and minor axis dimension $\sinh a$ where a is defined by:

$$a = 1/n \sinh^{-1}(1/\epsilon) \quad (2-2.15)$$

The parameter ϵ is related to the passband ripple in dB by:

$$\epsilon = (10^{0.1\epsilon_{dB}} - 1)^{\frac{1}{2}} \quad (2-2.16)$$

Using these quantities, the real and imaginary parts of the pole locations are given by Eqs. (2-2.17) and (2-2.18). Figure 2-2.3 shows the pole locations for a fifth order Chebyshev filter.

$$\text{Real part, } \sigma_k = -(\sinh a)(\sin \frac{2k-1}{2n}\pi) \quad (2-2.17)$$

$$\text{Imag part, } \omega_k = (\cosh a)(\cos \frac{2k-1}{2n}\pi) \quad (2-2.18)$$

$$k = 1, 2, \dots, n$$

(trig argument is in radians)

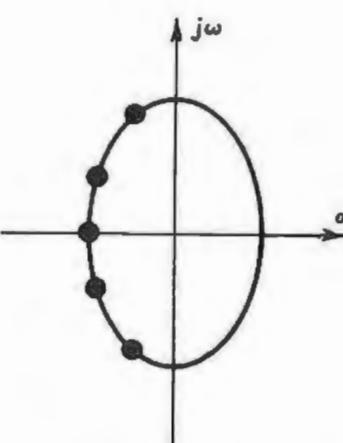


Figure 2-2.3 Chebyshev pole locations (5th order).

The passband edge of a Chebyshev filter is defined as the highest frequency where the response is ϵ_{dB} down. Remember, the Chebyshev passband response oscillates within a band of ϵ_{dB} . Fourth and fifth order Chebyshev responses are shown in Fig. 2-2.4.

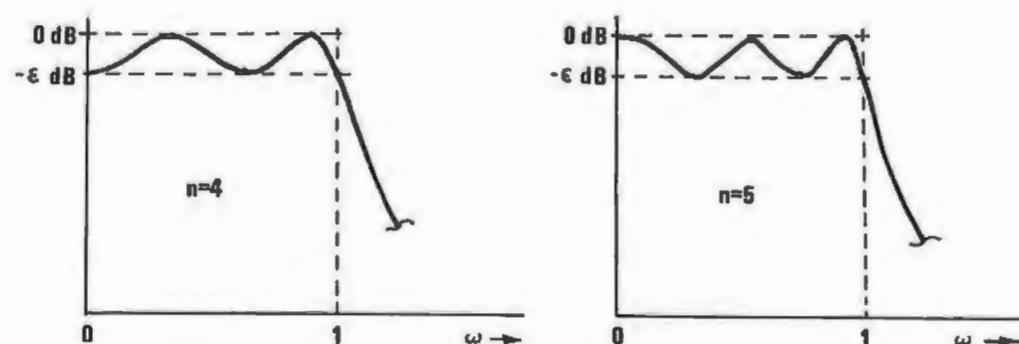


Figure 2-2.4 Chebyshev normalized lowpass filter responses.

The normalized frequency where the Chebyshev filter response is 3 dB down is given by the expression:

$$f_{-3dB} = \cosh \left\{ \frac{1}{n} \cosh^{-1} \left(\frac{1}{\epsilon} \right) \right\} \quad (2-2.19)$$

Comparing the equations that define the pole locations for the Butterworth and Chebyshev filters, one will notice that the only difference is the Chebyshev poles are modified by hyperbolic functions. If the sinh a and cosh a functions are defined to be unity, then the

Chebyshev equations become the Butterworth equations. This technique is used in the program. Chebyshev poles are always calculated; however, if Butterworth response is selected, the hyperbolic functions are not calculated, but are set equal to one in register storage.

Another difference between Butterworth and Chebyshev filters lies in the definition of the bandedge. Butterworth response is 3 dB down at the bandedge, and Chebyshev response is ϵ_{dB} down at the bandedge where ϵ_{dB} is the passband ripple in dB. Flag 1 is used to indicate the filter type, and is set for Butterworth. When the pole locations are calculated, flag 1 is tested to see what equation, if any, is to be used to convert the given passband edge frequency into the appropriate frequency for the filter type being used.

Program Listing I

```

001 *LBLA LOAD BUTTERWORTH FILTER ORDER
002 ST01 store n
003 EEX
004 ST05 cosh= 1 for Butterworth
005 ST06 sinh= 1 "
006 RCL1 recall n to display
007 RTN
008 *LBLB LOAD CHEB ORDER AND DB RIPPLE
009 ST0C store dB ripple
010 R↓
011 ST01 store n
012 RCLC calculate epsilon, ε
013 EEX
014 1 ε = √(1/Amax - 1)
015 ÷
016 10X
017 EEX
018 -
019 JX
020 1/X calculate sinh-1(1/ε)
021 ENT↑
022 X2
023 EEX
024 +
025 JX
026 +
027 RCL1 calculate sinh(1/n sinh-1(1/ε))
028 1/X
029 YX
030 ENT↑ sinh-1 x = ln(x + √(x2 + 1))
031 ENT↑ Y1/x = e^(1/n ln x)
032 ENT↑ Y = ex / e-x
033 1/X
034 -
035 ST06
036 R↓ calculate cosh(1/n sinh-1(1/ε))
037 1/X
038 +
039 ST05
040 2
041 ST=5
042 ST=6
043 RTN
044 *LBLC LOAD fo FOR LOWPASS CASE
045 CF0
046 GT01
047 *LBLe LOAD fo FOR HIGHPASS CASE
048 SF0
049 *LBL1
050 ST03 store fo
051 CLX fo = 0 for lowpass and
052 ST02 highpass cases
053 RCL3
054 RTN

```

REGISTERS

0 present frequency	¹ n	² f _o ²	³ bandwidth	⁴ f	⁵ cosh	⁶ sinh	⁷ Σ delay	⁸ π σ ² + ω ² / (ω ² - σ ²) ²	⁹ Σ phase
S0	S1	S2	S3	S4	S5	S6	S7	S8	S9
A σ _R	B ω _R	C A _{max}	D Δf	E Ω	F	G index	H	I	J

Program Listing II

```

055 *LBLC LOAD BW AND fo FOR BANDSTOP
056 SF0
057 ST01
058 *LBLe LOAD BW AND fo FOR BANDPASS
059 CF0
060 #LBL1
061 X2
062 ST02 calc & store fo2
063 R↓
064 ST03 store bandwidth
065 RTN
066 *LBLD START SWEEP
067 SPC
068 *LBL7
069 RCL8
070 PRTX
071 GSBE
072 RCL9
073 F1?
074 GT01
075 ST+8 linear sweep increment
076 GT07
077 *LBL1
078 STx8 log sweep increment
079 GT07
080 *LBLd SELECT LIN/LOG SWEEP
081 F1?
082 GT01
083 SF1
084 EEX
085 RTN
086 *LBL1
087 CF1
088 CLX
089 RTN
090 *LBLe LOAD SWEEP f start AND Δf
091 ST09
092 R↓
093 ST08
094 RTN
095 *RCLA LOAD ANALYSIS FREQUENCY
096 ST04
097 RCL2 store frequency and form:
098 RCL4
099 ÷
100 -
101 RCL3
102 ÷
103 F0? if bandstop, 1/Ω → Ω
104 1/X
105 ABS store |Ω|
106 ST0E
107 RCL1
108 ST0I initialize loop:
109 CLX n → RI
110 ST07 Σ7 = 0
111 ST09 ΤΤ8 = 1
112 EEX Σ9 = 0
113 ST08
114 *LBL0
115 RCL1
116 ENT↑
117 +
118 EEX calculate angle:
119 -
120 RCL1
121 ÷ ΘK = 90(2k-1)/n
122 9
123 0
124 X
125 EEX calculate sin θK & cos θK
126 →R
127 RCL5
128 X form and store ωK
129 ST0B
130 RCL6 form: ωK - Ω
131 -
132 X*Y
133 RCL6 form and store σK
134 X
135 ST0A
136 →P
137 X2 form and sum:
138 RCL8
139 X*Y
140 ÷
141 ST+7 σK2 + (ωK - Ω)2
142 RCL8
143 ÷ form: 1 / (σK2 + (ωK - Ω)2)
144 STx8
145 X*Y
146 ST+9 sum phase element
147 RCL8
148 X2 form in R8:
149 RCLB
150 X2
151 +
152 STx8 k=1 σK2 + (ωK - Ω)2
153 DSZ1 decrement k and test
154 GT08 for loop exit
155 RCL7
156 P;
157 ENT↑ calculate: Σ7 / 2π
158 +
159 ÷
160 RCL3
161 F0? jump if highpass or bandstop
162 GT08
163 ÷
164 RCL2
165 RCL4 lowpass or bandpass dΩ/dω
166 X2
167 =
168 EEX τg = {1 + fo2} Σ7 / 2π BW
169 +
170 X
171 GT09
172 *LBL8
173 X
174 RCL4
175 X2
176 RCL2 highpass or bandstop dΩ/dω
177 +
178 X
179 RCL4 τg = {f2 + fo2} ΒW / 2π · Σ7
180 X2
181 RCL2
182 -
183 X2
184 ÷
185 *LBL9
186 RCL8
187 LOG calculate and print
188 EEX amplitude response
189 1 in dB
190 X
191 PRTX
192 R↓
193 RCL9 calculate and print
194 F0? phase response in degrees
195 CHS
196 PRTX
197 R↓
198 PRTX print group delay
199 SPC
200 RTN

```

LABELS					FLAGS		SET STATUS		
A BUTTERWORTH	B LP: f _o	C BS: BW↑ f _o	D START SWEEP	E f → τ _g , etc	0 CLR: LP or BP SET: HP or BS	1 CLR: LINEAR SET: LOG	FLAGS	TRIG	DISP
a CHEBYCHEV	b HP: f _o	c BP: BW↑ f _o	d SELECT LOG/LIN SWP	e f _{start} ↑ Δf	0 CLR: LP or BP SET: HP or BS	1 CLR: LINEAR SET: LOG	0 ON OFF	DEG ■	FIX SCI
0 SUMMATION	1 MULTIPLE LABEL	2	3	4	2	2	1	GRAD RAD	ENG ■
5	6	7 SWEEP START	8 BS, HP OUTPUT	9 PRINT & SPACE SUBROUTINE	3	3	2	3	n 3

Suggested HP-67 program changes. The "print" command is used to output data in the program listing. These print commands are located at the following line numbers: 070, 191, 196, and 198. HP-67 users may prefer either a "pause" or "R/S" command replacing the "print" command at the above line numbers. If the R/S change is made, the program execution will stop at each data output point. To resume program execution, execute a "R/S" command from the keyboard.

PROGRAM 2-3 BUTTERWORTH AND CHEBYSHEV LOWPASS NORMALIZED COEFFICIENTS.

Program Description and Equations Used

This program calculates the normalized (1 ohm, 1 radian/second cut-off) element values for either the Butterworth (maximally flat) or Cheby-shev (equal ripple passband) all pole lowpass filter approximations. The filters can be either doubly terminated (resistors at both ends) or singly terminated (driven from a voltage or current source, i.e., R_T approaches infinity). Because of duality, two filter topologies exist for the ladder filter as shown in Fig. 2-3.1. These topologies are bilateral and passive; therefore, the voltage source can be placed in series with the left-hand termination resistor as shown, or in series with the right-hand termination resistor. By proper selection of the filter topology and input port designation, the singly terminated filter can be driven from either a current or voltage source and resistively terminated, or driven from a Thevenin (or Norton) equivalent source and terminated in either a short or open circuit.

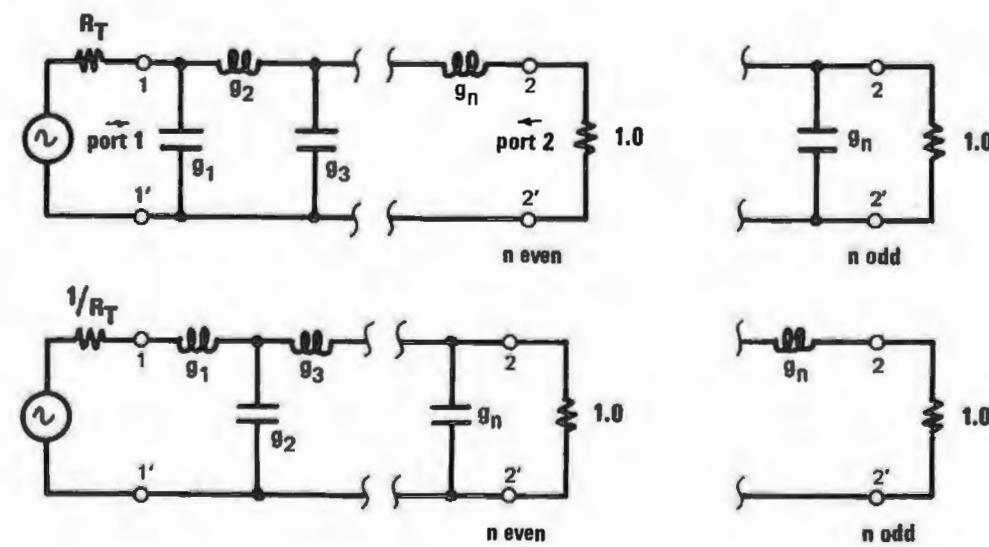


Figure 2-3.1 Lowpass ladder filter topologies.

The search for explicit formulas for ladder filter element values has extended over four decades. Bennett [7] provided the remarkably simple formula for equally terminated Butterworth filters in 1932.

Norton [39] provided the formulas for the open circuited Butterworth case in 1937. Belevitch [5] published formulas for the doubly terminated Chebyshev case in 1952. Orchard [40] gathered together this previous work and provided the missing fourth formula set for the open circuited Chebyshev case in 1953. Green [28] went on to generalize these formulas for any ratio of resistive terminations in 1954. These formulas had been numerically tested, but never formally proved. Doyle [22] provided a "hammer and tongs" brute force proof for the Butterworth case with arbitrary terminations. Meanwhile, in Japan, Takahasi [51], had made an ingenious proof of the formulas for the arbitrarily terminated Chebyshev case and extended it to the Butterworth case by a limiting process. Takahasi published his independent work in 1951 (in Japanese), but it was not discovered by the rest of the world until 1957.

Weinberg and Slepian [54] discuss Takahasi's results. Takahasi's results can also be found in the back of Weinberg's book [53].

The recursion relations given by Eqs. (2-3.1) through (2-3.16) are adapted from Takahasi. If the filter order is odd, the filter can be terminated by 1 ohm at one port and by any resistance 1 ohm or larger at the other port. By using the dual topology, the termination resistance can be any resistance 1 ohm or smaller (including 0 ohms). If the filter is an even ordered Chebyshev design, then the first port termination resistance must be larger than 1 ohm. The minimum value of this termination resistance is given by Eq. (2-3.18).

Takahasi's recursion relationships:

$$g_{r+1} = \frac{A \cdot s_r - \frac{1}{2} \cdot s_{r+\frac{1}{2}}}{g_r (\xi^2 + \eta^2 - \xi \eta c_r + s_r^2)} \quad (2-3.1)$$

where

$$r = 1, 2, \dots, n-1$$

$$g_1 = \frac{\sqrt{A} \cdot s_{\frac{1}{2}}}{R_T (\xi - \eta)} \quad (2-3.2)$$

$$s_q = 2 \cdot \sin\left(\frac{\pi \cdot q}{n}\right) \quad (2-3.3)$$

$$c_q = 2 \cdot \cos\left(\frac{\pi \cdot q}{n}\right) \quad (2-3.4)$$

For normalized lowpass Butterworth coefficients:

$$A = 1 \quad (2-3.5)$$

$$\xi = 1 \quad (2-3.6)$$

$$\eta = \left(\frac{R_T - 1}{R_T + 1} \right)^{1/n} \quad (2-3.7)$$

$$s_r^2 \equiv 0 \quad (2-3.8)$$

For normalized lowpass Chebyshev coefficients:

$$A = 4 \quad (2-3.9)$$

$$\xi = F(1) \quad (2-3.10)$$

$$\eta = F \left(1 - \frac{4 \cdot v R_T}{(1 + R_T)^2} \right) \quad (2-3.11)$$

$$v = \begin{cases} 1 + \xi^2, & n \text{ even} \\ 1, & n \text{ odd} \end{cases} \quad (2-3.12)$$

$$F(x) = u - \frac{1}{u} \quad (2-3.13)$$

$$u = \left(\sqrt{\frac{x}{\epsilon^2}} + \sqrt{\frac{x}{\epsilon^2} + 1} \right)^{1/n} \quad (2-3.14)$$

$$y = 10^{\frac{e \text{ dB}}{20}} \quad (2-3.15)$$

$$\epsilon^2 = y^2 - 1 \quad (2-3.16)$$

$$\omega_{-3 \text{ dB}} = \cosh \left(\frac{1}{n} \cosh^{-1} \frac{1}{\epsilon} \right) \quad (2-3.17)$$

$$R_L \Big|_{\substack{\min \\ n \text{ even}}} = \left(\frac{\sqrt{\frac{y+1}{y-1}} - 1}{\sqrt{\frac{y+1}{y-1}} + 1} \right)^2 \quad (2-3.18)$$


User Instructions

When the termination ratio is neither 0, ∞ , or as close as possible to 1, there are more than one possible set of ladder element values for the same filtering function. These alternate sets are synthesized by realizing the reflection zeros in the RHP, or RHP-LHP alternating rather than in the LHP. The closed form formulas realize the LHP reflection zero case. This realization generally results in a ladder filter with minimum sensitivity to component value changes. For a more comprehensive discussion of reflection zeros and order of realization, see Weinberg [53], chapter 13.

The program is set up to calculate the minimum termination resistance, and if the value loaded by the user is less than the minimum, the minimum value replaces the user loaded value.


When the termination resistance is allowed to approach infinity (or 0 using the dual topology), the filter only has one termination resistor, and is called "singly terminated." These singly terminated filters are used where it is inconvenient, or wasteful of power, to use the doubly terminated filter. Because the loaded Q's of the resonant circuits become higher as the unloaded end of the filter is approached, the singly terminated design is more difficult to align.

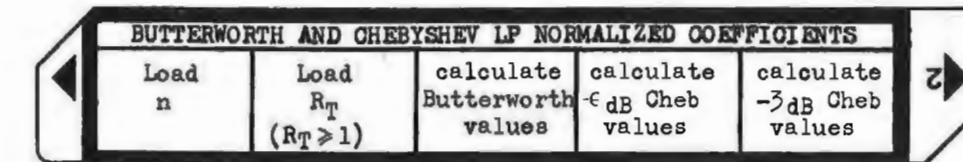Often, the LC filter is used as a basis for an active filter design such as Szentirmai's leapfrog topology [48], Bruton's frequency dependent negative resistor (FDNR) approach [10], or Orchard and Sheahans' type II active simulation [42]. Using the doubly terminated LC topologies for the active filter basis, will also mean that the active filters will be less critical toward alignment.



STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
1	Load both sides of magnetic card			
2	Load filter order ($n = 12$ maximum) If the normalized lowpass prototype is to be transformed to bandpass types 6, 7, 8, 9, 10, or 11, and Chebyshev response is desired, the filter order must be odd so the terminations will be equal resistance.	n	A	n
3	Load the termination resistance desired The termination resistance must be 1 or larger. For terminations less than 1 ohm (normalized) load the reciprocal value and use the dual topology. See note after step 7.	R_T	B	
4	For Butterworth coefficients		C	R_T space g_1 g_2 : g_n space $R_L = 1$
5	For Chebyshev coefficients that define a filter that is $-\epsilon$ dB down at $\omega = 1$ If even ordered Chebyshev has been selected, the minimum source resistance is calculated and is used if the resistance loaded in step 3 is smaller.	ϵ_{dB}	D	ω_{-3} dB space R_T space g_1 g_2 : g_n space $R_L = 1$

User Instructions

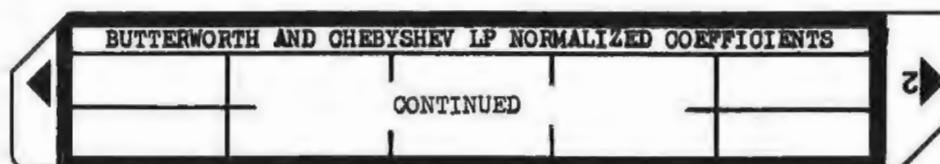

STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
6	For Chebyshev coefficients that define a filter that is 3 dB down at $\omega=1$. The minimum source resistance comment for even ordered Chebyshev filters in step 5 also applies here.	6dB	E	ω_{-3} dB space R_T space g_1 g_2 : g_n space R_L 1
7	Go back and repeat any step. The last calculated coefficients will be in storage for use by other programs in this section.			
	Notes on termination resistance: To enable the program to output coefficients for the singly terminated case, load 10^5 ohms for R_T if Chebyshev response is going to be selected, or load 10^9 ohms if Butterworth response is going to be selected. Either one of these values is a reasonable approximation to infinity when compared to one ohm. The maximum termination resistance in the Chebyshev case is limited to 10^5 ohms because of a small difference between big numbers problem. 10^5 ohms is a compromise between an approximation to infinity and the number of significant digits in the coefficients. With 10^5 ohms, the answers are significant to five places.			

Example 2-3.1

Find the normalized lowpass coefficients for a 4th order, $\frac{1}{2}$ dB ripple Chebyshev filter that is doubly terminated, and has the minimum termination resistance. The filter response should be 3 dB down at the passband edge ($\omega = 1$) relative to the response at dc.

HP-97 printout

```

4. GSBP    load filter order
1. GSBR    load termination resistance desired
.3 GBRZ   enter passband ripple in dB and calculate
           Chebyshev coefficients
914.626-03 ***  $\omega_{-3}$  dB (output)
1.98406+00 *** minimum termination resistance allowed at port 1
920.243-03 ***  $g_1$ 
2.58640+00 ***  $g_2$ 
1.30355+00 ***  $g_3$ 
1.82581+00 ***  $g_4$ 
1.00000-00 *** port 2 termination resistance

```

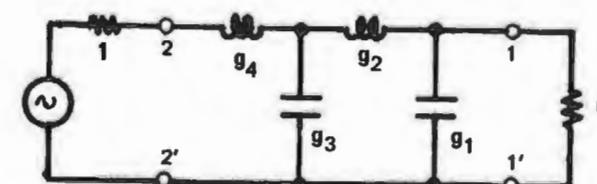


Figure 2-3.2 One topology for normalized lowpass filter (port ordering reversed).

Example 2-3.2

Find the normalized lowpass coefficients for a 10th order Butterworth filter that is singly terminated.

HP-97 printout

```

10. E:ELH load filter order
1.+.05 G3EE load termination resistance (use 105 for Chebyshev)
G5BC calculate Butterworth coefficients
1.00000+03 .xx termination resistance at port 1
1.56434+00 .xx g1
1.85316+01 .xx g2
1.81214+00 .xx g3
1.53653+00 .xx g4
1.51000+00 .xx g5
1.42053+00 .xx g6
1.34962+00 .xx g7
7e1.527+03 .xx g8
465.375+03 .xx g9
1E6.434+03 .xx g10
1.00000+01 .xx termination resistance at port 2

```

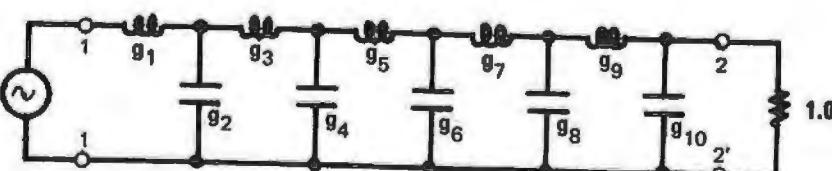


Figure 2-3.3 One form for normalized lowpass filter (dual topology used).

Program Listing I

2-3

061	*LBLH	LOAD FILTER ORDER	057	-
062	ST06	STORE FILTER ORDER	058	=
063	PI		059	N
064	X2Y	CALCULATE AND STORE π/n	060	RCLD
065	/		061	X2Y?
066	ST01		062	RJ
067	RCLE		063	GSB6
068	RTN		064	F29
069			065	F29
070			066	ST0D
071			067	EEX
072			068	GSB7
073			069	ST02
074			070	RCL3
075			071	1/X
076			072	JX
077			073	LSTX
078			074	EEX
079			075	-
080			076	$\omega_{-3dB} = \cosh\left(\frac{1}{n} \cosh^{-1}\frac{1}{\epsilon}\right) \rightarrow R_0$
081			077	+
082			078	GSB4
083			079	1/X
084			080	-
085			081	2
086			082	-
087			083	ST08
088			084	F29
089			085	1/X
090			086	GSE3
091			087	calculate
092			088	$\left\{ \begin{array}{l} 1+\epsilon^2, n \text{ even} \\ 1, n \text{ odd} \end{array} \right.$
093			089	calculate and store:
094			090	$\eta = F\left(1 - \frac{4\sqrt{R_T}}{(1+R_T)^2}\right) \rightarrow R_3$
095			091	X<0 default
096			092	CLX
097			093	GSB7
098			094	ST03
099			095	*LEL9
100			096	RCLD
101			097	P#S
102			098	CLRG
103			099	clear coefficient registers
104				
105				
106				
107				
108				
109				
110				
111				
112				

REGISTERS									
0	ω_{-3dB}	1	$\frac{\pi}{n}$	2	$\xi, 1$	3	$\epsilon^2, \eta, \lambda$	4	g_r
S0	g_1	S1	g_2	S2	g_3	S3	g_4	S4	g_5
A	g_{11}	B	g_{12}	C	g_{13}	D	R_T	E	$y, \sqrt{\frac{y+1}{y-1}}, c_{2r}$

Program Listing II

NOTE TRIG MODE

113	P+S	169	GT01
114	STOD	170	SPC
115	GSB3 print actual termination R	171	EEX
116	1/X	172	*LBL3 print and space subroutine
117	ST04 initialize registers	173	PRTX
118	EEX	174	SPC
119	1	175	RTN
120	ST01	176	*LBL5 subroutine to finish g_{r+1}
121	EEX	177	-
122	ST07	178	ST+4 calculation, store result,
123	.	179	RCL0
124	5	180	PCL4 and setup g_r for next
125	ST08 calculate and store:	181	ST+4 iteration
126	GSB8	182	ST+4
127	ST09	183	F0? x
128	ENT↑	184	ST01
129	F1?	185	PRTX
130	+ A ^{1/2} · S _r	186	RTN
131	STx4 if Chebyshev use A = 4,	187	*LBL6 subroutine to set flag 2 if filter order is odd
132	RCL2 otherwise use A = 1	188	RCL6
133	RCL3	189	2
134	GSB5	190	÷
135	*LBL1 recursion loop start	191	FRC
136	ISZI increment register index	192	X#0?
137	RCL9 S _{r+1/2} start g_{r+1} calculation	193	SF2
138	STx4	194	R↓
139	EEX	195	RTN
140	ST+8	196	*LBL7 subroutine to calculate:
141	RCL8	197	RCL3
142	GSB8 S _{r-1/2}	198	÷
143	STx4	199	STX
144	ST03	200	ENT↑ F(x) = u - $\frac{1}{u}$
145	4	201	X ²
146	F1? if Chebyshev, use A = 4	202	EEX
147	STx4	203	+
148	RCL7 finish g_{r+1} calculation	204	STX
149	GSB8 X ²	205	GSB4 u = $\sqrt{\frac{x}{\epsilon^2} + \sqrt{\frac{x}{\epsilon^2} + 1}}$
150	RCL2 X ²	206	1/X
151	X ²	207	STOE
152	F1? add s_r^2 if Chebyshev	208	RTN
153	+ RCL3 X ²	209	-
154	RCL3 X ²	210	RTN
155	X ²	211	*LBL4 subroutine to calculate:
156	+	212	RCL1
157	RCL1 1/X	213	2
158	RCL2 Y ^x	214	() ^{1/n} → Rx → Ry
159	RCL2 X ²	215	ENT↑ RTN
160	X ²	216	
161	RCL3 X ²	217	*LBL8 subroutine to calculate:
162	X ²	218	RCL1
163	GSB5 EEX	219	X ²
164	increment r	220	2 s _q = 2 sin $(\frac{\pi q}{n})$ → Rx
165	ST+7	221	→ R
166	RCL7	222	STOE c _q = 2 cos $(\frac{\pi q}{n})$ → R _E
167	RCL6 test for loop exit	223	R↓
168	X>Y?	224	RTN
NOTE TRIG MODE			
LABELS			
A filter order	B R _T	C Butterworth coefficients	D -6dB Cheb coefficients
a	b	c	d e
0 recursion loop setup	1 recursion loop start	2 Chebyshev -3dB jump	3 print & space
5 store g _{r+1}	6 SF2 if n odd	7 F(x)	8 s _q ε c _q
FLAGS			
0 -3dB Cheb	1 Chebyshev	FLAGS	TRIG
1	2	ON OFF	DEG
2	3	■	GRAD
3	3	■	RAD ■
SET STATUS			
0	1	2	3
1	2	3	4
2	3	4	5
3	4	5	6

PROGRAM 2-4 NORMALIZED LOWPASS TO BANDSTOP, LOWPASS, OR HIGHPASS LC LADDER TRANSFORMATIONS.

Program Description and Equations Used

This program transforms the normalized lowpass coefficients (1 ohm, 1 radian/sec) into the frequency and impedance scaled lowpass, highpass, or bandstop topologies. The normalized lowpass coefficients are obtained from register storage and either must be loaded by the user (for other than Butterworth and Chebyshev filters), or are generated and stored by Program 2-3 for the Butterworth and Chebyshev approximations.

Every linear, passive, lumped, time-invariant, bilateral electrical network has a dual topology. LC filters are a member of this class of networks; hence, two electrically equivalent networks can be formed from the transformation or scaling of the normalized lowpass structure. These two forms are designated as form 1, and form 2 in the program. Having two forms available provides the designer some relief from awkward component values, or the opportunity to choose the minimum inductor topology.


The program is separated into three parts which share common subroutines. These sections are 1) de-normalization parameter input (bandwidth, termination resistance level, and center frequency), 2) bandstop denormalization and transformation, and 3) lowpass and highpass denormalization and transformation. In analytical form, these transformations are discussed next.

Lowpass filters: No transformation is necessary for converting the normalized lowpass to the un-normalized lowpass filters. The normalized lowpass values need only be scaled to the desired operating impedance level and cutoff frequency. The object of the scaling procedure is to end up with filter elements that have the same impedance ratios to the termination resistance at the cutoff frequency as the normalized filter has at 1 radian/second to 1 ohm. The mechanics of this scaling procedure are:


$$L_{\text{scaled}} = (L_{\text{normalized}}) \cdot (R / (2\pi \cdot BW)) \quad (2-4.1)$$

$$C_{\text{scaled}} = (C_{\text{normalized}}) / (2\pi \cdot BW \cdot R) \quad (2-4.2)$$

The normalized L's and C's are equal to the g's from Program 2-3, and BW and R represent the cutoff frequency in Hz and the load resistance in ohms respectively. Figure 2-4.1 shows the two forms of the lowpass filter; either port can be designated as input, i.e., the input voltage source can go in series with either termination resistor.

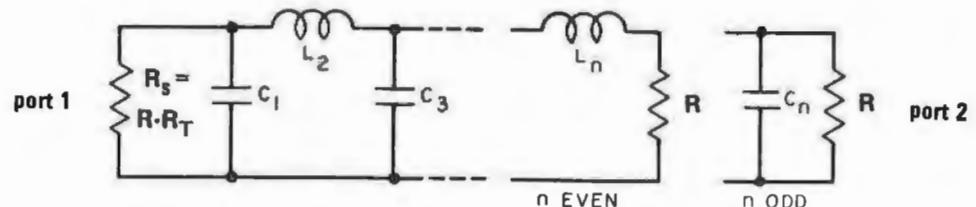

FORM 1

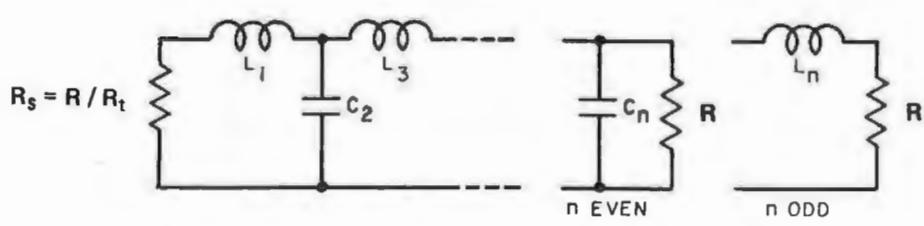

FORM 2

Figure 2-4.1 Two forms of lowpass filter.

Highpass filters: The highpass transformation is accomplished by replacing s by 1/s. Since sinusoidal frequencies are of primary interest, s may be replaced by $j\omega$, or 1/s by $-j/\omega$. Conceptually, this operation is equivalent to replacing each normalized lowpass capacitor with an inductor and vice-versa. The normalized values of the highpass elements are the reciprocals of the lowpass values, i.e., the g's calculated in Program 2-3 become 1/g's when converted to normalized highpass coefficients. Fig. 2-4.2 shows the two forms of the highpass filter, and the element values are calculated using Eqs. (2-4.1) and (2-4.2) with the normalized highpass coefficients. Either port can be designated as the input as in the lowpass case (or in any other passive LC case).

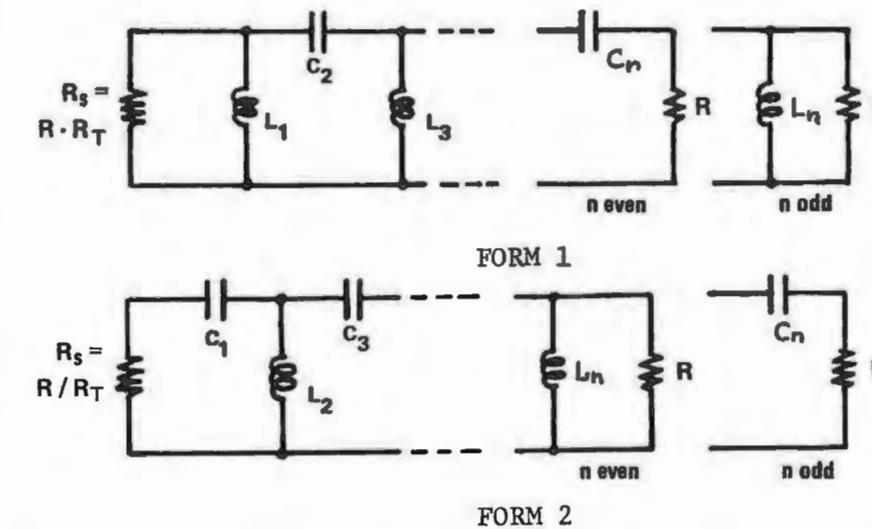


Figure 2-4.2 Two forms of highpass filter.

The highpass transformation may also be applied analytically; for example, the transformation is applied to the Butterworth normalized lowpass magnitude response equation (Eq. (2-4.3)) to convert it to the normalized highpass form (Eq. (2-4.4)).

$$|A(\omega)|_{\text{LP}} = \frac{1}{\sqrt{1 + \omega^{2n}}} \quad (2-4.3)$$

$$|A(\omega)|_{\text{HP}} = \frac{\omega^n}{\sqrt{1 + \omega^{2n}}} \quad (2-4.4)$$

For more information, see Weinberg [53]. Blinchikoff and Zverev [8] also has an excellent discussion of transformations both conventional as used herein, and unconventional to preserve LP transient characteristics.

Bandpass filters: The bandpass filter is a combination of a highpass and a lowpass filter. The loaded Q, Q_L , of the filter is a measure of the separation between the highpass and lowpass portions. To accomplish the transformation from normalized lowpass to un-normalized bandpass, s in the normalized lowpass expression is replaced by the function of s shown in Eq. (2-4.5).

$$s \Rightarrow Q_L \left\{ \frac{s}{\omega_0} + \frac{\omega_0}{s} \right\} \quad (2-4.5)$$

$$Q_L = \frac{f_0}{BW} \quad (2-4.6)$$

Where f_0 and BW are the center frequency and bandwidth in hertz.

Conceptually, the lowpass elements are replaced with new elements that exhibit the same impedance behavior at the bandpass filter center frequency as did the original elements at dc. Ideal inductors have zero reactance at dc, and are replaced with series resonant tank circuits which resonate at the bandpass filter center frequency, f_o . Ideal (lossless) series tank circuits have zero reactance at resonance. Likewise, each lowpass capacitor is replaced with a parallel resonant tank circuit which resonates at the bandpass filter center frequency. When the loaded Q is greater than 10 or so, the bandpass filter is called narrowband. In this case, other tank circuits can be synthesized to approximate the impedance behavior of the series and parallel resonant tank circuits for frequencies within the vicinity of the passband. Bandpass filters and narrowband transformations are discussed in Programs 2-5, 2-6, and 2-11.

Bandstop filters: The bandstop transformation is the reciprocal of the bandpass transformation, and is analogous to the low-pass-highpass transformation. Highpass filters are actually bandstop filters which have zero center frequency. To accomplish the bandstop transformation, s is replaced by:

$$s \Rightarrow \frac{1}{Q_L \left\{ \frac{s}{\omega_0} + \frac{\omega_0}{s} \right\}} \quad (2-4.7)$$

Conceptually the bandstop transformation is accomplished by designing a highpass filter whose cutoff frequency equals the bandwidth of the desired bandstop filter. Each shunt inductor in the highpass filter is series resonated with a capacitor at the desired center frequency of the filter. Likewise, each series capacitor is parallel resonated with an inductor at the desired filter center frequency.

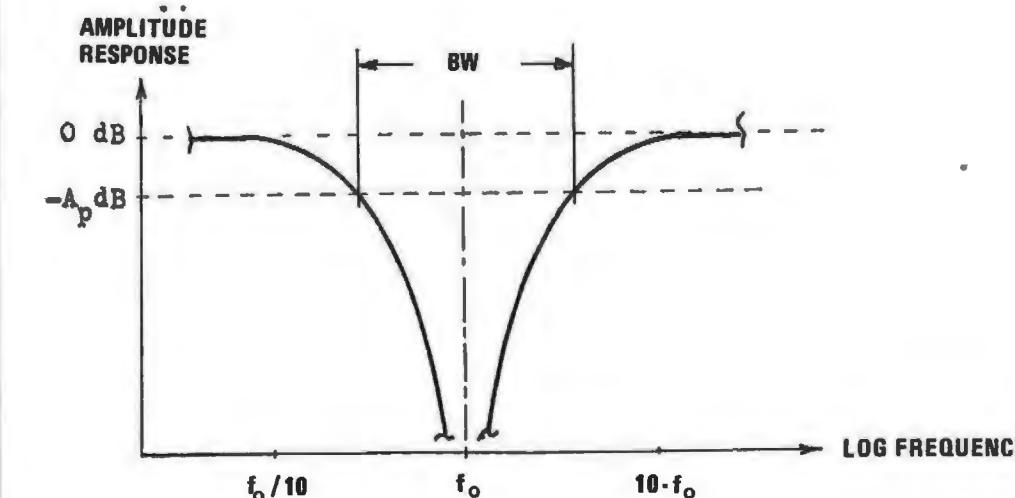


Figure 2-4.1 Bandstop filter parameters.

If g_1, g_2, \dots, g_n are the normalized lowpass coefficients and R_T is the normalized termination resistance, then one form of the bandstop filter is shown by Fig. 2-4.2 .

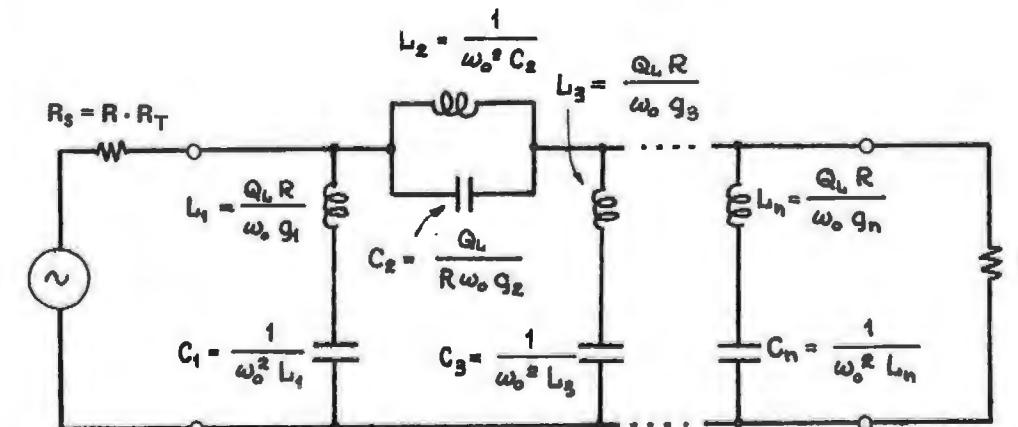


Figure 2-4.2 Bandstop filter form 1 (program output heading "21"), odd order filter shown; even order filter lacks last series tank circuit.

The other form of this filter is the dual of the first:

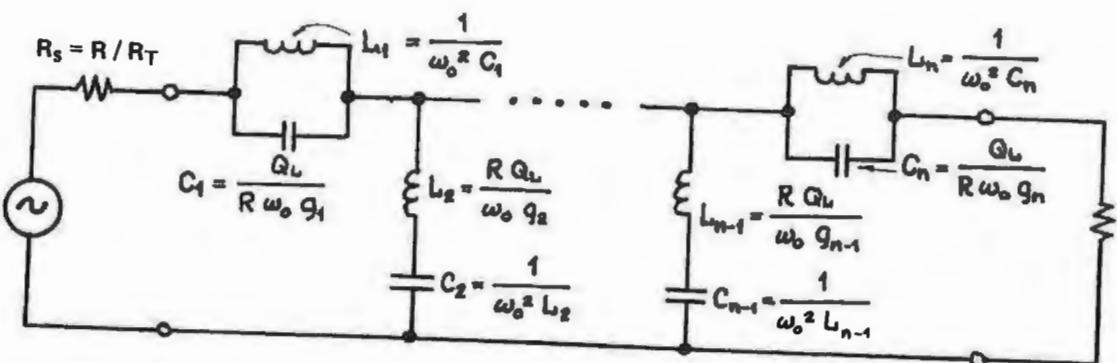


Figure 2-4.3 Bandstop form 2 (program output heading "22"), odd order filter shown; even order filter lacks last parallel tank circuit.

The program calculates both forms of these bandstop filters.

Filter physical realizability. The preceding transformations are used by this program and result in LC network schematics that will produce the desired response. Not all LC networks that can be drawn on paper as schematics are physically realizable. For example, a network branch consisting of a 1 μF capacitor in series with a 10 nh inductor would be nearly impossible to realize since the self inductance of the capacitor is much larger than the total required inductance. Table 2-4.1 is a reproduction of Table 7.1 from White [56], and shows the degree of physical realizability of lowpass and highpass filters. The physical realizability of a filter is assigned one of four possible scores. These scores are defined as follows:

Readily realizable (R): $1 \mu\text{h} \leq L \leq 1 \text{ h}$
 $5 \text{ pF} \leq C \leq 1 \mu\text{F}$

Practical (P): $200 \text{ nh} \leq L \leq 10 \text{ h}$
 $2 \text{ pF} \leq C \leq 10 \mu\text{F}$

M marginally practical (M): $50 \text{ nh} \leq L \leq 100 \text{ h}$
 $0.5 \text{ pF} \leq C \leq 500 \mu\text{F}$

Impractical (I): All element values that lie outside the marginal range, i.e.,

$L < 50 \text{ nh}$
 $L > 100 \text{ h}$
 $C < 0.5 \text{ pF}$
 $C > 500 \mu\text{F}$

The table headings are meant to indicate ranges of filter cutoff frequency and termination impedance level. These ranges are defined as follows:

Frequency,

- $f_o = 10 \text{ Hz}$ implies: $3 \text{ Hz} \leq f_o < 30 \text{ Hz}$
- $f_o = 100 \text{ Hz}$ implies: $30 \text{ Hz} \leq f_o < 300 \text{ Hz}$
- $f_o = 1 \text{ kHz}$ implies: $300 \text{ Hz} \leq f_o < 3 \text{ kHz}$
- $f_o = 10 \text{ kHz}$ implies: $3 \text{ kHz} \leq f_o < 30 \text{ kHz}$
- $f_o = 100 \text{ kHz}$ implies: $30 \text{ kHz} \leq f_o < 300 \text{ kHz}$
- $f_o = 1 \text{ MHz}$ implies: $300 \text{ kHz} \leq f_o < 3 \text{ MHz}$
- $f_o = 10 \text{ MHz}$ implies: $3 \text{ MHz} \leq f_o < 30 \text{ MHz}$
- $f_o = 100 \text{ MHz}$ implies: $30 \text{ MHz} \leq f_o < 300 \text{ MHz}$

At frequencies above 300 MHz, lumped element filters are generally replaced with transmission line type filters.

Impedance Level (source and load resistances equal)

- $R = 3 \text{ ohms}$ implies: $1 \leq R < 10$ (power filters)
- $R = 50 \text{ ohms}$ implies: $10 \leq R < 150$
- $R = 500 \text{ ohms}$ implies: $150 \leq R < 2.5k$
- $R = 10k \text{ ohms}$ implies: $2.5k \leq R < 50k$

Table 2-4.1 Physical realizability of lowpass and highpass filters.

R in ohms	Cutoff Frequency, f_c							
	10 Hz	100 Hz	1 kHz	10 kHz	100 kHz	1 MHz	10 MHz	100 MHz
3	I	M	M	P	R	P	M	I
50	M	M	M	R	R	R	R	M
500	M	P	R	R	R	R	R	R
10k	I	M	P	R	R	R	P	I

Courtesy, Don White Consultants, Inc.

Bandstop filter physical realizability must include one additional parameter, the loaded Q of the filter, Q_L . As Q_L becomes higher (filter

becomes more narrow) the separation in element value between the series tank elements and the parallel tank elements increases as Q_L . Table 2-4.2 is adapted from Table 7.2 in White and assigns realizability scores to bandstop (and bandpass) filters. The loaded Q ranges are defined as follows:

Loaded Q (Q_L), for bandpass and bandstop,

$$Q_L = 5 \text{ implies: } 3 \leq Q_L < 10$$

$$Q_L = 15 \text{ implies: } 10 \leq Q_L < 30$$

$$Q_L = 50 \text{ implies: } 30 \leq Q_L \leq 100$$


Table 2-4.2 Physical realizability of bandstop filters.

Filter Prototype		$f_0 = 1\text{kHz}$						$f_0 = 10\text{kHz}$											
		$Q_L = 5$			$Q_L = 15$			$Q_L = 50$			$Q_L = 5$			$Q_L = 15$			$Q_L = 50$		
Type		50	500	10K	50	500	10K	50	500	10K	50	500	10K	50	500	10K	50	500	10K
1st	I	P	P	I	I	I	I	I	I	I	M	R	P	I	M	P	I	M	P
	I	P	P	I	I	I	I	I	I	I	M	R	P	I	M	I	I	M	P
Filter Prototype		$f_0 = 100\text{kHz}$						$f_0 = 1\text{MHz}$											
		$Q_L = 5$			$Q_L = 15$			$Q_L = 50$			$Q_L = 5$			$Q_L = 15$			$Q_L = 50$		
Type		50	500	10K	50	500	10K	50	500	10K	50	500	10K	50	500	10K	50	500	10K
1st	P	R	R	P	P	I	M	M	I	P	R	P	P	P	I	M	P	I	
	P	R	R	P	P	I	M	M	I	P	R	P	P	P	I	M	M	I	
Filter Prototype		$f_0 = 10\text{MHz}$						$f_0 = 100\text{MHz}$											
		$Q_L = 5$			$Q_L = 15$			$Q_L = 50$			$Q_L = 5$			$Q_L = 15$			$Q_L = 50$		
Type		50	500	10K	50	500	10K	50	500	10K	50	500	10K	50	500	10K	50	500	10K
1st	M	P	M	I	P	I	I	I	I	I	I	I	I	I	I	I	I	I	I
	M	P	M	I	P	I	I	I	I	I	I	I	I	I	I	I	I	I	I

Courtesy Don White Consultants Inc.

As the loaded Q increases, the element value spread can become unmanageable. This problem can be reduced by using narrowband transformations which are used in Programs 2-5 and 2-6 for the bandpass case. Narrowband transformation schematics for the bandstop case may be found on p. 217 of the ITT handbook [44]. The concept of coupling and narrowband transformations was introduced by Milton Dishal [21], and expanded by Seymour Cohn [16] for the bandpass case.

User Instructions

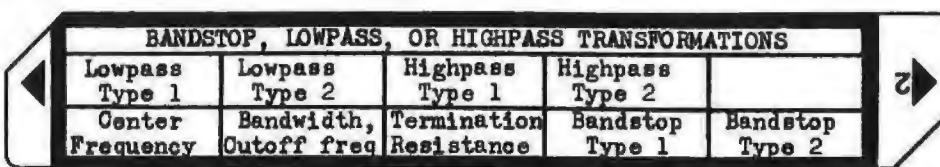

STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
1	Load both sides of magnetic card			
2	For lowpass filter component values:			
a)	load cutoff frequency in hertz	f_{cutoff}	<input type="checkbox"/> B <input type="checkbox"/> C	
b)	load termination resistance in ohms	R		
c)	for type 1 filter (capacitor first)*		<input type="checkbox"/> f <input type="checkbox"/> A	R_s
				C_1
				L_2
				\vdots
				$C_n \text{ or } L_n$
				R
d)	for type 2 filter (inductor first)*		<input type="checkbox"/> f <input type="checkbox"/> B	R_s
				L_1
				C_2
				\vdots
				$L_n \text{ or } C_n$
				R
3	For highpass filter component values:			
a)	load cutoff frequency in hertz		<input type="checkbox"/> B	
b)	load termination resistance in ohms		<input type="checkbox"/> C	
c)	for type 1 filter (inductor first)*		<input type="checkbox"/> f <input type="checkbox"/> C	R_s
				L_1
				C_2
				\vdots
				C_n
				R

User Instructions



STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
3	Highpass component values continued			
b)	for type 2 filter (capacitor first)*		<input type="checkbox"/> f <input type="checkbox"/> D	R_s
				C_1
				L_2
				\vdots
				$L_n \text{ or } C_n$
				R
4	For bandstop filter component values:			
a)	load filter center frequency in hertz	f_o	<input type="checkbox"/> A	
b)	load filter bandwidth in hertz	BW	<input type="checkbox"/> B	
c)	load termination resistance in ohms	R	<input type="checkbox"/> C	
d)	for type 1 filter (series tank first)*		<input type="checkbox"/> D	R_s
				C_1^{**}
				L_1
				C_2
				L_2
				\vdots
				C_n
				L_n
				R
e)	for type 2 filter (parallel tank first)*		<input type="checkbox"/> E	R_s
				C_1
				L_1
				\vdots
				C_n
				L_n
				R

NOTES:

- * All capacitor values are in farads, all inductor values are in henries and all resistor values are in ohms.
- ** In all section 2 programs where resonant tank components are printed, the capacitor is always printed first.

Example 2-4.1 Singly terminated lowpass filter

A maximally flat (Butterworth) lowpass filter must pass a 1 kHz signal with 1 dB or less attenuation relative to the filter response at dc, and must reject a 12 kHz signal by at least 75 dB. Program 2-1 is used to predict the required filter order, and -3 dB cutoff frequency (Butterworth cutoff frequency) with $A_{p\text{dB}} = 1 \text{ dB}$, $A_{s\text{dB}} = 75 \text{ dB}$, and $\lambda = 12$. A filter order of 3.75 is calculated, which is rounded to the next largest integer, 4. Re-entering the program with $A_{s\text{dB}} = 3$ and $n = 4$, yields $\lambda = 1.183301$, which means the 3 dB cutoff frequency is $(1000)(1.183301) = 1183.301 \text{ Hz}$.

Next, Program 2-3 is loaded to obtain the normalized lowpass coefficients for a singly terminated 4th order Butterworth filter. The coefficients are automatically stored for use by this program.

Load this program, load the above cutoff frequency, and select an operating impedance level from Table 2-4.1. An impedance level of 500 ohms will result in a readily realizable filter. Both the type 1 and type 2 topologies can be calculated and the most attractive one selected. The HP-97 printout for the above operations is shown on the next page.

Programs 3-1 and 3-2 can be used to design the inductors needed for this design. If an active filter approach can be considered, see Program 2-9 for a lowpass active filter design.

HP-97 printout for Example 2-4.1, lowpass filter design.

Load Program 2-1 to calculate required filter order:

```

G5B.. select Butterworth
1.00 G5BA load ApdB
75.00 G5BB load AsdB
12.00 G5BC load λ, and calculate n, the filter order
3.75 *** n (output)

3.00 G5BE load new AsdB
4.00 G5BC load integral filter order, n, and calculate λ
1.183301 *** λ (output)

```

Load Program 2-3 to generate and store the normalized lowpass coeffs.

```

4. G5Bh load filter order
1.+05 G5BE load termination resistance desired
G5BC calculate Butterworth coefficients
1.000000+09 *** RT (normalized)

1.53073+00 *** g1
1.57716+00 *** g2
1.08239+00 *** g3 } lowpass normalized coefficients
382.683-03 *** g4
1.00000+00 *** R (normalized)

```

Load this program (Program 2-4) to obtain un-normalized filter.

```

1181.301 G5BE load un-normalized cutoff frequency
500. G5BC load termination resistance, R
G5Ba calculate type 1 lowpass filter (capacitor first)

```


31. lowpass type 1 output code

500.0+09 *** R_s (open circuit)

```

412.5-09 *** C1
106.2-03 *** L2
291.7-05 *** C3
25.78-03 *** L4

```

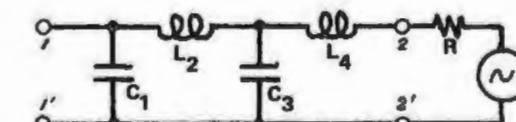

500.0+00 *** R

G5Bb calculate type 2 lowpass filter (inductor first)


32. lowpass type 2 output code

500.0-09 *** R_s (short circuit)

```

103.1-03 *** L1
425.0-09 *** C2
72.91-03 *** L3
103.1-09 *** C4

```

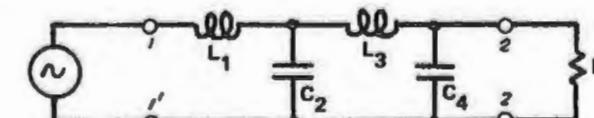

500.0+00 *** R

Example 2-4.2 Doubly terminated highpass filter

A highpass filter is required to keep the signal from a local CB transmitter from causing cross modulation interference in the tuner of a TV set. The filter will be placed in series with the 300 ohm balanced line from the antenna to the TV set, hence, the filter will be designed for a 300 ohm terminating impedance level. The filter must pass the TV spectrum which starts at 54 MHz, but must reject the CB radio band at 27 MHz. One dB of ripple is allowed across the TV spectrum, and at least 60 dB rejection is needed at the CB band frequencies. Because of the allowed ripple, a Chebyshev filter will be used. Program 2-1 calculates a minimum filter order of 7 as shown below along with the rest of the HP-97 printout for this design:

Load Program 2-1 to obtain minimum filter order required:

```

G3E6 select Chebyshev
1.00 G3E4 load ApdB
60.00 G3EE load AsdB
2.00 G3B2 load λ and calculate filter order, n
6.2d *** n (output)

7.00 G3B1 load integral filter order, n
1.78 *** λ where filter is 60 dB down (54/1.78 = 30.3)

2.00 G3E6 load λ and calculate AsdB
60.15 *** AsdB at 27 MHz

```

Load Program 2-3 to generate and store the normalized lowpass coefficients:

```

7. G3B4 load filter order
1. G3BB load termination resistance ratio
1. G3BD load Chebyshev passband ripple in dB and start
1.01721+00 *** normalized -3 dB frequency (output)

1.00000+00 *** RT (normalized)

2.10656+00 *** g1
1.11151+00 *** g2
3.09364+00 *** g3
1.17352+00 *** g4
3.05364+00 *** g5
1.11151+00 *** g6
2.16656+00 *** g7} normalized lowpass coefficients

1.00000+00 *** R (normalized)

```

This highpass example is for a balanced structure filter, and the program output is for an unbalanced structure (one side common). To convert the unbalanced structure to the balanced structure, capacitors are placed in each side of the filter, and their equivalent impedance is one-half the unbalanced value (twice the capacity).

Load this program, Program 2-4, to obtain the un-normalized filter:

54.466 GSBF	load cutoff frequency
300. GSBG	load denormalization resistance
GSEG	calculate type 1 highpass filter values
 41. highpass type 1 output code (inductor first)	
300.0+00 *** R _s	
408.1-05 *** L ₁	
8.833-12 *** C ₂	
265.8-05 *** L ₃	
8.372-12 *** C ₄	
265.8-05 *** L ₅	
8.833-12 *** C ₆	
408.1-05 *** L ₇	
300.0+00 *** R	
GSB _a calculate type 2 highpass filter values	
 42. highpass type 2 output code (capacitor first)	
300.0+00 *** R _s	
4.535-12 *** C ₁	
795.5-05 *** L ₂	
3.176-12 *** C ₃	
733.5-05 *** L ₄	
3.176-12 *** C ₅	
795.5-05 *** L ₆	
4.535-12 *** C ₇	
300.0+00 *** R	

Programs 3-5 and 3-6 can aid in the aircore inductor designs needed here.

Example 2-4.3 Bandstop filter

Consider implementing the filter cited in the previous example as a bandstop filter rather than as a highpass filter. The stopband required is from 26 MHz to 27 MHz. The center frequency of a bandstop (and bandpass) filter is the geometric mean of any two equal attenuation frequencies (this relationship does not hold for narrowband bandpass transformations for frequencies outside the passband). The center frequency of this bandstop filter is then 26.4953 MHz . If the upper -1 dB point is 54 MHz, then the lower -1 dB point is $(26.4953 \text{ MHz})^2 / (54 \text{ MHz}) = 13 \text{ MHz}$. The normalized frequency multiplier, λ , is the ratio between the passband and the stopband, or $\lambda = (54 - 13) / (27 - 26) = 41$. From Program 2-1, the filter order that meets these requirements is 2. Even ordered Chebyshev filters do not have equal termination resistance levels, and this filter is to be placed in a 300 ohm system (equally terminated). To satisfy all requirements including equal termination, a third order bandstop filter will be designed. The HP-97 printout for this filter design follows.

Load Program 2-1 to calculate the minimum filter order required:

```

GSBk select Chebyshev
1.00 GSBH load ApdB
60.00 GSBE load AsdB
41.00 GSBD load λ and calculate filter order, n
1.86 *** minimum n to meet requirements (use n = 2 min)

3.00 GSBC load n desired and calculate λ for AsdB = 60 dB
7.92 *** λ

41.00 } 1/λ form 1/λ
5.18 *** stopband bandwidth (MHz)
26.4953 GSBD enter center frequency (MHz) and calculate:
29.21 *** upper stopband edge (MHz)
24.03 *** lower stopband edge (MHz)

```

3. GSB4 load filter order
 1. GSB5 load termination resistance ratio desired
 1. GSB0 load Chebyshev passband ripple in dB and start
 λ for 3 dB bandwidth (output)

1.00000+00 *** R_T (normalized)
 2.02359+00 *** } normalized lowpass coefficients
 994.102-03 ***
 2.02359+00 ***

1.00000+00 *** R (normalized)

26.4553+06 GSB4 load filter center frequency
 41.+06 GSB5 load filter bandwidth
 300. GSB0 load de-normalization resistance level
 GSB0 calculate type 1 bandstop

21. type 1 bandstop heading (series tank first)

300.0+00 *** R_S

62.70-12 *** C₁

575.5-09 *** L₁


13.02-12 *** C₂

2.772-06 *** L₂

62.70-12 *** C₃

575.5-05 *** L₃

300.0+00 *** R

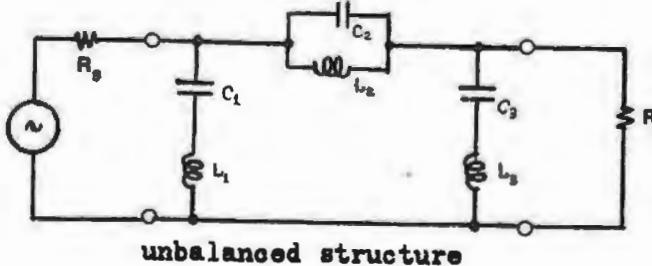

GSB5 calculate type 2 bandstop

22. type 2 bandstop heading (parallel tank first)

300.0+00 *** R_S

6.394-12 *** C₁


5.645-06 *** L₁

30.80-12 *** C₂

1.171-06 *** L₂

6.354-12 *** C₃

5.645-06 *** L₃

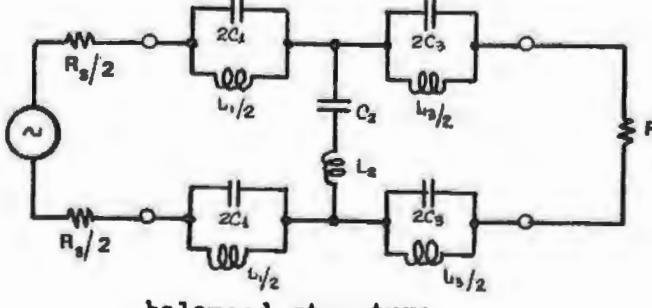

300.0+00 *** R

Program Listing I

<pre> 001 *LBLA LOAD CENTER FREQUENCY 002 Pi 003 ENT† 004 + 2πf_o → R0 005 X 006 ST08 007 RTN 008 *LBLB LOAD BANDWIDTH OR CUTOFF FREQ 009 Pi 010 ENT† 011 + 2πBW → R1 012 X 013 ST01 014 RTN 015 *LBLC LOAD DENORMALIZATION RESIST 016 ST02 R → R2 017 RTN 018 *LBLD BANDSTOP TYPE 1 ROUTINE 019 SPC 020 2 021 1 print heading "21" 022 PRTX 023 CF1 indicate type 1 topology 024 GT08 025 *LBLE BANDSTOP TYPE 2 ROUTINE 026 SPC 027 2 028 2 print heading "22" 029 PRTX 030 SF1 indicate type 2 topology 031 *LBL0 032 SF2 calculate and print R_S 033 GSB2 034 RCL2 035 RCL1 calculate and store: 036 X 037 RCL0 $\frac{R \cdot BW}{\omega_o^2} = \frac{R}{\omega_o \cdot Q_L} \rightarrow R4$ 038 X² 039 ÷ 040 ST04 041 RCL2 042 X² 043 ÷ $\frac{1}{R \cdot \omega_o \cdot Q_L} \rightarrow R5$ 044 ST05 045 CLX 046 ST07 initialize index registers 047 9 048 ST01 </pre>	<pre> 049 *LBL1 bandstop calculation loop 050 GSB9 increment indices and 051 XY? test for loop exit 052 GT04 053 SPC 054 RCL1 recall g_k 055 RCL4 recall R/(ω_o·Q_L) 056 CF0 set print order for type 1 057 F1? test for type 1 filter 058 GT06 059 CLX 060 RCL5 substitute 1/(R·ω_o·Q_L) in R_x 061 SF0 set print order for type 2 062 *LBL6 063 GSB8 gosub elt calculation & print 064 GSB9 increment indices and 065 XY? test for loop exit 066 GT04 067 SPC 068 RCL1 recall g_k 069 RCL5 recall 1/(R·ω_o·Q_L) 070 SF0 set print order for type 1 071 F1? test for type 1 filter 072 GT06 073 CLX 074 RCL4 substitute R/(ω_o·Q_L) in R_x 075 CF0 076 *LBL6 077 GSB8 gosub elt calculation & print 078 GT01 goto loop start 079 *LBL8 element calculation & print 080 X form and store g_k·R_x → R8 081 ST08 082 F02 if flag 0 print R8 083 PRTX 084 RCL0 calculate mating 085 X² resonant element: 086 X 087 1/X $C, L = \frac{1}{\omega_o^2 \cdot (L, C)}$ 088 PRTX 089 F02 if flag 0, return to 090 RTN main program 091 RCL8 092 PRTX recall and print R8 093 RTN return to main program 094 *LBL0 LOWPASS TYPE 1 ROUTINE 095 SPC 096 3 097 1 print heading "31" 098 PRTX 099 CF0 indicate lowpass filter 100 CF1 indicate type 1 filter 101 GSB7 calculate some constants 102 GT02 goto output routine </pre>																																																										
REGISTERS																																																											
<table border="1" style="width: 100%; border-collapse: collapse;"> <thead> <tr> <th>0</th><th>1</th><th>2</th><th>3</th><th>4</th><th>5</th><th>6</th><th>7</th><th>8</th><th>9</th> </tr> </thead> <tbody> <tr> <td>2πf_c</td><td>2πBW</td><td>R</td><td></td><td>scratch</td><td>scratch</td><td>n</td><td>k</td><td></td><td></td> </tr> <tr> <td>S0</td><td>S1</td><td>S2</td><td>S3</td><td>S4</td><td>S5</td><td>S6</td><td>S7</td><td>S8</td><td>S9</td> </tr> <tr> <td>g₁</td><td>g₂</td><td>g₃</td><td>g₄</td><td>g₅</td><td>g₆</td><td>g₇</td><td>g₈</td><td>g₉</td><td>g₁₀</td> </tr> <tr> <td>A</td><td>g₁₁</td><td>B</td><td>g₁₂</td><td>C</td><td>g₁₃</td><td>D</td><td>R_T</td><td>E</td><td>I index</td> </tr> </tbody> </table>										0	1	2	3	4	5	6	7	8	9	2πf _c	2πBW	R		scratch	scratch	n	k			S0	S1	S2	S3	S4	S5	S6	S7	S8	S9	g ₁	g ₂	g ₃	g ₄	g ₅	g ₆	g ₇	g ₈	g ₉	g ₁₀	A	g ₁₁	B	g ₁₂	C	g ₁₃	D	R _T	E	I index
0	1	2	3	4	5	6	7	8	9																																																		
2πf _c	2πBW	R		scratch	scratch	n	k																																																				
S0	S1	S2	S3	S4	S5	S6	S7	S8	S9																																																		
g ₁	g ₂	g ₃	g ₄	g ₅	g ₆	g ₇	g ₈	g ₉	g ₁₀																																																		
A	g ₁₁	B	g ₁₂	C	g ₁₃	D	R _T	E	I index																																																		

Program Listing II

LABELS					FLAGS	SET STATUS		
A	B	C	D	E	⁰ Highpass	FLAGS	TRIG	DISP
load f_0	load BW	load R	BS ₁	BS ₂	⁰ Highpass	ON OFF	USER'S CHOICE	
a LP ₁	b LP ₂	c HP ₁	d HP ₂	e	¹ Type 2	0	DEG	FIX
0 calculate BS coef	1 BS loop rtn	2 calc R _T	3 LP/HP loop rtn	4 print R	² lbl 2 return	1	GRAD	SCI
5	6 Local loop destination	7 LP/HP coeffs	8 bandstop output	9 index incr & loop exit test	3	2 RAD	ENG	n

HP-67 suggested program changes. A print or R/S routine has not been provided, although register 9 and label "e" could have been used for this purpose. The reason for this omission is to preserve the heading format. Any program statements placed between a numeric entry and a print statement cause the printed format to be in the set status of the program; however, by placing the print statement directly after the numeric entry (see lines 20 through 22), "21" is printed without trailing zeros.

On the HP-67, the "print" statement causes the program halt for 5 seconds and a flashing decimal point. This situation slows program execution and may not be desirable. The HP-67 user may wish to have the program stop at the data output points. To cause the program to stop at these points, change the program as follows: Delete steps 019 - 022, 026 - 029, 095 - 098, 104 - 107, 117 - 120, and 126 - 129. Change the "print" statements to "R/S" statements at the following line numbers: 083, 088, 092, 144, 157, 166, and 171. To restart program execution after a program halt, execute a "R/S" from the keyboard.

Remember, when deleting steps from a program, always work from the back of the program forward. By observing this convention, the line numbers of steps not yet deleted will remain unaltered.

PROGRAM 2-5 NORMALIZED LOWPASS TO BANDPASS FILTER TRANSFORMATIONS,
TYPES 1, 2, 6, AND 7.

Program Description and Equations Used

This program converts normalized lowpass filter element values to a set of four bandpass topologies [16], [21], [56]. The four topologies are shown in Fig. 2-5.1, and the parameter A_{ij} is defined by Eq. (2-5.1). Types 1 and 2 are exact transformations and will transform the lowpass response independent of the loaded filter Q (Eq. (2-4.7)). Types 6 and 7 of this program, and types 8, and 9 of Program 2-6 are narrowband approximations, and only provide accurate transformation results when the loaded Q is greater than 5, and preferably greater than 10.

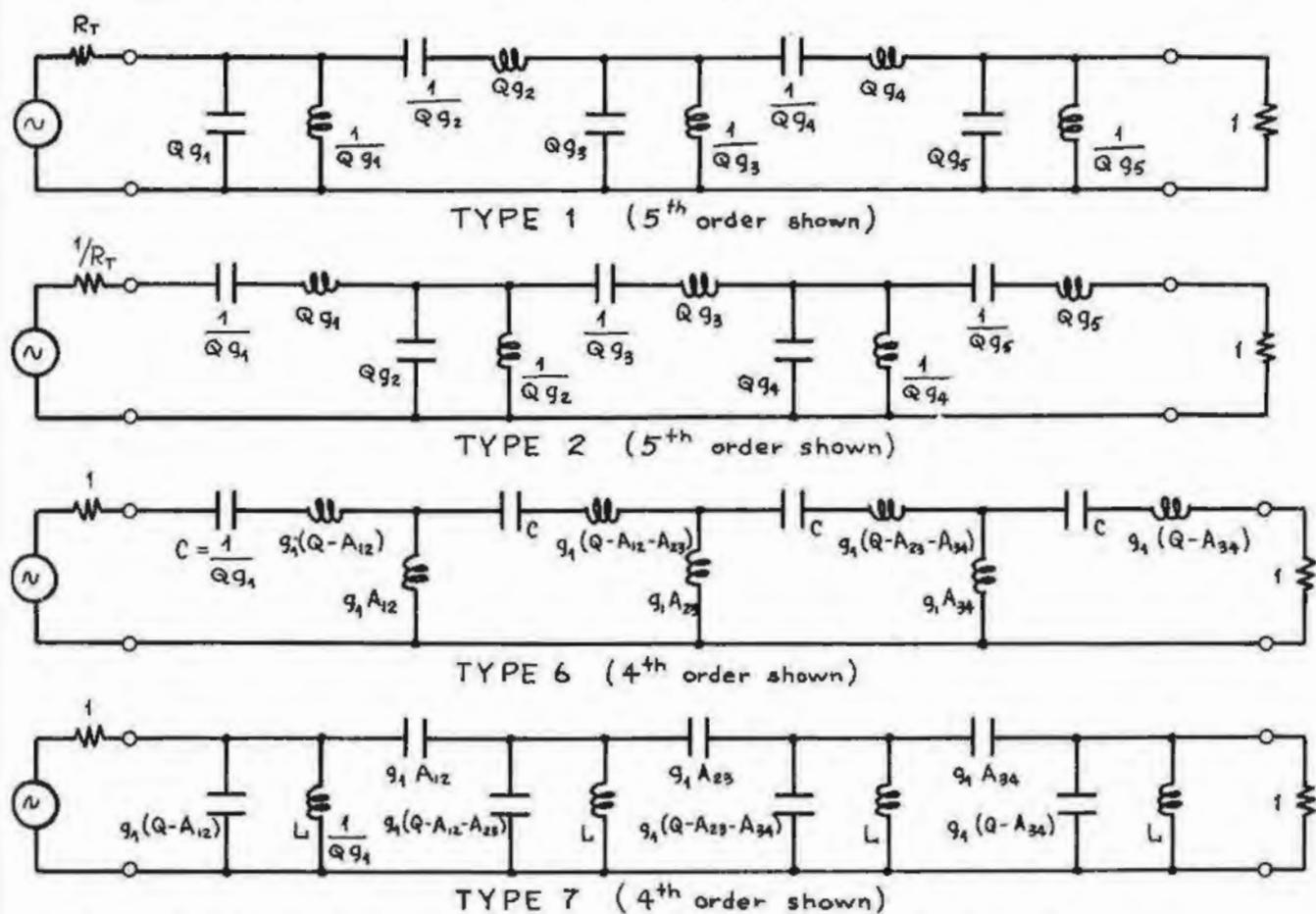


Figure 2-5.1 Bandpass filter topologies for types 1, 2, 6, & 7.

$$A_{ij} = (g_i \cdot g_j)^{-k_2} \quad (2-5.1)$$

Figure 2-5.2 is a reproduction of Table 7.2 in White [56] and is intended as a guide to the best suited filter topology for a particular application. The physical realizability of a filter topology is assigned one of four possible scores based upon element values. These scores are defined as follows:

Readily realizable (R):

$$\begin{aligned} 1 \mu h &\leq L \leq 1 h \\ 5 pF &\leq C \leq 1 \mu F \end{aligned}$$

Practical (P):

$$\begin{aligned} 0.2 \mu h &\leq L \leq 10 h \\ 2. pF &\leq C \leq 10 \mu F \end{aligned}$$

M marginally practical (M):

$$\begin{aligned} 50 nh &\leq L \leq 100 h \\ 0.5 pF &\leq C \leq 500 \mu F \end{aligned}$$

Impractical (I):

All element values that lie outside the range of marginal i.e.,

$$\begin{aligned} L &< 50 nh \\ L &> 100 h \\ C &< .5 pF \\ C &> 500 \mu F \end{aligned}$$

The table headings are meant to indicate ranges of loaded Q, filter center frequency, and termination resistance level. These ranges are:

Frequency;

$$\begin{aligned} f_o &= 10 Hz \text{ implies: } 3 Hz \leq f_o \leq 30 Hz \\ f_o &= 100 Hz \text{ implies: } 30 Hz \leq f_o \leq 300 Hz \\ f_o &= 1 kHz \text{ implies: } 300 Hz \leq f_o \leq 3 kHz \\ f_o &= 10 kHz \text{ implies: } 3 kHz \leq f_o \leq 30 kHz \\ f_o &= 100 kHz \text{ implies: } 30 kHz \leq f_o \leq 300 kHz \\ f_o &= 1 MHz \text{ implies: } 300 kHz \leq f_o \leq 3 MHz \\ f_o &= 10 MHz \text{ implies: } 3 MHz \leq f_o \leq 30 MHz \\ f_o &= 100 MHz \text{ implies: } 30 MHz \leq f_o \leq 300 MHz \end{aligned}$$

At frequencies above 300 MHz, lumped element filters are generally replaced with transmission line type filters.

Loaded Q (Q_L), for bandpass and bandstop,

$$\begin{aligned} Q_L = 5 &\text{ implies: } 3 \leq Q_L < 10 \\ Q_L = 15 &\text{ implies: } 10 \leq Q_L < 30 \\ Q_L = 50 &\text{ implies: } 30 \leq Q_L \leq 100 \end{aligned}$$

Impedance Level (source and load resistances equal)

$$\begin{aligned} R = 3 \text{ ohms} &\text{ implies: } 1 \leq R < 10 \text{ (power filters)} \\ R = 50 \text{ ohms} &\text{ implies: } 10 \leq R < 150 \\ R = 500 \text{ ohms} &\text{ implies: } 150 \leq R < 2.5k \\ R = 10k \text{ ohms} &\text{ implies: } 2.5k \leq R < 50k \end{aligned}$$

Band-Pass Filter Prototype		$f_o = 1\text{ kHz}$						$f_o = 10\text{ kHz}$												
		QL = 5			QL = 15			QL = 50			QL = 5			QL = 15			QL = 50			
Type		50	500	10K	50	500	10K	50	500	10K	50	500	10K	50	500	10K	50	500	10K	
1st		I	P	P	I	I	I	I	I	I	M	R	P	I	M	P	I	M	P	
2nd		I	P	P	I	I	I	I	I	I	M	R	P	I	M	P	I	M	P	
3rd		I	M	P	I	I	P	I	I	M	M	P	P	I	P	P	I	M	P	
4th		I	M	P	I	I	P	I	I	M	M	P	P	I	P	P	I	M	P	
5th		P	P	P	P	P	P	P	P	P	R	R	P	R	P	R	P	R	P	
6th		P	P	I	P	P	I	P	P	I	R	R	P	R	P	R	P	M	P	
7th		I	M	P	I	I	P	I	I	M	M	P	R	P	I	P	R	I	M	P
8th		M	P	I	M	P	I	M	P	I	P	R	P	P	P	P	P	P	M	M
9th		I	M	P	I	I	P	I	I	M	M	P	R	P	I	P	P	I	M	P
10th		M	P	M	P	R	P	R	R	R	P	R	P	R	R	R	R	R	R	R
11th		M	P	P	M	P	P	M	M	P	P	R	R	P	R	R	R	M	P	R
Band-Pass Filter Prototype		$f_o = 100\text{ kHz}$						$f_o = 1\text{ MHz}$												
		QL = 5			QL = 15			QL = 50			QL = 5			QL = 15			QL = 50			
Type		50	500	10K	50	500	10K	50	500	10K	50	500	10K	50	500	10K	50	500	10K	
1st		P	R	R	P	P	I	M	M	I	P	R	P	P	P	I	M	P	I	
2nd		P	R	R	P	P	I	M	M	I	P	R	P	P	P	I	M	M	I	
3rd		P	R	R	P	R	P	M	P	D	R	R	P	R	R	M	P	P	I	
4th		P	R	R	P	R	R	M	P	R	R	R	P	R	R	M	P	R	P	
5th		R	R	R	P	R	R	P	R	P	R	R	P	R	R	M	R	P	I	
6th		R	R	P	R	R	P	R	P	P	R	R	P	R	R	M	R	P	I	
7th		P	R	P	R	R	P	M	R	P	R	R	P	R	R	M	R	P	I	
8th		R	R	P	R	R	P	M	R	P	R	R	P	R	R	M	R	P	I	
9th		P	R	R	P	R	R	P	R	R	P	R	P	R	R	M	R	P	R	
10th		R	R	R	R	R	P	R	R	P	R	R	P	R	R	M	R	R	M	
11th		R	R	R	R	R	P	R	R	P	R	R	P	R	R	R	R	R	R	
Band-Pass Filter Prototype		$f_o = 10\text{ MHz}$						$f_o = 100\text{ MHz}$												
		QL = 5			QL = 15			QL = 50			QL = 5			QL = 15			QL = 50			
Type		50	500	10K	50	500	10K	50	500	10K	50	500	10K	50	500	10K	50	500	10K	
1st		M	P	M	I	P	I	I	I	I	I	I	I	I	I	I	I	I	I	
2nd		M	P	M	I	P	I	I	I	I	I	I	I	I	I	I	I	I	I	
3rd		P	R	M	R	P	I	I	M	I	M	I	I	I	I	I	I	I	I	
4th		M	R	R	I	P	R	I	M	R	I	M	R	I	I	P	I	M	I	
5th		P	R	M	P	I	P	M	I	M	M	I	I	I	I	M	I	I	I	
6th		R	R	M	P	P	I	P	M	I	P	M	I	M	I	I	M	I	I	
7th		M	R	P	I	P	P	I	P	P	P	I	P	M	I	I	I	M	I	
8th		R	R	M	R	P	I	P	M	I	P	M	I	P	I	I	M	I	I	
9th		M	R	R	I	P	R	I	M	R	I	M	R	I	I	P	I	I	M	
10th		P	R	I	P	M	I	P	M	I	P	M	I	M	I	I	M	I	I	
11th		M	R	M	M	P	M	I	P	M	I	M	I	I	M	I	I	I	I	

Fig. 2-5.2 Physical realizability of bandpass filters.

Courtesy Don White Consultants Inc.

To use the routines for types 6 through 9, the filter must have termination resistances as close to unity as possible. To achieve this result, a desired termination resistance level of 1.0 should be loaded into Program 2-3.

Of the filter types presented both in this program, and the accompanying program (types 1, 2, 6, 7, 8, 9, 10, and 11) only types 1, 2, 10, and 11 are exact transformations of the lowpass characteristic. All the remaining filter types are narrowband approximations, i.e., they will faithfully transform the lowpass characteristics within the passband and within a few octaves of the stopband. Types 6, 7, 8, and 9 do not have equal numbers of transmission zeros at both zero frequency and at infinite frequency. The result of this imbalance is to skew the filter response away from the frequency where the extra zeros exist. Figure 2-5.3 shows this occurrence.

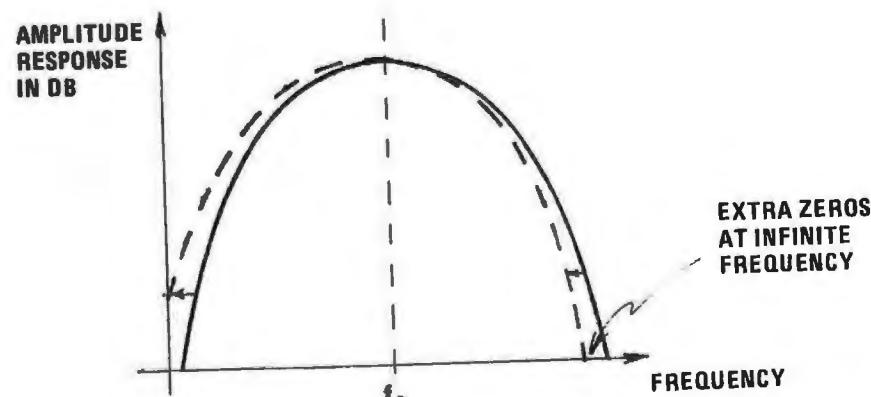


Figure 2-5.3 Bandpass filter response skewing due to extra transmission zeros at infinity.

One should not choose types 1, 2, 10, or 11 automatically. Types 1 and 2 may be difficult to realize in a narrowband application, and types 10 and 11 (also types 6 and 9) contain redundant inductors. Depending upon the frequency range and element values, these redundant inductors can be burdensome. As a guide, filters operating below 1 kHz may best be realized with an active filter (this subject is covered by other programs in this section); between 1 kHz and 100 kHz, the minimum inductor LC design should be considered and compared with active approaches; above 1 MHz the simplest LC topology should be sought to ease the tuning problem.

User Instructions

NORMALIZED LOWPASS TO BANDPASS TYPES 1, 2, 6, & 7				
	load center frequency	load bandwidth	load termination resistance	load filter # & start
1	Load both sides of program card			
2	Load center frequency in Hz	f_o	A	ω_o
3	Load bandwidth in Hz	BW	B	Q
4	Load termination resistance in ohms	R	O	R
5	Load filter type number and start	type	E	R
				tank C
				tank L
				cplg elt*
				tank C
				tank L
				cplg elt*
				tank C
				tank L
				:
				R _T
6	*The coupling element (L for type 6 or C for type 7) does not exist for types 1 or 2.			
	For another case goto steps 2 through 5 as applicable			

Example 2-5.1 Type 6 filter

A maximally flat passband (Butterworth) bandpass filter is to pass a 500 Hz band of frequencies centered around 10 kHz. In a bandpass (or bandstop) filter, the center frequency is the geometric mean of the upper and lower bandedge frequencies, i.e., $f_o = (9750 \cdot 10250)^{1/2}$, or $f_o = 9996.87$ Hz. The filter should reject by at least 30 dB those frequencies removed from the center frequency by more than 500 Hz. The required filter order is obtained from Program 2-1. Using this program, a minimum filter order of 5 is calculated given $A_s \text{dB} = 3$, $A_p \text{dB} = 30$, and $\lambda = 1000/500 = 2$. Program 2-3 is used to obtain the Butterworth normalized coefficients for use by this program.

The proper bandpass topology is selected from the table in Fig. 2-5.2 under the headings: $f_o = 10$ kHz, $Q_L = 10000/500 = 20$ (use $Q_L = 15$ column), and $R = 50$ to find that a type 6 is readily realizable, therefore a type 6 filter will be designed. The HP-97 printout for the above operations is shown below.

Load Program 2-1 to calculate minimum filter order:

```

GSEo      select Butterworth
3.00 GSEP  load ApdB
30.00 GSSE  load AsdB
2.00 GSBI  load λ and calculate n
4.39 ***   filter.order, n (output)

5.00 GSPI  load integral n and calculate λ
2.00 ***   λ for given ApdB and AsdB
2.00 GSBE  load λ and calculate AsdB
52.04 ***   AsdB

```

Load Program 2-3 to calculate normalized LP Butterworth coeffs:

```

5. GSEH  load filter order
1. GSSE  load desired termination resistance ratio
          GSEC  calculate Butterworth coefficients
          1.00000+00 *** RT (normalized port 1 termination resistor)

          616.034-03 *** 81
          1.61803+00 *** 82
          2.00000+00 *** 83 } normalized lowpass coefficients
          1.61803+00 *** 84
          616.034-03 *** 85

          1.00000+00 *** R (normalized port 2 termination resistor)

```

Example 2-5.1, continued:

Load Program 2-5 (this program) and calculate type 6 elements.

```

9996.87 GSBA load center frequency
500. GSBB load bandwidth
50. GSBC load termination resistance
6. GSBE load filter type desired and start

50.000+00 *** termination resistance

25.768-09 *** C1
9.3443-03 *** L1

491.97-06 *** L12

25.768-09 *** C2
9.0705-03 *** L2

273.48-06 *** L23

25.768-09 *** C3
9.2894-02 *** L3

273.48-06 *** L34

25.768-09 *** C4
9.0705-03 *** L4

491.97-06 *** L45

25.768-05 *** C5
9.3443-03 *** L5

50.000+00 *** termination resistance

```

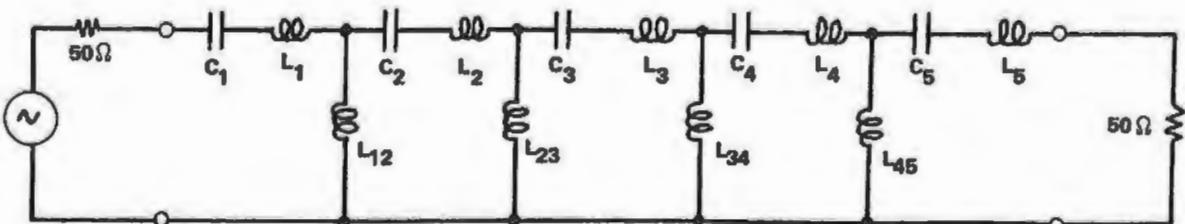


Figure 2-5.4 Type 6 bandpass filter schematic.

Type 6 tuning technique.* After the filter is designed, the inductors fabricated and adjusted, the capacitors obtained, and the filter constructed, the filter must be tuned. For series resonant tanks, such as in this filter and types 8 and 10, tuning is accomplished by decoupling individual tank circuits using open circuits.

Assume the inductors are wound on ferrite pot cores, and are the adjustable elements. Referring to Fig. 2-5.5, to tune L_1 temporarily open the circuit at "B" and tune L for series resonance of the L_1 , L_{12} , C circuit at the center frequency of the filter, 9996.87 Hz in this case.

To tune L_2 , L_{12} , L_{23} , and C , re-establish the connection at "B," and temporarily open the circuit at points "A" and "C." Tune L_2 for series resonance at the center frequency. Continue this procedure of opening adjacent tank circuits and tuning until all series resonant loops have been tuned to the filter center frequency.

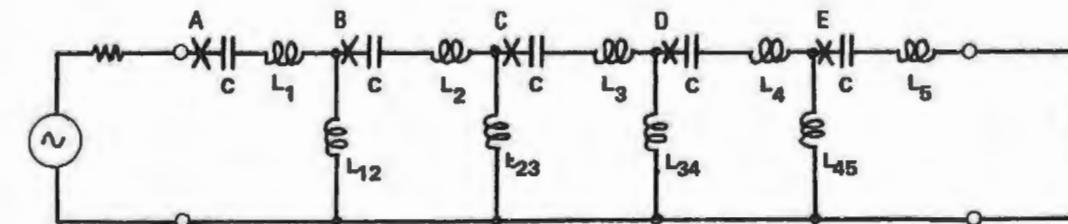


Figure 2-5.5 Type 6 filter showing circuit opens for tuning.

For information on ferrite pot core inductor design, see the Ferroxcube catalog "Linear Ferrite Materials and Components," and use Programs 3-1 and 3-2 to aid in the design of these inductors.

When designing the inductors, the designer must not allow the magnetic core excitation to drive the core near saturation. The voltage across an inductor is "Q" times the voltage across the series LC tank at

*For parallel tank filter tuning procedure, see the example in the type 8, 9, 10, and 11 transformations program.

resonance. With inductor Q's of 100 or better, inductor voltages can be large with respect to the voltage across the filter. The voltage across a filter element at center frequency is approximately

$$I_{in} \cdot X_{element} \text{ where } I_{in} \text{ is the filter input current and } X_{element} \text{ is the element reactance.}$$

Program Listing I

2-5

001 *LBLA	LOAD CENTER FREQUENCY	049 *LBL0	type 1 calculation start
002 PI		050 *LBL1	type 2 calculation start
003 ENT1	form and store:	051 GSB9	initialize flags & regs
004 +		052 *LBL2	types 1 & 2 loop start
005 X	2πf₀ → R₀	053 RCL?	
006 ST00		054 2	
007 RTN		055 ÷	
008 *LBLB	LOAD BANDWIDTH	056 FRC	
009 PI		057 X=0?	
010 ENT1	form and store:	058 SF2	
011 +		059 RCL1	
012 X		060 RCL1	
013 RCL0		061 X	form Q·g₁
014 X?Y	Q = $\frac{2\pi f_0}{2\pi BW} \rightarrow R_1$	062 F2?	
015 ÷		063 1/X	if branch even, form 1/Q·g₁
016 ST01		064 STOC	calculate and print
017 RTN		065 F0?	branch capacitor
018 *LBLE	LOAD TERMINATION	066 GSB8	
019 ST02	RESISTANCE	067 F1?	
020 RTN		068 GSB7	
021 *LBLE	LOAD FILTER TYPE (1,2,6,7)	069 RCLC	
022 ST01		070 F0?	
023 8	generate "ERROR" if other	071 GSB7	calculate and print
024 X?Y?	than filter types 1, 2,	072 F1?	branch inductor
025 GT00	6, or 7 loaded.	073 GSB8	
026 RCLI		074 SPC	
027 3	"ERROR" is generated by	075 DS2I	
028 X=Y?	calling unused label (a)	076 EEX	increment indices
029 GT0a		077 ST+7	
030 RCLI		078 RCL6	
031 4		079 RCL7	test for loop exit
032 X=Y?		080 X?Y?	
033 GT0a		081 GT02	
034 RCLI		082 RCLD	
035 5		083 F0?	
036 X=1?		084 1/X	calculate and print
037 GT0a		085 RCL2	termination resistance
038 RCLI	calculate indirect label	086 X	
039 2	corresponding to desired	087 GSB6	
040 ÷	filter type	088 GT0b	
041 ST01			
042 INT			
043 X?I			
044 FRC	set flag 0 if types 1		
045 SF0	or 7 are entered otherwise		
046 X=0?	clear flag 0		
047 CF0			
048 ST01			

REGISTERS									
0 2πf₀	1 Q	2 R	3	4 1 $\frac{R}{\omega_0 R}$ or $\frac{1}{\omega_0}$	5 R $\frac{1}{\omega_0}$ or $\frac{1}{\omega_0 R}$	6 n	7 k	8 gₙ	9 A _{i,i+1}
S0 g₁	S1 g₂	S2 g₃	S3 g₄	S4 g₅	S5 g₆	S6 g₇	S7 g₈	S8 g₉	S9 g₁₀
A g₁₁	B g₁₂	C types 6 & 7 common element	D R _T	E g _{i+1}	I index				

Program Listing II

LABELS					FLAGS	SET STATUS		
A	B	C	D	E	0 type 1 or 7	FLAGS	TRIG	DISP
a	b space & rtn	c	d	e	0 type 1 or 7	0 ON	DEG	FIX
0 type 1 start	1 type 2 start	2 types 1&2 loop start	3 types 6&7 start	4 types 6&7 loop start	1 type 2 or 6	1 OFF	GRAD	SCI
5 print common element	6 prt & space	7 CorL output	8 L or C output	9 initialize	2 even branch	2 RAD	ENG	n
					3	3		

HP-67 suggested program changes. The "print" mode of output can be changed to the "R/S" mode by changing like statements at line numbers 147, 152, and 178. The program execution will halt at each data output point and await restart by the user via the "R/S" key.

**PROGRAM 2-6 NORMALIZED LOWPASS TO BANDPASS FILTER TRANSFORMATIONS,
TYPES 8, 9, 10, AND 11.**

Program Description and Equations Used

This program converts normalized lowpass filter element values to a set of four bandpass filter topologies [16], [56]. These four topologies are shown in Fig. 2-6.1 in normalized form (1 ohm, 1 radian/sec center frequency). The parameter A_{1j} is defined by Eq. (2-5.1). Types 8 and 9 are narrowband transformations of types 2 and 1, while types 10 and 11 are exact transformations of types 2 and 1 obtained by applying Norton transformations to the shunt elements of type 2 to form type 10, or to the series elements of type 1 to form type 11. This transformation process is detailed in the equation derivation section following Example 2-6.2. The types 8 and 9 narrowband transformations will only provide accurate results when the loaded Q (ratio of center frequency to bandwidth) is greater than 5 or so. This restriction is not present with types 10 or 11. Because the type 8 or 9 coupling element causes extra zeros of transmission at either dc or infinite frequency, the frequency response will be skewed away from the extra transmission zero frequencies as implied by Fig. 2-5.3. Figure 2-5.2 should be consulted for picking the filter type best suited to the center frequency, loaded Q, and impedance level of the intended application.

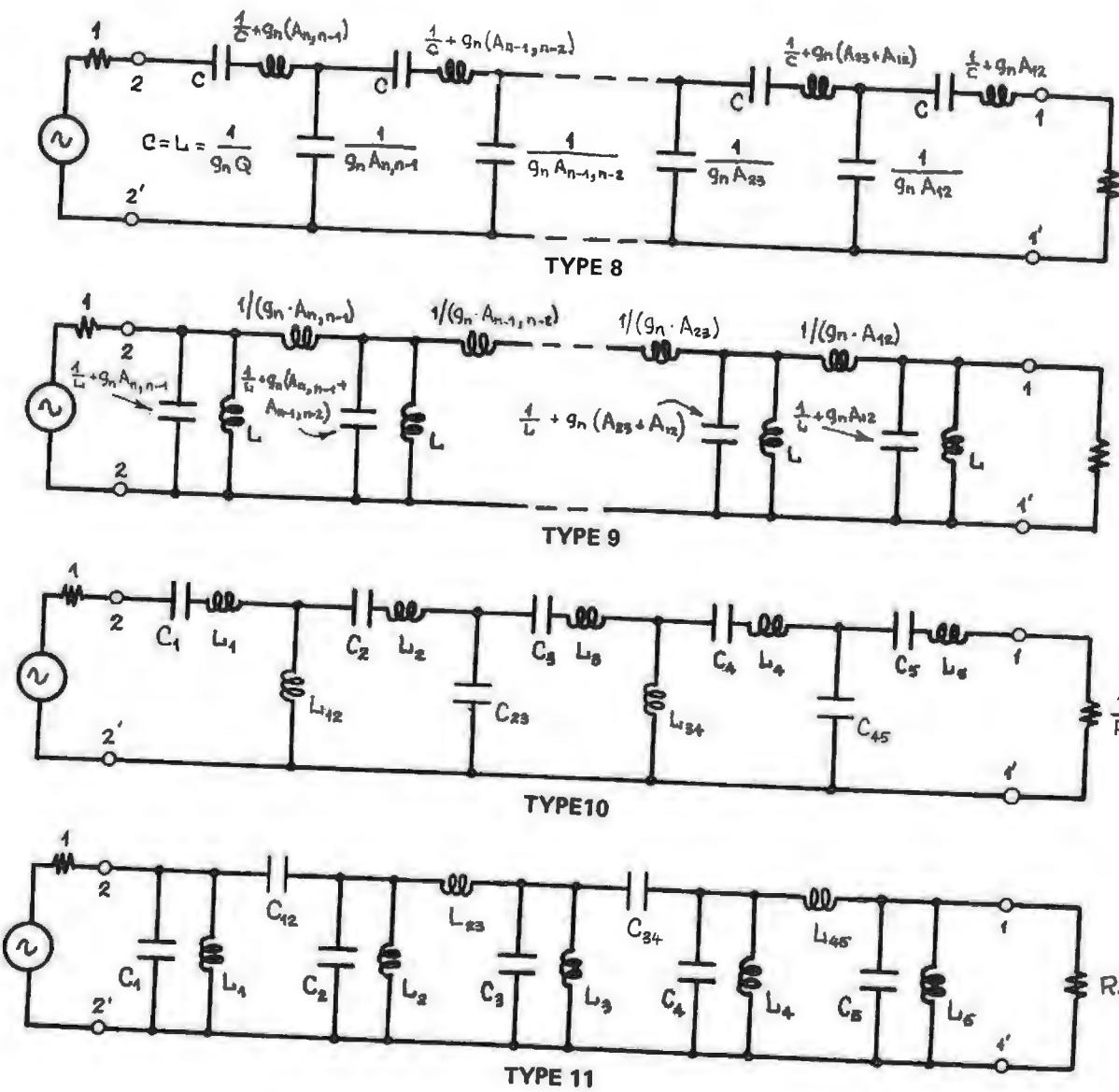


Figure 2-6.1 Normalized bandpass filter topologies for types 8, 9, 10, and 11.

Table 2-6.1 Types 10 and 11 normalized element values.

Type 10 element	Type 11 element	normalized element value
C_k	L_k	$\left(Q \cdot g_i - \frac{N_{i+2} - 1}{Q \cdot g_{i+1}} \right)^{-1}$
L_k	C_k	$Q \cdot g_i - \frac{N_i - 1}{Q \cdot g_{i-1}}$
$L_{k+1}, k+1$	$C_{k+1}, k+1$	$\frac{N_1}{Q \cdot g_{i-1}}$
C_{k+1}	L_{k+1}	$\frac{1}{Q \cdot g_n}$
L_{k+1}	C_{k+1}	$Q \cdot g_n$
$C_{k+1}, k+1$	$L_{k+1}, k+2$	$\frac{Q \cdot g_{i-1}}{N_i}$

$$N_i = \frac{1}{2} \left(1 + \sqrt{1 + 4Q^2 \cdot g_{i-1} \cdot g_n} \right) ; \quad g_{n+1} = 0$$

$$k = 1, 3, 5, \dots, n \quad (n \text{ must be odd})$$

$$i = n - k + 1$$

The reverse ordering of the normalized lowpass coefficients from the element subscripts occurs because the dual form of the normalized lowpass filter is used. The dual is required to place the 1 ohm resistor next to the first shunt capacitor which is required for types 8 and 9 when transforming even ordered filters. Since the same register setup and recall routine is used for types 10 and 11, the dual form is carried over for convenience (it is not required).

Types 10 and 11 can be redrawn to show the ladder structure as T's or pi's of inductors and capacitors as shown in Fig. 2-6.2.

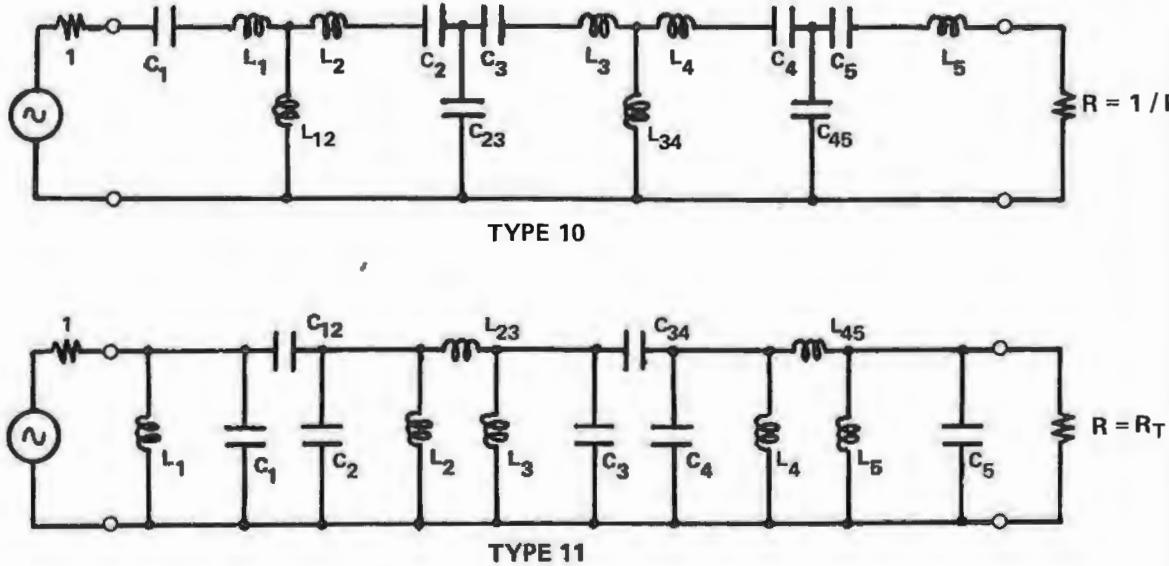


FIGURE 2-6.2 Types 10 and 11 showing T's and pi's of L's and C's.

These pi's and T's of inductors can be replaced with an active realization that contains only op-amps, resistors, and capacitors by using 2 back-to-back generalized impedance converter (GIC) circuits as detailed in Orchard and Sheahan's paper [42], and shown in Figs. 2-6.3 & 4.

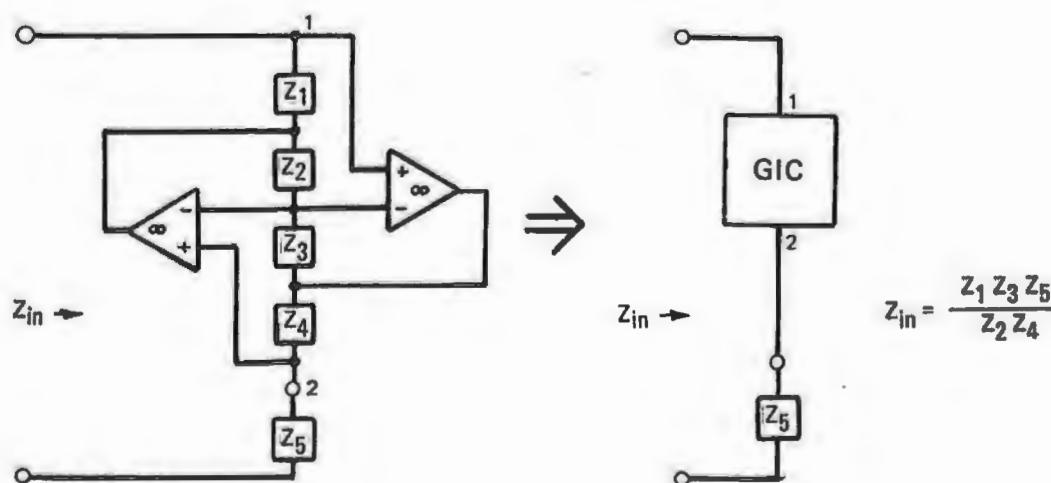


Figure 2-6.3 Antoniou GIC circuit [3].

If Z_1, Z_2, Z_3 , and Z_5 are resistors and Z_4 is a capacitor, then,

$$Z_{in} = \frac{R_1 R_3 R_5}{R_2} \cdot sC_4 = sL \quad (2-6.1)$$

Furthermore, if $R_2 = R_3$ (a Q enhancement condition), then,

$$L = R_1 C_4 R_5 \quad (2-6.2)$$

Two GIC circuits with the component selection outlined above can be combined to produce a circuit that simulates a T or pi of inductances. These circuits are shown in Fig. 2-6.4.

Aside from the elimination of inductors, this particular mechanization is very easy to tune. Changing resistor R_1 in the GIC alters the apparent inductance seen at the terminals. The capacitor, C_4 , needs to be stable (e.g., polystyrene or mica) but can have a large initial tolerance which is accommodated during the tuning procedure.

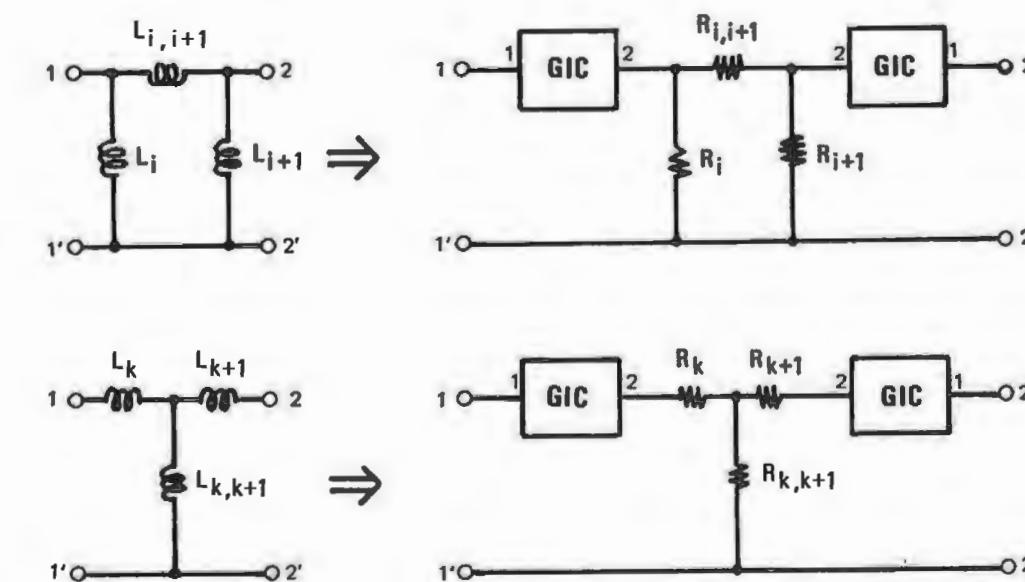


Figure 2-6.4 Pi or T inductance simulation circuits using GIC's.

The diagrams and discussion thus far have used the filters in normalized form, i.e., 1 ohm termination resistor, and 1 radian/second center frequency. The prototype filter is denormalized by

multiplying each normalized inductor by $2\pi f_o / R$, and dividing each normalized capacitor by $2\pi f_o R$, where f_o and R are the desired center frequency and termination resistance level respectively. The program accomplishes this denormalization by calling either subroutine 7 or 8. For types 8 and 10, subroutine 7 denormalizes capacitors and subroutine 8 denormalizes inductors, and the reverse is true for types 9 and 11.

Tuning procedure for types 7, 9, and 11*. After the component values have been calculated, the inductors designed,** fabricated and adjusted to value, and the capacitors selected and padded to the proper value, the filter may be assembled and tuned so it will exhibit the desired response.

Tuning is accomplished by adjusting each of the parallel tank elements. For low frequency filters, the inductor is usually chosen as the adjustable element. At higher frequencies the capacitor is usually chosen as the adjustable element. The resonance of the tank circuit must include the effects of the coupling elements. By temporarily shorting out adjacent tank circuits, the coupling element influence will be included. This tuning procedure is described next.

- 1) Temporarily place a short at location "B" and adjust C_1 (or L_1) to resonate the tank circuit at the center frequency of the filter, f_o . The connection (short) must be low inductance with respect to the other inductances in the circuit.
- 2) Remove the short at "B," and temporarily place shorts at locations "A" and "C." Adjust C_2 (L_2) for tank circuit resonance at the filter center frequency.
- 3) Continue shorting out adjacent tanks with low inductance shorts at locations "B" & "D," "C" & "E," and "D," and adjusting each resulting tank circuit for resonance at the filter center frequency, f_o . These steps will complete the tuning of the filter.

** For more information on inductor design, see the ferromagnetic core and air core inductor design programs contained in another section of this book. Also see the Ferroxcube Inc. publication "Linear Ferrite Materials and Components" for information on ferrite pot core inductor design.

* See program 2-5 for the type 6, 8, and 10 tuning procedure.


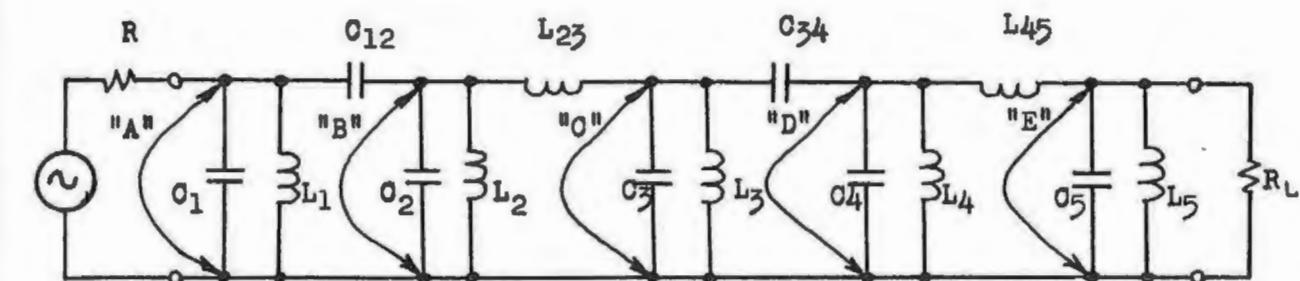


Figure 2-6.5 Circuit shorts for Types 7, 9, and 11 tuning.

User Instructions

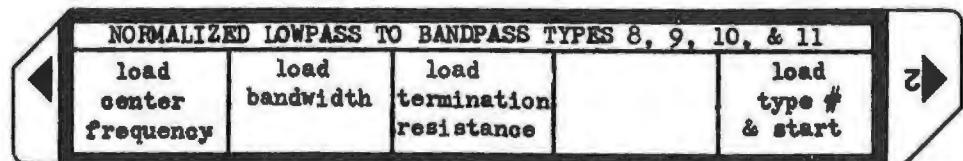

STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
1	Load both sides of program card (normalized lowpass coefficients and related parameters must be loaded into the registers either manually, or as output from Program 2-3)			
2	Load center frequency in Hz	f_0	A	ω_0
3	Load bandwidth in Hz	BW	B	Q
4	Load termination resistance in ohms	R	C	
5	Load type number of filter desired The tank capacitor is always printed first independent of filter type. *The coupling element will be as follows: Type 8, capacitor Type 9, inductor Type 10, alternating L's & C's Type 11, alternating C's & L's See Fig. 2-6-1 for more details.	8,9,10,11	E	load R C_{tank} L_{tank} $C_{\text{L cplg}}^*$ C_{tank} L_{tank} $C_{\text{L cplg}}^*$ C_{tank} ⋮ load R

Example 2-6.1 Type 10 Filter Design

A Chebyshev response bandpass filter is required to pass a 20 Hz band of information geometrically centered about 1000 Hz with 0.5 dB ripple or less, and to operate in a 1000 ohm system. The filter stopbandwidth is 60 Hz, and the filter should reject frequencies lying outside this band by at least 60 dB.

Referring to Fig. 2-5.2 under the headings $f = 1 \text{ kHz}$, $Q_L = 1000/20 = 50$, and $R = 500$, type 8 is practical, and type 10 is readily realizable. Since active inductor simulation is anticipated, type 10 will be selected.

Program 2-1 is used to calculate the filter order necessary to meet the requirements, and Program 2-3 is used to calculate and store the normalized lowpass coefficients for use by this program. The HP-97 printout for all these programs is shown below.

Load Program 2-1 and calculate required filter order

```
5. GSB4 select Chebyshev response
.50 G9E4 load ApdB
60.00 GEEB load AsdB
3.00 GEBE load λ and calculate minimum filter order
4.51 *** n, the minimum filter order (output)
```

```
3.00 GEBE load integral filter order and calculate λ
2.51 *** λ to meet ApdB and AsdB given n = 5
```

```
3.00 GEBE load λ required and calculate actual AsdB
61.40 *** AsdB for n = 5 and λ = 3
```

Load Program 2-3 and calculate Chebyshev LP normalized coefficients

```
5. GSBA load required filter order
1. GSBB load desired termination resistance ratio
.5 GSBD load Chebyshev passband ripple and start
1.05926+00 *** normalized -3dB frequency (output)
```

```
1.00000+00 ***  $R_T$  (normalized port 1 termination resistance)
```

```
1.70577+00 *** g1
```

```
1.22963+00 *** g2
```

```
2.54083+00 *** g3
```

```
1.22963+00 *** g4
```

```
1.70577+00 *** g5
```

```
1.00000+00 *** R (normalized port 2 termination resistance)
```

Example 2-6.1 (continued)

Load program 2-6 and calculate type 10 filter elements

1000. GSBA load center frequency
 20. GSBB load bandwidth
 1000. GSBC load termination resistor
 16. GSBE select filter type and start

1.00000+03 *** R

1.86608-09 *** C1
 13.3879+00 *** L1

188.752-03 *** L12

1.86608-09 *** C2
 13.5741+00 *** L2

134.199-09 *** C23

1.26442-09 *** C3
 20.0331+00 *** L3

188.752-03 *** L34

1.86608-09 *** C4
 13.5741+00 *** L4

134.199-09 *** C45

1.89203-05 *** C5
 13.5741+00 *** L5

1.00000+03 *** RT

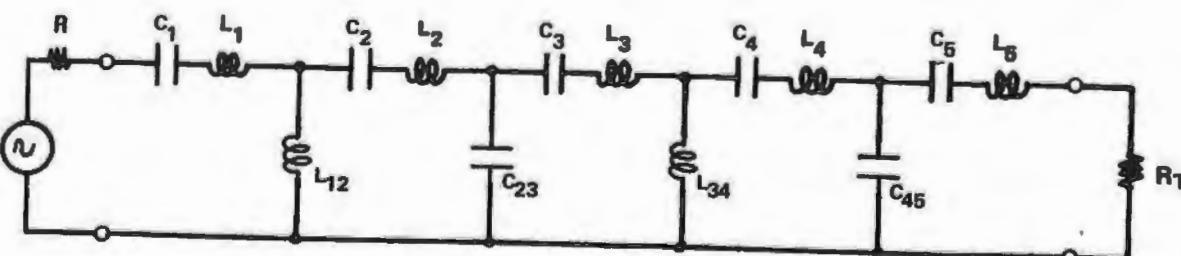


Figure 2-6.6 Type 10 bandpass filter schematic.

Example 2-6.2 Singly terminated type 10 filter design

Because the type 10 filter is an exact bandpass transformation of the lowpass prototype (as is the type 11), the terminating resistances need not be equal. This example will show the synthesis of a singly terminated type 10 filter, i.e., R_T is allowed to approach infinite resistance. The equally terminated filter case is the least sensitive to component value changes. When the filter is singly terminated, the operating Q's of the tank circuits become higher as the open (or shorted) end of the filter is approached. This means that the changes in tank Q's will have a greater effect on the overall operating Q of the tank in the filter, and hence, the filter response. The HP-97 printout for the singly terminated type 10 filter follows. Refer to Fig. 2-6.6 for the filter schematic.

Load Program 2-3

5. GSBA load n
 1.+05 GSBB load R_T ratio
 .5 GSBD load Chebyshev ripple
 1.05926+00 *** w_{-3dB} (output)
 100.000+03 *** RT
 1.53866+00 *** g1
 1.64272+00 *** g2
 1.81407+00 *** g3
 1.42917+00 *** g4
 852.839-03 *** g5
 1.00000+00 *** R

Load Program 2-6

```

1000. GSBA load fo
20. GSBB load bandwidth
1000. GSBC load termination R
10. GSBE select type & start

1.00000+03 *** R
3.73236-09 *** C1
6.66484+00 *** L1
124.064-03 *** L12
3.73236-09 *** C2
6.78668+00 *** L2
204.171-09 *** C23
1.76961-09 *** C3
14.3222+00 *** L3
115.645-03 *** L34
3.73236-09 *** C4
6.78668+00 *** L4
219.028-09 *** C45
2.08814-09 *** C5
12.2443+00 *** L5
10.0000-03 *** RT (short circuit)

```

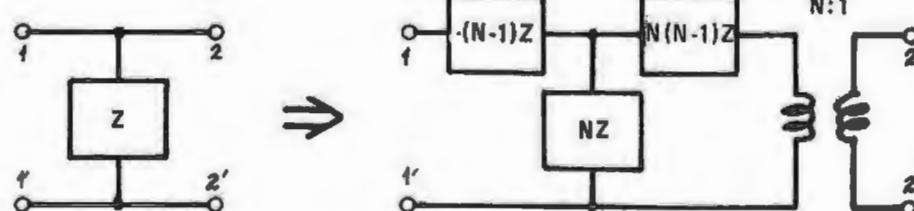
Derivation of types 10 and 11 transformations

Figure 2-6.7 Norton's second transformation.

Figure 2-6.7 shows one form of Norton's second transformation [39]. This transformation changes a single shunt impedance into a T of impedances, one of which is negative, plus an ideal transformer with turns ratio N. Figure 2-6.8 shows how a parallel resonant tank circuit can be changed into a section of a type 10 bandpass filter structure.

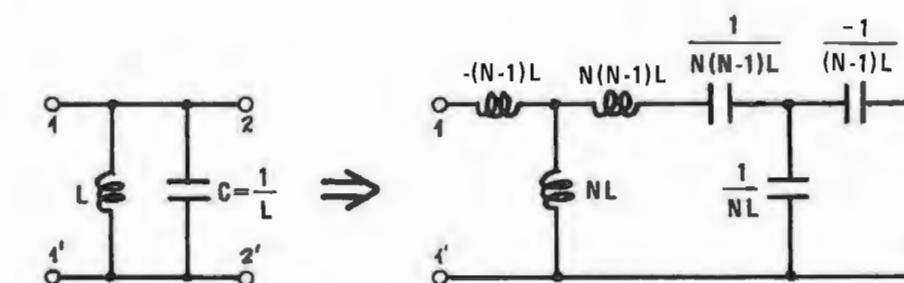


Figure 2-6.8 Norton's second transformation applied to a parallel LC tank circuit.

In Fig. 2-6.8, Norton's transformation has been applied back-to-back, i.e., the 2-2' terminals of the Norton transformation of the inductor have been connected to the 2-2' terminals of the Norton transformation of the capacitor. The same transformer ratio, N, is used for both transformations, therefore, the two ideal transformers are back-to-back providing an overall transformer ratio of unity and can be eliminated.

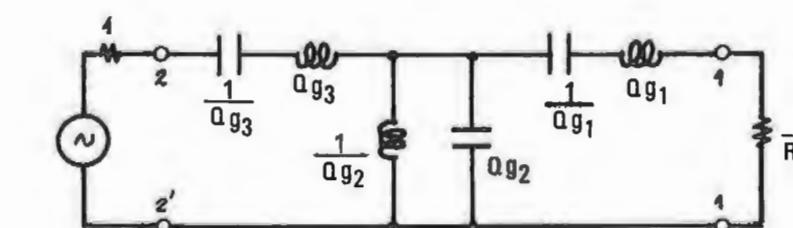


Figure 2-6.9 Type 2 normalized bandpass filter obtained from lowpass prototype (note port ordering).

Figure 2-6.9 shows a type 2 normalized bandpass filter obtained from the transformation of a lowpass prototype. The dual lowpass form is used (see Fig. 2-3.1 lower) and is scaled to a cutoff frequency of $1/Q$ (Q is the ratio of the filter center frequency to bandwidth); each frequency scaled series lowpass inductor is series resonated with a capacitor at $\omega = 1$, and each shunt scaled lowpass capacitor is parallel resonated with an inductor at $\omega = 1$. Next, the circuit of Fig. 2-6.8 is substituted for the parallel resonant tank, and the negative elements in the series arms combined with the positive series elements of Fig. 2-6.9. The results of this process yield the topology shown in Fig. 2-6.10. Higher ordered (odd order) filters are obtained by repeated application of this procedure.

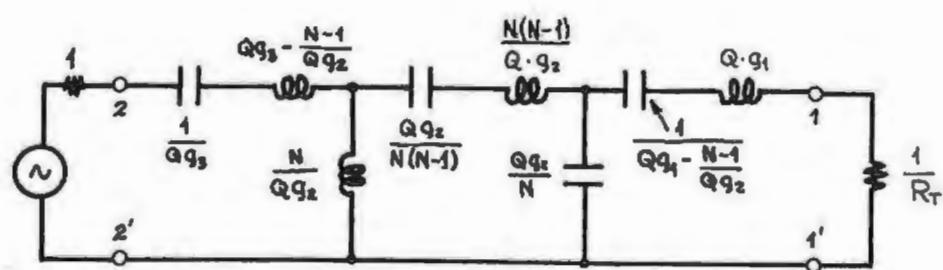


Figure 2-6.10 Type 10 normalized bandpass filter resulting from transformation.

The type 11 bandpass filter is shown in Fig. 2-6.1 and is the dual of the type 10 structure. Type 11 can be derived in a manner similar to the type 10 procedure by applying Norton's first transformation to a type 1 normalized bandpass filter. Norton's first transformation is shown in Fig. 2-8.1. Since type 11 is the dual of type 10 it can be more directly derived from the type 10 structure itself as shown by Fig. 2-6.1 and Table 2-6.1.

The value for N_1 given in Table 2-6.1 is derived by making the transformed tank capacitor (inductor) value the same as the first ladder tank capacitor (inductor) for type 10 (11), i.e.,

$$\frac{1}{Q \cdot g_n} = \frac{Q \cdot g_1 - 1}{N_1 \cdot (N_1 - 1)} \quad (2-6.3)$$

Solving for N_1 yields:

$$N_1 = \frac{1}{2} \left(1 + \sqrt{1 + 4Q^2 \cdot g_{1-1} \cdot g_n} \right) \quad (2-6.4)$$

Program Listing I

```

001 *LBLA LOAD CENTER FREQUENCY
002 F1
003 ENT1
004 +
005 X form and store  $2\pi f_0 \rightarrow R_0$ 
006 ST00
007 RTN
008 *LBLB LOAD FILTER BANDWIDTH
009 Pi
010 ENT1
011 +
012 X form and store:
013 RCL0
014 XZY  $Q_L = \frac{2\pi f_0}{2\pi BW} \rightarrow R_1$ 
015 =
016 ST01
017 RTN
018 *LBLC LOAD TERMINATION RESISTANCE
019 ST02
020 RTN
021 *LBLD LOAD FILTER TYPE AND START
022 2
023 ÷ calculate starting label
024 ST01 index
025 INT
026 4
027 -
028 X<0? generate "ERROR" if filter
029 GT0a type is less than 8
030 X#I store label index
031 SF0
032 FRC
033 X=0? set flag 0 if order is odd
034 CF0
035 GT0i goto starting label
036 *LBL0 type 8 and 9 routine
037 GSB9 initialize registers
038 RCLi recall and store  $g_1$  for
039 ST0E dual filter topology
040 ST08
041 RCL1 calculate and store common
042 X element value reciprocal
043 ST0C
044 CLX
045 ST09 initialize  $A_{01} = 0$ 
046 *LBL2 types 8 & 9 loop start
047 F1? print type 9 tank
048 GSB5 capacitor
049 DSZI increment indices
050 EEX
051 ST+7
052 RCLi recall  $g_{i+4}$ 
053 RCL8
054 XZY recall  $g_i$  and store  $g_{i+4}$ 
055 ST0E

056 X
057 JX calculate  $A_{i, i+1}$ 
058 1/X
059 RCL9
060 XZY
061 ST09 interchange  $A_{i-1, i}$  &  $A_{i, i+1}$ 
062 +
063 GSB0 form  $A_{i-1, i} + A_{i, i+1}$  and
output related element
064 RCL9
065 RCL8 calculate and output
066 X coupling element
067 GSB7 test for loop exit
068 SPC
069 RCL7
070 RCL6 test for loop exit
071 XZY?
072 GT02
073 F1? output type 9 tank
074 GSB5 capacitor
075 RCL9 output rest of last
076 GSB0 tank circuit
077 RCL2
078 GSB6 recall and print terminating
079 GT06 resistance value
080 *LBL8 types 8 & 9 output routine
081 RCL8
082 X output type 8 tank
083 RCLC capacitor, or type 9
084 +
085 GSB8 tank inductor
086 F0? output type 8 tank
087 GSB5 inductor
088 GT06
089 *LBL1 types 10 & 11 routine start
090 GSB9 initialize registers
091 *LBL3 types 10 & 11 loop start
092 RCL9  $Q \cdot g_{i+1}$ 
093 RCLi  $i = n, n-2, \dots, 1$ 
094 RCL1
095 X
096 ST09
097 XZY
098 RCL8  $N_{i+2} (N_{n+2} = 1)$ 
099 EEX
100 -
101 XZY
102 ÷
103 -
104 ST03  $Q \cdot g_i - \frac{N_{i+2}}{Q \cdot g_{i+1}}$ 
105 FJ? if first time through loop,
106 ST0C store value of first L or C
107 F1? output type 11 tank
108 GSB7 capacitor
109 2
110 ST+7 increment index, k

```

REGISTERS

0 $2\pi f_0$	1 Q_L	2 R	3 scratch	4,1 $\frac{R}{w_0 R}$	2,5 $\frac{R}{w_0}$	1,6 $\frac{1}{w_0}$	6 n	7 k	8 scratch	9 scratch
S0 g_1	S1 g_2	S2 g_3	S3 g_4	S4 g_5	S5 g_6	S6 g_7	S7 g_8	S8 g_9	S9 g_{10}	
A g_{11}	B g_{12}	C common element	D R_T	E N, g_{i-1}	I index					

Program Listing II

```

111 RCL6
112 RCL7 test for loop exit
113 XZY?
114 GT08
115 RCL9 calculate and store
116 DSZI transformer ratio for
117 RCLi Norton transformation:
118 RCL1
119 X
120 ST09
121 4  $N_i = \frac{1}{2}(1 + \sqrt{1 + 4Q^2 g_n g_{i-1}})$ 
122 X
123 RCLC
124 X
125 EEX
126 +
127 JX
128 EEX
129 +
130 2
131 ÷
132 ST0E
133 EEX calculate and print tank
134 -
135 RCL9 inductor for type 10 or
136 ÷ tank capacitor for type 11
137 -
138 GSB6
139 RCL3 print type 11 tank inductor
140 F0?
141 GSB7
142 SPC
143 RCL8 calculate and print
144 RCL9 coupling element, L for
145 ÷ type 10 or C for type 11
146 ST08
147 GSB8
148 SPC
149 RCLC print type 10
150 F1? tank capacitor
151 GSB7 print type 10 tank
152 RCLC inductor, or print type 11
153 GSB8 tank capacitor
154 RCL8
155 F0? print type 11
156 GSB7 tank inductor
157 SPC
158 RCL8 calculate and print
159 GSB7 coupling element, C for
160 SPC type 10 or L for type 11
161 DSZI decrement index and
162 GT03 return to loop start
163 *LBL0 last tank output
164 RCL9 C for type 10, or
165 GSB8 L for type 11

166 RCL3 output type 10
167 F0? tank inductor
168 GSB7 calculate and print
169 SPC termination resistance
170 RCL2
171 RCLD
172 F1?
173 1/X
174 X
175 GSB6
176 GT06
177 *LBL5 common element output subr
178 RCLC recall common element
179 *LBL7 L/C (odd/even) output subr
180 1/X
181 RCL5
182 X
183 PRTX
184 RTN
185 *LBL8 C/L (odd/even) output subr
186 RCL4
187 X
188 PRTX
189 RTN
190 *LBL9 initialization subroutine
191 SPC
192 SF1
193 F0? flag 1 flag 0
194 CF1
195 SF3
196 RCL0
197 1/X setup denormalization
198 ST04 constants for L's and C's
199 ST05 (register order changed
200 RCL2 depending upon filter type
201 F1? being odd or even)
202 1/X
203 ST=4
204 STx5
205 EEX
206 ST07
207 ST09 initialize registers
208 ST0E
209 RCL6
210 9 initialize normalized LP
211 + coef recall index register
212 ST01
213 RCL2 recall termination R
214 *LBL6 print and space subroutine
215 PRTX
216 *LBL6 space and return subroutine
217 SPC
218 RTN

LABELS
A load  $f_0$ 
B Load BW
C Load R
D
E Load type
0 type 9 or 11
1 type 8 or 10
2 types 8 & 9
3 types 10 & 11
4 types 8 & 9
5 print common elt.
6 print, spc, return
7 print Cor L
8 print L or C
9 initialize
10 first time thru loop

FLAGS
0 ON OFF
1 DEG
2 GRAD
3 RAD
4 FIX
5 SCI
6 ENG
7 n
8 5

SET STATUS
TRIG
DISP
0 ■
1 ■
2 ■
3 ■

```


HP-67 suggested program changes. To change from the "print" to "R/S" mode for program output, make the respective change at the following line numbers: 183, 188, and 217. The program will now stop at output points and await restart via the "R/S" command from the keyboard.

PROGRAM 2-7 WYE-DELTA TRANSFORMATIONS FOR R, L, OR C.


Program Description and Equations Used

This program performs the Y- Δ transformation for groups of three resistors, capacitors, or inductors. These transformations find use whenever awkward or physically impractical element values result from electrical network design. The resistive transformation is often used with operational amplifier summing network design to keep the resistor values low. The inductive and capacitive transformations can be of assistance in filter design.

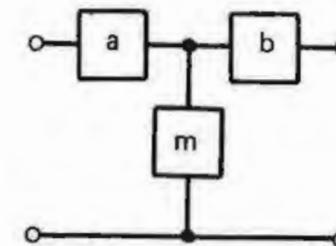The Y- Δ transformations for one-of-a-kind elements are summarized below:



"Y" topology

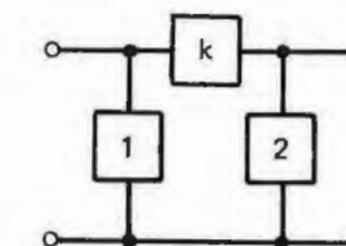

" Δ " topology

Figure 2-7.1 "Y" and " Δ " topology definitions.

For capacitors as network elements:

Y \rightarrow Δ

$$\begin{aligned}C_1 &= C_a \cdot C_m / \Sigma C \\C_2 &= C_b \cdot C_m / \Sigma C \\C_k &= C_a \cdot C_b / \Sigma C \\\Sigma C &= C_a + C_b + C_m\end{aligned}$$

$\Delta \rightarrow Y$

$$\begin{aligned}C_a &= \Sigma C / C_2 \\C_b &= \Sigma C / C_1 \\C_m &= \Sigma C / C_k \\\Sigma C &= C_1 C_2 + C_2 C_k + C_1 C_k\end{aligned}$$

User Instructions

For inductors or resistors as network elements (read L's as R's):

 $\Delta \rightarrow Y$

$$L_1 = \Sigma LL/L_b$$

$$L_2 = \Sigma LL/L_a$$

$$L_k = \Sigma LL/L_m$$

$$\Sigma LL = L_a L_b + L_a L_m + L_b L_m$$


 $Y \rightarrow \Delta$

$$L_a = L_1 \cdot L_k / \Sigma L$$

$$L_b = L_2 \cdot L_k / \Sigma L$$

$$L_m = L_1 \cdot L_2 / \Sigma L$$

$$\Sigma L = L_1 + L_2 + L_k$$

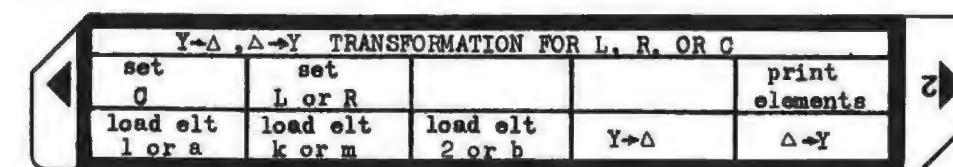

STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
1	Load program card (one sided card)			
2	Select element type: if capacitors if inductors, or resistors		<input type="checkbox"/> f <input type="checkbox"/> A <input type="checkbox"/> f <input type="checkbox"/> B	
3	Load element values Load element 1 or a Load element k or m Load element 2 or b		<input type="checkbox"/> A <input type="checkbox"/> B <input type="checkbox"/> C	
4	Select transformation type: Y → Δ transformation Δ → Y transformation		<input type="checkbox"/> D	element a element m element b $\Sigma a, m, b$ element 1 element k element 2 $\Sigma l, k, 2$
5	To print presently stored elements		<input type="checkbox"/> E	element 1 element k element 2 $\Sigma l, k, 2$ element a element m element b $\Sigma a, m, b$ <input type="checkbox"/> f <input type="checkbox"/> E elt 1,a elt k,m elt 2,b Σ elts.

Example 2-7.1

Convert the Y network of Fig. 2-7.2 into an equivalent Δ network. Compute the total capacitance both before and after the transformation.

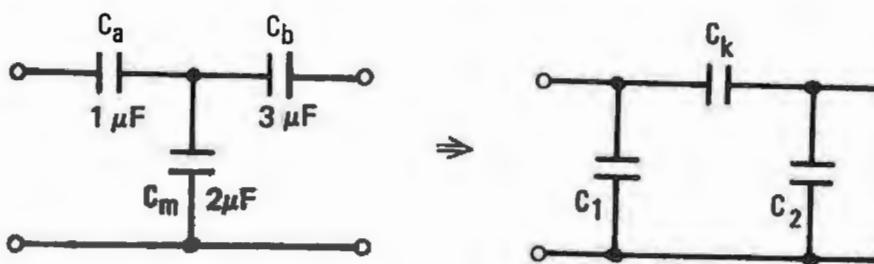


Figure 2-7.2 Capacitor networks for Example 2-7.1

HP-97 printout

```

...-06 33E4 Ca } load capacitor value
...-07 33E5 Cm }
...-07 33E6 Cb } select capacitors
33E7 G3BD perform Y→Δ transformation

1.000-05 *** Ca }
2.000-06 *** Cm } before transformation
3.000-06 *** Cb }
4.000-06 *** ΣC's }

733.3-05 *** C1 }
800.0-09 *** Ck }
.000-06 *** C2 } after transformation
.833-06 *** ΣC's }

```

As a result of the transformation, the total capacity has been reduced by 69.4%.

Example 2-7.2

A top coupled parallel resonant bandpass filter of the type 7 topology has been designed with the element values shown in Fig. 2-7.3. The 1 picofarad coupling capacitor is a problem since it is the same relative value as the parasitic (stray) capacities of the printed circuit board. By converting from a Δ capacitor configuration to a Y configuration, the minimum filter capacity is 202 pF as seen in Fig. 2-7.4, and the parasitic capacities of the printed circuit board are easily managed.

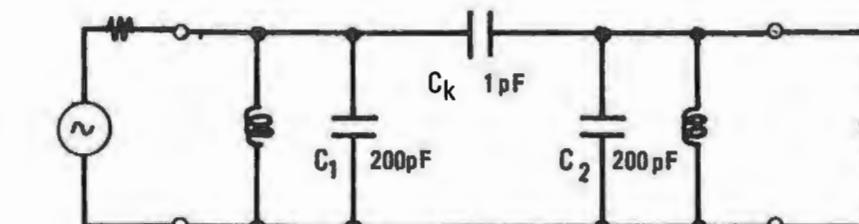


Figure 2-7.3 Type 7 filter design


HP-97 printout for $\Delta \rightarrow Y$ transformation

206.-12 GSE₂ C₁ }
 GSE₀ C₂ } load capacitor value
 . -12 GSE C_k
 GSE₂ select capacitors
 GSE₀ start Δ→Y transformation

200.0-12 *** C₁
 1.000-12 *** C_k
 200.0-12 *** C₂
 401.0-12 *** total capacity } summary before
 transformation

262.0-12 *** C^a
 40.40-09 *** C^m
 262.0-12 *** C^b
 40.80-09 *** total capacity } summary after
 transformation

Figure 2-7.4 Network after $\Delta \rightarrow Y$ transformation.

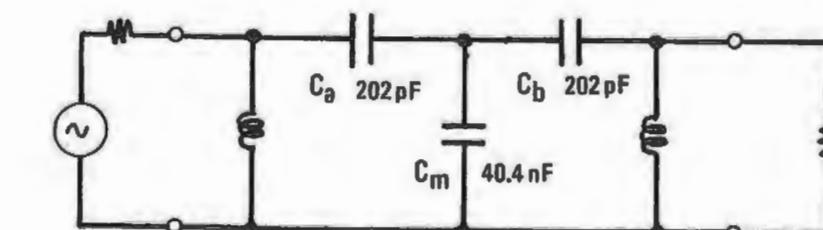

Program Listing

001 *LBLA LOAD element 1 or a									
002 STOA									
003 RTN									
004 *LBLB LOAD element k or m									
005 STOB									
006 RTN									
007 *LBLC LOAD element 2 or b									
008 STOC									
009 RTN									
010 *LBLD PRINT ELEMENTS									
011 SPC									
012 RCLA									
013 PRTX									
014 RCLB									
015 PRTX									
016 +									
017 RCLC									
018 PRTX									
019 +									
020 PRTX									
021 SPC									
022 RTN									
023 *LBLD START Y-Δ TRANSFORMATION									
024 GSBe print elements									
025 F0? jump if L or R									
026 GT00									
027 *LBLI Δ-Y for L or R, Y-Δ for 0									
028 RCLA form and store ΣX where									
029 RCLB X is L, R, or 0									
030 +									
031 RCLC									
032 +									
033 STOD									
034 RCLA calculate element a or 1									
035 RCLB and store in scratchpad									
036 x									
037 RCLD									
038 ÷									
039 STOE temporarily store element m or k in scratchpad									
040 RCLA calculate element m or k									
041 RCLC									
042 x									
043 RCLD									
044 ÷									
045 RCLE store element a or 1									
046 STOA									
047 R↓									
REGISTERS									
0	1	2	3	4	5	6	7	8	9
S0	S1	S2	S3	S4	S5	S6	S7	S8	S9
A element 1 or a	B element k or m	C element 2 or b	D ΣX or ΣXX	E X is L, R, or 0	F scratchpad	G 1			
L: load l or a	K: load k or m	C: load 2 or b	D: Y-Δ	E: Δ-Y	F: print elements	G: L or R	H: FLAGS	I: TRIG	J: DISP
a: set 0	b: set L, R	c: d:	e: print elements	f: L or R	0: ON OFF	1: USER'S CHOICE	2: DEG	3: FIX	
l: dest	R: dest	1: L or R	2:	3:	1: 0	2: 1	3: 2	4: RAD	5: SCI
5	6	7	8	9	3: 3			6: ENG	7: n
LABELS									
FLAGS									
SET STATUS									

PROGRAM 2-8 NORTON TRANSFORMATIONS.

Program Description and Equations Used

Two network equivalence transformations developed by Edward L. Norton are shown below. They can be extremely useful for modifying network element values or topology.

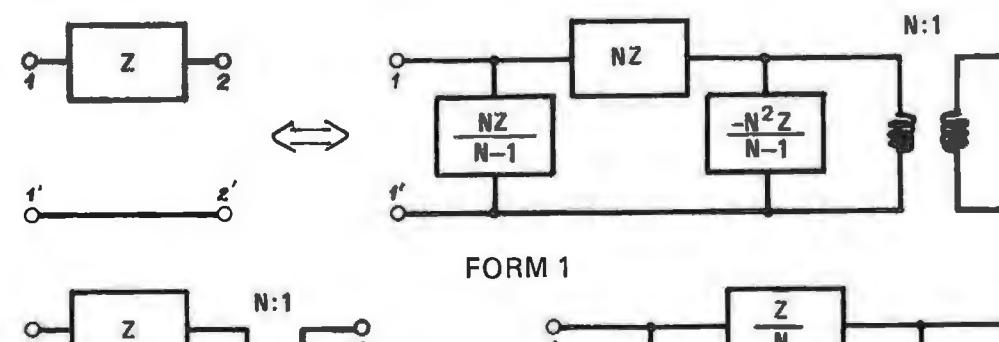


Figure 2-8.1 Two forms of Norton's first transformation.

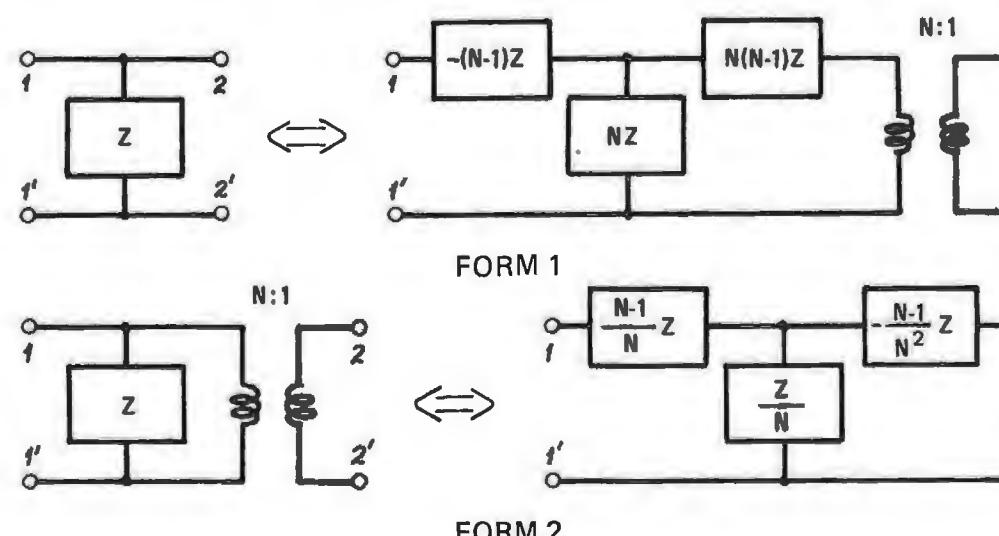


Figure 2-8.2 Two forms of Norton's second transformation.

Figure 2-8.1 shows two forms of Norton's first transformation, and Fig. 2-8.2 shows two forms of Norton's second transformation. The transformed network always contains a negative element, which is combined with a positive element not involved in the transformation. N must be chosen so this combination results in a zero or positive element value if the element is to be realized passively (there are active circuits which can simulate negative elements). When N is chosen so the negative and positive elements annihilate one-another, the overall network topology changes. This technique can be used to reverse an "L" network as shown in Fig. 2-8.3

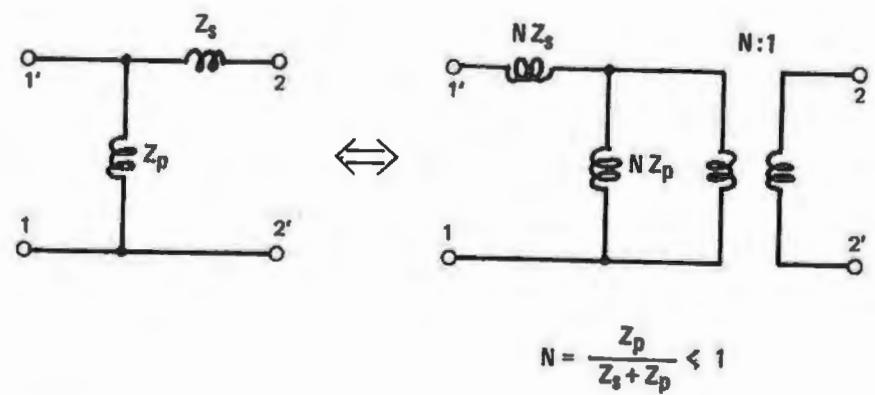


Figure 2-8.3 Norton transformation applied to an "L" network.

Chapter 10 of Zverev [58] has many examples of the application of Norton's transformations. Some insight into the power of Norton's transformations is related in the article "Reminiscences" by W.R. Bennett in CAS-24 no. 12 (Dec. 1977). Dr. Bennett recollects that Ed Norton could efficiently furnish a network to give a prescribed loss characteristic with the minimum number of elements by using only a very ordinary sliderule, his intuition, and his transformations.

This HP-67/97 program will transform either capacitors or inductors and resistors. Because the impedance of a capacitor is inversely proportional to the capacitance, multiplying an impedance by N has the effect of dividing the capacitance by N . Figure 2-8.4 shows form 1 of Norton's first transformation when the element being transformed is a capacitor.


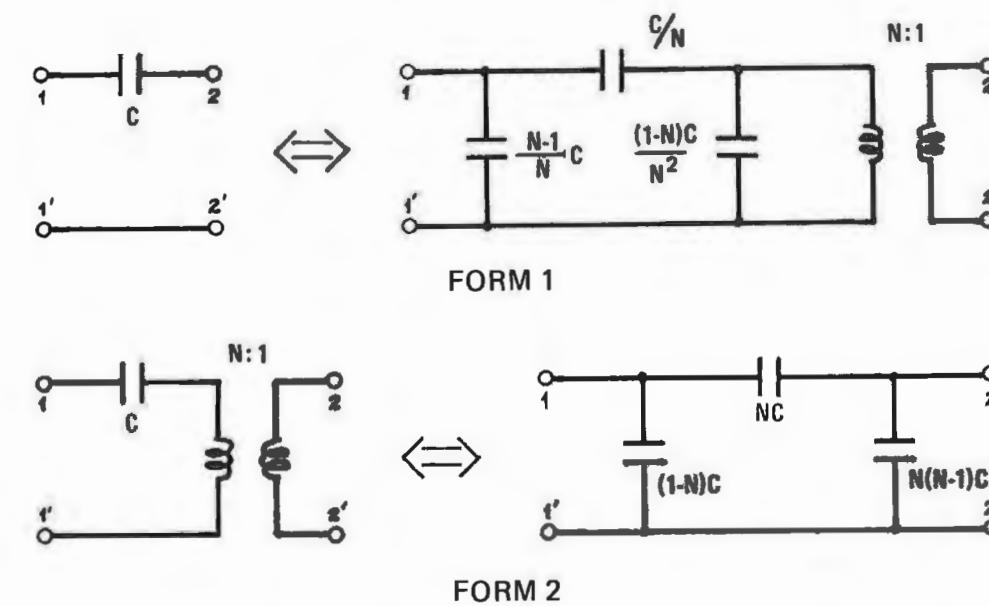


Figure 2-8.4 Norton's first transformation for capacitors.

The same reciprocal relations hold for Norton's second transformation as applied to capacitor networks.

User Instructions

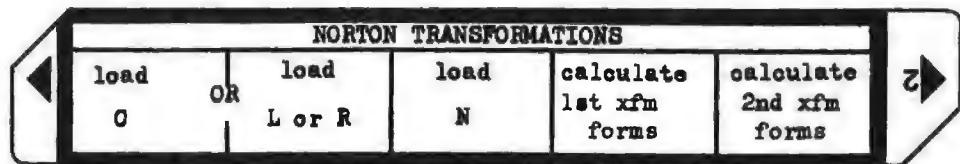

STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
1	Load program card			
2	If a capacitor network is being transformed, load capacitor value OR If an inductor or resistor network is being transformed, load L or R value	0	A	
3	Load ideal transformer ratio desired	N	B	
4	To calculate both forms of Norton's first transformation		C	
			D	shunt elt series elt shunt elt space xfrm ratio space space shunt elt series elt shunt elt
			E	form one { series elt shunt elt series elt space xfrm ratio space space series elt shunt elt series elt }
5	To calculate both forms of Norton's second transformation			

Example 2-8.1

An impedance stepdown of 3:1 is required at the output of the bandpass filter shown in Fig. 2-8.5. A transformer could be used to provide this function. Instead, use Norton's first transformation to provide the impedance stepdown without a transformer.

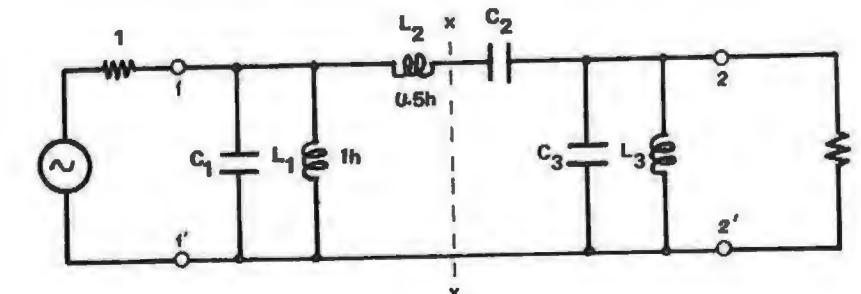


Figure 2-8.5 Bandpass filter network for Ex. 2-8.1.

A hypothetical $\sqrt{3}:1$ turns ratio transformer is inserted at x-x, and all network elements to the right scaled down in impedance by a factor of 3 as shown in Fig. 2-8.6.

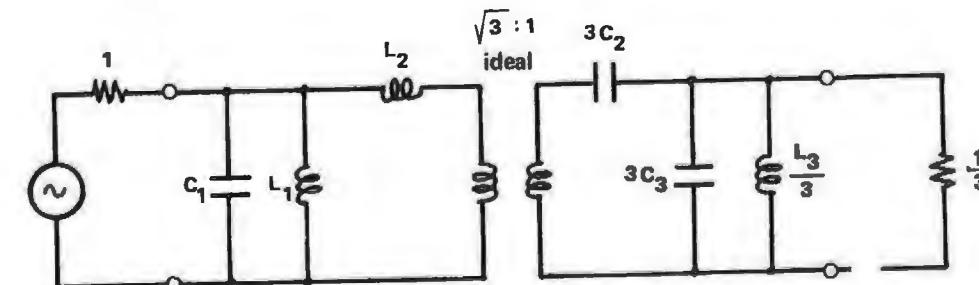


Figure 2-8.6 Network of Fig. 2-8.5 after insertion of hypothetical transformer.

Form 2 of Norton's first transformation is applied to L_2 and the transformer as shown in Fig. 2-8.7. The resulting negative shunt inductor is combined with L_1 as shown in Fig. 2-8.8.

HP-97 printout for Norton's first transformation

.5 GSBF L₂
 $\left. \begin{matrix} Z_a & 7X \\ Z_{SC} & \end{matrix} \right\} N$
 GSBG calculate Norton's first transformation
 $\left. \begin{matrix} 1.183+j0 \\ 0.666-j0 \\ -2.045+j0 \end{matrix} \right\} *** L_a, L_b, L_c$
 $1.771+j0 *** \text{ transformer ratio}$

$\left. \begin{matrix} -0.683-j0 \\ 0.886-j0 \\ 0.594-j0 \end{matrix} \right\} *** L_a, L_b, L_c$

form 1

form 2

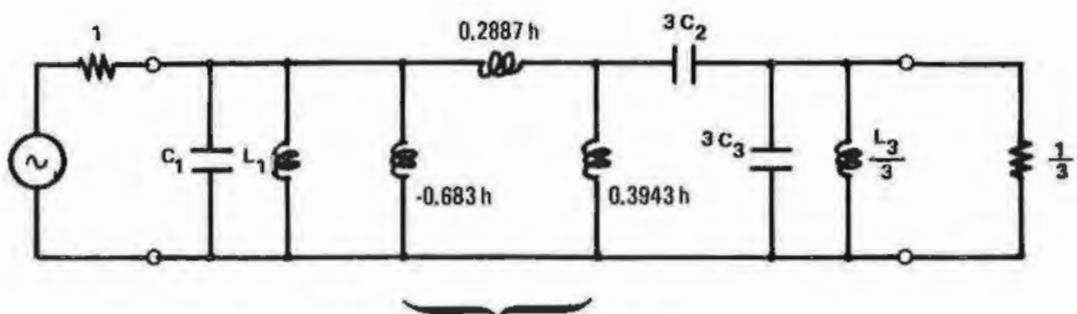
Norton equivalent
inductor and transformer

Figure 2-8.7 Network of Fig. 2-8.6 with form 2 of Norton's first transformation applied.

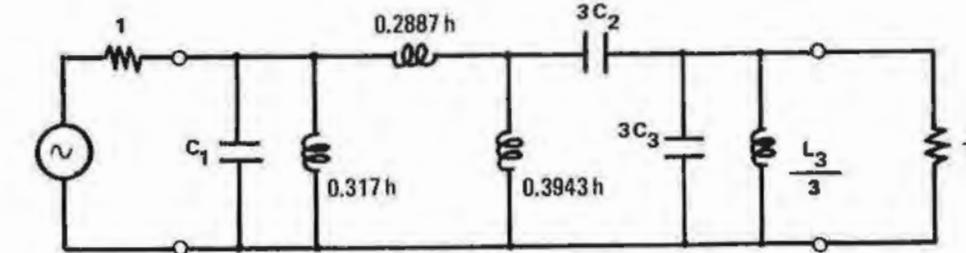


Figure 2-8.8 Final network with all negative elements absorbed.

Program Listing I

001	*LBL4	LOAD C							
002	SFC	indicate capacitor entry							
003	1/X	form and store reciprocal							
004	ST00	of entry							
005	1/X	restore entry							
006	RTN								
007	*LBL5	LOAD L OR R							
008	CFC	indicate L or R entry							
009	ST00	store entry							
010	RTN								
011	*LBL6	LOAD N							
012	ST01								
013	PTR								
014	*LBLD	CALCULATE FIRST TRANSFORM							
015	SPC								
016	RCL1								
017	RCL1	form 1 shunt element							
018	EEX	calculation							
019	-								
020	÷								
021	PCL0								
022	X								
023	ST02								
024	GSB0								
025	RCL0								
026	RCL1	form 1 series element							
027	X	calculation							
028	GSB0								
029	PCL2								
030	RCL1	form 1 shunt element							
031	X	calculation							
032	CHS								
033	GSB0								
034	SPC								
035	RCL1	recall and print transformer							
036	PRTX	turns ratio							
037	SPC								
038	SPC								
039	RCL0								
040	RCL1	form 2 shunt element							
041	EEX	calculation							
042	-								
043	÷								
044	ST02								
045	CHS								
046	GSB0								
047	RCL0								
048	RCL1	form 2 series element							
049	÷	calculation							
050	GSB0								
051	RCL2	form 2 shunt element							
052	GT01	calculation							
REGISTERS									
04 C or L	1 N	2 scratch	3	4	5	6	7	8	9
S0	S1	S2	S3	S4	S5	S6	S7	S8	S9
A	B	C	D	E	I				

Program Listing II

053	*LBL6	CALCULATE SECOND TRANSFORM												
054	SPC													
055	RCL0													
056	RCL1	form 1 series element												
057	EEX	calculation												
058	-													
059	X													
060	ST02													
061	CHS													
062	GSB0													
063	RCL0													
064	RCL1	form 1 shunt element												
065	X	calculation												
066	GSB0													
067	RCL2													
068	RCL1	form 1 series element												
069	X	calculation												
070	GSB0													
071	SPC													
072	RCL1	recall and print ideal												
073	PRTX	transformer turns ratio												
074	SPC													
075	SPC													
076	RCL1													
077	EEX													
078	-	form 2 series element												
079	RCL1	calculation												
080	÷													
081	RCL0													
082	X													
083	ST02													
084	GSB0													
085	RCL0													
086	RCL1	form 2 shunt element												
087	÷	calculation												
088	GSB0													
089	RCL2													
090	CHS													
091	*LBL1													
092	RCL1	form 2 series element												
093	÷	calculation												
094	GSB0													
095	SPC													
096	SPC													
097	RTN													
098	*LBL0	output subroutine												
099	F0?													
100	1/X													
101	PRTX													
102	RTN													
LABELS														
A	Load C	B	Load L	C	Load N	D	Calc type 1	E	Calc type 2	0	capacitor	FLAGS	SET STATUS	
a	b	c	d	e	f	g	h	i	j	0	ON OFF	FLAGS	TRIG	DISP
0	output subr.	1	2	3	4	5	6	7	8	1	■	USER'S CHOICE	DEG	FIX
5										2		GRAD	SCI	ENG
										3		RAD	n	

PROGRAM 2-9 BUTTERWORTH AND CHEBYSHEV ACTIVE LOWPASS FILTER DESIGN AND POLE LOCATIONS.

Program Description and Equations Used

This program calculates the pole locations and Sallen and Key topology element values for un-normalized Butterworth or Chebyshev all pole lowpass filter approximations.

The program is designed to allow the use of capacitors with specified values as might result from the actual capacity measurement of a selected capacitor. The design process starts by assuming that all resistors are equal to the design resistance level, and the capacitor values are calculated to meet the filter requirements. The user may select new capacitor values near the original values, and the program will calculate new resistor values to meet the filter requirements. These resistor values can generally be selected from the nearest standard 0.1% resistor values.

The normalized pole locations of a Butterworth lowpass filter lie on a circle of unit radius as shown by Fig. 2-2.1 with the generalized pole locations given by Eqs. (2-2.12) and (2-2.13). The normalized pole locations for a Chebyshev lowpass filter lie on an ellipse as shown by Fig. 2-2.3 with the generalized pole locations given by Eqs. (2-2.15), (2-2.16), (2-2.17), and (2-2.18).

Each complex conjugate pole pair can be expressed in either the cartesian (real and imaginary parts) or the polar (magnitude and angle) co-ordinate systems. A variation on the polar system allows the pole pair to be defined in terms of the natural frequency (polar radius), ω_n , and "Q," or quality factor. The relationship between these coordinate systems is shown in Fig. 2-9.1, and described by Eqs. (2-9.1) through (2-9.3).

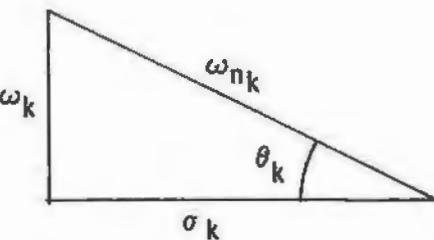


Figure 2-9.1 Co-ordinate system relationships.

$$\omega_{n_k} = \sigma_k^2 + \omega_k^2 \quad (2-9.1)$$

$$\theta_k = \tan^{-1}\left(\frac{\omega_k}{\sigma_k}\right) \quad (2-9.2)$$

$$Q_k = \frac{1}{2 \cos \theta_k} = \frac{\omega_{n_k}}{2\sigma_k} \quad (2-9.3)$$

The element values for the Sallen and Key type active resonator are easily expressed in terms of ω_n and Q as follows:

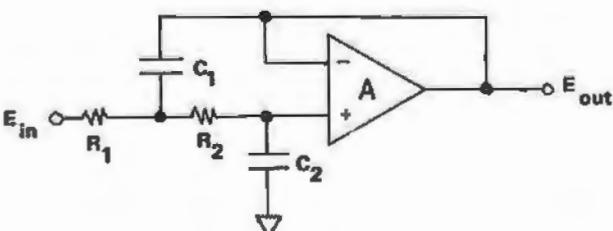


Figure 2-9.2 Sallen and Key active lowpass filter topology.

$$C_1 = \frac{Q(R_1 + R_2)}{\omega_n R_1 R_2} = \frac{2Q}{\omega_n R} \quad (2-9.4)$$

$$C_2 = \frac{1}{\omega_n Q (R_1 + R_2)} = \frac{C_1}{4Q^2} \quad (2-9.5)$$

$$R_1 = R_2 = R$$

The Sallen and Key resonator topology is chosen over other types because of the low parameter sensitivities to element changes. This type of filter synthesis is called the cascade method. Each pole pair is synthesized by an isolated op-amp resonator circuit. The entire filter is formed from a cascade of these resonator circuits. With each pole pair being independent, the overall filter sensitivities to component value changes are higher than an equivalent LC filter. See reference [49] (page 314) for more details.

If higher order filters are required (n greater than 9 or so), either the leapfrog (Szentirmai) topology using Deliyannis resonators [48], [20] or Cauer-Chebyshev filters using biquadratic sections [35] should be considered.

If the two capacitors in the Sallen and Key circuit are specified, then the following equations express the resistor values.

$$R_1 = \frac{1 + \sqrt{1 - 4Q^2C_2/C_1}}{2Q\omega_n C_2} \quad (2-9.6)$$

$$R_2 = \frac{1}{\omega_n^2 C_1 C_2 R_1} \quad (2-9.7)$$

To ensure the quantity under the radical is positive in the equation for R_1 , C_2 should be selected to be a lower value, and C_1 a higher value than given by Eqs. (2-9.4) and (2-9.5).

If the filter order is odd, then a real pole exists. A third order op-amp resonator circuit may be used to produce both the real pole and a complex conjugate pair. The lowest Q pole pair is selected for realization by this circuit to minimize sensitivities, and to keep the element value spread within bounds. The third order section topology is

shown in Fig. 2-9.3.

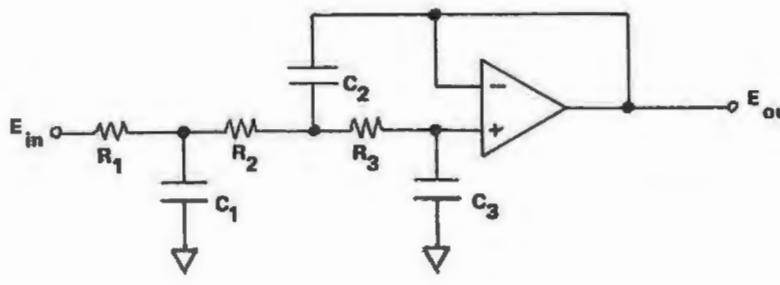


Figure 2-9.3 Third order op-amp resonator circuit.

$$\frac{E_{\text{out}}}{E_{\text{in}}} = \frac{1}{D(s)} \quad (2-9.8)$$

where

$$D(s) = s^3 C_1 C_2 C_3 R_1 R_2 R_3 + s^2 C_3 \{ C_1 R_1 (R_2 + R_3) + C_2 R_3 (R_1 + R_2) \} + s \{ C_1 R_1 + C_3 (R_1 + R_2 + R_3) \} + 1$$

$$\frac{E_{\text{out}}}{E_{\text{in}}} = \frac{1}{Cs^3 + Bs^2 + As + 1} = \frac{1}{\frac{s^2}{\omega_n^2} + \frac{s}{\omega_n Q} + 1} \cdot \frac{1}{\tau s + 1} \quad (2-9.9)$$

$$\text{for } R_1 = R_2 = R_3 = 1 \quad (2-9.10)$$

$$A = C_1 + 3C_3 = \tau + \frac{1}{\omega_n Q} \quad (2-9.11)$$

$$B = 2C_3(C_1 + C_2) = \frac{\tau}{\omega_n Q} + \frac{1}{\omega_n^2} \quad (2-9.12)$$

$$C_1 = C_1 C_2 C_3 = \frac{\tau}{\omega_n^2} \quad (2-9.13)$$

The equations for A, B, and C represent three equations in three unknowns, C_1 , C_2 , and C_3 . By algebraic manipulation, a cubic equation in C_1 alone may be obtained.

$$C_1^3 - C_1^2 (A) + C_1 (\frac{3}{2} B) - 3C = 0 \quad (2-9.14)$$

A Newton-Raphson iterative solution is used to find the real root of this equation (there will be at least one). Once C_1 is found, the remaining two capacitors are found as follows:

$$C_3 = \frac{A - C_1}{3} \quad (2-9.15)$$

$$C_2 = \frac{C}{C_1 C_3} \quad (2-9.16)$$

If the three capacitors are specified, then the transmission function (Eq. (2-9.9)) may be used to obtain three equations in terms of the three unknown resistors. Equating like powers of s , as before, these equations result:

$$A = C_1 R_1 + C_3 (R_1 + R_2 + R_3) = \tau + \frac{1}{\omega_n Q} \quad (2-9.17)$$

$$B = C_3 \{ C_1 R_1 (R_2 + R_3) + C_2 R_3 (R_1 + R_2) \} = \frac{\tau}{\omega_n Q} + \frac{1}{\omega_n^2} \quad (2-9.18)$$

$$C = C_1 C_2 C_3 R_1 R_2 R_3 = \frac{\tau}{\omega_n^2} \quad (2-9.19)$$

By algebraic manipulation, R_2 may be eliminated leaving two equations in two unknowns, R_3 as a cubic function of R_1 alone, and a quadratic equation in R_1 with R_3 as a parameter. The quadratic formula is used to reduce the second equation to R_1 as a function of R_1 alone. These two non-linear equations in two unknowns are solved using an iterative method given in an unpublished paper by Robert Esperti of Delco Electronics.

$$R_3 = \frac{1}{R_1^2 C_2 C_3} \left\{ R_1^2 (C_1 (C_1 + C_3)) + R_1^2 (AC_1) + R_1 (B) + \frac{C}{C_1} \right\} \quad (2-9.20)$$

$$R_1 = \frac{-b}{2a} + \sqrt{\left(\frac{b}{2a}\right)^2 - \frac{c}{a}} \quad (2-9.21)$$

$$\frac{-b}{2a} = \frac{A - C_3 R_3}{2(C_1 + C_3)} ; \quad \frac{c}{a} = \frac{C}{(C_1 + C_3) \cdot C_1 C_2 R_3} \quad (2-9.22)$$

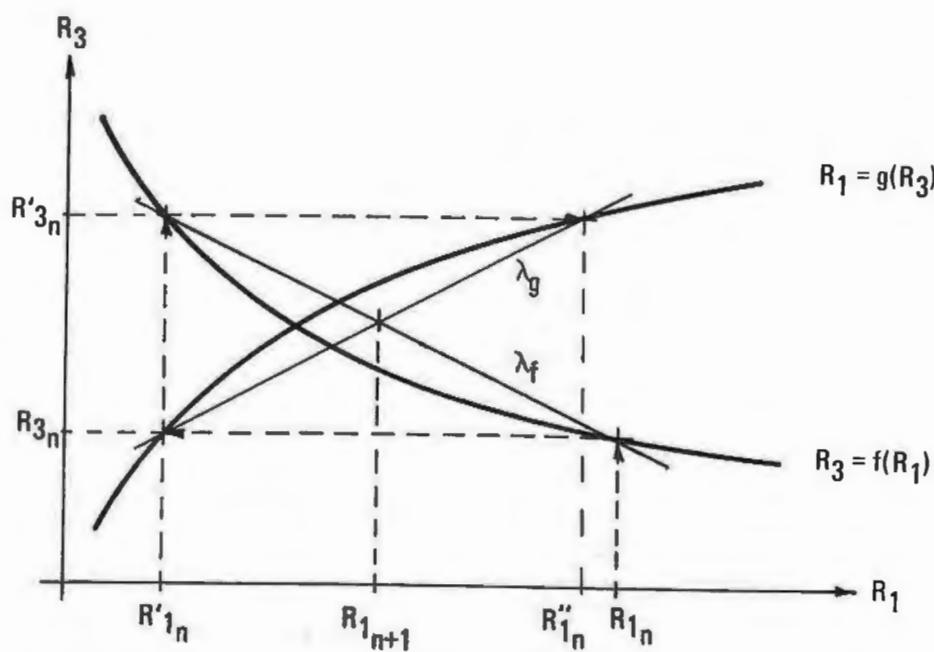


Figure 2-9.4 Esperti's iterative method.

Referring to Fig. 2-9.4, an initial guess for R_1 is made. The corresponding value for R_3 is calculated using $R_3 = f(R_1)$. The corresponding value for R_1 (say R'_1) is calculated using the above value for R_3 in $R'_1 = g(R_3)$. Using $R_3 = f(R'_1)$, a second value of R_3 is calculated; this value of R_3 is designated R''_3 . Finally, a second value of R_1 is calculated using $R_1 = g(R''_3)$; this value of R_1 is designated R''_1 . Straight lines designated λ_f and λ_g are drawn as shown. The intersection of these two lines defines the next guess for R_1 . The iteration is halted when the new and old values for R_1 agree within $10^{-6}\%$. The convergence of this method is quite fast with four iterations generally providing the above accuracy. Furthermore, the method will converge when direct substitution type iteration proves to be divergent.

The above procedure may be done algebraically to yield a recursion relationship as shown below:

$$R_{1,n+1} = R_{1,n} + \frac{g(f(R_{1,n})) - R_{1,n}}{1 - \frac{g(f(g(f(R_{1,n})))) - g(f(R_{1,n}))}{g(f(R_{1,n})) - R_{1,n}}} \quad (2-9.23)$$

The recursion relationship may be further reduced to an algorithm that can be used to program the HP-97. This algorithm is shown below:

$$R'_{1,n} = g(f(R_{1,n})) \quad (2-9.24)$$

$$R''_{1,n} = g(f(R'_{1,n})) \quad (2-9.25)$$

$$\delta = R'_{1,n} - R_{1,n} \quad (2-9.26)$$

$$\delta' = R''_{1,n} - R'_{1,n} \quad (2-9.27)$$

$$\epsilon = \frac{\delta}{1 - \delta'/\delta} \quad (2-9.28)$$

$$R_{1,n+1} = R_{1,n} + \epsilon \quad (2-9.29)$$


$$\text{Terminate if } \left| \frac{\epsilon}{R_{1,n+1}} \right| \leq 10^{-8} \quad (2-9.30)$$

Each time through the $R''_1 = g(f(R_1))$ calculation, the value of R_3 is stored in a scratchpad register. After the iteration loop termination, values for R_1 and R_3 will be at hand. The following formula relates R_2 to these resistors and the other known quantities:

$$R_2 = \frac{C}{C_1 C_2 C_3 R_1 R_3} \quad (2-8.31)$$


To simplify the initial guess for R_1 and to keep the range of numbers within bounds, the selected values for the capacitors are normalized to 1 ohm, 1 radian/second values for use by the program. After the corresponding normalized resistors are calculated, the resistance values are de-normalized before output.


User Instructions

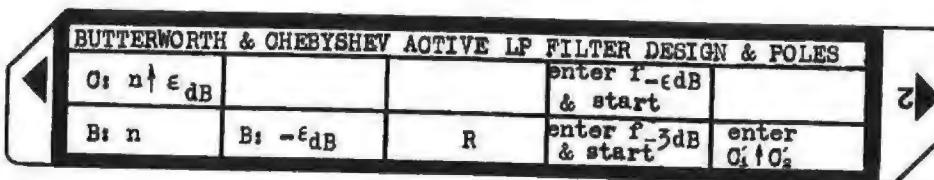

STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
1	Load both sides of program card # 1			
2	If Chebychev: enter filter order enter passband ripple go to step 4	n ε dB	ENT↑ F A	
3	If Butterworth: enter filter order if bandedge is defined by other than the -3dB point, enter the dB down defining the bandedge	n -εdB	A B	
4	Enter the design resistance level	R, Ω	O	
5	If bandedge is -3dB point, enter f-3dB & start f-3dB, Hz		D	If Cheb f-3dB see below for rest
6	If bandedge is -εdB point, enter f-εdB & start f-εdB, Hz		F D	If Buttw f-εdB space ωₙ Q C₁, F C₂, F stop
	The data is for the second order filter section, and alternate capacitor values entered in next step are also for the second order section. The third order section (for odd filter order) is output last and is described on the next page.			third order section output
7	If alternate capacitor values are desired, enter C₁ { to skip this step, press enter C₂ "E" without numeric entry } C₁, F C₂, F		ENT↑ E	R₁, Ω R₂, Ω
	After the second resistor value output, the program execution will automatically return to step six until all second order sections have been outputted. If the filter is odd order, the display will flash to indicate the reading of the second card is required.			

User Instructions

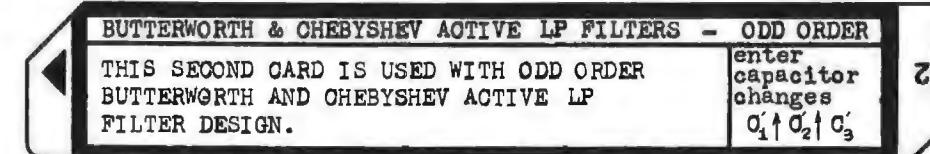

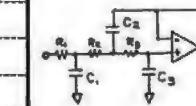STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
9	Read both sides of second card when display flashes with first program. Program operation will automatically resume after the second side of this card is read.			
10	The three capacitor values for the equal resistor topology will be printed.			
11	If alternate capacitor values are desired, key those values via key "E". If the third order section requirements cannot be met with those resistors, the program execution will halt displaying "ERROR". Press any key to clear the display, and enter another set of capacitors using key "E". By staying close to the capacitor values printed in step 2, the error situation will generally be avoided.		C₁, F C₂, F C₃, F ENT↑ ENT↑ E	R₁, Ω R₂, Ω R₃, Ω
12	To run another case, reload both sides of card 1, and return to step 3			

Example 2-9.1

A 1 dB ripple Chebyshev lowpass active filter must pass all frequencies between dc and 1000 Hz within 3 dB, and must reject all frequencies higher than 2000 Hz by more than 60 dB. Program 2-1 may be used to determine the necessary filter order. This program calculates a minimum filter order of 6.19, which is rounded to the next highest integer, 7. A 7th order, 1 dB ripple Chebyshev lowpass filter that is 3 dB down at 1000 Hz, will be 1 dB down at 983.1 Hz and 69.4 dB down at 2000 Hz ($\lambda = 2000/983.1 = 2.035$).

This program (Program 2-9) is used to calculate the element values for a 7th order, 1 dB ripple, 1000 Hz -3 dB cutoff frequency Chebyshev filter. A design resistance level of 10000 ohms is chosen which will make the capacitor values around $1/(2\pi fR) = 0.016 \mu F$.

PROGRAM INPUT

```
7. ENT† n
1. GSBa ε
          dB
10000. GSBC design resistance level
1000. GSBD -3dB frequency
983.1+00 *** -1dB frequency (output)
```

PROGRAM OUTPUT

```
section one
6.154+03 *** ωna
10.96+00 *** Qa
354.2-05 *** C1a
745.5-12 *** C2a
.47-06 ENT† C1a
750.-12 GSBE C2a} alternate values
14.83+03 *** R1a
5.052+03 *** R2a

section two
4.993+03 *** ωnb
3.156+00 *** Qb
126.4-09 *** C1b
3.173-09 *** C2b
.22-06 ENT† C1b
3.-09 GSBE C2b} alternate values
17.72+03 *** R1b
3.429+03 *** R2b

section three
2.965+03 *** ωn} of second order pair
1.297+00 *** Q
1.263+03 *** σ, real pole location
85.66-05 *** C1c
163.9-05 *** C2c
6.385-05 *** C3c
.1-06 ENT† C1c
.22-06 ENT† C2c} alternate values
6.2-05 GSBE C3c
8.800+03 *** R1c
6.113+03 *** R2c
12.82+03 *** R3c
```

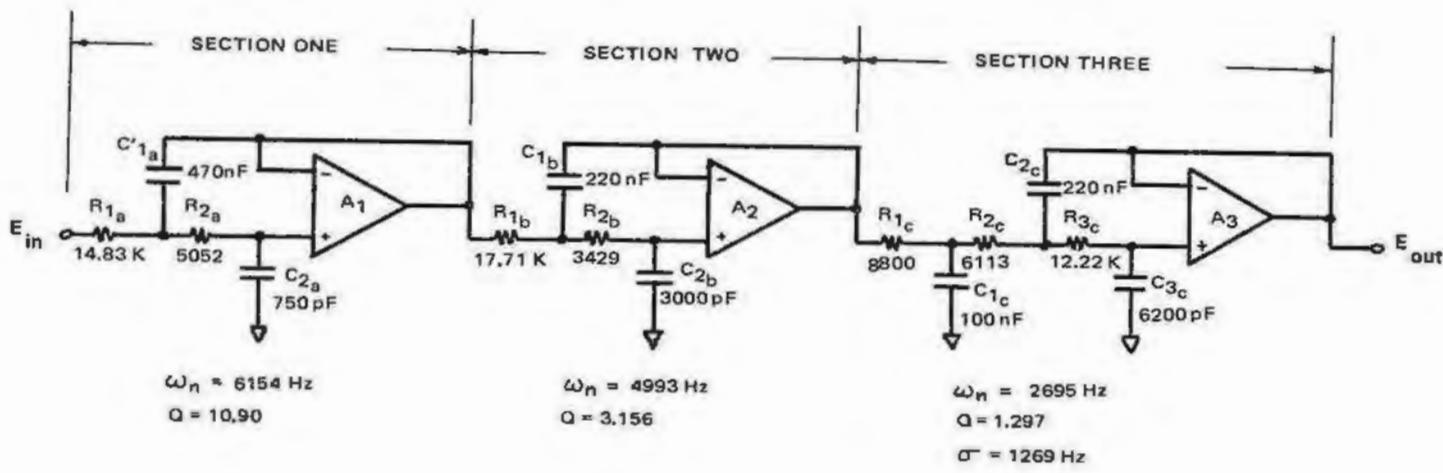


Figure 2-9.5 Overall active filter schematic:

7th order Chebyshev lowpass
1 dB passband ripple
-3 dB at 1000 Hz
-69.4 dB at 2000 Hz

Note: This ordering of the filter sections will result in the lowest output noise assuming the resistance levels in the resonator sections are low enough so the op-amp voltage noise dominates (see Program 1-6). Because the highest Q resonator is first, it will be prone to overload at frequencies near the resonant peak. For filters operating at higher signal levels where self noise is not a concern, the ordering of the sections should be reversed with the lowest Q section placed first.

Example 2-9.2

An active Butterworth lowpass filter must pass all frequencies between dc and 1000 Hz within 1 dB, and must reject all frequencies higher than 3000 Hz by at least 60 dB. Program 2-1 may be used to determine the minimum filter order. This program calculates a minimum filter order of 6.90, which is rounded to 7, the next highest integer. This filter will be 60.9 dB down at 3000 Hz ($\lambda = 3000/1000 = 3$).

This program (Program 2-9) is used to find the element values for a 7th order, 1000 Hz -1 dB cutoff, Butterworth lowpass active filter. A design resistance level of 10000 ohms will keep the capacitor values centered around $1/(2\pi fR) = 0.016 \mu F$.

PROGRAM INPUT

7. GSB_n n
 i. GSB_B ε_{dB}
 10000. GSBC R, design resist level
 1000. GSBA f-εdB
 1.101+03 *** f-3dB (output)

PROGRAM OUTPUT

section one
 6.920+03 *** ε_n
 2.247+00 *** Q_n
 64.34-09 *** C₁
 3.216-09 *** C₂
 68.-09 EHT₁ C'₁
 3000.-12 GSE_E C'₂} alternate values
 14.26+03 *** R₁
 7.180+03 *** R₂

section two
 6.920+03 *** ε_n
 801.5-03 *** Q_n
 23.10-09 *** C₁
 9.010-09 *** C₂
 24.-09 EHT₁ C'₁
 8200.-12 GSE_E C'₂} alternate values
 14.61+03 *** R₁
 7.164+03 *** R₂

section three
 6.920+03 *** ε_n} of second order pair
 555.6-03 *** Q_n
 6.920+03 *** σ
 19.32-09 *** C₁
 22.14-09 *** C₂
 7.058-09 *** C₃
 32.-05 EHT₁ C'₁
 22.-09 EHT₁ C'₂} alternate values
 6300.-12 GSE_E C'₃
 9.172+02 *** R₁
 7.670+03 *** R₂
 13.63+02 *** R₃

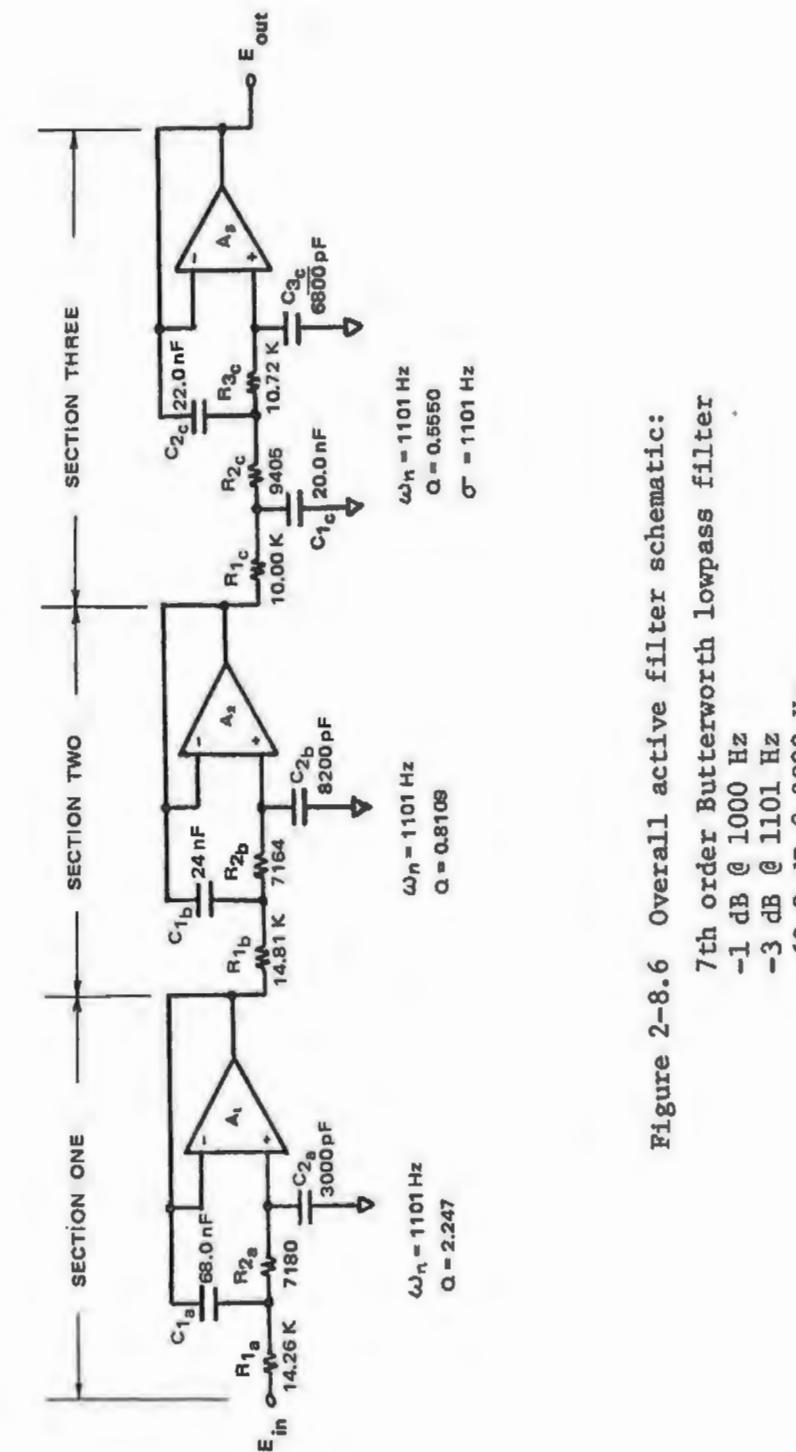


Figure 2-8.6 Overall active filter schematic:
 7th order Butterworth lowpass filter
 -1 dB @ 1000 Hz
 -3 dB @ 1101 Hz
 -60.9 dB @ 2000 Hz

Program Listing I

```

001 *LBLA BUTTERWORTH; LOAD n
002 SF1 indicate Butterworth
003 EEX setup registers;
004 STOB f-3dB/f-εdB = 1
005 STOD cosh a = 1
006 STOE sinh a = 1
007 R↓ recover n
008 GT08 goto filter order entry subr.
009 *LBLa CHEBYSHEV: LOAD n†εdB
010 STOB store εdB
011 R↓ recover filter order, n
012 CF1 indicate Chebyshev
013 GSBS gosub filter order entry subr.
014 RCLB
015 EEX
016 1 calculate;
017 ÷
018 10x 6 =  $\sqrt{10^{0.1\epsilon_{dB}} - 1}$ 
019 EEX
020 -
021 JX
022 1/X 1/ε → R5
023 ST05
024 ENT↑
025 X2 calculate and store:
026 EEX
027 +
028 ∫X a =  $\frac{1}{n} \sinh^{-1}\left(\frac{1}{\epsilon}\right) \rightarrow R2$ 
029 +
030 RCLA
031 1/X
032 YX
033 ST02
034 ENT↑
035 1/X calculate and store:
036 -
037 2
038 ÷ sinh a → RE
039 STOE
040 RCL2
041 ENT↑
042 1/X calculate and store:
043 +
044 2 cosh a → RD
045 ÷
046 STOD
047 GT05 go to data entry flag clear
048 *LBLB LOAD -εdB FOR BUTTERWORTH
049 EEX if bandedge is not defined
050 1 by -3dB point
051 ÷ calculate and store:
052 10x
053 EEX  $f_{-3dB} = [10^{0.1\epsilon_{dB}} - 1]^{\frac{1}{2n}} \rightarrow R_B$ 
054 - f-εdB
055 RCLA

```

REGISTERS									
⁰	¹	²	³	⁴	⁵	⁶	⁷	⁸	⁹
$2k - 1$	$2Q$	a or ω_n	ω_{-3dB}	O_1	$1/\epsilon$	R	ω_k	σ_k	scratch
S0	S1	S2	S3	S4	S5	S6	S7	S8	S9
A filter order, n	$\frac{\epsilon}{\epsilon_{dB}}$, 1, or $f = \frac{3dB}{f = 6dB}$	C	O_2	D	$\cosh a$ or 1	E	$\sinh a$ or 1	I	$\pi/(2n)$

Program Listing II

111	$\rightarrow R$	167	EEX R_1 calculation (continued)
112	RCLD calculate pole positions:	168	+
113	x	169	\sqrt{x}
114	ST07 $\sigma_k = (\sinh a)(\sin \frac{2k-1}{2n}\pi)$	170	EEX
115	X $\geq Y$	171	+
116	RCLC $\omega_k = (\cosh a)(\cos \frac{2k-1}{2n}\pi)$	172	RCL1
117	x	173	\div
118	ST08	174	RCL2
119	$\rightarrow P$	175	\div
120	RCL3	176	RCL9
121	x calculate ω_{nk} and Q_k	177	\div
122	PRTX	178	PRTX
123	ST02 $\omega_{nk}^2 = \sigma_k^2 + \omega_k^2$	179	RCL4
124	X $\leq Y$	180	x R_2 calculation:
125	COS $Q_k = 1/(2 \cos(\tan^{-1} \frac{\omega_k}{\sigma_k}))$	181	RCL9
126	1/X	182	x
127	ST01	183	RCL2 $R_2 = 1/(\omega_n^2 \cdot C_1 \cdot C_2 \cdot R_1)$
128	2	184	x $_2$
129	\div	185	x
130	PRTX	186	1/X
131	LSTX increment k by 2	187	PRTX
132	ST+0	188	*LBL4
133	F0? jump if n is even	189	RCL0
134	GT03	190	RCLA
135	RCL0	191	X $\geq Y?$
136	EEX odd order filter:	192	GT01
137	+ test for last section	193	SPC space paper upon loop exit
138	RCLA (3rd order section)	194	SPC
139	X $\leq Y?$	195	RTN
140	GT02	196	*LBL2 calculate real 3rd order pole
141	*LBL3 calculate O_1 for 2nd order	197	RCLC
142	RCL1	198	RCL3
143	RCL2	199	x
144	\div	200	PRTX
145	RCL6	201	*LBL0 wait loop for 2nd card read
146	\div	202	PSE
147	PRTX	203	GT00
148	ENT↑ save O_1 in stack	204	*LBL8 filter order entry subr
149	ENT↑	205	ST0A
150	RCL1 calculate C_2 for 2nd order	206	2
151	X $_2$	207	\div
152	\div	208	ENT↑ set flag 0 if n is even
153	PRTX $O_2 = \frac{O_1}{4 \cdot Q^2}$	209	INT
154	RTN	210	CF0
155	*LBL8 LOAD ALT CAPACITOR VALUES	211	X=Y?
156	F3?	212	SF0
157	F3? if numeric entry, store,	213	Pi
158	GT04 otherwise jump	214	RCLA calculate and store:
159	ST09	215	ENT↑
160	X $\geq Y$ calculate R_1 :	216	$\pi/(2n) \rightarrow R_I$
161	ST04	217	\div
162	\div	218	ST01
163	RCL1 $R_I = \frac{1 + \sqrt{1 - 4Q^2 \cdot O_2^2}}{2 \cdot Q \cdot \omega_n \cdot O_2}$	219	*LBL5 data entry flag clear subr
164	X $_2$	220	CF3
165	x	221	RTN
166	CHS		

Program Listing I

001 RCL7 ω_k for 3rd order section
 002 RCL8 σ_k
 003 RCL6 R
 004 P_S
 005 SF2
 006 ST06 store denormalization R
 007 R↓
 008 ST08 calculate and store:
 009 →P
 010 X² $\omega_n^2 = \omega_k^2 + \sigma_k^2$
 011 ST01
 012 2 $2\omega_k = \frac{\omega_n}{Q}$
 013 STx0 calculate and store:
 014 RCL4 calculate and store:
 015 RCL1
 016 X C = $\frac{\tau}{\omega_n^2}$
 017 1/X
 018 ST0C
 019 ST05 calculate and store:
 020 RCL6 calculate and store:
 021 RCL0
 022 + $B = \frac{\tau}{\omega_n Q} + \frac{1}{\omega_n^2}$ as
 023 X
 024 ST08 $(\frac{\tau}{\omega_n})(\frac{1}{\tau} + \frac{\omega_n}{Q})$
 025 ST04 calculate and store:
 026 RCL6 calculate and store:
 027 RCL0
 028 X A = $\gamma + \frac{1}{\omega_n Q}$ as
 029 RCL1
 030 +
 031 RCLC $(\frac{\tau}{\omega_n})(\omega_n^2 + \frac{\omega_n}{Q})$
 032 X
 033 ST0A 3 use register arithmetic
 034 STx4 to form and store:
 035 STx5 3B/2, and 30
 037 2
 038 ST=4
 039 ST03 initialize registers for
 040 EEX Newton-Raphson iteration
 041 CHS
 042 8
 043 ST09
 044 *LBL0 Newton-Raphson routine to
 045 RCL3 find the real 3rd order
 046 RCL3 root of $f(C_1) = 0$
 047 RCL3
 048 RCL4 calculate $f(C_1)$ as:
 049 X
 050 RCL4 $f(C_1) = C_1^3 - AC_1^2 + \frac{3B}{2}C_1 - 30$
 051 RCL5
 052 +
 053 X
 054 RCL5
 055 -

056 ST00
 057 CLX calculate $f'(C_1)$ as
 058 3
 059 X $f'(C_1) = 3C_1^2 - 2AC_1 + \frac{3B}{2}$
 060 RCL4
 061 2
 062 X
 063 -
 064 X
 065 RCL4
 066 +
 067 ST=0 form and store:
 068 RCL0
 069 ST-3 $C_{1n+1} = C_{1n} - \frac{f(C_{1n})}{f'(C_{1n})}$
 070 RCL3 iterate again if
 071 ÷
 072 ABS $\left| \frac{f(C_{1n})}{f'(C_{1n})} \right| > 10^{-8}$
 073 RCL9
 074 X_{ZY}?
 075 GT00 calculate and store:
 076 RCL4 calculate and store:
 077 RCL3
 078 -
 079 3 $C_3 = \frac{A - C_1}{3}$
 080 ÷
 081 ST04 calculate:
 082 RCL3 calculate:
 083 X
 084 RCLC $C_2 = \frac{C}{C_1 \cdot C_3}$
 085 X_{ZY}
 086 ÷
 087 RCL4 order C_1, C_2 , and C_3 in
 088 X_{ZY} the stack
 089 RCL3
 090 GSB9 restore P S order
 091 GSB1 denormalize and print
 092 GSB1 capacitors
 093 *LBL1
 094 RCL3 capacitor denormalization
 095 ÷
 096 RCL6 $C_{den} = C_{nor}/(\omega_{edB} \cdot R)$
 097 ÷
 098 PRTX
 099 R↓
 100 RTN

101 *LBL0 LOAD ALTERNATE CAPACITOR
 102 GSB9 VALUES FOR C_1, C_2 , & C_3
 103 RCL3
 104 P_S
 105 SF2
 106 R↓ initialize registers
 107 ST02 store C_1, C_2 , & C_3
 108 R↓
 109 ST01
 110 R↓

REGISTERS

0	1	2	3	4	5	6	7	8	9
$2k-1$			ω_{-3dB}		$1/\epsilon$	R	ω_k	σ_k	
$S_0 C_1, \frac{\omega_n}{Q}$	$S_1 C_2, \omega_n^2$	$S_2 C_3$	$S_3 R_1$	$S_4 R_1, \frac{3B}{2}$	$S_5 R_1, 30$	$S_6 R$	scratch	scratch	10^{-8}

A	$A = \gamma + \frac{1}{\omega_n Q}$	B	$B = \frac{\tau}{\omega_n Q} + \frac{1}{\omega_n^2}$	C	$C = \frac{\tau}{\omega_n^2}$	D	cosh a	E	sinh a	I	$C/(C_1 \cdot C_2)$
---	-------------------------------------	---	--	---	-------------------------------	---	--------	---	--------	---	---------------------

Program Listing II

111 ST00
 112 R↓
 113 RCL6 form $\omega_{edB} * R$
 114 X
 115 STx0
 116 STx1 normalize C_1, C_2, C_3
 117 STx2
 118 EEX store initial guess for R_1
 119 ST03
 120 RCLC
 121 RCL0 form and store: $\frac{C}{C_1 \cdot C_2}$
 122 ÷
 123 RCL1
 124 ÷
 125 ST01
 126 *LBL7 Expert iteration loop start
 127 RCL3 calculate and store:
 128 GSB8 $R_1 = f(g(R_1))$
 129 ST04
 130 GSB8 calculate and store
 131 ST05 $R_1 = f(g(R_1))$
 132 RCL4 calculate: $\delta = R'_1 - R_1$
 133 ST-5
 134 RCL3 calculate: $\delta' = R'_1 - R_1$
 135 ST-4
 136 RCL4
 137 X=0? $\delta = 0$ escape
 138 GT06
 139 EEX
 140 RCL5
 141 RCL4 form: $\Delta R_1 = \frac{\delta}{1 - \delta/\delta'}$
 142 ÷
 143 -
 144 ÷
 145 ST+3 form $R_{1n+1} = R_{1n} + \Delta R_1$
 146 RCL3
 147 ÷ iterate again if
 148 ABS $\left| \frac{\Delta R_1}{R_1} \right| > 10^{-8}$
 149 RCL9
 150 X_{ZY}?
 151 GT07
 152 *LBL6
 153 RCL1
 154 RCL2
 155 ÷ calculate $R_2 = \frac{C}{C_1 C_2 C_3 R_1 R_3}$
 156 RCL3
 157 ÷
 158 RCL8
 159 ÷
 160 RCL6
 161 STx3 denormalize resistors
 162 STx8
 163 X
 164 RCL3 print R_1, R_2 , and R_3
 165 PRTX
 166 X_{ZY}
 167 PRTX
 168 RCL8
 169 PRTX
 170 *LBL9
 171 F2? if flag 2, restore
 172 P_S P_S register order
 173 RTN
 174 *LBL8 subroutine for $R_1 = f(g(R_1))$
 175 RCL0
 176 RCL0 C₁ $R_2 = g(R_1)$
 177 RCL2 C₂ as defined by:
 178 +
 179 ST07 $R_3 = \frac{R_1^2 C_1 C_3 - R_1 R_3 C_1 C_2}{R_1^2 C_2 C_3}$
 180 X
 181 X
 182 RCL1 A
 183 RCL0 C₁
 184 X
 185 -
 186 X
 187 RCLB B
 188 +
 189 RCLC C
 190 RCL0 C₁
 191 ÷
 192 -
 193 RCL1 C₂
 194 RCL2 C₃
 195 X
 196 ÷
 197 X_{ZY}
 198 X²
 199 ÷
 200 ST08 store R_3
 201 RCL2 C₃; $R_1 = f(R_3)$ as defined by:
 202 X
 203 RCL1 A
 204 - $R_1 = -\frac{b}{2a} + \sqrt{\frac{b^2}{4a} - \frac{c}{a}}$
 205 CHS
 206 RCL7
 207 ENT↑ a = $C_1 + C_3$
 208 +
 209 ÷ $-b = A - C_3 R_3$
 210 ENT↑ c = $C/(C_1 C_2 R_3)$
 211 X²
 212 RCL1
 213 RCL8
 214 ÷
 215 RCL7
 216 ÷ $\frac{c}{a}$
 217 -
 218 IX
 219 + R_1
 220 RTN

LABELS				FLAGS		SET STATUS			
A	B	C	D	E	load C_1, C_2, C_3	0	FLAGS	TRIG	DISP
a	b	c	d	e	0	1	0	ON OFF	
Newton-Raphson	denormalize	2	3	4	2 P _S used odd # time	1	1	DEG RAD	SCI ENG
5	6	7	8	9	RTN	2	3	■	■
escape	Expert	routine go	R1-f/g(R1)	P _S routine		3	3		

HP-67 suggested program changes. Program space does not allow the addition of a print, R/S toggle and associated output routine. If the HP-67 user would like the program to stop instead of halting for 5 seconds (print command) change the "print" statements to "R/S" at the following line numbers: (program 1); 122, 130, 147, 153, 178, 187, and 200; (program 2); 098, 165, 167, and 169. To resume program execution with the above changes, execute a "R/S" command from the keyboard after each data output point.

PROGRAM 2-10 BUTTERWORTH AND CHEBYSHEV ACTIVE HIGHPASS FILTER DESIGN AND POLE LOCATIONS.

Program Description and Equations Used

This program calculates the normalized pole locations and provides element values for the un-normalized, unity gain Sallen and Key type second and third order highpass active resonator circuit. Higher order filters are formed by cascading second order sections, and one third order section if the filter order is odd. The program uses either the Butterworth (maximally flat) or Chebyshev (equiripple passband) all pole filter descriptions.

The program is designed to allow the use of specified capacitor values such as would result from the actual measurement of a standard value capacitor. The corresponding resistor values are calculated for each section. The nearest 1% standard value precision resistor will generally suffice for the calculated value.

The design process starts by finding the normalized lowpass pole locations for the desired filter type. If the passband cutoff frequency is different from the conventional definition of the bandedge, a scaling of the normalized cutoff frequency is done. The Butterworth amplitude response is 3 dB down at the passband edge, while the Chebyshev amplitude response is ϵ dB down at the passband edge, where ϵ dB is the passband ripple in dB. The scaling factor is K, and the normalized filter cutoff frequency is denoted by ω_n .

The normalized and scaled lowpass pole locations are sequentially found as complex conjugate pairs, and, if the filter order is odd, the real pole location. The lowpass, unity-gain, Sallen and Key, normalized active filter circuit element values may be found in terms of these pole locations. The element values of the highpass normalized active resonator may be found from the normalized lowpass structure. The normalized lowpass structure is transformed to the normalized highpass structure by replacing each lowpass resistor with a capacitor and vice versa.

The normalized highpass element values are the reciprocals of the corresponding converted lowpass element, i.e., a 2 farad capacitor becomes a $\frac{1}{2}$ ohm resistor. This conversion is equivalent to replacing s by $1/s$ in the lowpass transfer function equation. The un-normalized highpass equation is found by replacing s by ω_c/s , where $\omega_c = 2\pi f_c$, and f_c is the highpass cutoff frequency in hertz.

Each complex conjugate pole pair can be expressed in either the cartesian (real and imaginary parts) or the polar (magnitude and angle) co-ordinate system. A variation on the polar system allows the pole pair to be defined in terms of the natural frequency, ω_n , and "Q" or quality factor. The relationships between these co-ordinate systems is shown in Fig. 2-9.1 The Butterworth and Chebyshev pole locations are given in Program 2-2. By putting all the foregoing concepts together, the denormalized highpass element values can be expressed in terms of ω_n and Q with the second order circuit topology as shown in Fig. 2-10.1.

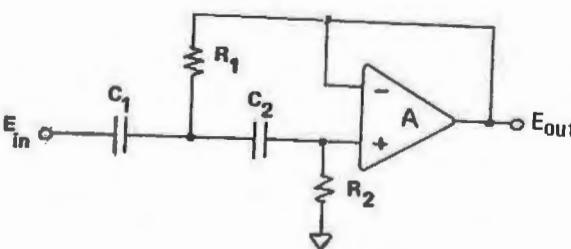


Figure 2-10.1 Highpass Sallen and Key circuit.

$$R_1 = \frac{\omega_n/\omega_c}{Q(C_1 + C_2)} \quad (2-10.1)$$

$$R_2 = \frac{(\omega_n/\omega_c)^2}{R_1 \cdot C_1 \cdot C_2} \quad (2-10.2)$$

The Sallen and Key unity-gain op-amp resonator is chosen over other types because of its low component count and low parameter sensitivities to element value changes (see [19]). High Q realizations are difficult with this resonator type since the resistor value spread is $4Q^2$ when the capacitor values are equal, however, this constraint is not a problem here since the pole Q's are rarely greater than 10.

High pole Q's occur with higher order filters (n greater than 9 or so). In these cases, the Szentirmai leapfrog topology [48], should be given consideration, or else an elliptic response lower order filter might meet the amplitude response requirements (the phase response will be less linear however).

All operational amplifiers have bandwidth limitations, i.e., the μ A-741 has unity open loop gain at 500 kHz typically. When the operating frequency range of the active filter contains frequencies that approach 1% of the op-amp unity gain crossover frequency (500 kHz for the μ A-741), then the contribution of the operational amplifier compensation pole and lower open loop gain must be considered. Program 1-3 can be used to calculate the pole location shifts. Positive and negative feedback resonators of the Deliyannis type can accommodate the op-amp compensation pole and open loop gain characteristic (see [19]).

If the filter order is odd, then a real pole exists. A third order op-amp active resonator circuit may be used to produce both the real pole and a complex conjugate pair. The lowest Q pole pair is chosen for realization by this circuit to keep the element value spread within bounds, and also to minimize sensitivities. The third order active highpass topology is shown in Fig. 2-10.2.

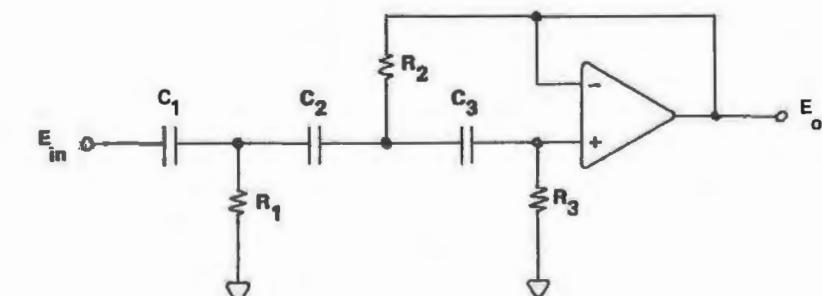


Figure 2-10.2 Third order highpass active filter section.

The transfer function in terms of the R's and C's assuming an ideal operational amplifier is:

$$\frac{E_{out}}{E_{in}} = \frac{s^3 R_1 R_2 R_3 C_1 C_2 C_3}{D(s)} \quad (2-10.3)$$

where

$$D(s) = s^3 R_1 R_2 R_3 C_1 C_2 C_3 + s^2 R_2 \{R_3 C_2 C_3 + R_1 \Sigma CC\}$$

$$+ s \{R_1(C_1+C_2) + R_2(C_2+C_3)\} + 1$$

and

$$\Sigma CC = C_1 C_2 + C_2 C_3 + C_1 C_3 \quad (2-10.4)$$

The resistor values may be obtained from the capacitor values and the pole locations by the simultaneous solution of three equations in three unknowns. These three equations are generated by equating like powers of s between the desired transfer function as expressed with the pole locations and the above transfer function. The desired transfer function in terms of the complex conjugate pole pair as expressed through ω_n and Q, and the real pole location, $1/\tau$, is:

$$\frac{E_{out}}{E_{in}} = \frac{s^3 \left(\frac{1}{\omega_c \tau}\right) \cdot \left(\frac{\omega_n}{\omega_c}\right)^2}{\left\{\frac{s}{\omega_c \tau} + 1\right\} \left\{s^2 \left(\frac{\omega_n}{\omega_c}\right)^2 + s \left(\frac{1}{Q}\right) \left(\frac{\omega_n}{\omega_c}\right) + 1\right\}} \quad (2-10.5)$$

or, in descending powers of s:

$$\frac{E_{out}}{E_{in}} = \frac{s^3 \left(\frac{\omega_n}{\omega_c}\right)^2 \cdot \left(\frac{1}{\omega_c \tau}\right)}{s^3 \left(\frac{\omega_n}{\omega_c}\right)^2 \left(\frac{1}{\omega_c \tau}\right) + s^2 \left(\frac{\omega_n}{\omega_c}\right)^2 \left(1 + \frac{1}{\omega_n Q \tau}\right) + s \left(\frac{\omega_n}{\omega_c}\right) \left(\frac{1}{Q} + \frac{1}{\omega_n \tau}\right) + 1} \quad (2-10.6)$$

The resulting three equations in three unknowns are:

$$R_1 R_2 R_3 C_1 C_2 C_3 = \left(\frac{\omega_n}{\omega_c}\right)^2 \left(\frac{1}{\omega_c \tau}\right) \quad (2-10.7)$$

$$R_2 (R_3 C_2 C_3 + R_1 \Sigma CC) = \left(\frac{\omega_n}{\omega_c}\right)^2 \left(1 + \frac{1}{\omega_n Q \tau}\right) \quad (2-10.8)$$

$$R_1 (C_1 + C_2) + R_2 (C_2 + C_3) = \left(\frac{\omega_n}{\omega_c}\right) \left(\frac{1}{Q} + \frac{1}{\omega_n \tau}\right) \quad (2-10.9)$$

After algebraic manipulation, a cubic equation in R_1 alone is obtained:

$$R_1^3 K_3 + R_1^2 K_2 - R_1 K_1 + K_0 = 0 \quad (2-10.10)$$

where the constants K_3 , K_2 , K_1 , and K_0 are defined by:

$$K_3 = - (C_1 + C_2)(C_1 \Sigma CC) \quad (2-10.11)$$

$$K_2 = \left(\frac{1}{Q} + \frac{1}{\omega_n \tau}\right) (C_1 \Sigma CC) \left(\frac{\omega_n}{\omega_c}\right) \quad (2-10.12)$$

$$K_1 = \left(1 + \frac{1}{\omega_n Q \tau}\right) (C_1 (C_2 + C_3)) \left(\frac{\omega_n}{\omega_c}\right)^2 \quad (2-10.13)$$

$$K_0 = (C_2 + C_3) \left(\frac{1}{\omega_c \tau}\right) \left(\frac{\omega_n}{\omega_c}\right)^2 \quad (2-10.14)$$


The program uses a Newton-Raphson iterative solution to find the real root of Eq. (2-10.10) for R_1 (there will be at least one real root). The details of the Newton-Raphson technique are shown in Program 1-5.

Once R_1 has been obtained, the values for R_2 and R_3 are obtained using the following equations:

$$R_2 = \left(\frac{1}{C_2 + C_3}\right) \left\{ \frac{\omega_n}{\omega_c} \left(\frac{1}{Q} + \frac{1}{\omega_n \tau}\right) - R_1 (C_1 + C_2) \right\} \quad (2-10.15)$$


$$R_3 = \left(\frac{\omega_n}{\omega_c}\right)^2 \left(\frac{1}{\omega_c \tau}\right) \left(\frac{1}{R_1 R_2 C_1 C_2 C_3}\right) \quad (2-10.16)$$

User Instructions

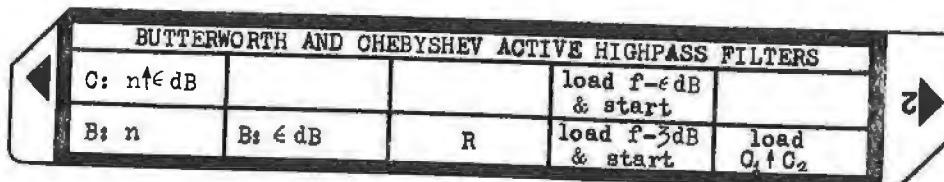

STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
1	Read both sides of program card one			
2	If Chebyshev response is desired: a) Load filter order b) Load passband ripple in dB c) go to step 4	n ε dB	ENT↑ F A	
3	If Butterworth response is desired: Load filter order If the passband edge is defined at other than the -3dB point, enter the bandedge attenuation in dB (attenuation is expressed as a positive number)	n dB	A B	
4	Load operating resistance level *** The calculated resistor values will usually be within a decade of this value.	R	O	
5	If the passband edge is defined by the -3dB amplitude response point, enter f-3dB *** *The Chebyshev bandedge is usually defined by the -εdB point since the passband response oscillates within a band εdB wide. If a Chebyshev response has been selected, the frequency where the amplitude response exits the εdB ripple band will be printed. go to step 7 (read step 6 commentary)	f-3dB	D f-εdB*	See step 6 continuation on next page for rest of output.
6	If the passband edge is defined by the -εdB point, enter f-εdB *** **If Butterworth response has been selected, the frequency where the response is 3dB down will be printed.	f-εdB	F D f-3dB**	

User Instructions

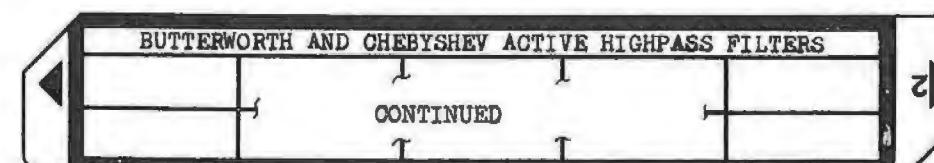

STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
6	The design capacitance value is outputted.*** If this value is unacceptable from a circuit or practicality point of view, alter the design resistance level accordingly using key "C", then recalculate the design capacitance level using key "D". The design cutoff frequency need not be re-entered even though the original frequency entry was via keys "F", "D". When an acceptable design capacitance level has been found, continue program output by using "R/S".	new R	C D R/S	Cdesign new Cdes ωn Q1 stop
7	Enter capacitor values to be used in this second order filter section ***	C1 C2 space	ENT↑ E	R1 R2 n2 Q2 stop
	Keep entering capacitor values for succeeding sections until all second order sections have been defined.	C1 C2 • • • R2n	ENT↑ E	R12 • • • R2n odd order filter: last sect
	If an odd order filter is being designed, the last printout will be a set of three numbers, and the display will flash to indicate that the loading of the second card is required. It is not necessary to stop the program, just insert the second card into the card reader and read both sides.	C1 C2 • • • C1n C2n R2n odd order filter: last sect	ENT↑ ENT↑ E	ωn Q 1/τ flashing display
	After the second card reading is complete, load the three capacitor values to be used with this third order filter section using key "E".	C1 C2 C3	ENT↑ ENT↑ E	R1 R2 R3
	*** The unit of resistance is ohms, capacitance is farads, and frequency is hertz.			

Example 2-10.1

A fifth order, $\frac{1}{2}$ dB passband ripple Chebyshev active highpass filter is to have 3 dB or less attenuation at 10 Hz. A National Semiconductor type LF-156 bi-fet operational amplifier is chosen as the active element in the filter.

Design an active filter to meet these specifications and choose the operating resistance level to achieve the lowest capacitance values in the filter without affecting the dc drift characteristics of the operational amplifier by more than 10%. The operating temperature range is -25°C to $+85^{\circ}\text{C}$.

From the LF-156 data sheet, the maximum input bias current occurs at the highest operating temperature, $+85^{\circ}\text{C}$, and is approximately 1 nA. The typical input offset voltage is 3 millivolts. The resistance level that will generate 0.3 millivolts with 1 nA flowing is:

$$R = (3 \times 10^{-4} \text{ V}) / (1 \times 10^{-9} \text{ A}) = 300 \text{ k}\Omega$$


The filter is then designed with this value in mind as the largest resistance value which has an effect on the dc output of the last filter stage. Being a highpass filter, each stage of the filter blocks the dc voltage present from the preceding stage.

The filter design will be done twice, once with $300 \text{ k}\Omega$ as the design resistance level to determine the value of R_2 in the last (third order) section. The operating resistance level is then scaled to cause the highest resistance value (R_2) to be $300 \text{ k}\Omega$. The HP-97 printout for these operations is shown on the next page.

In the second run of the program, the design capacitance level is $0.1749 \mu\text{F}$. The nearest larger standard capacitor value is $0.22 \mu\text{F}$. The filter will require five capacitors, therefore, five $0.22 \mu\text{F}$ mylar capacitors were drawn from stock, and their capacitances measured. The measured values were: $0.2236 \mu\text{F}$, $0.2014 \mu\text{F}$, $0.1965 \mu\text{F}$, $0.2173 \mu\text{F}$, and $0.2542 \mu\text{F}$. The filter resistances are designed around these capacitor values.

Example 2-10.1 printout

FIRST PROGRAM RUN	SECOND PROGRAM RUN
LOAD FIRST PROGRAM CARD	LOAD FIRST PROGRAM CARD
5. ENT† load filter order	5. ENT†
.5 GSBE load passband ripple	.5 GSBE
300000. GSBC load design resist	90.99+03 GSBC load new design
10. GSBD load -3dB frequency	resistance level
10.59+00 *** - $\frac{1}{2}$ dB frequency (o/p)	10. GSBD
53.05-05 *** design capacitance	10.59+00 ***
R/E level (output)	174.9-03 *** new design capacitor
continue execution	R/S value (output)
960.8-33 *** ω_n first section	960.8-03 *** ω_n
4.545+00 *** Q enter first section	4.545+00 *** Q
53.05-09 ENT† GSBE design capacitance	.2236-06 ENT† Q_1 first section
31.71+03 *** R ₁ first section	.2014-06 GSBE Q_2 selected caps
2.628+06 *** R ₂ resistor values	7.916+03 *** R ₁ first section
651.9-03 *** ω_n	655.9+03 *** R ₂ resistor values
1.178+00 *** Q second section	651.9-03 *** ω_n
342.1-03 *** 1/ τ LOAD SECOND CARD	1.178+00 *** Q second section
53.05-09 ENT†	342.1-03 *** 1/ τ LOAD SECOND CARD
ENT† enter design cap	.1965-06 ENT† Q_1 second section
GSBE	.2173-06 ENT† Q_2 input (third
90.47+02 *** R ₁ } second section	.2542-06 GSBE Q_3 order filter)
43.86+03 *** R ₂ } resistor values	24.17+03 *** R ₁ second section
985.1+03 *** R ₃ }	9.014+03 *** R ₂ resistor values
965.1+03 ENT†	247.8+03 *** R ₃
300.+03 \div scale design	
1/ τ	
303.3-03 *** resistance level	
300000. to make R ₃ become	
90.99+03 *** 300 k Ω	

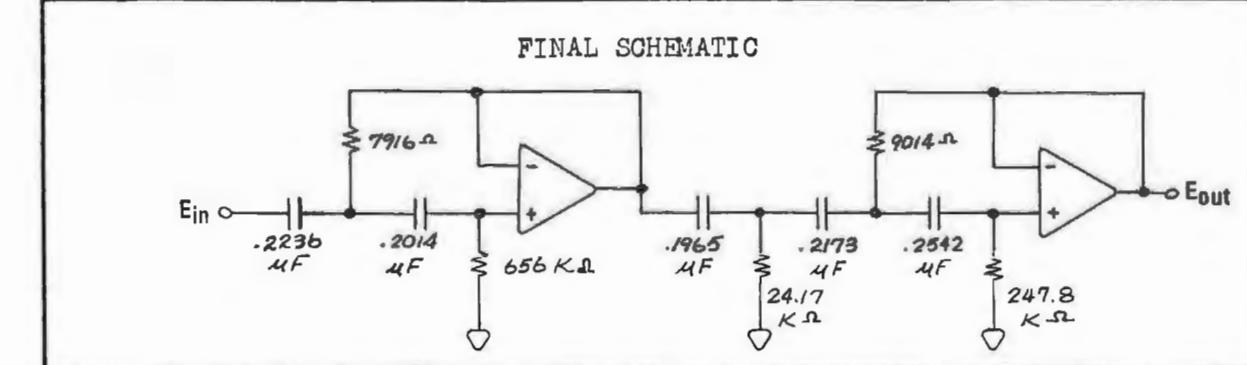

Program Listing I

```

001 *LBLA BUTTERWORTH: LOAD n
002 SF1 indicate Butterworth
003 EEX setup registers:
004 STOB f-3dB/f-εdB = 1
005 STOD cosh a = 1
006 STOE sinh a = 1
007 GSB5
008 GT06
009 *LBLB CHEBYSHEV: LOAD n f-εdB
010 CF1 indicate Chebyshev
011 STOB store εdB
012 GSB5 go sub input routine
013 RCLB calculate:
014 EEX
015 1 ε = (100.1εdB - 1)1/2
016 ÷
017 10x
018 EEX
019 -
020 JX
021 1/X store 1/ε → R5
022 ST05
023 ENT↑ calculate and store:
024 X2
025 EEX
026 +
027 JX a =  $\frac{1}{n} \sinh^{-1}\left(\frac{1}{\epsilon}\right) \rightarrow R2$ 
028 +
029 RCLA
030 1/X
031 YX
032 ST02
033 ENT↑ calculate and store:
034 1/X
035 -
036 2 sinh a → RE
037 ÷
038 STOE
039 RCL2 calculate and store:
040 ENT↑
041 1/X
042 +
043 2 cosh a → RD
044 ÷
045 STOD
046 LSTX calculate and store:
047 RCL5
048 ENT↑
049 X2
050 EEX  $\frac{f-\epsilon dB}{f-3dB} = \cosh\left(\frac{1}{n} \cosh^{-1}\left(\frac{1}{\epsilon}\right)\right)$ 
051 -
052 JX
053 +
054 RCLA
055 1/X
056 YX
057 ENT↑
058 1/X
059 +
060 ÷
061 STOB
062 GT06
063 *LBLB LOAD ε dB for Butterworth
064 EEX calculate and store:
065 1
066 ÷
067 10x
068 EEX
069 -  $f-3dB = \left[10^{0.1\epsilon dB} - 1\right]^{\frac{1}{2n}}$ 
070 RCLB
071 1/X
072 YX
073 JX
074 1/X
075 STOB
076 GT06
077 *LBLC LOAD OPERATING RESISTANCE
078 ST06 LEVEL
079 GT06
080 *LBLD LOAD f-3dB and START
081 STOC temporarily store f-3dB
082 F1? jump if Butterworth
083 GT00
084 RCLB recall Cheb denorm ratio
085 ST03
086 ÷ form -εdB frequency
087 F3? print f-εdB if data entered
088 GSB4
089 RCLC recall f-3dB
090 *LBLd LOAD f-εdB and START
091 STOC temporarily store frequency
092 RCLB recall Buttr denorm ratio
093 F1? if Buttr, store ratio
094 ST03
095 ÷ if Butterworth, calculate
096 F1? and print f-3dB
097 PRTX
098 *LBL0
099 SPC
100 CF2
101 RCLC
102 ENT↑ if flag 3, 2nfc → R5
103 +
104 PI
105 X
106 F3?
107 ST05
108 RCL5
109 RCL6 calculate and print
110 X nominal capacitor value

```

REGISTERS

⁰ 2k-1	¹ Q	² a or ω _n	³ K	⁴ C ₁	⁵ ω _c , 1/ε	⁶ R	⁷ ω _n /ω _c	⁸	⁹ C ₂
S0	S1	S2	S3	S4	S5	S6	S7	S8	S9
A filter order, n	B εdB, 1, f-3dB	C cutoff frequency	D cosh a or 1	E sinh a or 1	F π/2n				

Program Listing II

```

111 1/X print design capacitance
112 PRTX
113 SPC stop program execution and
114 R/S await operator decision
115 EEX setup for next loop
116 ST00
117 *LBL1 second order filter loop
118 SPC
119 RCL0 calculate normalized
120 RCLI pole locations:
121 X
122 EEX
123 +R σk = (sinh a)(sin((2k-1)π/2n))
124 RCLD
125 X ωk = (cosh a)(cos((2k-1)π/2n))
126 X+Y
127 RCLC
128 X
129 +P calculate ωn,k and Qk, scale
130 RCL3 ωn,k for proper normalized
131 X bandedge
132 PRTX
133 ST02 ωn,k = [ωk2 + σk2]1/2 · (K)
134 X+Y
135 COS
136 ENT↑ Qk =  $\frac{1}{2 \cos(\tan^{-1} \frac{\omega_k}{\sigma_k})}$ 
137 +
138 1/X
139 ST01
140 PRTX
141 2 increment 2k by 2
142 ST+0
143 F0? if even order filter, rtn
144 RTN and await capacitor values
145 RCL0 odd order filter:
146 RCLB jump if last section
147 X?Y?
148 GT02
149 RTN await capacitor values
150 *LBL0 LOAD CAPACITOR VALUES
151 F2? reject input if 3rd order
152 GT03 section has been outputted
153 ST09 store C2
154 X+Y store C1
155 ST04
156 + calculate and print R1
157 RCL1
158 X R1 =  $\frac{\omega_n/\omega_c}{Q(C_1 + C_2)}$ 
159 RCL2
160 RCL5
161 ÷
162 ST07
163 X+Y
164 ÷
165 PRTX

```

NOTE TRIG MODE

LABELS				FLAGS	SET STATUS			
A Buttr load n	B Buttr load εdB	C LOAD R & START	D LOAD f-3dB & LOAD CAPACITORS	⁰ n even	¹ Buttr	FLAGS	TRIG	DISP
a Cheb load n dB	b	c	d LOAD f-εdB & START	0 ON OFF	1 DEG	2 RAD	3 FIX	
0 2nf calc	1 2nd order filter loop	2 3rd order filter loop	3 print & set flag	2 go to wait loop	3 data in	4 SCI	5 ENG	6 n 3
5 entry subroutine	6 exit subroutine	7	8	9				

Program Listing I

```

001 R/S cancel pause after card read
002 *LBL0 LOAD C1+C2+C3 and START
003 SPC
004 GSB9 test for PzS
005 PzS execute and signal PzS
006 SF2
007 ST03 store O3
008 R↓ store O2
009 ST02
010 R↓ store O1
011 ST01
012 RCL2 calculate and store:
013 x
014 RCL2 O1. ΣOO → R7
015 RCL3
016 x
017 +
018 RCL3
019 RCL1
020 x
021 +
022 RCL1
023 x
024 ST07
025 GSB9 PzS and reset flag 2
026 RCL5 obtain and store ωo
027 ST01
028 RCL6
029 RCL3 calculate 1/τ
030 x
031 RCL1 recall: Q
032 RCL2 ωn
033 RCL6 R
034 PzS execute and signal PzS
035 SF2
036 ST08 store R
037 R↓ store ωn
038 ST04
039 R↓
040 1/X form and store 1/Q
041 ST06
042 X↑Y store 1/τ
043 ST05
044 x
045 RCL4
046 + form C1(1/τQ + ωn)
047 RCL1
048 x
049 RCL2
050 RCL3 form and store O2 + O3
051 +
052 ST0A
053 x
054 RCL4 form and store:
055 x
056 RCLI K1 = ωn²(1/τQ + ωn)C1(O2+O3)
057 x²
058 ÷
059 ST0B
060 RCL4
061 RCLI
062 ÷
063 x² form and store:
064 RCLI
065 ÷
066 RCL5 K0 = (ωn²/τ)(O2 + O3)(1/ωc)
067 x
068 RCLA
069 x
070 ST0A
071 RCL5
072 RCL4
073 RCL6
074 x
075 +
076 RCL7
077 x
078 RCLI K2 = (1/τ + ωn)(O1ΣOO)1/ωc
079 ÷
080 ST0C
081 RCL1
082 RCL2
083 +
084 RCL7
085 x
086 CHS K3 = -(O1 + O2)(O1ΣOO)
087 ST0D
088 RCL0
089 EEX form and store 10⁻⁸·R
090 8 for iteration loop
091 ÷ exit test
092 ST09

```

REGISTERS

0	1	2	3	4	5	6	7	8	9
S0 R1	S1 C1	S2 O2	S3 C3	S4 ωn	S5 1/τ	S6 1/Q	S7 O1. ΣOO	S8 f/f'	S9 10⁻⁸·R
A K0	B -K1	C K2	D K3	E sinh a or 1	F 1	G ωc	H	I	J

Program Listing II

```

093 *LBL0 Newton-Raphson loop for R1
094 RCL0
095 RCL0
096 RCL0 form and store:
097 RCLD
098 x
099 RCLC f(R1) = K3R1³ + K2R1² + K1R1 + K0
100 +
101 x
102 RCLB
103 -
104 x
105 RCLA
106 +
107 ST08
108 CLX
109 +
110 +
111 +
112 RCLD f'(R1) = 3K3R1² + 2K2R1 + K1
113 x
114 RCLC
115 ENT†
116 +
117 +
118 x
119 RCLB
120 -
121 ST=8 form -ΔR1 = f(R1)/f'(R1)
122 RCL8 form R1n+1 = R1n + ΔR1
123 ST=0
124 ABS iterate again if
125 RCL9 |ΔR1| ≥ 10⁻⁶ · R1
126 X≤Y? 127 ST08
128 RCL0 recall and print R1
129 PRTX
130 RCL5
131 RCL4
132 RCL6 calculate and print R2
133 x
134 +
135 RCLI R2 = 1/ωc(1/τ + ωn/Q) - R1(O1+O2)
136 ÷
137 RCL1
138 RCL2
139 +
140 RCL0
141 x
142 -
143 RCL2
144 RCL3
145 +
146 ÷
147 PRTX
148 RCL0
149 x
150 RCLI
151 x
152 RCL2
153 x
154 RCL3
155 x
156 1/X R3 = (1/ωc²) ωn²/τ
157 RCL4
158 RCLI
159 ÷
160 x²
161 x
162 RCLI
163 ÷
164 RCL5
165 x
166 PRTX
167 SPC
168 *LBL9
169 F2? if flag 2, execute PzS
170 PzS
171 RTN

```

LABELS					FLAGS		SET STATUS		
A	B	C	D	E load capacitors	0	1	FLAGS	TRIG	DISP
a	b	c	d	e	0	1	ON OFF	DEG GRAD RAD	FIX SCI ENG n 3
0 Newton-Raphson	1	2	3	4	2	PzS			
5	6	7	8	9	3				

PROGRAM 2-11 DELIYANNIS POSITIVE AND NEGATIVE FEEDBACK ACTIVE RESONATOR DESIGN (USED FOR ACTIVE BANDPASS FILTERS).

Program Description and Equations Used

Active filter resonators are constrained by component value ranges (10 ohms to 10 megohms, 100 pF to 10 μ F), operational amplifier gain-bandwidth limitations, and overall circuit sensitivities. The Deliyannis resonator circuit allows high Q realizations and also compensates for the finite gain and bandwidth of the operational amplifier [20].

This resonator synthesizes a second order pole pair of given ω_n and Q. The natural frequency, ω_n , and the quality factor, Q, are provided as outputs from the active Butterworth and Chebyshev filter programs contained in this section.

This resonator type has the ability to synthesize a resonator with infinite Q. The infinite Q resonator is used in the interior stages of the Szentirmai leapfrog filter topology [48]. The leapfrog active filter is a direct simulation of a passive LC filter, and generally has the same low sensitivity characteristics of the LC topology. When narrowband active filters are required, the leapfrog topology will be one of the viable candidates for filter realization (also see the GIC realization in Program 2-6).

The circuit for the Deliyannis second order bandpass circuit is shown in Fig. 2-11.1.

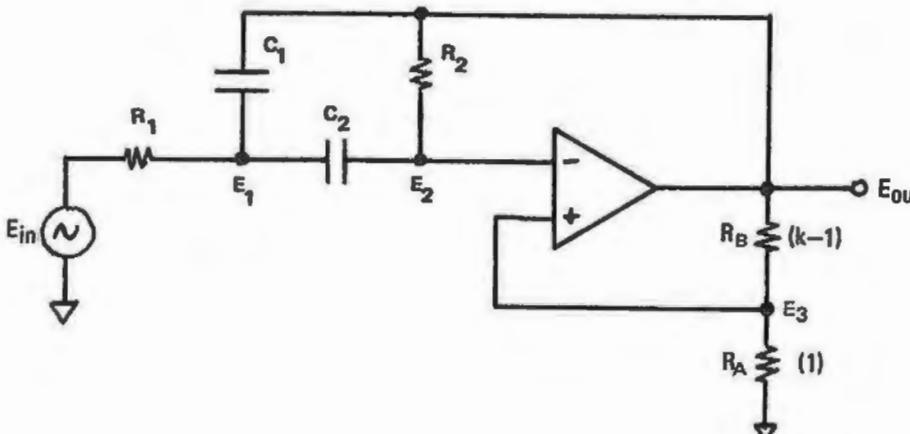


Figure 2-11.1 Deliyannis bandpass resonator circuit.

The transmission function is obtained using nodal analysis. In matrix form, the nodal equations are:

$$E_{out} = A(s)[E_3 - E_2], \text{ (op-amp transmission fcn)} \quad (2-11.1)$$

$$\begin{bmatrix} \frac{1}{R_1} + s(C_1 + C_2) & \{-sC_2\} \\ \{-sC_2\} & \{\frac{1}{R_2} + sC_2\} \end{bmatrix} \cdot \begin{bmatrix} E_1 \\ E_2 \end{bmatrix} = \begin{bmatrix} \frac{1}{R_1} & sC_1 \\ 0 & \frac{1}{R_2} \end{bmatrix} \cdot \begin{bmatrix} E_{in} \\ E_{out} \end{bmatrix} \quad (2-11.2)$$

where

$$E_3 = E_{out}/k \quad (2-11.3)$$

Solving for E_2 from Eqs. (2-11.1) and (2-11.3):

$$E_2 = E_{out} \left[\frac{1}{k} - \frac{1}{A(s)} \right] \quad (2-11.4)$$

The transmission function is first obtained for the general case using $A(s)$, then more specifically using $A(s) = A_0/(\tau s)$. The passive sensitivities may be obtained from the general solution, and the active sensitivities obtained from the specific solution, $A(s) = A_0/(\tau s)$.

The matrix equation is rewritten to bring $1/k - 1/A(s)$ inside the coefficient matrix, and to bring all dependent variables to the right

hand side of the equation:

$$\begin{bmatrix} \left\{ \frac{1}{R_1} + s(C_1 + C_2) \right\} & \left\{ -s[C_1 - C_2 \left(\frac{1}{k} - \frac{1}{A(s)} \right)] \right\} \\ \left\{ -sC_2 \right\} & \left\{ \left(\frac{1}{R_2} \right) \left(\frac{1}{k} - \frac{1}{A(s)} - 1 \right) + sC_2 \left(\frac{1}{k} - \frac{1}{A(s)} \right) \right\} \end{bmatrix} \cdot \begin{bmatrix} E_1 \\ E_{out} \end{bmatrix} = \begin{bmatrix} \frac{1}{R_1} \\ 0 \end{bmatrix} \cdot E_{in} \quad (2-11.5)$$

Cramer's rule is used to find the expression for E_{out}/E_{in} , the filter transmission function.

$$\frac{E_{out}}{E_{in}} = \frac{s}{s^2 + s \left\{ \frac{1}{R_2 C_1} + \frac{1}{R_2 C_2} + \frac{1}{R_1 C_1} \cdot \frac{1/A(s) - 1/k}{1 + 1/A(s) - 1/k} \right\} + \frac{1}{R_1 R_2 C_1 C_2}} \quad (2-11.6)$$

The passive sensitivities may be evaluated assuming the op-amp to be ideal, i.e., the open loop gain is allowed to approach infinity. In this situation, the transmission function becomes:

$$\frac{E_{out}}{E_{in}} = \frac{\frac{ks}{R_1 C_1 (k-1)}}{s^2 + s \left\{ \frac{1}{R_2 C_1} + \frac{1}{R_2 C_2} - \frac{1}{(k-1) R_1 C_1} \right\} + \frac{1}{R_1 R_2 C_1 C_2}} \quad (2-11.7)$$

The coefficients of the denominator of this equation may be compared with the like coefficients in the standard second order form to derive expressions for ω_n and Q. The standard second order form of the transmission function is:

$$\frac{E_{out}}{E_{in}} = \frac{ks}{s^2 + \frac{\omega_n}{Q} s + \omega_n^2} \quad (2-11.8)$$

The following expressions for ω_n , Q, and K are obtained:

$$K = -\frac{k}{R_1 C_1 (k-1)} \quad (2-11.9)$$

$$\omega_n = (R_1 R_2 C_1 C_2)^{-\frac{1}{2}} \quad (2-11.10)$$

$$Q = \frac{\sqrt{\frac{R_2^2}{R_1}}}{\sqrt{\frac{C_2}{C_1}} + \sqrt{\frac{C_1}{C_2}} - \frac{1}{k-1} \cdot \frac{R_2}{R_1} \cdot \sqrt{\frac{C_2}{C_1}}} \quad (2-11.11)$$

Let $\mu = R_2/R_1$, and $\delta = C_2/C_1$, then:

$$Q = \frac{\sqrt{\mu \delta}}{\delta + 1 - \mu \delta / (k-1)} \quad (2-11.12)$$

The denominator of Eq. (2-11.12) can be made arbitrarily small by proper choice of μ . The denominator can be made to vanish completely causing Q to become infinite, thus generating the infinite Q resonator required for the interior stages of the leapfrog filter topology.

Sensitivities are a way of expressing how much a given parameter, say Q, is affected by a change in one of the circuit elements. The general convention is to express sensitivities as a dimensionless number formed from the ratio of individual percentage changes:

$$S_R^Q = \lim_{\Delta R \rightarrow 0} \frac{\Delta Q/Q}{\Delta R/R} = \frac{R}{Q} \cdot \frac{\partial Q}{\partial R} \quad (2-11.13)$$

Applying this definition to the expressions for μ_n , Q, and K, the following passive sensitivities result:

$$S_{R_1}^{\omega_n}, R_2, C_1, C_2 = -\frac{1}{2} \quad (2-11.14)$$

$$S_{R_1}^Q = -S_{R_2}^Q = -\frac{1}{2} - Q \frac{\sqrt{\mu \delta}}{k-1} \quad (2-11.15)$$

$$S_{C_1}^Q = -S_{C_2}^Q = -\frac{1}{2} + Q \sqrt{\mu \delta} \left(\frac{1}{\mu} - \frac{1}{k-1} \right) \quad (2-11.16)$$

$$S_{R_B}^Q = -S_{R_A}^Q = Q \frac{\sqrt{\mu \delta}}{k-1} \quad (2-11.17)$$

$$S_{R_1}^K, C_2 = -1 \quad (2-11.18)$$

$$S_{R_A}^K = -S_{R_B}^K = 1/k \quad (2-11.19)$$

The break frequency of the open loop transmission function of most operational amplifiers is around 10 Hz, and the gain-bandwidth product (GBP) is about 10^6 Hz thus, the finite gain characteristics of the op-amp begin to affect the active filter response when kilohertz frequencies are involved. In this frequency range, the operational amplifier transmission function, $A(s) = A_o/(1 + \tau s)$, may be approximated by $A(s) = A_o/\tau s$. With this approximation, the active filter transmission function becomes:

$$\frac{E_{out}}{E_{in}} = \frac{s}{s^2 + s \left\{ \frac{1}{R_2 C_1} + \frac{1}{R_2 C_2} + \frac{1}{R_1 C_1} \cdot \frac{\tau s/A_o - 1/k}{1 + \tau s/A_o - 1/k} \right\} + \frac{1}{R_1 R_2 C_1 C_2}} \quad (2-11.20)$$

This expression is expanded, and like powers of s collected to form the final expression for the active filter transmission function:

$$\frac{E_{out}}{E_{in}} = \frac{s \frac{-k}{R_1 C_1}}{D(s)} \quad (2-11.21)$$

where

$$D(s) = s^3 \frac{k \tau}{A_o} + s^2 \left\{ k-1 + \frac{k \tau}{A_o} \left(\frac{1}{R_2 C_1} + \frac{1}{R_2 C_2} + \frac{1}{R_1 C_1} \right) \right\}$$

$$+ s \left\{ (k-1) \left(\frac{1}{R_2 C_1} + \frac{1}{R_2 C_2} \right) - \frac{1}{R_1 C_1} + \frac{\tau k}{A_o R_1 R_2 C_1 C_2} \right\} + \frac{k-1}{R_1 R_2 C_1 C_2}$$

The denominator is factored into a single pole and a complex conjugate pair:

$$\frac{E_{out}}{E_{in}} = \frac{\frac{s}{H} \cdot \frac{\omega_n Q}{\omega_n^2}}{\left(\frac{s}{\sigma} + 1 \right) \left(\frac{s^2}{\omega_n^2} + \frac{s}{\omega_n Q} + 1 \right)} \quad (2-11.22)$$

The natural frequency, ω_n , and the quality factor, Q, are derived by equating like powers of s between Eqs. (2-11.21) and (2-11.22):

$$\omega_n = \frac{1}{R_1 R_2 C_1 C_2} \cdot \sqrt{1 - \frac{\tau k^2}{A_o(k-1) R_1 C_1}} \quad (2-11.23)$$

$$BW = \frac{\omega_n}{Q} = \left\{ \frac{1}{R_2 C_1} + \frac{1}{R_2 C_2} + \frac{1}{R_1 C_1 (k-1)} \right\} \left\{ 1 - \frac{\tau k^2}{A_o (k-1) R_1 R_2} \right\} \quad (2-11.24)$$

From these equations, the active sensitivities are derived:

$$S_{A/\tau}^Q = S_{A/\tau}^Q = \frac{1}{2} \cdot \frac{\omega_n^2}{A_o} \cdot \left(\frac{k}{k-1} \right)^2 \cdot \sqrt{\mu \delta} \quad (2-11.25)$$

$$\text{where } \mu = R_2/R_1 \quad (2-11.26)$$

$$\text{and } \delta = C_2/C_1 \quad (2-11.27)$$

as defined previously. The objective is to choose μ or δ to strike a happy medium between the active and the passive sensitivities (see [19], p. 319).

The Designers Guide to Active Filters [26], has the set of equations that generate the element values for this positive and negative feedback biquad. The point is made that by choosing $\delta < 1$ some of the active sensitivities may be reduced at the expense of resistor value spread (μ increases).

Equations (2-11.28) through (2-11.42) are used by the HP-67/97 program. The equation solution starts with a choice for the capacitor ratio, δ , and positive feedback ratio, k , and the operational amplifier dc gain, A_o , and gain bandwidth product, GBP. The resonant frequency is f_o and $p = 1/k$ ($f_a = 1/(2\pi\tau)$).

$$\Omega = f_a/f_o = GBP/(f_o A_o) \quad (2-11.28)$$

$$\gamma = A_o \Omega = GBP/f_o \quad (2-11.29)$$

$$d = 1/Q \quad (2-11.30)$$

$$\beta = \Omega - p\gamma = (1 - \frac{A_o}{k}) \quad (2-11.31)$$

$$m = \gamma + \beta = \Omega \left\{ 1 + A_o \left(1 - \frac{1}{k} \right) \right\} \quad (2-11.32)$$

$$a_2 = (\delta + 1) \{ m(m-d) + 1 \} \quad (2-11.33)$$

$$a_1 = \delta m - (\delta + 1) \beta - (m-d)(md-1) \quad (2-11.34)$$

$$a_0 = m(\beta-d) + 1 \quad (2-11.35)$$

$$\left. \begin{array}{l} C_1 = 1 \\ C_2 = \delta \end{array} \right\} \text{normalized values} \quad (2-11.36)$$

The quadratic equation is used to find the positive real root (R_1) of:

$$a_2 R_1^2 + a_1 R_1 + a_0 = 0 \quad (2-11.38)$$

i.e.,

$$R_1 = \frac{-a_1}{2a_2} + \sqrt{\left(\frac{a_1}{2a_2} \right)^2 - \frac{a_0}{a_2}} \quad (2-11.39)$$

then

$$R_2 = \frac{m(\delta+1) R_1 - (dm-1)}{(R_1 - \beta) \delta} \quad (2-11.40)$$

H is the gain of the filter at resonance:

$$H = \frac{-R_2 \cdot \delta \cdot Q}{1 - \frac{1}{k} + \frac{1}{A_o}} \quad (2-11.41)$$

A parasitic pole also exists. The location of this pole is at $-\sigma$, where:

$$\sigma = \frac{m}{\delta R_1 R_2} \quad (2-11.42)$$

The normalized transmission function with the above element values becomes:

$$G(s) = \frac{E_{out}}{E_{in}} = \frac{\frac{H}{Q} s}{\left(s^2 + \frac{s}{Q} + 1 \right) \left(\frac{s}{\sigma} + 1 \right)} \quad (2-11.43)$$

The design of this filter type is somewhat cut and try if low sensitivities are to be achieved. The program is written to take the desired resonant frequency, the operational amplifier parameters, the capacitor ratio, one capacitor value, and the positive feedback ratio, and provides the remaining element values.

Because the resonator design exhibits a gain, H , at resonance, the input resistor, R_1 , may be split into two resistors to provide a Thevenin equivalent circuit with gain $H_{desired}/H = 1/H'$ and impedance R_1 . This equivalent circuit is shown in Fig. 2-11.2.

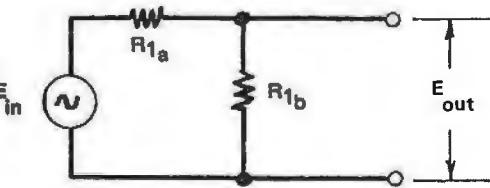


Figure 2-11.2 Equivalent input resistor network.

$$E_{out}/E_{in} = 1/H' = R_{1b}/(R_{1a} + R_{1b}) \quad (2-11.44)$$

$$R_{equiv} = (R_{1a} \cdot R_{1b})/(R_{1a} + R_{1b}) = R_1 \quad (2-11.45)$$

Equation (2-11.44) is solved for $R_{1a} + R_{1b}$, and substituted into Eq. (2-11.45) to yield an expression for R_{1a} :


$$R_{1a} = H' \cdot R_1 \quad (2-11.46)$$

Substituting Eq. (2-11.46) into Eq. (2-11.44) yields an expression for R_{1b} :

$$R_{1b} = R_{1a}/(H' - 1) \quad (2-11.47)$$

Equations (2-11.46) and (2-11.47) are used by the program to split the input resistor and provide the desired resonator gain at the resonant frequency.

User Instructions

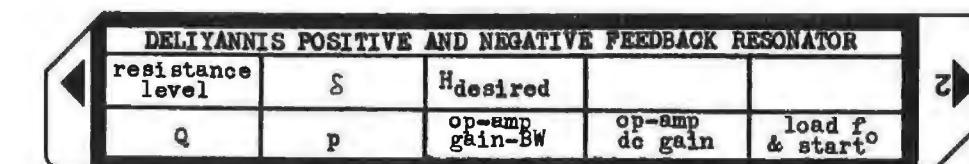

STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
1	Load both sides of program card			
2	Load Q, the quality factor	Q	A	
3	Load p, the positive feedback ratio ($p = 1/k$)	p	B	
4	Load R, the operating resistance level	R, Ω	f A	
5	Load S, the ratio of C_2 to C_1 (Eq. (2-10.27))	S	f B	
6	Load desired gain at resonance	$H_{desired}$	f C	
7	Load op-amp gain-bandwidth product	GBP, Hz	C	
8	Load op-amp dc gain	A_0	D	
9	Load resonant frequency desired and start	f_o, Hz		R_1 R_2 H σ R_B
note: Flag 3 is tested on all input routines to determine whether input or output of the respective parameter is desired. If an input key ("A" - "D" and "a" - "c") is keyed without numeric entry, or following the clear key (e), the presently stored parameter will be displayed.				
10	Go back and change any parameters in any order, and rerun program. The center frequency need not be reloaded unless it is being changed.			R_1 R_2 C_1 C_2 R_{1a} R_{1b} $S_{C_{1a}, R_{1a}, C_{1b}, R_{1b}}$ $S_{R_{1a}}^{\omega_n} - S_{R_{1b}}^{\omega_n}$ $S_{R_{1a}}^{\alpha} - S_{R_{1b}}^{\alpha}$ $S_{C_{1a}}^{\alpha} - S_{C_{1b}}^{\alpha}$ $S_{A_{1a}}^{\omega_n} - S_{A_{1b}}^{\omega_n}$

Example 2-11.1

A second order Deliyannis resonator is to be designed using a type 741 operational amplifier. The operational amplifier characteristics and resonator specifications are:

Center frequency:	1000 Hz
Q:	100
gain at resonance:	1.0
capacitor ratio:	1.0
p, positive fdbk ratio:	0.04
resistance level:	10000 Ω
op-amp gain-bandwidth:	500000 Hz
op-amp dc gain:	100000

Find the element values and calculate the sensitivities for this design. Investigate the effect of different values of positive feedback on the component value spread and sensitivities. The HP-97 printout for this problem is shown on the next page, and the schematic is shown in Fig. 2-11.3.

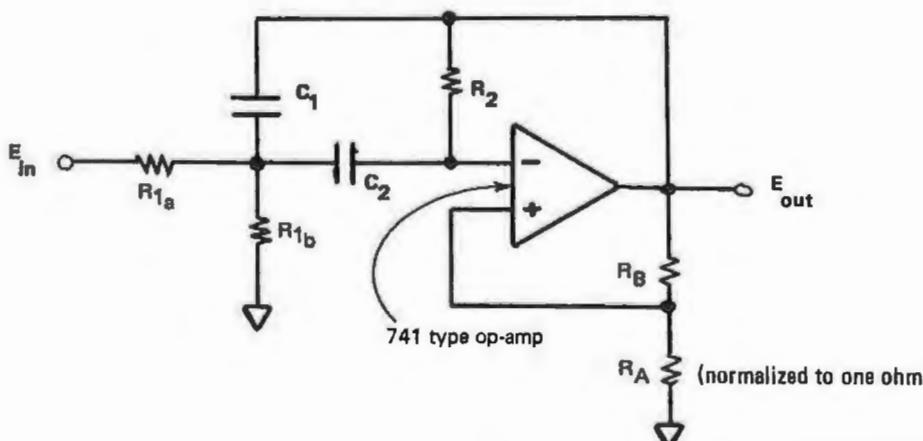


Figure 2-11.3 Deliyannis resonator schematic.

HP-97 printout for Example 2-11.1

100. GSBA load Q
 10000. GSBA load denormalization resistance level, R
 .04 GSBB load positive feedback ratio, p
 1. GSBC load capacitor ratio, S
 1. GSBD load gain desired at resonance, Hdesired
 500000. GSBC load op-amp GBP
 100000. GSBD load op-amp dc gain, A_o
 1000. GSBE load f_o and start

145.770-03 *** R₁
 6.75947+00 *** R₂
 -704.104+00 *** H
 487.151+00 *** S
 24.00000+00 *** R_B (R_A = 1) } normalized values
 (C₁ = 1)

10.00000+03 *** R₁
 463.707+03 *** R₂
 2.32001-09 *** C₁
 2.32001-09 *** C₂ } denormalized values

7.04104+06 *** R_{1A} Thevenin equivalent input resistor pair
 10.0142+03 *** R_{1B}
 -500.000-03 *** S_{R₁, R₂, C₁, C₂, R_B}
 28.3733+00 *** S_{R₁}, -S_{R₂}
 -28.8733+00 *** S_{R₁}, -S_{R₂}
 -14.1882+00 *** S_{C₁}, -S_{C₂}
 7.38889-03 *** S_{A/T}, -S_{A/T}

The following printouts have all parameters the same except the positive feedback ratio, p. Notice passive sensitivities increase and active decrease.

1.-09 GSBE p GSBE	.004 GSBE p GSBE	.4 GSBE p GSBE
3.79141-03 ***	46.3615-03 ***	577.077-03 ***
172.670+00 ***	20.6707+00 ***	1.71635+00 ***
-17.2668+03 ***	-2.07535+03 ***	-286.053+00 ***
763.761+00 ***	519.661+00 ***	302.893+00 ***
1.00000+09 ***	249.000+00 ***	1.50000+00 ***
10.00000+03 ***	10.00000+03 ***	10.00000+03 ***
455.423+06 ***	4.45860+06 ***	29.7421+03 ***
60.3422-12 ***	737.866-12 ***	9.18446-09 ***
60.3422-12 ***	737.866-12 ***	9.18446-09 ***
172.668+06 ***	20.7535+06 ***	2.86053+06 ***
10.00000+03 ***	10.00000+03 ***	10.0351+03 ***
-500.000-03 ***	-500.000-03 ***	-500.000-03 ***
21.3406-06 ***	8.48006+00 ***	114.973+00 ***
-500.021-03 ***	-8.98008+00 ***	-115.473+00 ***
-31.4320-03 ***	-4.24420+00 ***	-57.4880+00 ***
213.406-03 ***	21.2853-03 ***	4.79053-03 ***

Program Listing I

001 *LBLA	LOAD Q
002 1/X	
003 ST00	store d = 1/Q
004 GT00	
005 *LBLB	LOAD DENORMALIZATION
006 ST08	RESISTANCE LEVEL
007 GT00	
008 *LBLB	LOAD p
009 ST01	
010 GT00	
011 *LBLB	LOAD C1/C2 RATIO
012 ST02	
013 GT00	
014 *LBLC	LOAD OP-AMP GBP
015 ST03	
016 GT00	
017 *LBLC	LOAD H_desired
018 P±S	
019 ST00	
020 P±S	
021 GT00	
022 *LBLD	LOAD OP-AMP A _o
023 ST04	
024 *LBLD	clear flag 3 subroutine
025 CF3	
026 RTN	
027 *LBLE	LOAD f _o AND START ANALYSIS
028 F3?	store f _o if entered
029 ST05	from keyboard
030 SPC	
031 RCL3	
032 RCL5	$\gamma = \frac{A_o}{f_o} \rightarrow R_A$
033 ÷	
034 ST0A	
035 RCL4	
036 ÷	
037 RCLA	
038 RCL1	$\beta = \frac{\gamma}{A_o} - \frac{\gamma}{k} \rightarrow R_B$
039 x	
040 -	
041 ST0B	
042 RCLA	
043 +	$m = \gamma + \beta$
044 ST0C	
045 RCL2	
046 EEX	$\delta + 1 \rightarrow R_9$
047 +	
048 ST09	
049 x	$R_2 = \frac{m(\delta+1)R_1 - (dm-1)}{(R_1 - \beta)\delta}$
050 RCLC	
051 RCL0	$m-d \rightarrow R_E$
052 -	
053 ST0E	
054 x	
055 RCL9	$a_2 = (\delta+1)\{m(m-d)+1\} \rightarrow R_D$
REGISTERS	
⁰ d = $\frac{1}{Q}$	¹ p = $\frac{1}{K}$
² $\delta = \frac{C_2}{C_1}$	³ op-amp GBP
⁴ op-amp dc gain, A _o	⁵ f _o
⁶ H, or a_1/a_2	⁷ R ₂ δ, or A_1
⁸ resistance level	⁹ $\delta+1$, or $Q/\sqrt{45}$
S ₀ H_desired	S ₁
	S ₂
	S ₃
	S ₄
	S ₅
	S ₆
	S ₇
	S ₈
	S ₉
A γ	B β
C m or $\epsilon = \frac{1}{k-1}$	D a ₂ , or R ₁
	E m-d, or R ₂
	F dm-1, or -0.5

Program Listing II

056 +	111 ST07	166 RCL6	
057 ST00	112 EEX	167 EEX	$R_{1b} = \frac{R_{1a}}{\frac{H_{actual}}{H_{desired}} - 1}$
058 RCL2	113 RCL1	168 -	
059 RCLC	114 -	169 ÷	
060 x	115 RCL4	170 GSB9	
061 RCL9	$a_1 = \delta m - (\delta+1)\beta - (m-d)(dm-1)$	171 - $R_2 \cdot \delta \cdot Q$	
062 RCLB	116 1/X	172 5	-0.5 - R _I
063 x	117 +	173 CHS	
064 -	118 ÷	174 ST01	
065 RCLC	119 RCL0	175 PRTX	print: S _{0n} , C _n , R ₁ , R ₂
066 RCL0	120 -	176 RCLC	
067 x	121 ST06	177 RCLD	$H = \frac{R_2}{R_1} \rightarrow R_7$
068 EEX	122 CHS	178 ÷	
	123 PRTX	179 ST07	
	124 RCLC	180 RCL2	
	125 RCLD	181 x	
	126 ÷	182 JX	
	127 RCL7	183 RCL9	$S_{R_B}^Q = -S_{R_A}^Q = Q \frac{\sqrt{\mu \delta}}{k-1}$
	128 ÷	184 ÷	
	129 PRTX	185 ST09	
	130 RCL1	186 RCLC	
	131 1/X	187 x	
	132 EEX	188 PRTX	
	133 -	189 CHS	
	134 GSB9	190 RCL1	$S_{R_4}^Q = -S_{R_2}^Q = -\frac{1}{2} - Q \frac{\sqrt{\mu \delta}}{k-1}$
	135 1/X	191 +	
	136 ST0C	192 PRTX	
	137 RCL8	193 RCL7	
	recall and print	194 1/X	
	138 PRTX	195 RCLC	
	denormalized R ₁	196 -	
	139 RCLC	197 RCL9	$S_{C_1}^Q = -S_{C_2}^Q = -\frac{1}{2} + Q \frac{\sqrt{\mu \delta}}{k-1} \left(\frac{1}{\mu} - \frac{1}{k-1} \right)$
	140 x	198 x	
	141 RCLD	199 RCLI	
	142 ÷	200 +	
	143 PRTX	201 PRTX	
	144 RCL5	202 RCL9	
	calculate and print	203 RCL0	
	145 Pi	204 x	
	denormalized C ₁ :	205 RCLA	
	146 x	206 ENT↑	
	147 ENT↑	207 +	
	148 +	208 ÷	
	149 RCL8	209 RCLC	$S_{A_{fr}}^{\omega} = -S_{A_{fr}}^Q = \frac{\sqrt{\mu \delta}}{2} \cdot \frac{\omega_n \tau}{A_o} \cdot \left(\frac{k}{k-1} \right)^2$
	150 x	210 RCL1	
	151 RCLD	211 ÷	
	152 ÷	212 x ²	
	153 1/X	213 x	
	154 PRTX	214 *LBL9	print and space subroutine
	155 RCL2	215 PRTX	
	calculate and print	216 SPC	
	156 x	217 RTN	
	157 GSB9		
	denormalized C ₂		
	158 P±S		
	calculate Thevenin		
	159 RCL0		
	equivalent for R ₁ to provide		
	160 P±S		
	desired gain at resonance:		
	161 ST÷6		
	162 RCL6		
	163 RCL8		
	164 x	$R_{1a} = \frac{H_{actual}}{H_{desired}} \cdot R_1$	
	165 PRTX		

LABELS		FLAGS		SET STATUS	
A Load Q	B Load p	C Load GBP	D Load A _o	E Load f _o & Start	0
a Load R	b Load S	c Load H_desired	d	e	FLAGS ON OFF
0	1	2	3	4	TRIG 0 DEG 1 GRAD 2 RAD
5	6	7	8	9 Print & Space	DISP USER'S CHOICE FIX SCI ENG n
				3 Data entry	

PROGRAM 2-12 ELLIPTIC FILTER ORDER AND LOSS POLE LOCATIONS.

Program Description and Equations Used

This program finds the lowest elliptic (also called Cauer-Chebyshev) lowpass filter order that will meet the requirements for A_{max} , A_{min} , f_{max} , and f_{min} . These parameters are defined with the aid of Fig. 2-12.1.

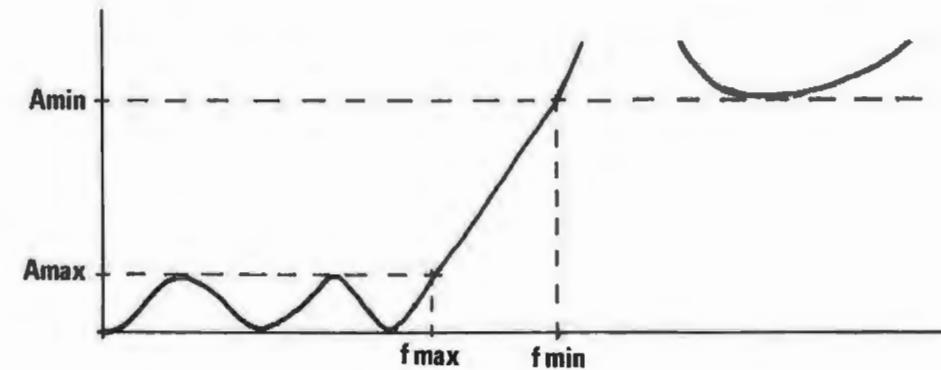


Figure 2-12.1 Elliptic filter loss function, where:

A_{max} : maximum passband ripple in dB

A_{min} : minimum stopband attenuation in dB

f_{max} : maximum passband frequency (passband edge)

f_{min} : minimum frequency where A_{min} is achieved.

The program also calculates the attenuation pole frequencies. From these frequencies the filter response at any frequency outside the passband may be determined by using the Z transformation. This transformation technique is described in the next program, and also in chapter 8 of Daniels' book [17]. The analog Z transformation should not be confused with the digital z transformation.

The elliptic filter response is not monotonic in the stopband as can be seen in Fig. 2-12.1. This stopband response is the characteristic difference between the Chebyshev and elliptic filter responses. Both filter types have equiripple behavior in the passband, but Chebyshev

(and Butterworth) filters have all attenuation poles located at infinite frequency, while elliptic filters have finite attenuation poles. Because of these finite attenuation poles, the elliptic filter has a sharper transition from passband to stopband for a given filter order.

The elliptic response also has its drawbacks. As the transition band becomes sharper (the filter more selective) the transfer function phase angle changes more rapidly with frequency, and so the group delay becomes peaked near the passband edge frequency. Uniform group delay is required for filters that must process pulses without exhibiting ringing amplitude responses; thus, the transmission function of the elliptic filter tends toward the optimum only from the point of view of the attenuation requirement.

If the LC filter is being designed as a basis for an active filter design such as the leapfrog topology, or an elliptic response is being contemplated for active simulation by cascaded active resonators, the elliptic filter transmission zero (attenuation pole) simulation will require a biquadratic resonator circuit. The designer should always compare the sensitivities of the elliptic active filter circuit versus the sensitivities of a higher order all-pole active design which meets the overall same specifications. In general, as the active resonator circuit becomes more complicated, or the operating gain-bandwidth requirements approach the op-amp gain-bandwidth, the circuit sensitivities become worse, and the final filter design may not meet the specification requirements when component drift due to temperature and aging is considered.

The following formulas are discussed in detail in the equation derivation section and the results brought forward. The loss function, L , is defined by Eq. (2-12.1) (refer to Fig. 2-12.1).

$$L^2 = \frac{10^{0.1} A_{\min} - 1}{10^{0.1} A_{\max} - 1} \quad (2-12.1)$$

Furthermore, x_L^{-1} is the ratio of the lowpass stopband edge frequency to the lowpass passband edge frequency (refer to Fig. 2-12.1):

$$x_L^{-1} = \frac{f_{\max}}{f_{\min}} \quad (2-12.2)$$

The minimum elliptic filter order that will meet the requirements for A_{\max} , A_{\min} , f_{\max} , and f_{\min} is calculated from Eq. (2-12.28).

$$n = \frac{K(x_L^{-1}) \cdot K'(L^{-1})}{K'(x_L^{-1}) \cdot K(L^{-1})} \quad (2-12.30)$$

where $K(\)$ is the complete elliptic integral of the first kind, and $K'(\)$ is the complementary complete elliptic integral of the first kind. These functions are defined by Eqs. (2-12.11) through (2-12.14) and are calculated by a truncated infinite series as given by Eqs. (2-12.18) through (2-12.21).

The loss poles of the elliptic filter transfer function are given by Eqs. (2-12.31) and (2-12.32).

$$x_v = \frac{x_L}{x_{zv}} \quad (2-12.31)$$

where

$$x_{zv} = \begin{cases} \operatorname{sn} \left\{ \frac{2v}{n} K(x_L^{-1}), x_L^{-1} \right\} & n \text{ odd} \\ \operatorname{sn} \left\{ \frac{2v-1}{n} K(x_L^{-1}), x_L^{-1} \right\} & n \text{ even} \end{cases} \quad (2-12.32)$$

The elliptic sine is evaluated by means of a Fourier series given by Eqs. (2-12.24) and (2-12.25).

The even ordered elliptic filters have a stopband loss that approaches a constant, finite value as the frequency approaches infinity, i.e., the even ordered elliptic filter does not have a loss pole at infinite frequency. The lossless LC synthesis of such a filter cannot be done without the use of mutual inductive coupling between the filter sections. On the other hand, active filter realizations can be done without the loss pole locations being a constraint.

A special form of the Möbius transformation (a bilinear change of variables) may be applied to the even ordered elliptic loss pole frequencies to move the highest frequency loss pole to infinity and thereby allow LC synthesis without mutual inductance. The even ordered elliptic filter element value tables in Zverev [58], already have this transformation applied, hence $x_L^{-1} = \sin \theta$ only for odd order filters (θ is the tabulated modular angle).

The general form of the Möbius transformation is:

$$s^2 = \left\{ \frac{\Omega_C^2 - \Omega_B^2}{\Omega_B^2 - \Omega_0^2} \Omega_B^2 \right\} \cdot \left\{ \frac{s^2 + \Omega_0^2}{s^2 + \Omega_C^2} \right\} \quad (2-12.3)$$

This transformation converts frequencies as follows:

- 1) $s = j\Omega_0$ to $s = 0$
- 2) $s = j\Omega_B$ to $s = j\Omega_B$ (no change in passband edge)
- 3) $s = j\Omega_C$ to $s = \infty$


It is not desired to transform the dc, or zero frequency, location in the lowpass filter, hence, $\Omega_0 = 0$; furthermore, the loss poles lie directly on the $j\omega$ axis so the transformation need only apply to $s = j\omega$, thus Eq. (2-12.3) becomes:

$$\omega^2 = (\Omega_C^2 - \Omega_B^2) \frac{\Omega^2}{\Omega_C^2 - \Omega^2} \quad (2-12.4)$$

The program calculates and prints (displays) the original even-ordered pole locations as calculated from Eq. (2-12.32) applies Eq. (2-12.4), and prints and stores the transformed pole locations. For odd-ordered filters, the program calculates, prints, and stores the finite loss pole locations from Eq. (2-12.32) without transformation. In both the even and odd cases, the loss pole frequencies are stored in normalized form ($\Omega=1$), but are denormalized for printout or display.

The normalized loss pole frequencies are used by the next program in this section to calculate the filter attenuation at any frequency within the passband or the stopband by using the Z transform.

User Instructions

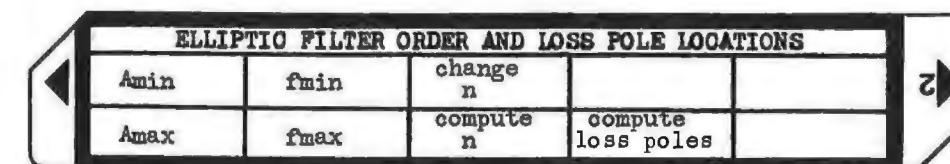

STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
1	Load both sides of magnetic card			
2	Load maximum passband ripple in dB	Amax	A	
3	Load minimum stopband loss in dB	Amin	f A	
4	Load passband cutoff frequency	fmax	B	
5	Load minimum stopband loss frequency	fmin	f B	
6	Calculate filter order to meet requirements	0		n n*
	<p>*The first n will be the result of the calculations and will generally not be an integer. The second n is the next highest integer, and is the stored value. Both values are given so the designer can get a feeling for the design margin. If the two values are close, the next higher filter order might be considered.</p> <p>If the program stops displaying "Error", the input data for Amax and Amin are too far apart (.005dB and 100dB for example) and calculations for $K(L^{-1})$ exceed the precision capability of the HP-97. The filter order may be obtained from the Kawakami CC nomograph [4], [5], and the program restarted with step 7. Step 8 will still run correctly.</p>			
7	To change filter order (integers only)	n	f 0	
8	To calculate loss poles (frequencies of maximum attenuation)	D	f ₁ f ₂ : f _{n/2} ** space f ₁ ' *** f ₂ ' : f _{(n-1)/2}	
	<p>**The number of loss poles will be the integral part of $n/2$, i.e., a fifth order filter will have two loss poles.</p> <p>***If n is even, the Möbius transformation is done to ensure a loss pole at infinity. The primed frequencies (f') are the Möbius transformed frequencies. The highest original loss frequency has been transformed to infinite frequency, and is not printed out, i.e., a sixth order filter only has two transformed loss frequencies printed out. The original frequency, $f_{n/2}$, is the transformed fmin frequency.</p>			

Example 2-12.1

Compute the filter order and loss pole locations for an elliptic filter to meet the following specifications.

A_{max} = .28 dB ($\rho = 25\%$, A_{max} = $-10 \log(1-\rho^2)$)
A_{min} = 63 dB
f_{max} = 1000 Hz
f_{min} = 2000 Hz

HP-97 input/output

```
.28 G5Br load Amax
63.00 G5Ba load Amin
1000.00 G5Bf load fmax
2000.00 G5Ft load fmin
G5BC calculate minimum filter order
4.97 *** actual calculated filter order, n
5.00 *** nearest integral value for n to meet specs
G5BD calculate loss pole locations
3250.804880 ***
2089.246505 ***
```

These results may be checked by comparing them to the 30° modular angle filter design shown in the "Catalog of Normalized Lowpass Models" on page 220 of Zverev [58].

Example 2-12.2

Compute the minimum filter order and loss pole locations for an elliptic filter which meets the following specifications:

A_{max} = .1773 dB ($\rho = 20\%$, A_{max} = $-10 \log(1-\rho^2)$)
A_{min} = 78 dB
f_{max} = 1000 Hz
f_{min} = 2000 Hz

```
.1773 G5BA load Amax
78.00 G5Ba load Amin
1000.00 G5Bf load fmax
2000.00 G5Bb load fmin
G5BC calculate minimum filter order
5.96 *** actual calculated filter order, n
6.00 *** nearest integral n to meet specs
G5BD calculate loss pole locations:
7235.802719 ***
2732.053611 ***
2061.105330 ***
2922.132266 ***
2129.548771 *** } untransformed loss poles
} also represents transformed fmin
} transformed loss pole locations
```

Derivation of Equations Used

The elliptic response is governed by the Chebyshev rational function, which is a ratio of polynomials. The development of the Chebyshev rational function in terms of elliptic functions is beyond the scope of this discussion. This development is discussed in Chapter 5 of Daniels' book [17]. A few highlights of the Chebyshev rational function and elliptic functions will be used to show the development of the equations used by this program.

The Chebyshev response becomes the elliptic response when the Chebyshev polynomial, T_n(x), is replaced by the Chebyshev rational function, R_n(x,L), in the filter transfer function (Feldtkeller equation).

$$|H(j\omega)|^2 = 1 + |K(j\omega)|^2 \quad (2-12.5)$$

$$\text{for Chebyshev response, } |K(j\omega)|^2 = \epsilon^2 \cdot T_n(x) \quad (2-12.6)$$

$$\text{for elliptic response, } |K(j\omega)|^2 = \epsilon^2 \cdot R_n^2(x, L) \quad (2-12.7)$$

Hence, the elliptic attenuation function is:

$$A(\omega)_{dB} = 20 \cdot \log |H(j\omega)| \quad (2-12.8)$$

$$= 10 \cdot \log \left\{ 1 + \epsilon^2 \cdot R_n^2(x, L) \right\};$$

$$\text{where } x = \omega/\omega_{max} = f/f_{max} \quad (2-12.9)$$

The Chebyshev rational function, $R_n(x, L)$, has the following properties (also see Fig. 2-11.2).

- 1) R_n is odd when n is odd and vice versa.
- 2) All the zeros of R_n lie within the interval $-1 < x < 1$, while all the poles lie outside this interval.
- 3) $R_n(x, L)$, like $T_n(x)$, oscillates between ± 1 for $-1 < x < 1$. This interval defines the passband.
- 4) $R_n(1, L) = +1$ (passband edge).
- 5) $|R_n| > L$ (oscillates outside of L) for $|x| > x_L$, where x_L is defined as the first value of x where $R_n(x, L) = L$, and hence, A_{min} is achieved (defines stopband).

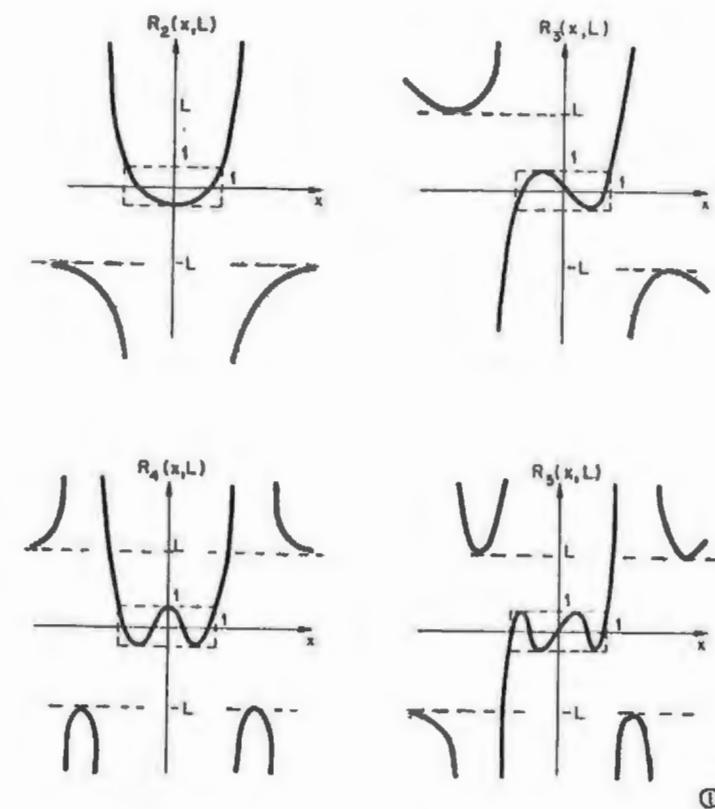


Figure 2-11.2 Chebyshev rational functions for $n = 2$ to 5 .

By using Eq. (2-12.8) and condition 5, an expression for L can be found in terms of the filter parameters A_{min} and ϵ .

$$L^2 = \frac{10^{0.1A_{min}} - 1}{\epsilon^2} \quad (2-12.10)$$

Since $A(\omega) = A_{max}$ at the passband edge, f_{max} , condition 4 and Eq. (2-12.8) can be used to find an expression for ϵ .

$$\epsilon^2 = 10^{0.1A_{max}} - 1 \quad (2-12.11)$$

Not surprisingly, this is the same expression as is used in the Chebyshev case, and for the same reasons (condition 3).

By putting Eqs. (2-12.10) and (2-12.11) together, the expression for L is obtained:

$$L^2 = \frac{10^{0.1A_{min}} - 1}{10^{0.1A_{max}} - 1} \quad (2-12.12)$$

ELLIPTIC FUNCTIONS

There are three kinds of elliptic integrals (see Abramowitz and Stegun, [1]). Only the elliptic integral of the first kind is needed for elliptic filters. The elliptic integral of the first kind is defined by the following equation:

$$u(\phi, k) = \int_0^\phi \frac{dx}{(1 - k^2 \cdot \sin^2 x)^{\frac{1}{2}}} \quad (2-12.13)$$

The two variables, ϕ and k , are called the amplitude and modulus respectively. Some elliptic function tables [1], and some elliptic filter tables [58], are parametric in terms of the modular angle, θ , instead of the modulus, k . The modular angle is defined by:

$$k = \sin \theta \quad (2-12.14)$$

The complete elliptic integral of the first kind results when ϕ , the limit of integration, is taken as $\pi/2$ radians. This value, $u(\pi/2, k)$ is defined as $K(k)$.

Figure 2-12.3 shows $u(\phi, k)$ parametric with the modular angle, θ . $u(\phi, k)$ has been normalized with respect to $K(k)$. Figure 2-12.4 shows the complete elliptic integral, $K(k)$ by itself.

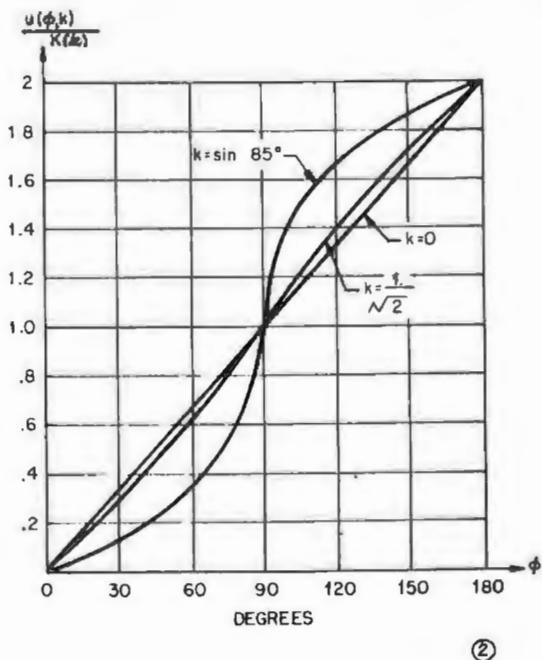


Figure 2-12.3 Elliptic integral.

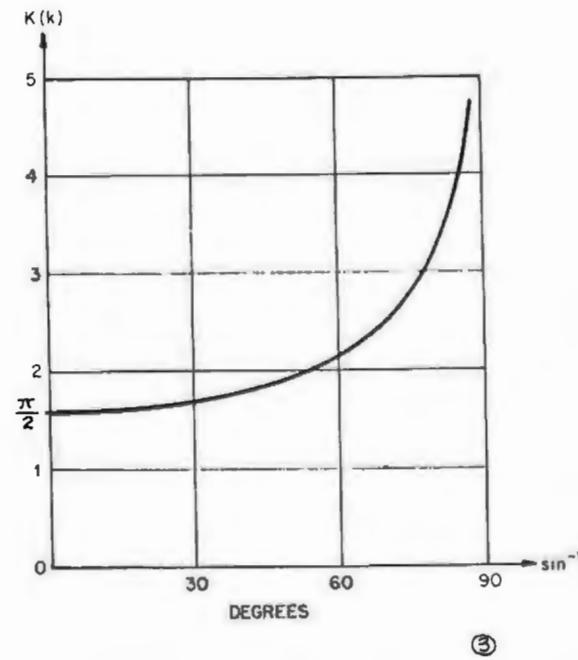


Figure 2-12.4 Complete elliptic integral.

The complementary modulus is defined in terms of the modulus, k , or the modular angle, θ , as:

$$k' = (1 - k^2)^{\frac{1}{2}} = \cos \theta \quad (2-12.13)$$

The complementary complete elliptic integral is defined in terms of the complementary modulus:

$$K'(k) = K(k') = u(\pi/2, k') \quad (2-12.16)$$

The elliptic sine is an elliptic function, and is defined in a somewhat reverse manner from the elliptic integral:

$$u(\phi, k) = \int_0^\phi (1 - k^2 \cdot \sin^2(x))^{-\frac{1}{2}} dx \quad (2-12.17)$$

$$\text{sn}(u, k) = \sin \phi \quad (\text{elliptic sine}) \quad (2-12.18)$$

$$\text{cn}(u, k) = \phi \quad (\text{elliptic cosine}) \quad (2-12.19)$$

The definition is "reverse" since the limit of integration, ϕ , must be found to yield the "input," $u(\phi, k)$ and k . Figure 2-12.5 shows the elliptic sine and elliptic cosine functions.

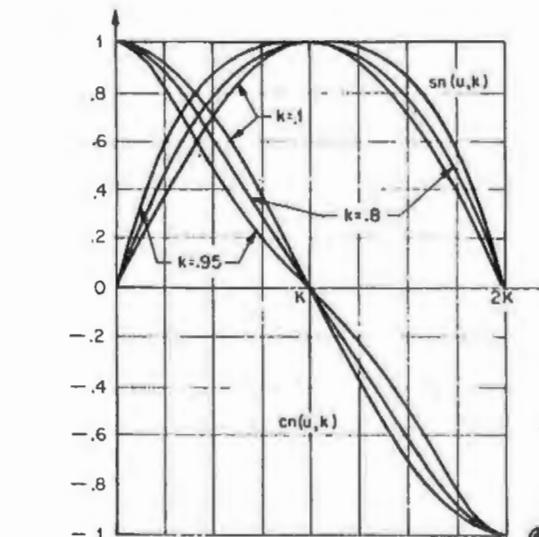


Figure 2-12.5 Elliptic sine and cosine functions.

CREDITS: 1, 2, 3, & 4: Reproduced from "Approximation Methods for Electronic Filter Design," by R.W. Daniels, copyright, © 1974, by Bell Telephone Labs, Inc., used with permission of McGraw-Hill Book Company, Inc., New York, N.Y.

Luckily, there are rapidly converging series expansions for both $K(k)$ and $\text{sn}(u,k)$, [12], and the programmable calculator can be used to perform the iterative calculations. These series expansions are:

Complete elliptic integral

$$K(k) = \frac{\pi}{2} \prod_{m=0}^{\infty} (1 + k_{m+1}) ; \quad (2-12.20)$$

where

$$k_{m+1} = (1 - k_m')/(1 + k_m') \quad (2-12.21)$$

$$k_m' = (1 - k_m^2)^{\frac{1}{2}}, \text{ (complementary modulus)} \quad (2-12.22)$$

$$k_0 \equiv k \quad (2-12.23)$$

The terms of the infinite product expansion rapidly converge toward unity. The series is terminated when $k_m < 10^{-9}$. This accuracy is generally achieved in four iterations or less.

Elliptic sine

The elliptic sine is calculated from the following Fourier series:

$$s_n(u,k) = \frac{2\pi}{K(k) \cdot k} \sum_{m=0}^{\infty} \left\{ \frac{q^{m+\frac{1}{2}}}{1 - q^{2m+1}} \right\} \cdot \sin \left((2m+1) \frac{\pi u}{2K(k)} \right) \quad (2-12.24)$$

where q is Jacobi's nome (also called modular elliptic function):

$$q = e^{-\frac{\pi K'(k)}{K(k)}} \quad (2-12.25)$$

The series is terminated when $(q^{m+\frac{1}{2}})/(1 - q^{2m+1}) < 10^{-9}$

This particular algorithm for the elliptic sine is only one of many which can be used to calculate the function. For sharp cutoff filters, the convergence is slow; however, of all the algorithms researched by the author, the Fourier series method could be coded to fit into the HP-97 program memory and still leave enough room for the coding needed for the rest of the program.

If more registers were available, the descending Landen transformation method could have been combined with the calculation of $K(k)$ to simultaneously yield $K(k)$ and $\text{sn}(u,k)$ as outlined in Skwirzynski and Zdunek's article [46]. If more program space were available, the

elliptic sine could be calculated from the ratios of sums of hyperbolic sines and cosines as recommended by Orchard [41]. Also, if more program space were available, the calculation of the transmission zeros could be done directly from adaptations of the elliptic sine as represented by infinite products of hyperbolic tangents given by Amstutz [2] or as interpreted by Geffe [27]. Darlington's algorithm [18] is used in Program 2-15, and is a concise method for calculating the transmission zeros and poles when the filter order is odd.

Filter order calculation: Just as the trigonometric sine is periodic, so is the elliptic sine, although the elliptic sine is doubly periodic with a real period of $4 \cdot K(k)$, and an imaginary period of $2 \cdot K'(k)$. The Chebyshev rational function, $R(x,L)$ may be expressed in terms of the complete elliptic integral and the elliptic sine. By relating the real and imaginary periods of the elliptic sine function to the real and imaginary periods of the Chebyshev rational function, two equations in two unknowns, C and n , may be formulated. These equations are:

Chebyshev rational function and elliptic functions

$$R_n(x,L) = \begin{cases} \text{sn} \left(uL/C, L^{-1} \right) & n \text{ odd} \\ \text{sn} \left(uL/C + (-1)^{\frac{n}{2}} \cdot K(L^{-1}), L^{-1} \right) & n \text{ even} \end{cases} \quad (2-12.26)$$

where C is a constant, and u is the solution to:

$$x = \text{sn}(x_L^{-1} \cdot u, x_L^{-1}) \quad (2-12.27)$$

Simultaneous equations in C and n:

$$x_L^{-1} \cdot K(x_L^{-1}) = n \cdot C \cdot L^{-1} \cdot K(L^{-1}) \quad (\text{real periods}) \quad (2-12.28)$$

$$x_L^{-1} \cdot K'(x_L^{-1}) = C \cdot L^{-1} \cdot K'(L^{-1}) \quad (\text{imaginary periods}) \quad (2-12.29)$$

Eliminating C by simultaneous solution of Eqs. (2-12.28) and (2-12.29) results in the following expression for the filter order, n :

$$n = \frac{K(x_L^{-1}) \cdot K'(L^{-1})}{K'(x_L^{-1}) \cdot K(L^{-1})} \quad (2-12.30)$$

where x_L^{-1} is defined by Eq.(2-12.2) and L^{-1} by Eq. (2-12.18):

$$x_L^{-1} = (f_{\max})/(f_{\min})$$

$$L^{-1} = \left\{ \frac{10^{0.1A_{\max}} - 1}{10^{0.1A_{\min}} - 1} \right\}^{\frac{1}{2}}$$

The loss poles of the elliptic filter transfer function, Eq. (2-12.5), are given by:

$$x_v = \frac{x_L}{x_{zv}} \quad (2-12.31)$$

where:

$$x_{zv} = \begin{cases} \operatorname{sn}\left(\frac{2v}{n} K(x_L^{-1}), x_L^{-1}\right) & n \text{ odd} \\ \operatorname{sn}\left(\frac{(2v-1)}{n} K(x_L^{-1}), x_L^{-1}\right) & n \text{ even} \end{cases} \quad v = 1, 2, \dots, n \quad (2-12.32)$$

In Eq. (2-12.22) k becomes x_1^{-1} for the above elliptic sine computation, hence:

$$x_v = \frac{K(x_L^{-1})}{2\pi\Sigma} \quad (2-12.33)$$

where Σ is the term summation in Eq. (2-12.24).

Program Listing I

REGISTERS									
⁰ Amax	¹ Amin	² fmax	³ fmin	⁴ n	⁵ scratch	⁶ index, v	⁷ $K(x_L^{-1})$	⁸ $K'(x_L^{-1})$	⁹ x_L^{-1}
$S_0(\pi v)/n$	$S^1 2m + 1$	$S^2 \frac{q^{m+1/2}}{1-q^{2m+1}}$	$S^3 \Sigma$	S^4	S^5	S^6	S^7	S^8	S^9
loss pole storage registers									
A	B	C	D	E	F	G	H	I	J
← loss pole storage →		10^{-10}	NINF (used by next program)	scratchpad	storage reg. index				

```

001 *LBLA LOAD Amax (passband ripple)
002 ST00
003 RTN
004 *LBLB LOAD Amin (min stopband loss)
005 ST01
006 RTN
007 *LBLB LOAD fmax
008 ST02
009 RTN
010 *LBL6 LOAD fmin
011 ST03
012 RTN
013 *LBLC calculate filter order, n
014 RCL2 compute and store
015 RCL3  $\div x_L^{-1} = \frac{f_{\max}}{f_{\min}} \rightarrow R9$ 
016  $\div$ 
017 ST09
018 GSB5 compute and store
019 ST04  $K(x_L^{-1}) \rightarrow R4 \rightarrow R7$ 
020 ST07
021 RCL9 compute and store
022 GSB4  $K'(x_L^{-1}) \rightarrow R8$ 
023 ST08
024 ST=4 continue n calculation
025 RCL0 compute and store
026 GSB7
027 RCL1
028 GSB7  $L^{-1} = \sqrt{\frac{10^{0.1A_{\max}} - 1}{10^{0.1A_{\min}} - 1}} \rightarrow R_E$ 
029  $\div$ 
030 JX
031 ST0E
032 X? generate error message if
033 RCLC  $L^{-1}$  is smaller than  $10^{-5}$ 
034 X>Y?
035 GT09 call to unused label: "ERROR"
036 RCL0 compute:  $K'(L^{-1})$ 
037 GSB4
038 STx4 continue n calculation
039 RCL0 compute:  $K(L^{-1})$ 
040 GSB5
041 ST=4 finish n computation
042 RCL4 recall n
043 SPC
044 PRTX print non-integral n
045 EEX convert n to next highest
046 STOD integer, print and store
047 +
048 INT
049 PRTX
050 *LBLc LOAD ALTERNATE n VALUE
051 ST04
052 GT03
053 *LBLD CALCULATE LOSS POLES
054 DSP9 set display format
055 1 initialize index register
056 3

```

Program Listing II

```

113 GT01
114 RCL3 recall summation & compute sn:
115 P2S
116 ENT↑
117 +  $\frac{\operatorname{sn}(x, x_L^{-1})}{x_L} = \frac{2\pi \sum}{K(x_L^{-1})}$ 
118 PI
119 X
120 RCL7
121 =
122 1/X compute and store normalized
123 ISZI loss pole locations
124 STO1
125 RCL2 denormalize and print loss
126 X pole locations
127 PRTX
128 EEX increment register index
129 ST+6
130 RCL6 test for loop exit:
131 ENT↑
132 + loop if n > 2v
133 RCL4
134 X>Y?
135 GT00
136 SPC
137 F0? jump if n is odd
138 GT03
139 1 initialize index register
140 4 and store highest register
141 XZI number for later exit test
142 STOE
143 RCLI recall  $\Omega_c$ 
144 X2 store  $\Omega_c^2$ 
145 ST05
146 *LBL2 Möbius transformation loop
147 ISZI calculate Möbius transform
148 RCLI for even ordered lowpass:
149 X2
150 RCL5
151 LSTX
152 X2
153 -  $\omega^2 \cdot (\Omega_c^2 - 1) \frac{\Omega^2}{\Omega_c^2 - \Omega^2}$ 
154 RCL5
155 EEX
156 -
157 X
158 ABS
159 JX
160 DSZI
161 STO1 store normalized & xmed
162 ISZI loss pole location
163 RCL2 denormalize and print loss
164 X pole location
165 PRTX
166 RCLI
167 RCL6
168 RCL6
169 X>Y? test for loop exit
170 GT02
171 DSZI restore highest reg. index
172 2 NINF - 2 for transformed
173 ST00 even ordered filters
174 *LBL3
175 DSP2 set original display format
176 SPC
177 RTN return control to keyboard
178 *LBL4 compute K(k)
179 X2
180 CHS form complementary modulus:
181 EEX
182 +
183 JX
184 *LBL5 compute K'(k)
185 ST05 store argument, k
186 PI initialize product register
187 2
188 +
189 ST06
190 *LBL6 complete elliptic integral
191 EEX
192 RCL5
193 X2
194 -  $K(x) = \frac{\pi}{2} \prod_{m=0}^{\infty} (1 + k_m)$ 
195 JX
196 EEX
197 XZI
198 -  $k_{m-1} = \frac{1 - k_m}{1 + k_m}$ 
199 LSTX
200 EEX
201 +
202 -
203 ST05
204 EEX
205 +
206 STX6
207 RCL5
208 EEX
209 CHS test for loop exit:
210 1 loop if  $k_m > 10^{-10}$ 
211 0
212 STOC
213 X>Y?
214 GT06
215 RCL6 recall K(k)
216 RTN return to main program
217 *LBL7 subroutine to compute:
218 EEX
219 1  $10^{0.1A} - 1$ 
220 -
221 10X
222 EEX
223 -
224 RTN

```

LABELS					FLAGS			SET STATUS		
^A load Amax	^B load fmax	^C calc n	^D calc loss poles	^E	0	n odd	FLAGS	TRIG	DISP	
^a load Amin	^b load fmin	^c enter n	^d	^e	1		ON OFF	DEG GRAD RAD	FIX SCI ENG	
⁰ sn(u,k)	¹ sn loop start	² Möbius transform	³ jump dest	⁴ K(k)	2		■ ■ ■	■ ■ ■	■ ■ ■	
⁵ K'(k)	⁶ K'(k) loop	⁷ conversions	⁸	⁹	3		3			

PROGRAM 2-13 RESPONSE OF A FILTER WITH CHEBYSHEV PASSBAND AND ARBITRARY STOPBAND LOSS POLES.

Program Description and Equations Used

This program will calculate the passband and stopband attenuation of lowpass, highpass, bandpass, and bandstop filters having Chebyshev (equi-ripple) passbands and arbitrary stopband losspole locations. The elliptic filter is a special case of this filter class in that the loss pole locations are chosen to provide equi-ripple stopband behavior.

Bandpass and bandstop filters are assumed to be the classic transformations of the lowpass structure, i.e., equal numbers of attenuation poles on either side of the passband, and geometrical symmetry of those poles about the center frequency. The program is designed to take either stored normalized lowpass loss pole frequencies provided by Program 2-12, or to accept normalized lowpass loss pole frequencies, number of poles at infinite frequency, and passband ripple as provided by the user.

This program is adapted from an unpublished HP-67/97 elliptic stopband attenuation program written by Philip R. Geffe. The basis of the program is the Z transformation, and the associated loss function, L(Z). This function allows the calculation of the stopband attenuation of equi-ripple passband elliptic filters from a knowledge of the loss pole frequencies only [17]. The transformed variable, Z, is defined by:

$$Z^2 = (s^2 + \omega_B^2)/(s^2 + \omega_A^2) \quad (2-13.1)$$

This function spreads the passband ($s = j\omega_A$ to $j\omega_B$) over the entire imaginary Z axis, and spreads the stopbands along the real Z axis. Although use of the Z transform allows greater numerical accuracy due to the spreading out of the passband poles, the prime reason for its use in this program is the mathematical expressions for elliptic filters are simpler in the Z domain than in the s domain.

Given a filter with equiripple passband extending from ω_A to ω_B , having NZ attenuation poles at the origin, N finite loss poles, and NINF

attenuation poles at infinite frequency, the loss function in terms of Z is:

$$L(Z) = \left\{ \frac{Z + \omega_B/\omega_A}{Z - \omega_B/\omega_A} \right\}^{\frac{NZ}{2}} \left\{ \frac{Z + 1}{Z - 1} \right\}^{\frac{NINF}{2}} \prod_{i=1}^N \frac{Z + z_i}{Z - z_i} \quad (2-13.2)$$

If $L(Z)$ represents a normalized lowpass filter, then $\omega_A = 0$, $\omega_B = 1$, and $NZ = 0$. Letting $s = j\Omega$, Z and $L(Z)$ become:

$$Z = (1 - 1/\Omega^2)^{\frac{1}{2}} \quad (2-13.3)$$

$$L(Z) = \left\{ \frac{Z + 1}{Z - 1} \right\}^{\frac{NINF}{2}} \prod_{i=1}^N \frac{Z + z_i}{Z - z_i} \quad (2-13.4)$$

The attenuation function, $A(\Omega)$, is defined in terms of the loss function, $L(Z)$, as follows:

$$A(\Omega) = 10 \cdot \log \left\{ 1 + \frac{\epsilon^2}{4} \left(L(Z) + \frac{(-1)^{NINF}}{L(Z)} \right)^2 \right\} \quad (2-13.5)$$

$$\epsilon^2 = 10^{0.1A_{max}} - 1 \quad (2-13.6)$$

In the stopband, the attenuation function may be simplified:

$$A(\Omega) = 10 \log \left[1 + \frac{\epsilon^2}{4} \left\{ |L(Z)| + 1/|L(Z)| \right\}^2 \right] \quad (2-13.7)$$

The filter passband ripple (A_{max}) may sometimes be expressed in terms of a reflection coefficient, ρ . The relationship between these quantities is:

$$A_{max} = -10 \log (1 - \rho^2) \quad (2-13.8)$$

Within the normalized lowpass passband ($\Omega < 1$), Z becomes purely imaginary. Equation (2-13.4) may be rewritten in exponential form to eliminate the need for complex arithmetic:

$$L(Z) = e^{jB} \quad (2-13.9)$$

where

$$B = \frac{NINF}{2} \tan^{-1} \left\{ \frac{-2|z|}{|z|^2 - 1} \right\} + \sum_{i=1}^N \tan^{-1} \left\{ \frac{-2|z|z_i}{|z|^2 - z_i^2} \right\} \quad (2-13.10)$$

substituting Eq. (2-13.9) into (2-13.5) yields:

$$A(\Omega) = 10 \log (1 + \epsilon^2 \cos^2 B) \text{ for } NINF \text{ even,} \quad (2-13.11)$$

and

$$A(\Omega) = 10 \log (1 + \epsilon^2 \sin^2 B) \text{ for } NINF \text{ odd.} \quad (2-13.12)$$

The program uses Eqs. (2-13.3) through (2-13.12) to find the filter loss at any frequency. Two ancillary relations are used to convert unnormalized bandpass or bandstop frequencies to the normalized lowpass frequency, Ω . Lowpass and highpass filters are only special cases of bandpass and bandstop filters respectively, in that the center frequency is zero. These two ancillary equations are:

Bandpass to normalized lowpass

$$\Omega_{BP} = \frac{1}{BW} \left\{ f_o - \frac{f_o^2}{f} \right\} \quad (2-13.13)$$

where

BW = bandwidth

f_o = center frequency


Bandstop to normalized lowpass

$$\Omega_{BS} = 1/\Omega_{BP} \quad (2-13.14)$$

Equation (2-13.4) will predict the stopband attenuation for even ordered elliptic filters of Cauer types A and B (the Möbius transformation - see previous program for description). The type A, even-ordered filter has no attenuation poles at infinite frequency, and can only be realized with mutual inductive coupling between filter sections, while the Möbius transformed pole locations (type B) can be realized with a ladder structure containing only L's and C's. The even ordered type B ladder structure possesses a double pole of attenuation at infinite frequency.

Equation (2-13.4) will not work with the pole locations resulting from a transformation to Cauer type C filters (equal resistive termination for even-ordered elliptic filters), i.e., one must use types A and B only. See Saal and Ulbrich [45] for details.

User Instructions

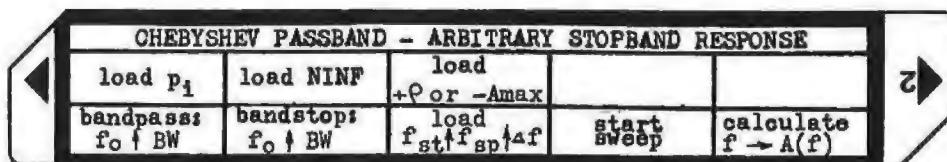

STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
1	Load both sides of magnetic card			
2	If this program is being used concurrently with Program 2-11, the loss poles, Amax, and NINF are already stored by that program. Go to step 6 and continue.			
3	Load normalized loss pole frequencies	setup p_1 p_2 \vdots p_n	$f \uparrow A$ R/S R/S : R/S	
4	Load number of loss poles at infinite frequency	NINF	$f \uparrow B$	
5	Load either the reflection coefficient or the passband ripple in dB (related quantities). The program differentiates the quantities by sign. Both quantities are normally positive	Reflection coefficient or Passband ripple in dB (note sign)	$f \uparrow C$ $f \uparrow C$	Amax
6	Select filter type: Bandpass or Lowpass: The lowpass filter is a special case of the bandpass filter in that the center frequency is zero. The bandwidth is the lowpass cutoff frequency.	f_o BW	ENT↑ A	
	Bandstop or Highpass: The highpass filter is a special case of the bandstop filter in that the center frequency is zero. The bandwidth is the highpass cutoff frequency.	f_o BW	ENT↑ B	

User Instructions



STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
7	Load denormalized stopband frequency and calculate stopband attenuation	f	E	$A(f)$
8	If a sweep of frequencies is desired: a) Load sweep parameters The frequency increment is either an additive delta, or a multiplicative delta depending upon lin/log sweep. If linear sweep is desired, then the increment should be entered as a negative quantity, i.e., for 100 Hz linear steps, the increment should be entered as -100. Whether the increment is linear or logarithmic, the sweep will be always in the direction of increasing frequency.	f_{start} f_{stop} f_{incr}	ENT↑ ENT↑ C	
b) Start sweep		D	f $A(f)$ space f $A(f)$:	
9	Go back to any step desired, modify, and rerun program			

Example 2-13.1

An elliptic bandpass filter is required to pass frequencies between 5 kHz and 15 kHz with 0.0436 dB ripple or less (10% reflection coefficient), and reject frequencies lying outside a 4.1 kHz to 19 kHz band by at least 60 dB. Find the minimum filter order that will satisfy these requirements, and predict the stopband response.

The center frequency is the geometric mean of the upper and lower passband edge frequencies. Likewise, the stopband edge frequencies must be geometrically symmetrical about the center frequency. In this example, the above frequencies do not satisfy this requirement, hence, the narrowest stopband with geometric symmetry must be defined. The filter center frequency is calculated from the passband edge frequencies:

$$f_o = (5000 \cdot 15000)^{1/2} = 8660.25 \text{ Hz}$$

The narrowest stopband may be found by calculating the geometrical mapping frequencies to the given stopband frequencies, and taking the narrowest set:

$$f_u = f_o^2 / 4100 = 18292.68 \text{ Hz}$$

$$f_L = f_o^2 / 19000 = 3947.37 \text{ Hz}$$

The narrowest stopband is 4100 Hz to 18292.68 Hz for a stopband width of 14192.68 Hz.

The stopband and passband data are loaded into Program 2-12 to find the minimum filter order and loss pole locations. Because bandpass data was loaded, the loss pole frequencies that are output represent loss pole bandwidths, or the separation of loss pole frequencies in the upper and lower stopbands that are geometrically related to the filter center frequency. To convert these bandwidths into loss pole frequencies, the subprogram contained in Program 2-1 can be used. These equivalent bandpass loss pole frequencies are not necessary for proper operation of this program, but are calculated for information only. They can also be useful when tuning the final filter. All normalized loss pole information is automatically stored by Program 2-12 for use by this program.

Example 2-13.1 continued

Load Program 2-12 and calculate filter order and loss poles.
 .0436 GSBA load Amax
 60.00 GSBe load Amin
 10000.00 GSBE load fmax (passband bandwidth)
 14192.68 GSBD load fmin (stopband minimum bandwidth)

GSBC calculate minimum filter order

6.72 ***
 7.00 *** minimum integral filter order, n

GSBD calculate loss pole bandwidths

28.69564+03 *** loss pole bandwidth #1
 17.08915+03 *** loss pole bandwidth #2
 14.44925+03 *** loss pole bandwidth #3

Load Program 2-1 to calculate loss pole locations from loss pole bandwidths.

28695.64 ENT† load loss pole bandwidth #1
 8660.25 GSBD load fo
 31106.69 *** upper BP loss pole frequency #1
 2411.05 *** lower BP loss pole frequency #1

17089.19 ENT† load loss pole bandwidth #2
 8660.25 GSBD load fo
 20710.53 *** upper BP loss pole frequency #2
 3621.34 *** lower BP loss pole frequency #2

14449.25 ENT† load loss pole bandwidth #3
 8660.25 GSBD load fo
 18502.71 *** upper BP loss pole frequency #3
 4053.46 *** lower BP loss pole frequency #3

Load this program (Program 2-13) and calculate filter response.

8660.25 ENT† load fo
 10000.00 GSBA load passband width and select bandpass
 2000.00 ENT† load f-start
 5000.00 ENT† load f-stop
 -200.00 GSBC load f-increment (a negative value means linear sweep increments)
 GSBD start sweep:
 the output is on the next page.

(sweep step size changes were made between output segments)

PROGRAM OUTPUT FOR EXAMPLE 2-13.1					
LOWER STOPBAND		PASSBAND		UPPER STOPBAND	
2000.00	f	5000.0000	10000.0000	f	15000.00
68.02	A(f) dB	0.0436	0.0434	A(f)	0.04
2200.00		5500.0000	10500.0000	16000.00	31000.00
73.03		0.0020	0.0342	12.98	100.57
2400.00		6000.0000	11000.0000	17000.00	32000.00
98.12		0.0389	0.0115	31.72	82.55
2600.00		6500.0000	11500.0000	18000.00	33000.00
73.25		0.0002	0.0000	52.97	76.47
2800.00		7000.0000	12000.0000	19000.00	34000.00
67.19		0.0248	0.0144	64.35	73.25
3000.00		7500.0000	12500.0000	20000.00	35000.00
64.45		0.0434	0.0389	68.65	71.15
3200.00		8000.0000	13000.0000	21000.00	36000.00
63.90		0.0234	0.0385	77.55	69.63
3400.00		8500.0000	13500.0000	22000.00	37000.00
66.45		0.0016	0.0082	66.70	68.49
3600.00		9000.0000	14000.0000	23000.00	38000.00
84.71		0.0065	0.0098	64.24	67.60
3800.00		9500.0000	14500.0000	24000.00	39000.00
66.03		0.0293	0.0430	63.83	66.89
4000.00		15000.0000		25000.00	40000.00
67.53		0.0438		64.45	66.31
4200.00				26000.00	41000.00
49.19				65.75	65.84
4400.00	NOTE:	The display was changed manually to DSP4 for the passband printout, then changed back to DSP2 for the upper stopband output.		27000.00	42000.00
32.55				67.65	65.45
4600.00				28000.00	43000.00
18.89				70.25	65.13
4800.00				29000.00	44000.00
5.63				73.91	64.66
5000.00					45000.00
0.04					64.64

Example 2-13.2

Compute the minimum stopband attenuation of an eleventh order, 20% reflection coefficient, 75 degree modular angle elliptic filter (see p. 326 of Saal and Ulbrich [45]).

Load Program 2-12 and calculate filter order and loss pole locations.

```

1.00 ENT†
.20 X²
-
L05
10.00 ×
CHS
.1772677 *** } calculate Amax = 10 log (1 - ρ²)

GSEH load Amax
100.00 GSEo load dummy Amin large enough to cause "error" halt
1.00 GSEb load normalized passband edge
75.00 D=R
SIN
1/V } calculate stopband edge from modular angle
1.035276 *** } GSEb load normalized stopband edge
GSEC start filter order calculation (computes K(k))
ERROR program halt since L⁻¹ is too small
ii. GSEc load desired filter order

GSBD output loss pole locations and store for next program
2.232241138 ***
1.744326302 ***
1.126566299 ***
1.051117341 ***
1.037513514 ***


```

Load this program (Program 2-13) and calculate filter response.

```

0.000 ENT†
1.000 GSEH load filter center frequency (lowpass)
1.000 GSBD load bandwidth (normalized for this example)
1.000 GSBE load number of poles at infinity
75.000 SIN } calculate normalized stopband edge frequency
1/V
GSBE calculate stopband loss at this frequency
60.806 *** minimum stopband loss in dB (Amin defined at fmin)

```

Program Listing I

001 *LBL0 - SETUP LOSS POLE ENTRY
 002 1
 003 3 initialize index register
 004 ST01
 005 SF2 indicate initialization reqd
 006 *LBL0
 007 R/S enter normalized loss pole
 008 ISZI
 009 ST01
 010 GT00
 011 *LBLb LOAD NINF, the number of
 012 ST0D lowpass loss poles at
 013 GT06 infinite frequency
 014 *LBLc LOAD ω_0 or A_{max}
 015 X<0? if negative entry, jump
 016 GT01
 017 X² calculate:
 018 CHS
 019 GSB7 $A_{max} = |10 \log(1 - \rho^2)|$
 020 *LBL1
 021 ABS store $|A_{max}|$
 022 ST00
 023 GT06 goto space and return
 024 *LBLA LOAD f_0 & BW for bandpass
 025 CF0 indicate bandpass
 026 GT01
 027 *LBLB LOAD f_0 & BW for bandstop
 028 SF0 indicate bandstop
 029 *LBL1 store BW (bandwidth)
 030 ST09
 031 R↓
 032 X² form and store f_0^2
 033 ST08
 034 GT06 goto space and return
 035 *LBLC LOAD f-start, f-stop, Δf
 036 P/S store f-increment (Δf)
 037 ST01
 038 R↓ store f-stop
 039 ST02
 040 R↓ store f-start
 041 ST00
 042 P/S restore register order
 043 GT06 goto space and return
 044 *LBLD START SWEEP
 045 P/S
 046 RCL0 recall and print
 047 P/S present frequency
 048 PRTX
 049 GSBE calculate and print $A(f)$
 050 P/S recall frequency increment
 051 RCL1
 052 X<0?
 053 ST-0 if increment negative,
 054 X<0? use additive delta
 055 GT01
 056 STX0 if plus, use product delta

REGISTERS

0 Amax	1 $\epsilon^2/4$	2	3	4	5 L	6 scratch	7 "13"	8 f_0^2	9 BW
Sopresent freq	S1 freq	S2 stop freq	S3	S4	S5	S6	S7	S8	S9
loss pole storage registers									
A loss pole storage		B		C	10 ⁻⁹	D NINF	E I_{max}	F storage register index	

Program Listing II

169 EEX
 170 $\rightarrow R$ form sin β , and cos β
 171 F1? recall sin $\beta \rightarrow Rx$ if NINF odd
 172 X² Y
 173 ENT prepare to double Rx
 174 *LBL5 Output routine; form
 $\epsilon^2/4 (L+1/L)^2$ if stopband
 175 +
 176 X²
 177 RCL1 $\epsilon \sin \beta$ if passband
 178 X $\cos \beta$
 179 GSB7 calculate and print
 180 RND 10 log(1 + Rx)
 181 PRTX
 182 *LBL6 space and return subroutine
 183 SPC
 184 RTN
 185 *LBL7 subroutine to calculate:
 186 EEX
 187 + 10 log(1 + (-))
 188 LOG
 189 EEX
 190 1
 191 X
 192 RTN
 193 *LBL8 initialization routine
 194 RCLI store highest loss pole
 195 ST0E register number
 196 RCL0
 197 EEX calculate and store:
 198 1
 199 \div $\frac{\epsilon^2}{4} = 10^{0.1A_{max}} - 1$
 200 10^x
 201 EEX 4
 202 -
 203 4
 204 \div
 205 ST01
 206 1 store index register
 207 3 initialization, and
 208 ST07 initialize index register
 209 ST01
 210 *LBL9 loss pole Z transform loop
 211 ISZI increment index register
 212 EEX calculate and store:
 213 RCLI
 214 X² $Z_i = (1 - 1/(p_i)^2)^{1/2}$
 215 1/X where p_i are the normalized
 216 loss pole frequencies
 217 X
 218 ST01
 219 RCLI test for loop exit
 220 RCLE
 221 X#Y?
 222 GT09
 223 RTN return to main program

LABELS

A BANDPASS	B BANDSTOP	C f _{start} f _{stop}	D START SWEEP	E f → A(f)	F bandstop	G FLAGS	H SET STATUS	
for BW	for BW	load	SWEEP	e	0 bandstop	FLAGS	TRIG	DISP
a losspole entry	b load	c load	d	e	1 NINF odd	0 ON OFF	DEG ■	FIX ■
freq	S1 freq	S2 stop freq	S3	S4	S5	1 ■	GRAD ■	SCI ■
freq	inor	freq	S3	S4	S5	2 ■	RAD ■	ENG n. 2
loss pole storage registers								
5 output routine		6 space & return		7 A(f)	8 init	9 losspole xfms	3 passband	

**PROGRAM 2-14 POLE AND ZERO LOCATIONS OF A FILTER WITH CHEBYSHEV
PASSBAND AND ARBITRARY STOPBAND LOSS POLE LOCATIONS.**

Program Description and Equations Used

This program calculates the complex zero locations of the filter transfer function, $H(s) = E_{in}/E_{out}$, from the loss pole frequencies (frequencies of infinite attenuation). The zero locations are also called the natural modes of $H(s)$. The pole locations of $H(s)$, are the loss pole frequencies and lie on the $j\omega$ axis. The transmission function, $T(s)$, is the reciprocal of the filter transfer function, and may be more familiar to some readers. When active elliptic filters are being designed [35], one approach is to divide the transmission function into bi-quadratic factors with each factor (second order pole pair, and second order zero pair) being synthesized with a separate active network [38].

The loss pole frequencies can be supplied by the user in the case of arbitrary stopband, equiripple passband filters, or can be generated by Program 2-12 for elliptic filters (equiripple stopband and passband).

This program works in the Z-domain to spread out the pole and zero frequencies, and enhance the numerical accuracy of the final output. The s-domain frequencies are Z transformed using Eq. (2-14.1), which is the normalized lowpass form of the more generalized Z transform.

$$Z^2 = 1 + \frac{1}{s^2} \Big|_{s=j\omega} = 1 - \frac{1}{\omega^2} \quad (2-14.1)$$

The filter transfer function is a rational function, i.e., it is a ratio of polynomials:

$$H(s) = \frac{e(s)}{q(s)} \quad (2-14.2)$$

This transfer function is related to the filter characteristic function, $K(s)$, by the Feldtkeller equation:

$$H(s)H(-s) = 1 + K(s)K(-s) \quad (2-14.3)$$

where the characteristic function has been defined in terms of the Chebyshev rational function, $R(x, L)$, by Eq. (2-12.3), and also is a ratio of polynomials:

$$K(s) = \frac{f(s)}{q(s)} \quad (2-14.4)$$

Expanding the Feldtkeller equation to remove the denominator polynomial, $q(s)$, yields:

$$e(s)e(-s) = q(s)q(-s) + f(s)f(-s) \quad (2-14.5)$$

If the normalized lowpass Z transformation of these s-domain polynomials are defined by:

$$F(Z) \Leftrightarrow f(s)/s^m \quad | \quad (2-14.6)$$

$$Q(Z) \Leftrightarrow q(s)/s^m \quad | \quad (2-14.7)$$

where

$$Z_i^2 = 1 + \left(\frac{\omega_i}{s}\right)^2 \quad (2-14.8)$$

$$N_{\text{INF}} = \text{number of attenuation poles at } \infty \quad (2-14.9)$$

$$N = \text{number of finite loss pole freqs} \quad (2-14.10)$$

then the Z transform equivalent of Eq. (2-14.5) becomes:

$$E(Z)E^*(Z) = Q^2(Z) + F^2(Z) \quad (2-14.11)$$

where

$$E(Z) \Leftrightarrow e(s)/s^m \quad (2-14.11a)$$

$$E^*(Z) \Leftrightarrow e(-s)/s^m \quad (2-14.11b)$$

The derivation of $Q^2(Z)$ and $F^2(Z)$ in terms of the Z transformed loss pole frequencies, Z_i , is done later and the results brought forward:

$$Q^2(Z) = (1-Z^2)^{N_{\text{INF}}} \prod_{i=1}^N (z^2 - Z_i^2)^2 \quad (2-14.12)$$

$$F^2(Z) = \epsilon^2 (EVA(Z))^2 \quad (2-14.13)$$

$$A(Z) = (Z+1)^{N_{\text{INF}}} \prod_{i=1}^N (Z + Z_i)^2 \quad (2-14.14)$$

The program Z transforms the loss pole frequencies using Eq. (2-14.1) then forms $E(Z)E^*(Z)$ using Eqs. (2-14.11), (2-14.12), (2-14.13), and (2-14.14). The roots of $E(Z)E^*(Z)$ are found using the secant iteration method (described later), and exist as quads, i.e.:

$$(Z+\sigma+j\omega)(Z+\sigma-j\omega)(Z-\sigma+j\omega)(Z-\sigma-j\omega) = Z^4 + pZ^2 + q \quad (2-14.15)$$


Equation (2-14.1) may be used in reverse to convert Eq. (2-14.15) to the s-domain equivalent. The right half s plane (RHP) poles are assigned to $e(-s)$, and the LHP poles assigned to $e(s)$. These LHP poles represent the natural modes of the filter, and may be defined by a natural frequency, ω_n , and a quality factor, Q:

$$\omega_n = (1+p+q)^{\frac{1}{2}} \quad (2-14.16)$$

$$Q = \left[2 \left\{ 1 - (1 + \frac{p}{2})(1 + p + q) \right\} \right]^{\frac{1}{2}} \quad (2-14.17)$$

The natural frequency and Q represent the program output.

User Instructions

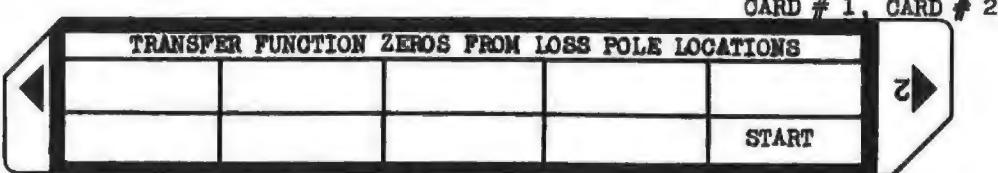

STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
	NOTE: This program takes loss pole frequencies stored in registers S4 through S8. Program 2-11 automatically stores the loss pole frequencies in these registers. If the loss pole frequencies are provided by the user, they should be loaded before proceeding.			
1	Load both sides of program card one			
2	Start program execution		E	flashing display
3	Insert second card into card reader, this card will be read by the program at the appropriate time. If the card is not inserted, the display will flash when the second card is to be read.			
4	Read both sides of second program card. The program execution will automatically resume. If the first program is halted (R/S key) when the display flashes, the second program execution may be resumed by depressing key "E" after the second card loading.			ω_{n_N} Q_N space $\omega_{n_{N-1}}$ Q_{N-1} ⋮ ω_{n_1} Q_1 space σ_o (if odd)

Example 2-14.1

Find the natural modes for the elliptic filter given in Example 2-12.2.

Load Program 2-11 and calculate loss pole frequencies.

1.00 ENT1
.20 X2
-
LOG
16.00 x
CHS
DSP6
DSP6
0.177288 ***
DSP2
GSBA

} convert 20% reflection coefficient into passband ripple in dB using:

$$Ap_{dB} = -10\log(1-\rho^2)$$

ApdB, passband ripple in dB

78.00 GSBD
1.00 GSBB
2.00 GSBB
GSBC
load stopband attenuation reqd, AsdB
load normalized cutoff frequency
load normalized minimum stopband frequency
calculate minimum filter order

5.90 ***
6.00 ***
calculated filter order
nearest integral filter order

GSBD
7.235803+00 ***
2.732051+00 ***
2.061105+00 ***
} untransformed even order
loss pole frequencies

2.922133+00 ***
2.129549+00 ***
} Möbius transformed loss pole frequencies

Load this program (Program 2-14) and calculate the natural modes.

GSBE start E(Z)E*(Z) calculation

0.83278696 *** ω_{n_1}
1.57099957 *** Q_1
1.03809259 *** ω_{n_2}
5.89989189 *** Q_2
0.50679327 *** ω_{n_3}
0.62665541 *** Q_3
} complex zero locations describing natural modes

The complex zero locations may be converted from the ω_n and Q description to real and imaginary parts to enable checking results against elliptic filter tables (see p. 248 of Zverev [58]). Equations (2-9.1), (2-9.2), and (2-9.3) are used for the conversion.

1.57059957 ENT†	load Q_1 and calculate θ_1
+ i/X COS-†	
71.44174416 ***	θ_1 (degrees)
.83278696 →R	load ω_{n1} and calculate real and imag parts
0.26505003 ***	σ_1
X#Y	
0.78948249 ***	ω_1
5.89989185 ENT†	load Q_2 and calculate θ_2
+ 1/X COS-†	
85.13850531 ***	θ_2 (degrees)
1.03805259 →R	load ω_{n2} and calculate real and imag parts
0.08797556 ***	σ_2
X#Y	
1.03435603 ***	ω_2
.62665941 ENT†	load Q_3 and calculate θ_3
+ 1/X COS-†	
37.07171237 ***	θ_3 (degrees)
.50079327 →R	load ω_{n3} and calculate real and imag parts
0.39957373 ***	σ_3
X#Y	
0.30188530 ***	ω_3

Derivation of Equations Used

The characteristic function, $K(s)$, is a ratio of polynomials as indicated by Eqs. (2-14.4) and (2-12.3). The denominator of this function is already known in terms of the loss pole frequencies. In low-pass form, this polynomial is:

$$q(s) = \prod_{i=1}^N (s^2 + \omega_i^2) \quad (2-14.18)$$

$H(s)$, the filter transfer function, is described in terms of the polynomials of the characteristic function by Eqs. (2-14.2) and (2-14.5). Since $H(s)$ describes a realizable transfer function, the zeros of $H(s)$ must lie in the LHP. With this condition in mind, the LHP zeros of $e(s)$ $e(-s)$ are assigned to $e(s)$ and the RHP zeros assigned to $e(-s)$. This root splitting brings us to the concept of a quad. Assume that $e(s)$ is represented by complex conjugate root pairs and a real root if $e(s)$ is odd, i.e.,

$$e(s) = (s + \sigma_0) \prod_{i=1}^N \{ s^2 + s(2\sigma_i) + \sigma_i^2 + \omega_i^2 \} \quad (2-14.19)$$

Then the right half s-plane roots are represented by $e(-s)$:

$$e(-s) = (-s + \sigma_0) \prod_{i=1}^N \{ s^2 - s(2\sigma_i) + \sigma_i^2 + \omega_i^2 \} \quad (2-14.20)$$

hence:

$$e(s) e(-s) = (-s^2 + \sigma_0^2) \prod_{i=1}^N \{ s^4 + s^2[2(\omega_i^2 - \sigma_i^2) + (\omega_i^2 + \sigma_i^2)^2] \} \quad (2-14.21)$$

This concept is illustrated in Fig. 2-14.1.

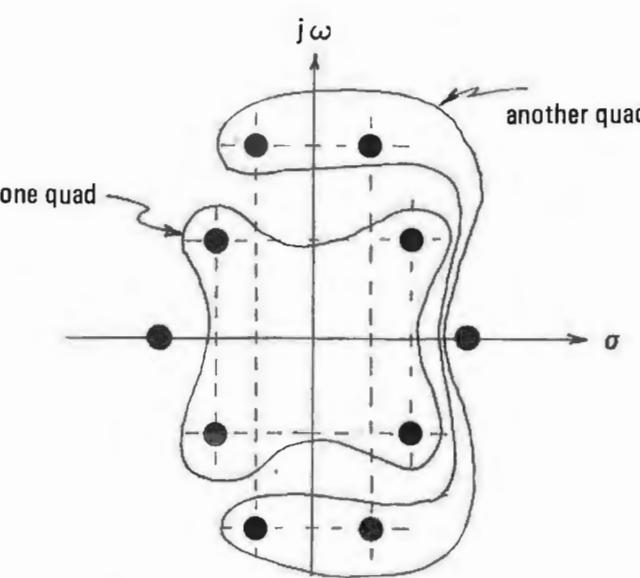


Figure 2-14.1 Concept of a quad.

The importance of this concept is once one root of $e(s) e(-s)$ is found, three other roots of the quad are also defined, and may be removed to reduce the order of $e(s) e(-s)$ by four.

The Characteristic Function in Terms of the Transformed Variable

The actual finding of the polynomials of $H(s)$ is done in the Z -plane rather than the s -plane for two reasons: 1) The solution is numerically more accurate because the roots are spread out and the small difference between big numbers problem is much reduced. 2) The expressions for $F^2(Z)$ and $Q^2(Z)$ are much simpler in terms of the transformed loss pole frequencies than are $f^2(s)$ and $q^2(s)$ in terms of the actual loss pole frequencies, ω_i . These transformations are defined as follows:

$$F(Z) \Leftrightarrow \frac{f(s)}{(s^2 + \omega_a^2)^{m/2}} \quad (2-14.22)$$

$$Q(Z) \Leftrightarrow \frac{q(s)}{(s^2 + \omega_a^2)^{m/2}} \quad (2-14.23)$$

where

$$Z^2 = \frac{s^2 + \omega_b^2}{s^2 + \omega_a^2} \quad (2-14.24)$$

and

$$m = NZERO + NINF + N \quad (2-14.25)$$

$$NZERO = \text{number of attenuation poles at dc} \quad (\text{equals zero for lowpass filters}) \quad (2-14.26)$$

$$NINF = \text{number of attenuation poles at infinity} \quad (2-14.9)$$

$$N = \text{number of finite loss pole frequencies} \quad (2-14.10)$$

In the normalized lowpass case, the lower bandedge transformation frequency, ω_a , is dc ($\omega_a = 0$), and the upper bandedge transformation frequency, ω_b , is unity. Under these conditions the Z transformation becomes:

$$F(Z) \Leftrightarrow \frac{f(s)}{s^m} \quad (2-14.6)$$

$$Q(Z) \Leftrightarrow \frac{q(s)}{s^m} \quad (2-14.7)$$

with

$$Z^2 = 1 + 1/s^2, \text{ or for } s = j\omega, Z^2 = 1 - 1/\omega^2$$

The lowpass form of $q(s)$ is given by Eq. (2-14.18):

$$q(s) = \prod_{i=1}^N (s^2 + \omega_i^2)$$

The Z transformed equivalent is:

$$Q(Z) \Leftrightarrow \frac{1}{s^m} \prod_{i=1}^N (s^2 + \omega_i^2) \quad (2-14.27)$$

$$= \frac{1}{s^{NINF}} \prod_{i=1}^N \left(\frac{s^2 + \omega_i^2}{s^2} \right) \quad (2-14.28)$$

The filter poles can be found from the zeros of the attenuation function, Eq. (2-13.5), i.e.,

$$1 + \frac{\epsilon^2}{4} \left\{ L(z) + \frac{(-1)^{N_{\text{INF}}}}{L(z)} \right\}^2 = 0 \quad (2-14.29)$$

where $L(z)$ is defined by Eq. (2-13.4):

$$L(z) = \left\{ \frac{z+1}{z-1} \right\}^{\frac{N_{\text{INF}}}{2}} \cdot \prod_{i=1}^N \frac{z+z_i}{z-z_i} \quad (2-13.4)$$

then $Q(z)$, as defined by Eq. (2-14.28), is the common denominator for Eq. (2-14.29). The quantity inside the brackets of Eq. (2-14.29) can be written in terms of $Q(z)$ and $A(z)$ (Eq. (2-14.14)) as follows:

$$L(z) + \frac{(-1)^{N_{\text{INF}}}}{L(z)} = \frac{A(z) + (-1)^{N_{\text{INF}}} \cdot A(-z)}{Q(z)} \quad (2-14.30)$$

Fortunately, the sign of $(-1)^{N_{\text{INF}}}$ causes the numerator to be an even polynomial in Z as is required for the resulting polynomials of the Chebyshev rational function to be Hurwitz.

Thus, the equation whose zeros are to be found is:

$$1 + \frac{\epsilon^2}{4} \left\{ \frac{A(z) + (-1)^{N_{\text{INF}}} \cdot A(-z)}{Q(z)} \right\}^2 = 0 \quad (2-14.31)$$

Because of the even numerator polynomial, Eq. (2-14.31) becomes:

$$1 + \frac{\epsilon^2}{4} \left\{ \frac{2 \cdot \text{Ev } A(z)}{Q(z)} \right\}^2 = 0 \quad (2-14.32)$$

Cancelling out constants and placing the entire expression over a common denominator yields:

$$Q^2(z) + \epsilon^2 \{ \text{Ev } A(z) \}^2 = 0 \quad (2-14.33)$$

Substituting $F(z)$ from Eq. (2-14.13) results the desired expression for the transfer function zeros:

$$Q^2(z) + F^2(z) = 0 \quad (2-14.34)$$

Secant iteration method

The secant iterative method finds the values for the variable, x , where the function $f(x) = 0$ (zeros of x). It is similar to the

Newton-Raphson method except the derivative of the function is numerically approximated from the present and past values of $f(x)$:

$$x_{i+1} = x_i - f(x_i) \left\{ \frac{x_i - x_{i-1}}{f(x_i) - f(x_{i-1})} \right\} \quad (2-14.35)$$

where x_i is the present estimate for the variable.

The iteration is continued until the correction term magnitude becomes smaller than a given error radius. For this program, that error radius is chosen to be 10^{-9} .

Two values for x are needed to start the secant iteration, a past value and a present value. In this program, the past value is chosen as 0 and the present value as 1460° . As the iteration starts, the method may not converge, but may get sent far away from the desired solution. This can happen if the present and past estimates lie on opposite sides of a saddle (see Fig. 2-14.3). To help force convergence, the magnitude of the correction radius is limited to 0.1. When the iteration starts, the estimates have a random nature, but can't get far away from the origin. As a zero is approached, the method rapidly converges.

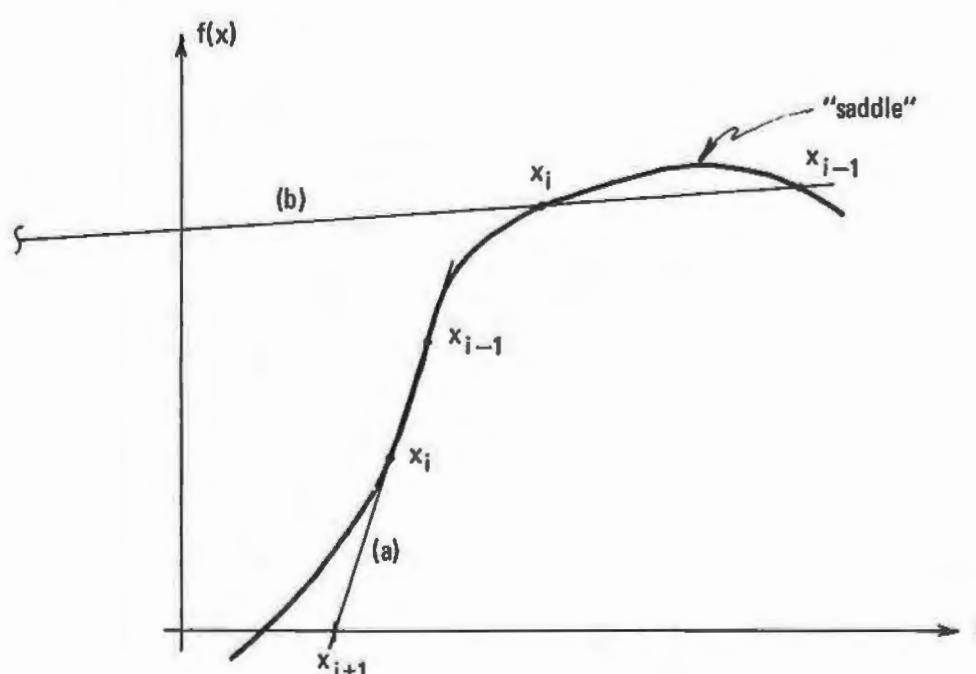


Figure 2-14.3 Secant method, two cases a) normal convergence, and b) divergence caused by the presence of a "saddle" in the function.

Figure 2-14.3 shows a two dimensional representation of the method, but in the present instance, the application is three dimensional because of the complex nature of the variable. As each complex zero is found, three others are defined automatically because of the quadrangle symmetry (quads) in the zeros of the filter transfer function (see Fig. 2-14.1), thus the order of the equation may be reduced by four through polynomial division. If the filter order is odd, a real zero exists in the transfer function. After all quads have been removed from the transfer function, the remainder will be the real zero. This technique is used herein, zeros are removed from $E(Z)E^*(Z)$ until a second order polynomial or less remains. If the filter order is even, no remainder exists, but if the filter order is odd, the second order remainder represents the LHP and RHP parts of the real zero. The RHP zero is discarded since it belongs to $H(-s)$, and the LHP zero location is transformed back to the s-domain for output.

2-14, CARD 1

Program Listing I

ALGORITHM TO FORM $E(Z)E^*(Z)$
FROM $F^2(Z) + Q^2(Z)$

001 *LBL E START	057 RCLP
002 RCLI store index number of	058 X#Y? test for loop exit
003 STOB highest register w/ coeffs	059 GT01
004 RCLB	060 CLX start A(Z) calculation
005 EEX	061 STOA
006 1 calculate ϵ^2	062 J initialize index register
007 \div	063 STOI
008 10 ^X $\epsilon^2 = 10^{0.1\text{dB}} - 1$	064 P±S place $Q^2(Z)$ in secondary regs
009 EEX	065 EEX initialize polynomial
010 -	066 STOB product registers
011 RCLD	067 RCLB
012 + store NINF + ϵ^2	068 EEX reduce highest loss pole
013 STOD	069 1 register number by 10 to
014 1	070 - reflect P±S of registers
015 3 initialize index register	071 STOB
016 STOI	072 *LBL2 A(Z) calculation loop start
017 *LBL0 Z transform loss pole freqs	073 ISZI
018 ISZI	074 RCLI $A(Z) = (Z+1)^{NINF} \prod_{i=1}^N (Z + Z_i)^2$
019 EEX	075 JX
020 RCLI	076 STOC $Z_i \rightarrow R_c$
021 X ² $Z_1^2 = 1 - 1/\omega_i^2$	077 GSB9 multiply existing polynomial
022 1/X	078 GSB9 product by $(Z + Z_1)^2$
023 -	079 RCLI
024 STOI	080 RCLB
025 RCLI	081 X#Y? test for loop exit
026 RCLB	082 GT02
027 X#Y? test for loop exit	083 EEX
028 GT00	084 STOC setup to form $(Z + 1)^{NINF}$
029 RCLD	085 GSB9 multiply existing polynomial
030 INT set flag 2 if NINF = 2	086 F0?
031 2	087 GSB9 by $(Z + 1)^{NINF}$, (NINF = 1 or 2)
032 CF0	088 EEX calculate highest register
033 X=Y?	089 RCLB number containing polynomial
034 SF0	090 RCLB coefficients:
035 EEX start $Q^2(Z)$ calculation	091 +
036 STOA	092 5
037 CHS	093 + 2B + 10 + F0 \rightarrow RB
038 STOC form and store $(1 - Z^2)^{NINF}$	094 F0?
039 F0?	095 +
040 CHS for NINF = 1 or 2	096 STOB
041 STOI	097 STOI initialize index register
042 CHS	098 *LBL3
043 STOB	099 ISZI clear registers not contain-
044 F0?	100 CLX ing polynomial coefficients
045 GSB9	101 STOI
046 1	102 P±S
047 3 initialize index register	103 STOI
048 STOI	104 P±S
049 *LBL1 $Q^2(Z)$ calculation loop	105 RCLI
050 ISZI	106 1
051 RCLI	107 9 test for loop exit
052 CHS	108 X#Y?
053 STOC $Q^2(Z) = (1 - Z^2)^{NINF} \prod_{i=1}^N (Z^2 - Z_i^2)$	109 GT03
054 GSB9	110 RCLB form $(E_v A(Z))^2$:
055 GSB9 $-Z_i^2 \rightarrow R_c$	111 RCL2
056 RCLI	112 X
REGISTERS	
Q ₀ , A ₀ , A ₀	Q ₁ , A ₁ , A ₂
S ₀ Q ₀ , F ₀	S ₁ Q ₁ , F ₁
Q ₂ , A ₂ , A ₄	Q ₃ , A ₃ , A ₆
S ₂ Q ₂ , F ₂	S ₃ Q ₃ , F ₃
Q ₄ , A ₄ , A ₈	Q ₅ , A ₅ , A ₁₀
S ₄ Q ₄ , F ₄ , Z ₁	S ₅ Q ₅ , F ₅ , Z ₂
Q ₆ , A ₆ , A ₁₂	Q ₆ , F ₆ , Z ₃
S ₆ Q ₆ , F ₆ , Z ₄	S ₇ Q ₇ , F ₇ , Z ₄
Q ₇ , A ₇ , A ₁₄	Q ₈ , A ₈ , A ₁₆
S ₇ Q ₇ , F ₇ , Z ₄	S ₈ Q ₈ , F ₈
Q ₉ , A ₉ , A ₁₈	S ₉ Q ₉ , F ₉
A Q & F index	
B highest reg. number used	
C Z_i^2	
D $\epsilon^2 + NINF$	
E Z index	
F index	

Program Listing II

```

113 ST01 A2' = 2A0A2
114 ST+1
115 RCL0
116 RCL6 (NOTE: the primed coeffs
117 x represent the coeffs of
118 RCL2 A2(Z). After this part
119 RCL4 of the program is done
120 x the coefficients of
121 + A2(Z) have replaced the
122 ST03 coeffs of A(Z).)
123 ST+3 A6' = 2(A0A6 + A4A6)
124 RCL2
125 RCL8
126 x
127 RCL4 A10' = 2(A2A8 + A4A6)
128 RCL6
129 x
130 +
131 ST05
132 ST+5
133 RCL6
134 RCL8
135 x A14' = 2A6A8
136 ST07
137 ST+7
138 6 initialize index register
139 ST01
140 RCL8 A16' = A8
141 STx8
142 RCL4
143 x A12' = A62 + 2A4A8
144 GSB7
145 RCL2
146 x
147 RCL8
148 JX A8' = A42 + 2(A2A6 + A0A8)
149 RCL0
150 x
151 +
152 GSB7
153 RCL0
154 x A4' = A22 + 2A0A4
155 GSB7
156 RCL0 A0' = A0
157 STx0
158 RCLD recall ε2
159 FRC
160 STx0
161 STx1 form F2(Z) = ε2(EV(A(Z)))2
162 STx2
163 STx3
164 STx4
165 STx5
166 STx6
167 STx7
168 STx8

169 9
170 ST01 initialize index register
171 *LBL4
172 DSZI
173 SF2 form E(Z)E*(Z)
174 RCL1
175 P±S E(Z)E*(Z) = Q2(Z) + F2(Z)
176 ST+i
177 P±S
178 F2?
179 GT04 test for loop exit
180 *LBL5
181 PSE wait loop for 2nd card read
182 GT05
183 *LBL7 A2(Z) calculation subr
184 RCL1 forms:
185 STxI
186 R↓ R(i)2 + 2(Rx), and returns
187 ST+i
188 ST+i R(i) → Rx
189 R↑
190 DSZI
191 DSZI
192 RTN
193 RTN

194 *LBL9 polynomial multiplication
195 SF2 flag 2 indicates 1st time
196 RCL1 initialize index register
197 X±I with Q or F index
198 STOE save existing index
199 *LBL8 polynomial mult loop
200 RCL1
201 ISZI
202 RCLC ak+1 = C · ak+1 + ak
203 F2? C = 0 for k = n
204 CLX
205 STxI
206 R↓
207 ST+i
208 CF1 decrement I register, and
209 DSZI set flag 1 if I ≠ 0
210 SF1
211 DSZI decrement I register
212 F1? test for loop exit
213 GT09
214 RCLC finish poly multiplication
215 STx0 a0 = C · a0
216 RCL1 restore pre-existing index
217 ST01 increment F or Q index
218 RCL1
219 EEX
220 +
221 ST0A
222 RTN return to main program

```

LABELS					FLAGS			SET STATUS		
A	B	C	D	E START	0 NINF = 2	FLAGS	TRIG	DISP		
a	b	c	d	e	1	0 ON	■			
0 Z _i calc	1 Q ² (Z)	2 A(Z)	3 clear unused reg	4 E(Z)E*(Z)	2 I = ∅	1	DEG			
5 wait loop	6	7 F ² (Z) subr	8 multiply	9 multiply	3	2	GRAD			
						3	RAD			
							n	2		

Program Listing I

SECANT ITERATION TO FIND
ROOTS OF E(Z)E*(Z)

```

001 *LBL1 START SECANT ITERATION
002 EEX
003 CHS set correction radius for
004 9 loop exit
005 STOE
006 *LBL2 secant outer loop start
007 CLX
008 ST00 set Z0 = 0 + j0
009 ST01
010 ST05
011 P±S
012 RCL0 set F(Z0) = E0 + j0
013 P±S
014 ST04
015 6 set Z1 = 1∠60°
016 0
017 ENT↑
018 EEX
019 →R
020 ST02
021 X±Y
022 ST03
023 *LBL6 prepare for polynomial
024 RCL2 evaluation:
025 RCL3
026 x form Z2 = (σ - jω)2;
027 ENT↑
028 +
029 ST04 Im(Z2) = 2σω → RD → R7
030 ST07
031 RCL2
032 X2
033 RCL3 Re(Z2) = σ2 - ω2 → R0 → R6
034 X2
035 -
036 ST0C
037 ST06
038 RCLB set index to highest register
039 ST0I number that has coefficients
040 RCLI start polynomial evaluation
041 STx6 by forming E2nZ2
042 STx7
043 *LBL1 polynomial eval loop start,
044 DSZI decrement register index
045 RCLI recall E2k
046 ST+6 add_to_calculation real part
047 RCLI
048 EEX test for loop exit
049 1
050 X=Y?
051 GT02
052 RCL6 perform complex multiply
053 RCLC by Z2 on the ongoing
054 x calculation
055 RCL7

```

shift register contents,
Z_k becomes Z_{k-1}, and
F(Z_k) becomes F(Z_{k-1}) for
the next iteration

REGISTERS										
⁰ Re Z _{k-1}	¹ Im Z _{k-1}	² Re Z _k	³ Im Z _k	⁴ ReF(Z _{k-1})	⁵ ImF(Z _{k-1})	⁶ ReF(Z _k)	⁷ ImF(Z _k)	⁸ scratch	⁹ scratch	
S0 E ₀	S1 E ₂	S2 E ₄	S3 E ₆	S4 E ₈	S5 E ₁₀	S6 E ₁₂	S7 E ₁₄	S8 E ₁₆	S9 E ₁₈	
A	B highest register #	C Re(Z _k ²)	D Im(Z _k ²)	E error radius for loop exit	F index					

Program Listing II

<pre> 111 R↓ 112 RCL9 apply Z correction: 113 X↑Y 114 →R $Z_{k+1} = Z_k - \Delta Z$ 115 ST-2 116 X↑Y 117 ST-3 118 RCL8 119 RCLE test for loop exit 120 X≤Y? 121 GT08 122 *LBL3 Z factor output and 123 RCL3 polynomial deflation by 124 X² degree 4, i.e., the quad is: 125 RCL2 126 X² $Z^4 + pZ^2 + q$ 127 - 128 ENT↑ $p = 2((\text{Im } Z_1)^2 - (\text{Re } Z_1)^2)$ 129 + 130 STOC $p \rightarrow RQ$ 131 RCL3 132 X² 133 RCL2 134 X² $q = ((\text{Im } Z_1)^2 + (\text{Re } Z_1)^2)^2$ 135 + 136 X² 137 STOD $q \rightarrow RD$ 138 + calculate and output the 139 EEX s-plane LHP complex-conjugate 140 + pole pair natural frequency: 141 JX 142 1/X $\omega_n = (1 + p + q)^{-\frac{1}{2}}$ 143 JX 144 PRTX calculate and output pole 145 EEX pair "Q": 146 LSTX 147 RCLC 148 2 149 ÷ 150 EEX 151 + 152 X 153 - 154 ENT↑ 155 + 156 1/X 157 JX 158 PRTX print Q 159 SPC 160 RCLB set index to highest register 161 ST01 number that has coefficients 162 *LBL5 polynomial deflation loop 163 RCLI 164 RCLC 165 X </pre>	<pre> 166 ISZI let the primed values 167 RCLI represent the coeffic- 168 RCLO ients of the deflated 169 X polynomial: 170 + 171 DSZI $E'_k = E_k - pE'_{k+2} - qE'_{k+4}$ 172 DSZI 173 ST-i 174 RCLI 175 1 176 3 test for loop exit 177 X≤Y? 178 GT05 179 *LBL6 move coefficients down two 180 RCLI register numbers in storage 181 DSZI so E_0 resides in register S_0 182 DSZI 183 STO↓ 184 ISZI 185 ISZI 186 ISZI 187 RCLB 188 RCLI test for loop exit 189 X≤Y? 190 GT06 191 DSZI 192 CLX 193 STO↓ clear top two registers. 194 DSZI 195 STO↓ 196 DSZI 197 RCLI store index number of highest 198 STOB register containing coeffs 199 1 200 2 201 X≤Y? test for outer loop exit 202 GT0e 203 EEX 204 1 if filter order is even, 205 RCLI exit loop here 206 X≤Y? 207 RTN 208 RCLI calculate real pole location 209 DSZI in s-plane for odd ordered 210 RCLI filter 211 X↑Y 212 ÷ 213 ABS $C_0 = (E_2/E_0 - 1)^{-\frac{1}{2}}$ 214 EEX 215 - 216 JX 217 1/X 218 PRTX 219 SPC 220 RTN </pre>									
LABELS										
A	B	C	D	E	START	0	FLAGS	SET STATUS		
a	b	c	d	e	main loop start	1		FLAGS	TRIG	DISP
poly eval	1 poly eval	2 ΔZ calc	3 factor output	4		1	0 1 2 3	ON OFF	DEG GRAD RAD	SCI ENG n 8
5 poly deflate	6 coef reorder	7	8	9		3				

PROGRAM 2-15 DARLINGTON'S ELLIPTIC FILTER ALGORITHMS.

Program Description and Equations Used

This program calculates the normalized transmission function pole and zero locations, and minimum stopband rejection for odd order elliptic filters. The program is based on Professor Sidney Darlington's paper which describes simple elliptic filter algorithms using transformations on elliptic sines and their moduli [18], and his unpublished HP-65 program on the same subject.

The output data is normalized to the passband cutoff frequency (f_p), however, the algorithm is normalized to the geometric mean of the passband and stopband edge frequencies as shown by Fig. 2-15.1.

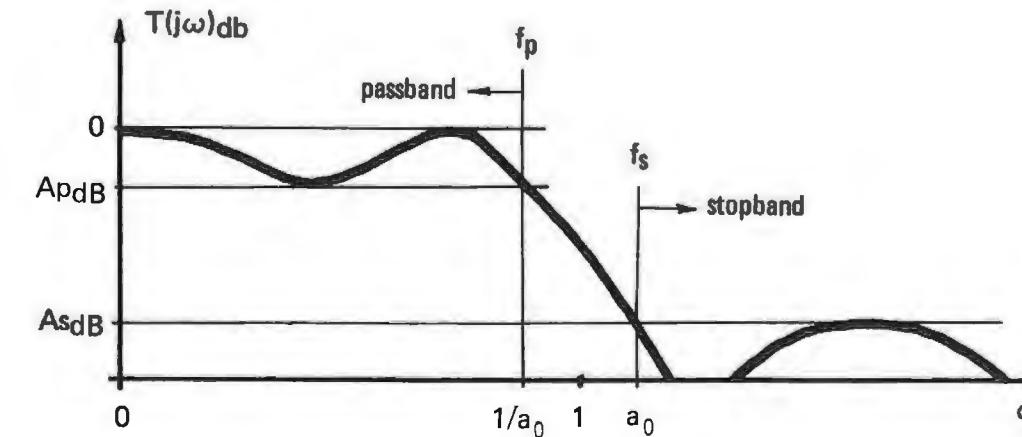


Figure 2-15.1 Definition of elliptic filter terms.

Thus, the transition ratio, λ , becomes:

$$\lambda = \frac{f_s}{f_p} = \frac{a_0}{1/a_0} = a_0^2 \quad (2-15.1)$$

or

$$a_0 = \sqrt{\lambda} \quad (2-15.2)$$

The filter transmission function, $T(s)$, is the reciprocal of the filter transfer function, $H(s)$, which is related to the filter characteristic function, $K(s)$, through the Feldtkeller equation:

$$|T(j\omega)|^2 = \frac{\text{power out}}{\text{power in}} = \left| \frac{1}{H(j\omega)} \right|^2 = \frac{1}{1 + \epsilon^2 |K(j\omega)|^2} \quad (2-15.3)$$

where the characteristic function is the Chebyshev rational function described in Program 2-12. Darlington's algorithms are a very elegant way of approximating the Chebyshev rational function using simple recursive relationships. These relationships can also be used to find the LHP poles and zeros of:

$$T(s)T(-s) = \frac{1}{1 + \epsilon^2 K(s)K(-s)} \quad (2-15.4)$$

Normalized transmission zero frequencies. If Y_0 represents geometrically normalized frequency (Fig. 2-15.1) and Y_{0k} ($k = 1, 2, \dots, \frac{n-1}{2}$) represents the normalized transmission zero frequencies where n is the filter order, then the characteristic function for odd order, equiripple passband, lowpass filters is given by:

$$|K(Y_0)|^2 = |J_0 \cdot F_o(Y_0)|^2 \quad (2-15.5)$$

where J_0 is a constant and

$$F_o(Y_0) = Y_0 \prod_{k=1}^{(n-1)/2} \frac{1 - Y_{0k}^2 Y_0^2}{Y_0^2 - Y_{0k}^2} \quad (2-15.6)$$

For the elliptic filter case (equal ripple passband and stopband):

$$\epsilon^2 = 10^{0.1 A_{dB}} - 1 \quad (2-15.7)$$

$$J_0 = F_o(a_0) \quad (2-15.8)$$

$$F_o\left(\frac{1}{Y_0}\right) = \frac{1}{F_o(Y_0)} \quad (2-15.9)$$

These quantities and Y_{0k} may be found through recursive use of a variable transformation which spreads out the transition interval.

Let $a_{k+1} = a_k^2 + \sqrt{a_k^4 - 1}$ (2-15.10)

then, given a_0 as defined by Eq. (2-15.2), find and store a_1, a_2, a_3 , and a_4 . Four applications of the recursion formula will provide precision which will be calculator limited rather than algorithm limited (see p. 37 of [18]).

Let h represent the index for the transmission zero frequencies; $h = 1, 2, \dots, (n-1)/2$, then let

$$Y_{4h} = \frac{a_4}{\cos \{ (2h-1)(90/n) \}} \quad (2-15.11)$$

and recursively calculate:

$$Y_{(k-1)h} = \frac{1}{2a_k} (Y_{kh} - 1/Y_{kh}) \quad (2-15.12)$$

$$k = 4, 3, 2, 1$$

The transmission zero frequencies normalized with respect to the passband edge are:

$$a_0 \cdot Y_{0h} \quad (2-15.13)$$

Minimum stopband rejection. The minimum stopband rejection for elliptic filters first occurs at the stopband frequency edge (geometrically normalized frequency a_0) and may be found from J_0 and Eqs. (2-15.4), (2-15.5), and (2-15.8), i.e.:

$$A_{dB} = 10 \log (1 + \epsilon^2 J_0^2 J_0^{-2}) \quad (2-15.14)$$

J_0 is found from another recursion relationship; let

$$J_4 \cong 2^{n-1} \cdot a_4^n = \frac{(2 \cdot a_4)^n}{2} \quad (2-15.15)$$

then recursively calculate and store J_k 's using:

$$J_{k-1} = \frac{1}{2} \sqrt{(J_k - 1/J_k)} \quad (2-15.16)$$

$$k = 4, 3, 2, 1$$

Transmission function pole locations. Let s_{oh} represent the complex pole location, and let

$$J_o \cdot s_{oo} = 1/\epsilon \quad (2-15.17)$$

Then recursively calculate:

$$s_{(k+1)o} = J_k \cdot s_{ko} + \sqrt{(J_k \cdot s_{ko})^2 + 1} \quad (2-15.18)$$

$k = 0, 1, 2$

As the index increases, the terms $J_k \cdot s_{ko}$ become numerically very large since the J_k 's increase nearly geometrically for J_k large. To avoid numeric overflow (10^{99}) use:

$$s_{4o} \approx 2 \cdot J_3 \cdot s_{3o} \quad (2-15.19)$$

Calculate and store:

$$s_{5o} = \left\{ \frac{J_4}{s_{4o}} + \sqrt{\left(\frac{J_4}{s_{4o}} \right)^2 + 1} \right\}^{\frac{1}{n}} \quad (2-15.20)$$

To calculate the pole locations, let:

$$s_{5h} = s_{5o} \cdot e^{jh(\pi/n)} \quad (2-15.21)$$

$h = 0, 1, 2, \dots, (n-1)/2$

Using complex arithmetic, recursively calculate:

$$s_{(k-1)h} = \frac{1}{2 \cdot a_{k-1}} (s_{kh} - 1/s_{kh}) \quad (2-15.22)$$

$k = 5, 4, 3, 2, 1$

The pole locations normalized to the passband edge are given by:

$$s_{oh} \cdot a_o \quad (2-15.23)$$

The subroutine that calculates Eq. (2-15.22) may seem obscure to some readers. The particular coding that is used minimizes the amount of data that must undergo polar-to-rectangular and rectangular-to-polar conversions, and hence, maximizes the numerical accuracy of the routine. The normal format for the pole locations is polar as given by Eq. (2-15.21). In general, let:

$$s_{kh} = \rho_{kh} \cdot e^{j\beta_{kh}} \quad (2-15.24)$$

In rectangular format, Eq. (2-15.24) becomes:

$$s_{kh} = \rho_{kh} \cos \beta_{kh} + j \rho_{kh} \sin \beta_{kh} \quad (2-15.25)$$

For the reciprocal case, let:

$$\frac{1}{s_{kh}} = \frac{1}{\rho_{kh}} e^{-j\beta_{kh}} \quad (2-15.26)$$

which using rectangular format becomes:

$$\frac{1}{s_{kh}} = \frac{1}{\rho_{kh}} \cos \beta_{kh} - j \frac{1}{\rho_{kh}} \sin \beta_{kh} \quad (2-15.27)$$

hence,

$$s_{kh} - \frac{1}{s_{kh}} = \left(\rho_{kh} + \frac{1}{\rho_{kh}} \right) \cos \beta_{kh} + j \left(\rho_{kh} - \frac{1}{\rho_{kh}} \right) \sin \beta_{kh} \quad (2-15.28)$$

or,

$$s_{kh} - \frac{1}{s_{kh}} = \left(1 + \frac{1}{\rho_{kh}^2} \right) \rho_{kh} \cos \beta_{kh} + j \left(1 - \frac{1}{\rho_{kh}^2} \right) \rho_{kh} \sin \beta_{kh} \quad (2-15.29)$$

In Eq. (2-15.29), the terms $\rho_{kh} \cos \beta_{kh}$ and $\rho_{kh} \sin \beta_{kh}$ are the output components of a polar-to-rectangular conversion, and ρ_{kh} is saved in the last x register, and has not undergone any conversion. The stack is used to hold the intermediate parts of Eq. (2-15.29). A rectangular-to-polar conversion then completes the subroutine.

User Instructions



STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
1	Load both sides of program card			
2	Select print or R/S option (toggle)		f E f E f E ⋮	0 (R/S) 1 (print) 0 (R/S)
3	Load passband ripple in dB or reflection coefficient	ApdB P	A chs A	ϵ^2 ϵ^2
4	Load stopband to passband frequency ratio	λ	B	
5	Load filter order (must be odd)	n	C	
6	Calculate normalized transmission zero frequencies and minimum stopband loss		D	Ω_1 Ω_2 ⋮ Ω_{n-1} Ω_n AsdB
7	Calculate real and imaginary parts of normalized transmission function poles		E	Re S ₀₁ Im S ₀₁ Re S ₀₂ Im S ₀₂ ⋮ Re S _{0n} Im S _{0n}

Example 2-15.1

Find the transmission function poles and zeros for a 9th order, elliptic filter having a 85° modular angle, and 50% reflection coefficient. Also calculate the minimum stopband attenuation in dB. Compare the results to the output of Program 2-11.

PROGRAM 2-15 INPUT	PROGRAM 2-15 OUTPUT
-.5 GS6A 55. SIN 1.% 1.003819836+00 GS6E 9. GS6C	GSBD calc xmsn 0's 1.004553794+00 *** z1 1.014264420+00 *** z2 1.071140576+00 *** z3 1.449931830+00 *** z4 33.62429965+00 *** AsdB min GSBE calc xmsn fcn poles 372.8205714-03 *** Re p ₀ 8.000000000+00 *** Im p ₀ 182.7207935-03 *** Re p ₁ 735.3062101-03 *** Im p ₁ 41.73031646-03 *** Re p ₂ 351.5234634-03 *** Im p ₂ 7.869871966-03 *** Re p ₃ 992.6118076-03 *** Im p ₃ 3.121142401-03 *** Re p ₄ 995.5098960-03 *** Im p ₄

Load Program 2-12 and calculate transmission zeros (loss poles) for the same conditions.

PROGRAM 2-12 INPUT	PROGRAM 2-12 OUTPUT
1. ENT1 .5 X ²	GSBC calculate filter order
- calculate LOG and load	8.352734615+00 *** calc order
10. x Ap _{dB} for CHS 50% refl	9.000000000+00 *** integral order to meet specs
i.249367366+00 *** coef GSBA	GSBD calculate xmsn zero freq's
38. GSBA load As _{dB}	1.449931862+00 *** z ₄
1. GSBB load f _p	1.071140568+00 *** z ₃
85. SIN calculate and 1/X load f _s for 1.003815838+00 *** 85° modular GSBe angle	1.014284418+00 *** z ₂
	1.004553794+00 *** z ₁

Comparing these results to those obtained from Program 2-15, differences exist in the 9th and 10th places sometimes. It is the author's opinion that the output from Program 2-12 is accurate to 2 parts in 10¹⁰, since the elliptic sine algorithm and complete elliptic integral algorithm have been checked against the elliptic function tables in Abramowitz and Stegun [1] and disagree by at most one in the least significant digit of the HP-97 output (see Program 5-1 for details).

Program Listing I

REGISTERS	
0 a ₀	1 a ₁
S0 J ₄	S1 J ₃
A ε ²	B λ
C n	D s
E 90/n	F register index

```

001 *LBLA LOAD ApdB or -ρ
002 X<0? test for -ρ
003 GTOa calculate and store:
004 EEX
005 1
006 ÷ ε2 = 10ApdB - 1
007 10x
008 EEX
009 -
010 STOA
011 GT09
012 *LBLB calculate and store:
013 X2
014 CHS
015 EEX
016 +
017 1/X ε2 =  $\frac{1}{1-\rho^2} - 1$ 
018 EEX
019 -
020 STOA
021 GT09
022 *LBLC LOAD λ, the stopband to passband frequency ratio
023 STOB
024 GT09
025 *LBLD LOAD n, the filter order (must be odd)
026 STOC
027 GT09
028 *LBLD CALC xmsn zeros & AsdB
029 9 calculate and store:
030 0
031 RCLC  $\frac{90}{n} \rightarrow R_E$ 
032 ÷
033 STOE
034 EEX
035 STOI initialize k+1, 2h-1
036 ST09
037 RCLB  $a_o = \sqrt{f_s/f_p}$ 
038 JX
039 GSB7
040 GSB7  $a_{k+1} = a_k^2 + \sqrt{a_k^4 - 1}$ 
041 GSB7 k = 0, 1, 2, 3
042 GSB7
043 *LBLD
044 3 initialize k-1
045 STOI
046 RCL4 calculate
047 RCL9
048 RCLC  $Y_{4h} = \frac{a_4}{\cos\{(2h-1)\frac{90}{n}\}}$ 
049 X
050 COS
051 ÷ h = 1, 2, ...,  $\frac{n-1}{2}$ 
052 SF0 indicate early subr exit
053 *LBL1  $Y_{(k-1)h} = \frac{1}{2a_k} (Y_{kh} - \frac{1}{Y_{kh}})$ 
054 GSB8
055 RCLi k = 4, 3, 2
056 ÷
057 DSZI test for loop exit
058 GT01
059 GSB8 Yo ao = xmen zero freq
060 GSBd print xmen zero freq
061 2 increment 2h-1
062 ST+9
063 RCL9
064 RCLC
065 X>Y? test for loop exit
066 GT00
067 GSB9 space if flag 1 is set
068 EEX initialize k-1
069 STOI
070 RCL4 calculate and store:
071 ENT↑
072 +
073 RCLC  $J_4 \cong \frac{(2a_4)^n}{2}$ 
074 YX
075 2
076 ÷
077 P2S
078 ST08
079 CF0 indicate full subr
080 GSB8
081 GSB8  $J_{k-1} = \sqrt{\frac{1}{2} (J_k - \frac{1}{J_k})}$ 
082 GSB8 k = 4, 3, 2, 1
083 GSB8 calculate and print:
084 P2S
085 X2
086 X2
087 RCLA
088 X
089 EEX  $A_{dB} = 10 \log(1 + \epsilon^2 J_o^{-4})$ 
090 +
091 LOG
092 1
093 0
094 X
095 PRTX
096 GT09 goto space and return subr
097 *LBL7 subroutine to calculate:
098 X2
099 ENT↑
100 X2
101 EEX
102 -
103 JX  $a_{k+1} = a_k^2 + \sqrt{a_k^4 - 1}$ 
104 +
105 STO;
106 ISZI
107 RTN

```

Program Listing II

		LABELS		FLAGS		SET STATUS		
A	B	C	D	E	0	FLAGS	TRIG	DISP
LOAD	ApdB	LOAD A	LOAD n	CALC zeros	CALC poles	subr exit		
^a calc ϵ^2	b	c	d	prt-R/S	e	print?	1 print	
⁰ h loop	¹ k loop	² k loop	³ k loop	⁴ h loop	²			
⁵ subr	⁶ subr	⁷ subr	⁸ subr	⁹ subr	³			

```

108 *LBL8 subroutine to calculate:
109 ENT†
110 1/X
111 +
112 2
113 ÷
114 F0? test for early exit
115 RTN
116 JX
117 STOI  $J_{k-1} = \sqrt{\frac{1}{2}(J_k - \frac{1}{J_k})}$ 
118 ISZI
119 RTN
120 *LBL8 CALCULATE POLE LOCATIONS
121 3
122 STOI initialize 3-k
123 RCL A
124 JX  $J_0 S_{00} = \frac{1}{\epsilon}$ 
125 1/X
126 P2S
127 *LBL2 calculate:
128 GSB6  $S_{(k+1)_0} = J_k S_{k0} + \sqrt{J_k^2 S_{k0}^2 + 1}$ 
129 RCL I
130 X
131 DSZI test for loop exit
132 GT02
133 ENT† to avoid overflow, use:
134 +
135 RCL I
136 P2S
137 X2Y
138 =
 $S_{50} = \left\{ \frac{J_4}{S_{40}} + \sqrt{\left(\frac{J_4}{S_{40}}\right)^2 + 1} \right\}^{\frac{1}{n}}$ 
139 GSB6
140 RCL C
141 1/X
142 YX
143 STOD
144 CLK initialize 2h
145 STO9
146 *LBL4 pole location calc loop
147 4
148 STOI initialize k-1
149 RCL9
150 RCL E
151 X  $S_{5h} = S_{50} e^{jh\frac{\pi}{n}}$ 
152 RCL D
153 *LBL3 h = 0, 1, 2, ...,  $\frac{n-1}{2}$ 
154 GSB5  $S_{(k-1)h} = \frac{1}{2} a_{k-1} (S_{kh} - \frac{1}{S_{kh}})$ 
155 RCL I
156 ÷
157 DSZI test for loop exit
158 GT03
159 GSB5 finish pole location
160 +R
161 GSB4 calculation and print
162 pole locations
163 X2Y
164 GSB5

```

```

165 2
166 STO‡
167 RCL E
168 RCL C
169 M+Y†
170 GTC4
171 *LBL3 increment 2h
172 F1†
173 SF1
174 RTN
175 STO‡
176 *LBL4 space and return subr
177 +F
178 LSTO
179 1/Y
180 .2
181 EE†
182 -
183 .
184 LSTA
185 2
186 +
187 F†
188 *
189 MZ†
190 +F
191 2
192 +
193 RTN
194 *LBL5 subroutine to calculate:
195 ENT†
196 M2
197 EE†
198 +
199 f†
200 +
201 RTN
202 *LBL6 print or R/S subroutine
203 F1†
204 PRTH
205 F1†
206 RTN
207 RME
208 RTN
209 *LBL7 PRINT-R/S TOGGLE
210 CF1
211 CLK clear flag 1 and place
212 RTN a zero in the display
213 *LBL8
214 SF1
215 EE†
216 RTN set flag 1 and place
a one in the display

```

Part 3

ELECTROMAGNETIC COMPONENT DESIGN

PROGRAM 3-1 FERROMAGNETIC CORE INDUCTOR DESIGN – MAGNETICS.

Program Description and Equations Used

This program calculates the various parameters relating to inductor or transformer design on closed magnetic cores. Given the core relative permeability (μ), the core length (l_c), the core area (A), the air gap (l_{air}), the required inductance (L), the dc current (I_{dc}), the applied ac voltage (E), and the excitation frequency (f), the program will calculate the number of turns required (N), the core H (oersteds) and B (gauss) resulting from the dc excitation, the ac excitation, and the total from both excitations. The dimensions of the core and air-gap can be entered in either centimeter or inch units. Program 3-2 will calculate the wire size and winding resistance given the window area and mean turn length. The program will also calculate the coil inductance if the number of turns, the core permeability and dimensions, and the air gap dimensions are given.

If the inductance in millihenries per 1000 turns is given (the A_L value) along with the core dimensions and permeability, the effective air gap will be calculated and stored in place of the given air gap. The inductance or turns, and core excitation will then be calculated on the basis of the calculated air gap.

The magnetic equations used are:

$$H = \frac{0.4 \mu NI}{l_c + \mu_c l_{air}} \quad (3.1.1)$$

$$E = 10^{-8} \cdot N \frac{d\phi}{dt} = 10^{-8} NA \frac{dB}{dt} \quad (3-1.2)$$

where I is the current in the coil. Equation (3-1.2) can be rearranged to yield B, the core flux density:

$$B = \frac{10^8}{NA} \int E \cdot dt \quad (3-1.3)$$

If $E = \sqrt{2} \cdot E_{\text{rms}} \cdot \sin(2\pi ft)$ is the sinewave excitation, then:

$$B_{\text{peak}} = \frac{10^8 \cdot E_{\text{rms}}}{\sqrt{2}\pi \cdot A \cdot N \cdot f} \quad (3-1.4)$$

If E is a symmetrical squarewave with voltage E_{pk} as shown by Fig. 3-1.1, then:

$$B_{\text{peak}} = \frac{10^8 \cdot E_{\text{pk}}}{4 \cdot A \cdot N \cdot f} \quad (3-1.5)$$

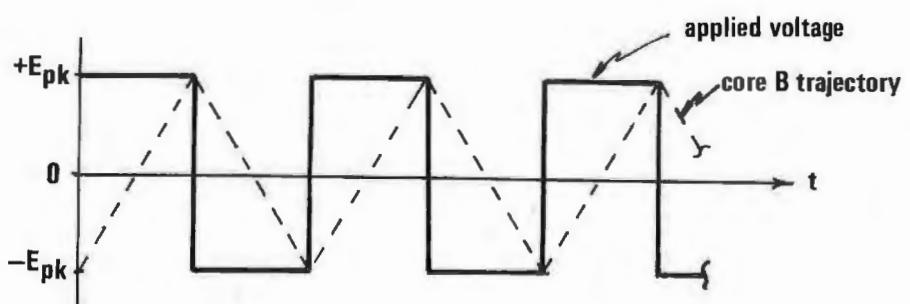


Figure 3-1.1 Square wave coil excitation and magnetic flux density trajectory.

Remembering the differential relationship between current and voltage in an inductor, $E = L(dI/dt)$, an expression can be derived relating the inductance, L , to the magnetic circuit quantities:

$$B = \mu H \quad (3-1.6)$$

From Eqs. (3-1.2) and (3-1.6):

$$E = 10^{-8} N \cdot A \cdot \mu \frac{dH}{dt} \quad (3-1.7)$$

From Eq. (3-1.1):

$$\frac{dH}{dt} = \frac{0.4 \mu N}{\ell_c + \mu \ell_{\text{air}}} \cdot \frac{dI}{dt} \quad (3-1.8)$$

Combining Eqs. (3-1.7) and (3-1.8) yields the inductance expression:

$$E = \frac{0.4 \pi N^2 A \cdot 10^{-8}}{\ell_c + \mu \ell_{\text{air}}} \cdot \frac{dI}{dt} \quad (3-1.9)$$

hence

$$L = \frac{0.4 \pi N^2 \mu A \cdot 10^{-8}}{\ell_c + \mu \ell_{\text{air}}} \quad (3-1.10)$$

This equation may be rearranged to yield the equivalent air gap if the inductance per turn squared and core dimensions are known:

$$\ell_{\text{air}} = \frac{0.4 \pi N^2 A \cdot 10^{-8}}{L} - \frac{\ell_c}{\mu}, \text{ cm} \quad (3-1.11)$$

Generally the inductance index in millihenries per 1000 turns is provided by the core manufacturer:

$$L^* = \text{millihenries per 1000 turns} \quad (3-1.12)$$

hence,

$$\ell_{\text{air}} = \frac{4 \pi A}{L^*} - \frac{\ell_c}{\mu} \text{ cm} \quad (3-1.13)$$

Equation (3-1.10) can be rearranged to yield an expression for N , the number of turns, required to achieve a given inductance, L :

$$N = \left\{ \frac{(L_c + \mu \ell_{\text{air}}) \cdot 10^8}{0.4 \pi \mu A} \right\}^{1/2} \quad (3-1.14)$$

The program uses these equations as follows: Labels "A," "a," "B," and "b" are used to load and store the core parameters. The actual stored parameters are in centimeters, and entries with inch units (Labels "A" and "B") are converted before storage. Label "C" uses Eq. (3-1.14) to calculate N given L . Label "c" uses Eq. (3-1.10) to calculate L given N . Label "d" uses Eq. (3-1.13) to calculate the equivalent air gap given the inductance index, L^* . The new air gap dimension replaces the presently stored air gap dimension. Label "D" uses Eq. (3-1.1) to calculate the dc magnetizing force, H , given the dc current through the core. Since the number of turns are required for this calculation, the use of "C" or "c" must precede the use of "D." The dc flux density, B_{dc} , is calculated using Eq. (3-1.6). Label "E" uses Eq. (3-1.4) to calculate the peak core flux density given the ac coil excitation. The flux in the core will vary sinusoidally with sinusoidal excitation. The peak ac magnetizing force is calculated using Eq. (3-1.6). The peak ac and dc core magnetic parameters are added together and printed to provide the peak excitation in the core. The peak excitation should be kept below the magnetic saturation level of the core material for linear operation. Label "e" uses Eq. (3-1.5) to calculate peak core flux density from squarewave coil excitation, and provides a summary as above.

User Instructions

INDUCTOR DESIGN - MAGNETICS				
$\mu \cdot l_c + A_c$ cm	l_{air} cm	$N \rightarrow L$	L^* , mh 1000T	E_{pk} , fHz H, Bac, pk
$\mu \cdot l_c + A_c$ inches	l_{air} inches	$L \rightarrow N$	$I_{dc} \rightarrow H, B_{dc}$	E_{rms} , fHz H, Bac, pk


2

STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
1	Load both sides of magnetic card			
2	Load magnetic core parameters			
a)	for dimensions in inches			
i)	relative permeability of core	μ	ENT ↑	
ii)	effective core length	l_c	ENT ↑	
iii)	effective core cross-sectional area	A_c	A	μ
b)	for dimensions in centimeters			
i)	relative permeability of core	μ	ENT ↑	
ii)	effective core length	l_c	ENT ↑	
iii)	effective core cross-sectional area	A_c	f A	μ
3	Load air gap length (if L^* is to be used, skip this step)			
a)	for dimensions in inches	l_{air}	B	l_{air} , cm
b)	for dimensions in centimeters	l_{air}	f B	l_{air} , cm
4	Load L^* (mh/1000T) if air gap is unknown	L^*	f D	l_{air} , cm
5	To calculate the number of turns to achieve a given inductance	L, h	C	N
6	To calculate the inductance given the number of turns	N	f C	L, h
7	Load dc coil current	I_{dc}	D	H_{dc} , Oe B_{dc} , G
8	If sinewave ac coil excitation is present			
a)	load the rms voltage	E_{rms} , V	ENT ↑	
b)	load the frequency	f, Hz	E	H_{ac} pk, Oe H_{dc} , Oe H_{total} , Oe B_{ac} pk, G B_{dc} , G B_{total} , G

User Instructions

INDUCTOR DESIGN - MAGNETICS				
		CONTINUED		

STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
9	If square-wave coil excitation is present a) load the peak voltage (see Fig. 3-1.1) b) load the frequency	E_{pk} , f, Hz	ENT ↑ f E	H_{ac} pk, Oe H_{dc} , Oe H_{total} , Oe B_{ac} pk, G B_{dc} , G B_{total} , G
10	To obtain the wire size and winding resistance for the above winding, load Program 3-2.			

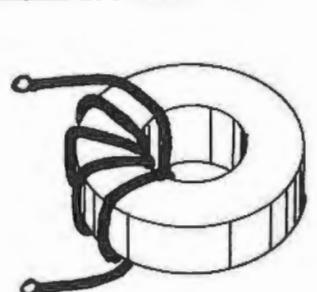Example 3-1.1

$$\mu_e = 2500$$

$$L^* = 1100 \text{ mh}/1000T$$

Design an inductor to have an inductance of 20 millihenries using the above core (a Ferroxcube 266CT1253B7). The operating frequency is 10 kHz, and the applied ac voltage is 1 Vrms sinewave. There will be 1 mA of dc flowing in the winding.

The core physical constants are needed first:

$$A = (.125)(.375 - .187)/2 = 11.8 \times 10^{-3} \text{ inches}^2$$

$$l_c = \pi(.375 + .187)/2 = .883 \text{ inches (mfgr says .852 in)}$$

$$l_{air} = 0 \text{ (no air gap)}$$

These dimensions along with $\mu_e = 2500$ are loaded using the A & B keys.

2500. ENT[†] μ_e
.852 ENT[†] l_c , inches
11.8-03 GSE4 A, inches²



0. GSE5 l_{air}
1100. GSE5 L* (mh/1000T)
4.062-02 *** l_{air} calculated, cm

.020 GSE5 L required, h
134.6+00 *** N calculated (use 135T)

1.03 GSE5 Idc, amps
77.93-03 *** Hdc, oersteds
194.6+00 *** Bdc, gauss

1. ENT[†] Vrms
10000. GSE5 freq, Hz, sinewave
87.71-03 *** Hac peak, oersteds
77.93-03 *** Hdc
165.6-03 *** H total
219.3+00 *** Bac peak, gauss
194.6+00 *** Bdc
414.1+00 *** B total

Since the core saturates at around 2500 gauss, and this design only excites the core to 414 gauss peak, the design appears adequate from a magnetics standpoint.

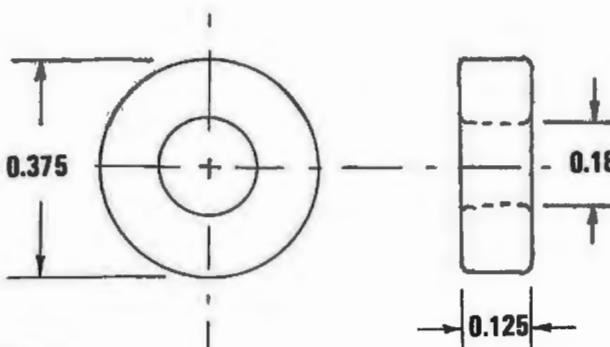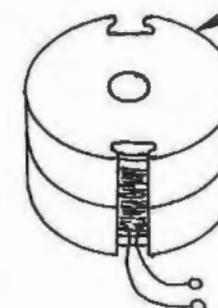Example 3-1.2

Ferrite pot core: Ferroxcube 2213C A400 3B7

$$l_c = 3.15 \text{ cm}$$

$$A_c = 0.635 \text{ cm}^2$$

$$\mu_e = 1845$$

$$L^* = 400 \text{ mh}/1000T$$

$$B_{max} < 2000 \text{ gauss for stable inductance}$$

This pot core is to be used in a tank circuit of a class A tuned amplifier operating at 50 kHz. The dc current is 30 mA, and the applied ac voltage is 10 Vrms. The required inductance is 40 mh (the resonating capacitor is 253 pF). Calculate the effective air gap, the number of turns required, the dc and ac core excitation, and the peak flux density. The following HP-97 printout shows the data entry and calculated parameter output.

1845. ENT[†] μ_e
3.15 ENT[†] l_c , centimeters
.635 GSE4 A, cm²

400. GSE4 L* (mh/1000T)
18.24-03 *** l_{air} calculated

	PREG
.040 GSE5 L required, h	1.845+03 0
316.2+00 *** N calculated (use 316)	3.150+00 1
	635.0-03 2
.030 GSE5 Idc, amps	10.24-03 3
323.9-03 *** Hdc, oersteds	316.2+00 4
597.6+00 *** Bdc, gauss	50.00+03 5
	323.9-03 6
10. ENT [†] Vrms	597.6+00 7
50000. GSE5 Freq, Hz, sinewave	0.000+00 8
12.15-03 *** Hac peak, oersteds	22.42+00 9
323.3-03 *** Hdc,	10.00+00 A
336.1-03 *** H total,	30.00-03 B
	4.000+06 C
22.42+00 *** Bac peak, gauss	400.0+00 D
597.6+00 *** Bdc,	0.000+00 E
620.0+00 *** B total,	0.000+00 I

A printout of the registers reveals this stored information:

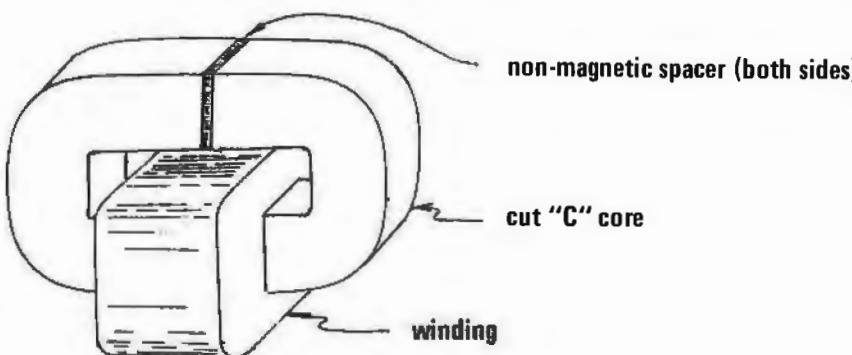
Example 3-1.3

Figure 3-1.2 Inductor on cut C-core.

An inductor to carry dc is needed for the power separation assembly at the end of a coax cable. One ampere dc must flow through the inductor without forcing the B-H loop into a nonlinear region. The inductance needed is 1 henry. Ac signals of 10 Vrms across a frequency band covering 10 Hz to 1000 Hz will be applied in addition to the dc current. A tentative selection is a cut "C" core (see Fig. 3-1.2) with dimensions $A_c = 1.0 \text{ in}^2$, $\ell_c = 6 \text{ inches}$, and $\mu = 1000$ (silicon steel). To ensure linear inductance, the peak flux level in the core should not exceed 10000 gauss.

1000. ENT1 μ	
6. ENT1 ℓ_c , inches	
. GSBA A_c , inches 2	
.062 GSBE ℓ_{air} , inches (.031 each side)	.125 GSBE new air gap, inches (0.625" each side)
1. GSBC L, h, required	GSBC recalculate N
1.460+03 *** N, # turns calc	2.026+03 *** N, # turns
1. GSBD Idc, amps	GSBD recalc, H, Bdc
10.62+00 *** Hdc, oersteds	7.651+00 *** Hdc, oersteds
10.62+03 *** Bdc, gauss	7.651+03 *** Bdc, gauss
10. ENT1 Vrms	GSBE recalc H, Bac, etc.
10. GSBE freq, Hz, sinewave	1.722+00 *** Hac peak, oersteds
2.390+00 *** Hac peak, oersteds	7.651+00 *** Hdc,
10.62+00 *** Hdc,	9.373+00 *** H total,
13.01+00 *** H total, "	
2.390+03 *** Bac peak, gauss	1.722+03 *** Bac peak, guass
10.62+03 *** Bdc "	7.651+03 *** Bdc,
13.01+03 *** B total, "	9.373+03 *** B total, "
B total exceeds 10000 gauss, use a thicker spacer (larger air gap).	
B total is less than 10000 gauss, magnetic design is complete.	

Program Listing I

001 *LBLA LOAD CORE PARAMS, CM UNITS	052 *LBLC LOAD NUMBER OF TURNS								
002 ST02 store core area	053 F3? if numeric input,								
003 R↓	054 ST04 store value								
004 ST01 store core length	055 RCL4 calculate and store $L \cdot 10^8$:								
005 R↓	056 X ²								
006 ST06 store core permeability	057 GSB6								
007 F2? test for initialization	058 \div								
008 GSB5	059 RCL2 $L \cdot 10^8 = \frac{0.4\pi N^2 \mu A}{l_c + \mu l_{\text{air}}}$								
009 GT04 goto spc, CF3 and rtn	060 X								
010 *LBLA LOAD CORE PARAMS, IN. UNITS	061 RCL0								
011 F2? test for initialization	062 X								
012 GSB5	063 ST0C								
013 RCLI convert area in in ² to cm ²	064 RCL4								
014 X ² and store	065 \div								
015 X	066 GT03 goto print subroutine								
016 ST02	067 *LBLD LOAD Idc								
017 R↓	068 F3? if numeric input,								
018 RCLI convert core length in in.	069 ST0B store value								
019 X to cm and store	070 RCLB calculate and print Hdc:								
020 ST01	071 GSB6								
021 R↓	072 \div								
022 ST06 store core permeability	073 RCL4								
023 GT04 goto spc, CF3 and rtn	074 X $H_{dc} = \frac{0.4\pi NI}{l_c + \mu l_{\text{air}}}$								
024 *LBLB LOAD AIR GAP LENGTH, INCHES	075 PRTX								
025 F2? test for initialization	076 ST06								
026 GSB5	077 RCL0								
027 RCLI convert air gap length	078 X calculate and store Bdc								
028 X to cm	079 ST07 $B_{dc} = \frac{\mu \cdot H_{dc}}{l_c}$								
029 *LBL6 LOAD AIR GAP LENGTH, CM	080 GT03 goto print subroutine								
030 F2? test for initialization	081 *LBLd LOAD L*, MH PER 1000 TURNS								
031 GSB5	082 ST0D								
032 ST03 store air gap length in cm	083 1/X calculate and store								
033 GT04 goto spc, CF3, and rtn	084 4 equivalent air gap:								
034 *LBLC LOAD INDUCTANCE REQUIRED	085 X								
035 F3? if no numeric input, jump	086 PI								
036 F.? if	087 X								
037 GT00 calculate and store $L \cdot 10^8$	088 RCL2 $l_{\text{air}} = \frac{4\pi A}{L^2} - \frac{l_c}{\mu}$								
038 RCL4	089 X								
039 X calculate and store the	090 RCL1								
040 ST0C number of turns required	091 RCL0								
041 *LBL0 by using Eq. (3-1.14)	092 \div								
042 RCL0 calculate and store the	093 -								
043 GSB6 number of turns required	094 ST03								
044 X by using Eq. (3-1.14)	095 GT03 goto print subroutine								
045 RCL2 $N = \left\{ \frac{L(l_c + \mu l_{\text{air}}) \cdot 10^8}{0.4\pi \mu A_c} \right\}^{1/2}$									
046 \div									
047 RCL0									
048 \div									
049 \sqrt{x}									
050 ST04									
051 GT03 print number of turns									
REGISTERS									
0 μ	1 l_c	2 A_c	3 l_{air}	4 N	5 f	6 H_{dc}	7 B_{dc}	8	9 $B_{ac, pk}$
S0	S1	S2	S3	S4	S5	S6	S7	S8	S9
A V_{ac}	B I_{dc}	C $L \times 10^8$	D L^*	E 10^8	I 2.54				

Program Listing II

NOTE FLAG SET STATUS

		LABELS		FLAGS		SET STATUS		
$A_{ut} l_c \uparrow A_c [in]$	$B_{air} [in]$	C $L \rightarrow N$	D $I_{dc} \rightarrow H_{dc}, B_{dc}$	E $V_{rms} f_{Hz} \rightarrow H_{dc}, B_{dc}$	0	FLAGS	TRIG	DISP
$\mu_{air} \uparrow A_c [cm]$	$b_{air} [cm]$	C $N \rightarrow L$	D Load L^*	E $V_{ok} \uparrow P_{H_{dc}} \rightarrow H_{dc}, B_{dc}$	1	ON OFF		
0 loop c destination	1 ac flux output routine	2 ac flux output routine	3 print, space, CF3, rtn	4 space CF3, rtn	2 store constants	0	DEG	FIX
5 initialize constants	6 $I_c + H_c l_{air}$ 0.4π	7	8	9	3 data entry	1	GRAD	SCI
						2	RAD	ENG
						3	■	n 3

096 *LBL1	LOAD E_{rms} , f_{Hz} ; CALC H, B	150 *LBL5	initialization subroutine
097 F3?	jump if no numeric entry	151 EEX	
098 GT01	store frequency	152 8	generate and store 10^8
100 ST05		153 ST0E	
101 X2Y		154 R↓	recover x register
102 STOA	store rms voltage	155 2	
103 *LBL1	setup for B_{peak} calculation	156 .	
104 RCLA		157 5	generate and store 2.54
105 2		158 4	
106 JX	$k = \sqrt{2} \pi$	159 ST0I	
107 PI		160 R↓	recover x register
108 X		161 RTN	return to main program
109 GT02	goto B calculation	162 *LBL6	common magnetics subroutine
110 *LBL6	LOAD E_{pk} , f_{Hz} ; calc H, B	163 RCL3	
111 F3?	jump if no numeric entry	164 RCL0	
112 F3?	jump if no numeric entry	165 X	calculate:
113 GT01	store frequency	166 RCL1	
114 ST05		167 +	$\frac{L_e + \mu_{air}}{0.4 \pi}$
115 X2Y		168 PI	
116 STOA	store peak voltage	169 .	
117 *LBL1	setup for B calculation	170 4	
118 RCLA		171 .	
119 4		172 .	
120 *LBL2	common B calculation routine	173 RTN	return to main program
121 .			
122 RCL5			
123 .			
124 RCL2			
125 .	$B_{peak} = \frac{10^8 \cdot E}{kANf}$		
126 RCL4			
127 .			
128 RCL6			
129 X			
130 ST09	store $B_{ac, pk}$		
131 RCL0	calculate and print $H_{ac, pk}$		
132 .			
	$H = B/\mu$		
133 PRTX			
134 RCL6	recall and print H_{dc}		
135 PRTX			
136 +			
137 PRTX	calc and print H_{total}		
138 SPC			
139 RCL9	recall and print $B_{ac, pk}$		
140 PRTX			
141 RCL7	recall and print B_{dc}		
142 PRTX			
143 +	calculate B_{total}		
144 *LBL3	print and space subroutine		
145 PRTX			
146 *LBL4	space and OF3 subroutine		
147 SPC			
148 CF3			
149 RTN			

NOTE FLAG SET STATUS

PROGRAM 3-2 FERROMAGNETIC CORE INDUCTOR DESIGN - WIRE SIZE.

Program Description and Equations Used

This program is a companion program to Program 3-1. Given the window area and the number of turns (stored by companion program), this program will calculate the wire size with heavy insulation (class 2) that will fill the window area. If the length of the mean turn is known, the program will also calculate the winding resistance.

The program is also designed to provide information on the wire diameter over class 2 insulation and wire resistance in ohms/inch given the wire size in AWG. The program will also calculate the AWG given the wire diameter over class 2 insulation.

The operation of the program centers around the logarithmic relationship between AWG and the wire cross-sectional area. This logarithmic relationship is:

$$\text{AWG} = \frac{1}{b} \ln \frac{\text{diameter in inches}}{a} \quad (3-2.1)$$

where $a' = 0.3245574964$
 $b' = -0.1159489227$ } bare wire

$a = 0.3137250775$ } wire with class 2
 $b = -0.1097881513$ } insulation

If the total area for a winding of N turns is known, then the area for one turn may be calculated. If the wire is assumed to just fit inside a square with the wire diameter tangent to the sides of the square, then the waste space due to wire stacking can be accommodated (see Fig. 3-6.2). The wire diameter becomes the square root of the square's area. The program uses this algorithm. Once the wire diameter is found, the AWG can be calculated using the logarithmic relationships. The constants for heavy insulation are used. The AWG that is used and is output is the upward rounded value of $(1.5 + \text{calculated AWG})$.

The wire resistance per unit length is inversely proportional to

User Instructions

the copper cross-section, hence, the wire size in AWG also bears a logarithmic relationship to the wire resistance. When the wire resistance is desired as a function of the wire AWG, the relationship becomes exponential:

$$R/\ell \text{ (ohms/inch)} = c \cdot e^{(d \cdot \text{AWG})} \quad (3-2.2)$$

where $c = 8.371747114 \times 10^{-6}$ } annealed
 $d = -.2317635483$ } copper wire

This exponential relationship is used in conjunction with the mean turn length and the number of turns to calculate the total resistance of the winding. The window area and mean turn length may be entered in either units of inches or centimeters. Centimeter dimensions are converted to inch dimensions before storage within the program.

If the AWG is known and the overall wire diameter including the heavy insulation is desired, Eq. (3-2.1) can be rearranged to yield:

$$\text{diameter in inches} = a \cdot e^{(b \cdot \text{AWG})} \quad (3-2,3)$$

This equation is evaluated under label e.

INDUCTOR DESIGN - WIRE SIZE AND RESISTANCE				
window area, cm ²	mean turn length, cm	change # of turns	AWG → ohms inch	wire diam. — AWG
window area, in ²	mean turn length, in	calculate AWG	calculate winding R	AWG → wire diameter

STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
1	Load both sides of magnetic card			
2	Enter window area available for winding a) for dimensions in square inches b) for dimensions in square centimeters	A_w , in ² A_w , cm ²	<input type="checkbox"/> A <input checked="" type="checkbox"/> f <input type="checkbox"/> A	
3	Enter the length of a mean turn (a turn through the middle of the winding) a) for dimensions in inches b) for dimensions in centimeters	l_t , in l_t , cm	<input type="checkbox"/> B <input checked="" type="checkbox"/> f <input type="checkbox"/> B	
4	To change the number of turns, or to enter the number of turns if the previous program was not run	N	<input checked="" type="checkbox"/> f <input type="checkbox"/> C	
5	Calculate the wire AWG that will fill the window area. Heavy insulation (class 2) is assumed.		<input type="checkbox"/> D	AWG
6	Calculate the winding resistance in ohms		<input type="checkbox"/> D	R, ohms
7	To find the AWG given the wire diameter over heavy insulation in inches	D _w	<input checked="" type="checkbox"/> f <input type="checkbox"/> E	AWG
8	To find the wire diameter over heavy insulation given AWG	AWG	<input type="checkbox"/> E	D _w , in
9	To find the wire resistance per inch of annealed copper wire given AWG	AWG	<input checked="" type="checkbox"/> f <input type="checkbox"/> D	ohms/in

Program Listing I

Example 3-2.1

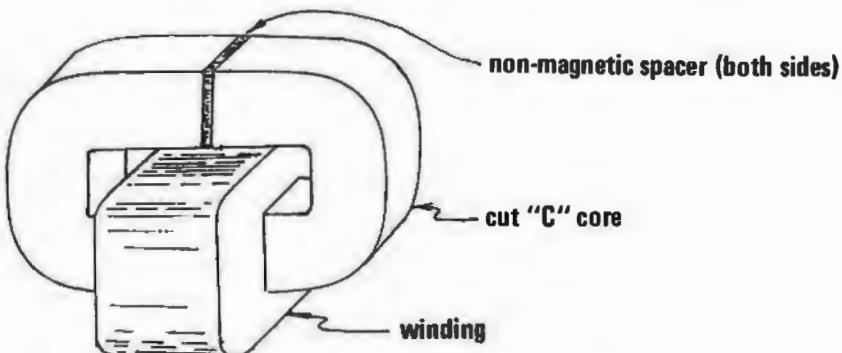


Figure 3-2.1 Inductor on cut C-core.

The inductor in Fig. 3-2.1 was designed to carry dc in Example 3-1.3. If the winding window area is 2 square inches, and the mean turn length is 6 inches, what wire size will fill the winding window, and what will be the total winding resistance?

2. GSB4 window area in square inches
 5. GSB5 mean turn length in inches
 5551 start wire size calculation
 12. *** wire size in AWG
 GSB0 start winding resistance calculation
 16.67+00 *** winding resistance in ohms

001 *LBL0 LOAD WINDOW AREA IN cm ²	057 *LBL4 print, spc, & eng3 subr									
002 F0? test for initialization	058 PRTX									
003 GSB2	059 SPC									
004 RCLI	060 ENG									
005 X ² convert area to inches ²	061 DSP3									
006 =	062 RTN									
007 *LBLA LOAD WINDOW AREA IN in ²	063 *LBL5 AWG to ohms/inch subroutine									
008 STOA store window area	064 GSB0 interchange registers									
009 F0? test for initialization	065 RCL3									
010 GSB2	066 X use Eq. (3-2.2) for									
011 RTN return control to keyboard	067 e ^x conversion									
012 *LBL6 LOAD MEAN TURN LENGTH IN cm	068 RCL2									
013 F0? test for initialization	069 X									
014 GSB2	070 GT01 test for register interchg									
015 RCLI convert length to inches	071 *LBL6 wire diameter to AWG subr									
016 =	072 GSB0 interchange registers									
017 *LBLB LOAD MEAN TURN LENGTH IN in	073 RCL0									
018 STOC store mean turn length	074 = use Eq. (3-2.1) for									
019 F0? test for initialization	075 LN conversion									
020 GSB2	076 RCL1									
021 RTN return control to keyboard	077 =									
022 *LBLc LOAD NUMBER OF TURNS CHANGE	078 .									
023 STO4 store new number of turns	079 5									
024 RTN	080 +									
025 *LBLc CALCULATE WIRE AWG	081 FIX									
026 RCLA calculate wire diameter:	082 DSP0									
027 RCL4	083 RND									
028 = d = $\sqrt{\frac{A_{\text{window}}}{n}}$	084 GT01 interchange registers									
029 IX	085 *LBL0 register interchange subr									
030 GSB6 calculate AWG from wire diam	086 F0? test for initialization									
031 EEX using Eq. (3-2.1)	087 GSB2									
032 +	088 P+S									
033 STOB	089 SF2									
034 GT04 goto print, space & dsp subr	090 RTN									
035 *LBLD CALCULATE WINDING RESISTANCE	NOTE: To change from the "print" to "R/S" mode for output, change the "print" statement at line 058 to a "R/S" statement.									
036 RCLB use Eq. (3-2.2) to calc										
037 GSB5 ohms/inch										
038 RCLC										
039 X multiply by total winding										
040 RCL4 length to get total										
041 X resistance										
042 GT04 print resistance										
043 *LBLd CONVERT AWG TO OHMS/INCH										
044 GSB5 perform conversion										
045 GT04 print result										
046 *LBLe CONVERT WIRE DIAMETER TO AWG										
047 GSB6 perform conversion										
048 GT04 print result										
049 *LBLf CONVERT AWG TO WIRE DIAMETER										
050 GSB0 interchange registers										
051 RCLI										
052 X use Eq. (3-2.3) for										
053 e ^x conversion										
054 RCL0										
055 X										
056 GSB1 interchange registers										
REGISTERS										
0	1	2	3	4	N	5	6	7	8	9
S0 .3137250775	S1 -.1097881513	S2 x10 ⁻⁶ 8.371747114	S3 .231765483	S4	S5	S6	S7	S8	S9	
A Window Area, in ²	B AWG	C Mean Turn, in	D	E	I 2.54					

Program Listing II

NOTE FLAG SET STATUS

LABELS						FLAGS			SET STATUS		
A load window area in in ²	B load mean turn in inches	C calculate AWG	D calculate Winding R	E AWG \rightarrow wire diam	F store constants	0	ON	OFF	DEG	TRIG	DISP
a load window area in cm ²	b Load mean turn in cm	c	d	e wire diam \rightarrow AWG	f	1			SCI		
0 PzS SF2	1 PzS if F2	2 Constant storage	3	4 Print & space	5 PzS used	2	1		RAD		
5 AWG \rightarrow Ω/in	6 wire diam \rightarrow AWG	7	8	9	3	3	2	■	ENG	n	0

PROGRAM 3-3 TRANSFORMER LEAKAGE INDUCTANCE AND WINDING CAPACITANCES.

Program Description and Equations Used

This program will calculate the leakage inductance and winding capacitances of a two winding transformer. Both the interwinding capacitance and winding self-capacitances are calculated. The output for both the leakage inductance and winding capacitances are reflected to the primary winding.

Leakage inductance. The total magnetic flux in a transformer is composed of the mutual flux and the leakage flux. The mutual flux follows the core path and links both primary and secondary windings, and results in the mutual, or open-circuit inductance of the transformer. The leakage flux is the relatively small flux which originates in the primary winding and does not link the secondary winding, or vice-versa, and results in the leakage inductance. The leakage flux will be less as the primary and secondary windings are interleaved up to the limit imposed by the space occupied by the insulation between windings. To a degree, the interleaving process is self-defeating, as too much interleaving generates much nonconductive space, and most of the leakage flux flows therein.

Of the many formulas that have been derived for the calculation of leakage inductance, the one by Fortescue [25] is generally accurate and errs, if at all, on the conservative side:

$$L_{\text{leak}} = 10.6 \times 10^{-9} \frac{N^2 \cdot MT(2nc + a)}{n^2 b} \quad (3-3.1)$$

where

L_{leak} = leakage inductance in henries, referred to the winding having N turns (the primary in this program)

MT = mean-turn length in inches for the whole coil (both windings)

n = number of dielectrics between windings

- a = winding buildup in inches
 b = winding traverse in inches
 c = dielectric thickness between windings in inches

Interleaving provides the greatest reduction in leakage inductance when the dielectric height, c , is small compared to the window height. When nc is comparable to the window height, the leakage inductance does not decrease substantially as the number of interleaves, n , is increased. The lowest leakage inductance will be obtained with a transformer having a small number of turns, a short mean turn length, and a low, wide winding window.

The term "a" in Eq. (3-3.1) refers to the total winding buildup composed of the primary buildup, the secondary buildup, and the insulation layers buildup. If a_p represents the buildup of all the primary interleaves, and a_s represents the buildup of all the secondary interleaves, then:

$$2nc + a = 3nc + a_p + a_s \quad (3-3.2)$$

The basis for Eq. (3-3.2) may be seen from Fig. 3-3.1.

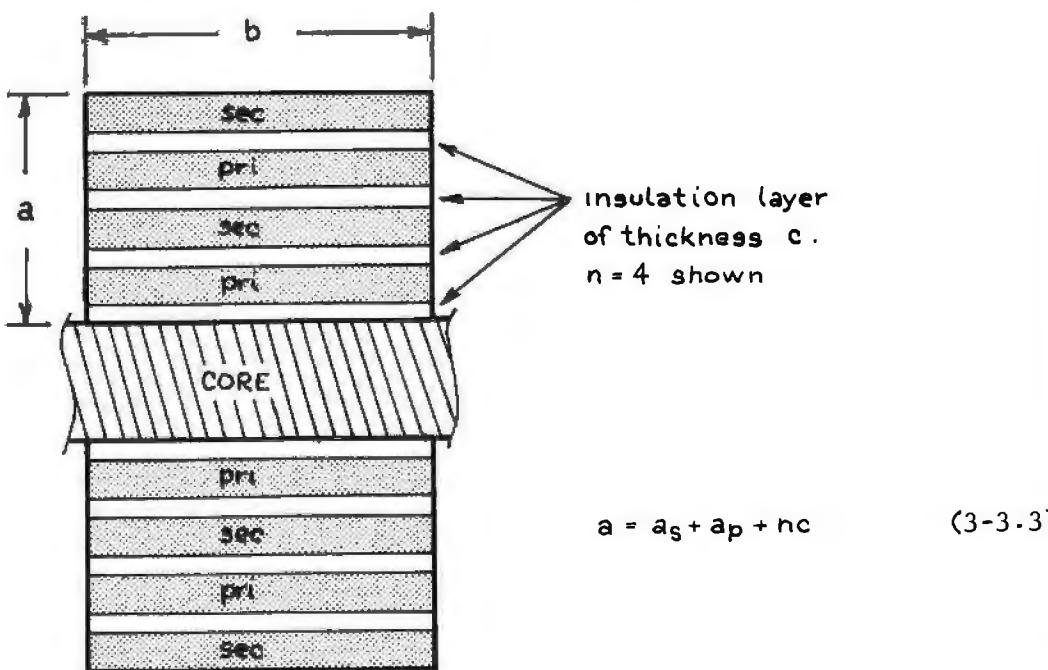


Figure 3-3.1 Cross-section of transformer winding on a core leg.

Interwinding capacitance. The interwinding capacitance is the primary-secondary capacitance. This capacitance is calculated by considering

the primary and secondary windings as single conducting sheets separated by the dielectric formed by the insulating layer and wire insulation. The capacitance of two flat plates separated by a dielectric is:

$$C = .225 \times 10^{-12} \epsilon \frac{A}{t} \quad (3-3.4)$$

where

ϵ is the relative dielectric constant of the dielectric
 A is the area of one plate in inches²
 t is the dielectric thickness in inches

For the transformer

$$A = n \cdot M \cdot b \quad (3-3.5)$$

and

$$t = c + t_{\text{primary wire insulation}} + t_{\text{secondary wire insulation}} \quad (3-3.6)$$

The wire insulation thickness for heavy insulation (heavy formvar, etc.) can be obtained from the wire AWG. The AWG is obtained from the wire diameter over class 2 insulation by using Eq. (3-2.1), where the wire diameter is calculated by assuming the wire plus insulation just fits in a box as shown by Fig. 3-6.2. The wire diameter over the insulation then becomes:

$$t_{\text{wire, primary}} = \sqrt{\frac{a \cdot b}{N_p}} \quad (3-3.7)$$

and

$$t_{\text{wire, secondary}} = \sqrt{\frac{a \cdot b}{N_s}} \quad (3-3.8)$$

The diameter of the bare wire is obtained from AWG by using Eq. (3-2.3). Hence, the thickness of the wire insulation is:

$$t_{\text{wire insulation}} = \frac{1}{2} (t_{\text{wire + insulation}} - t_{\text{wire}}) \quad (3-3.9)$$

The wire insulation thickness calculations are performed in the subroutine under label 6 in the HP-67/97 program.

Winding self-capacitance. In a multilayer winding, the voltage between layers is zero at one end of the layer, and $2E/N_L$ at the other where

E is the total winding voltage, and N_L is the number of layers. This voltage gradient model serves as the basis for the total winding capacity as given by Reuben Lee [36].

$$C_i = 1.333 \frac{C_{L_i}}{N_{L_i}} \left\{ 1 - \frac{1}{N_{L_i}} \right\} \quad (3-3.10)$$

$i = \text{pri or sec}$

C_{L_i} is the layer-to-layer capacitance, and is found from Eq. (3-3.4) where

$$A = MT \cdot b \quad (3-3.11)$$

and

$$t = t_d + 2t_{\text{wire insulation}} \quad (3-3.12)$$

The basis of Eqs. (3-3.11) and (3-3.12) are shown by Fig. 3-3.2.

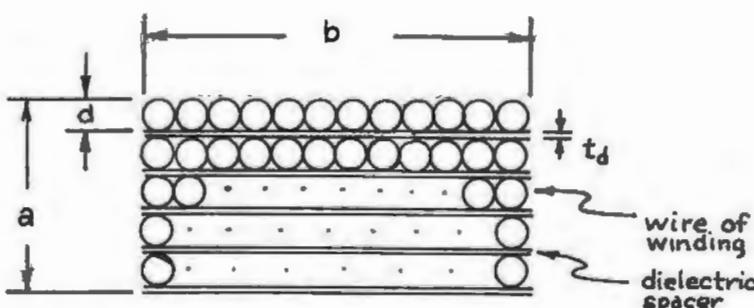


Figure 3-3.2 Cross-section of a winding showing dimensioning.

The number of layers is needed for Eq. (3-3.10) and is found from the number of turns, the interwinding dielectric thickness, and the winding dimensions. The wire cross-sectional area (per Fig. 3-6.2) and the dielectric cross-sectional area must equal the total area available for that winding, i.e.,

$$\frac{N_L}{L} (d + t_d) = a \quad (3-3.13)$$

$$\text{volume} = a \cdot b = \underbrace{N_L \cdot t_d \cdot b}_{\text{spacer volume}} + \underbrace{N \cdot d^2}_{\text{wire volume}} \quad (3-3.14)$$

Substituting Eq. (3-3.13) into (3-3.14) and solving for N_L yields:

$$N_{L_i} = \frac{N_i d_i}{b_i} \quad (3-3.15)$$

where d is the quadratic solution to:

$$N_i d_i^2 + (N_i t_{d_i})^{d_i} - a_i b_i = 0 \quad (3-3.16)$$

$i = \text{pri or sec}$

The program calculates the secondary winding capacity and reflects it to the primary winding:

$$C_{\text{sec}} @ \text{primary} = C_{\text{sec}} \cdot \left(\frac{N_s}{N_p} \right)^2 \quad (3-3.17)$$

The total winding capacity seen at the primary is the sum of the reflected secondary winding capacitance, and the primary winding capacitance.

3-3 User Instructions

TRANSFORMER LEAKAGE L AND WINDING C				
winding traverse	$N_p \uparrow N_s$	# of dielectrics	print?	Calculate Leakage C winding C interwinding
pri buildup \uparrow sec buildup	average mean turn length	$t_{dp} \uparrow t_{ds} \uparrow t_d$	$\epsilon_{pri} \epsilon_{sec} \epsilon_{sp}$	

STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
1	Load both sides of program card (note flag status)			
2	Load both sides of data card			
3	Select print or R/S option using toggle		f D f D f D :	0, R/S 1, print 0, R/S
4	Load winding traverse in inches	b, in	f A	
5	Load winding buildup in inches: a) primary buildup b) secondary buildup	a _p , in a _s , in	ENT ↑ A	
6	Load number of turns: a) primary turns	N _p	ENT ↑ f B	
7	load average mean-turn length for the whole transformer winding in inches	MT, in	B	
8	load the number of dielectrics	n	f C	
9	load dielectric thickness in inches: a) primary interwinding dielectric b) secondary interwinding dielectric c) primary-secondary dielectric	t _{dp} , in t _{ds} , in t _d , in	ENT ↑ ENT ↑ C	
10	Load relative dielectric constants: a) average for primary interwinding dielectric and wire insulation b) average for secondary interwinding dielectric and wire insulation c) primary-secondary spacer	ϵ_{pri} ϵ_{sec} ϵ_{sp}	ENT ↑ ENT ↑ D	

3-3 User Instructions

TRANSFORMER LEAKAGE L AND WINDING C				
		CONTINUED		

STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
11	Calculate L's and C's		E	
	Primary leakage inductance			L _{leak} , h
	Secondary wire AWG			space
	Number of secondary winding layers			AWG, sec
	Secondary winding C reflected to primary, F			# layers
	Primary wire AWG			0 _{sec@pri}
	Number of primary layers			space
	Primary winding capacity in farads			AWG, pri
	Total winding capacity reflected to primary			# layers
	primary-secondary interwinding capacitance, F			C _{primary}
				C _{total}
				space
				C _{pri-sec}
12	Data review: Go back and key any entry key without keying in any numeric entry to view the presently stored variable. See Example 3-3.1.			

Example 3-3.1

Find the primary leakage inductance and winding capacitances of a transformer having the following specifications:

traverse: 2"

number of pri-sec dielectrics: 4 (3 interleaves)

dielectric thickness: 0.050"

pri-sec insulator dielectric constant: 10

mean turn length for whole transformer: 5"

Primary

number of turns: 100

buildup: 0.25"

interwinding dielectric thickness: 0.002"

average interwinding dielectric and wire insulation
dielectric constant: 10

Secondary

number of turns: 1000

buildup: .0.3"

interwinding dielectric thickness: 0

average interwinding dielectric and wire insulation
dielectric constant: 5

HP printout for Example 3-3.1

2. GSBo winding traverse

.25 ENT† primary winding buildup
.3 GSBA secondary winding buildup

100. ENT† primary winding turns

1000. GSBB secondary winding turns

5. GSBB mean turn length for whole transformer

4. GSBo number of pri-sec dielectrics

.002 ENT† primary interwinding dielectric thickness
0. ENT† secondary interwinding dielectric thickness
.05 GSBC pri-sec dielectric thickness

10. ENT† average primary dielectric constant

5. ENT† average secondary dielectric constant

10. GSBD pri-sec dielectric, dielectric constant

GSBE calculate L's and C's
19.05-06 *** primary leakage inductance, henrys

24.00+00 *** secondary wire AWG
24.49+00 *** number of secondary layers
23.19-09 *** secondary interwinding C seen @ primary, F

14.00+00 *** primary wire AWG
6.972+00 *** number of primary layers
678.8-12 *** primary interwinding capacity, F
23.87-09 *** total interwinding capacity @ primary, F

1.699-09 *** pri-sec winding capacity, F

Program Listing I

Data Review printout for Example 3-3.1

GSBo
 2.000+00 *** traverse

 GSBA
 360.0-03 *** secondary winding buildup
 250.0-03 *** primary winding buildup

 GSBb
 1.000+03 *** secondary turns
 100.0+00 *** primary turns

 GSBB
 5.000+00 *** mean turn length

 GSBo
 4.000+00 *** number of dielectrics

 GSBC
 50.00-03 *** primary-sec dielectric thickness
 0.000+00 *** secondary interwinding dielectric thickness
 2.000-03 *** primary interwinding dielectric thickness

 GSBD
 10.00-00 *** pri-sec dielectric, dielectric constant
 5.000+00 *** secondary average dielectric constant
 10.00+00 *** primary average dielectric constant

001	*LBLA	I/O PRIMARY & SEC BUILDUP	057	GT08
002	EEY		058	*LBL2
003	GSB6		059	CFO
004	0		060	CLX
005	GT01		061	GT08
006	*LBLA	I/O WINDING TRAVERSE (b)	062	*LBLB CALCULATE L's & G's calculate leakage inductance
007	2		063	PZS
008	GT01		064	RCL4
009	*LBLB	I/O AVERAGE MEAN TURN (MT)	065	PZS
010	3		066	RCL4
011	GT01		067	RCL9
012	*LBL6	I/O PRIMARY AND SEC TURNS	068	=
013	5		069	X ²
014	GSB6		070	X
015	4		071	RCL3
016	GT01		072	X
017	*LBLC	I/O DIELECTRIC THICKNESSES	073	RCL9
018	8		074	$L_{\text{leak}} = \frac{10.6 N_o^2 \cdot MT \cdot (3n_c + d_p + d_s)}{10^9 n^2 b}$
019	GSB6	I/O pri-sec spacer thickness	075	X
020	7	I/O secondary intrawinding	076	3
021	GSB6	dielectric thickness	077	X
022	6	I/O primary intrawinding	078	RCL0
023	GT01	dielectric thickness	079	+
024	*LBLC	I/O NUMBER OF DIELECTRICS	080	RCL1
025	9		081	+
026	GT01		082	X
027	*LBLD	I/O DIELECTRIC CONSTANTS	083	RCL2
028	1	I/O dielectric constant	084	=
029	2	of pri-sec spacer	085	GSB3
030	GSB6		086	RCL1 calculate and store
031	1	I/O secondary insulation	087	RCL2 2-t wire, secondary
032	1	dielectric constant	088	X
033	GSB6		089	RCL5
034	EEX	I/O primary insulation	090	=
035	1	dielectric constant	091	RCL7
036	*LPL1	subroutine to I/O last item	092	GSB6
037	GSB6		093	STOB
038	GT08		094	RJ recover d/b
039	*LBL0	main I/O subroutine	095	RCL5 recall N _a
040	STOI	store index	096	GSB5 calc secondary capacitance
041	RJ	recover entry	097	PZS
042	F39	if flag 3, set flag 1	098	RCL1
043	SF1		099	PZS
044	F19	if flag 1, store entry	100	RCLB
045	STOI		101	RCL7
046	F19	if flag 1, recover	102	+
047	RJ	previous entry	103	GSB4
048	F19	if flag 1, return	104	X
049	RTN		105	RCL5 reflect secondary capaci-
050	RCLI	recall and print item	106	RCL4 tance to primary:
051	GT07		107	=
052	*LBLD	PRINT-R/S TOGGLE	108	X ²
053	F07		109	X
054	GT02		110	STOC
055	SF0		111	GSB3
056	EEY		112	RCL0
REGISTERS				
0 a _p , pri buildup	1 secondary buildup	2 b, winding traverse	3 MT, mean turn length	4 N _p
S0 ε _{pri}	S1 ε _{sec}	S2 ε _{spacer}	S3 225×10^{-15}	S4 10.6×10^{-9}
A 2x primary wire insulation thickness	B 2x secondary wire insulation thickness	C C sec, or d sec	S6 k ₁ = 3137250775	S6 k ₁ ' = .3245574964
			S7 k ₂ = -.1097881513	S8 k ₂ ' = -.01159489227
			D	E 1.33333 ...
				I Index or scratchpad

Program Listing II

NOTE FLAG SET STATUS

		LABELS		FLAGS		SET STATUS		
A I/o of pri & sec buildup	B I/o of mean turn length	C I/o of dielectric thick	D I/o of relative dielectric const	E calculate L & C's	0 print	FLAGS	TRIG	DISP
A I/o winding traverse	b I/o turns N _p , N _s	c I/o of # of dielectrics	d print or R/S toggle	e	0 input	0 ■	DEG	FIX
Q/I/o subroutine	I/O subroutine	2 print or R/S toggle	3 print or R/S and space	4 capacitance Subroutine	1 input	1 ■	GRAD	SCI
5 winding C subroutine	6 wire diameter	7 print or R/S subroutine	8 space & CF1, 5 subr	9	2 input	2 ■	RAD	ENG ■
					3 input	3 ■		n 3

```

113 RCL2 calculate and store
114 Y
115 RCL4 2. twire, primary
116 +
117 RCL6
118 GSB6
119 STD4
120 R+ calc primary capacitance
121 RCL4
122 GSB5
123 P+S
124 RCL0
125 P+S
126 RCLA
127 RCL6
128 +
129 GSB4
130 X
131 GSB7
132 RCLC calculate and print:
133 +
134 GSB3 Cpri = N2.0sec
135 RCL9 calculate interwinding cap.:
136 P+S
137 RCL2
138 P+S
139 X
140 RCLA
141 RCLB
142 +
143 2
144 =
145 RCL8
146 +
147 GSB4
148 *LBL3 print or R/S subroutine
149 GSB7
150 GT08
151 *LBL4 capacity subroutine
152 =
153 RCL3 MT
154 X
155 RCL2 b
156 X
157 P+S
158 RCL3 .225 x 10-12
159 P+S
160 X
161 RTN
162 *LBL5 intrawinding capacity subr
163 X
164 GSB7 calc and print # of layers
165 1/X
166 ENT1 calculate winding capacity
167 ENT1 terms

```

```

168 EEX
169 X#
170 -
171 X
172 RCL6
173 X
174 RTN
175 *LBL6 wire AWG and insulation thk.
176 2 calculate wire diameter:
177 +
178 STOJ
179 X2
180 +
181 JX
182 RCLI
183 -
184 STOI
185 RCL2 calculate d/b
186 =
187 RCLI calculate insulation thick.
188 RCLI calculate wire AWG
189 P+S
190 RCL5 k1
191 =
192 LN
193 RCL7 k2
194 =
195 ENT+
196 ENT+
197 EEX calculate and print
198 + integral wire size
199 INT
200 GSB7
201 R+
202 RCL8 calculate bare wire
203 Y diameter from AWG
204 ex
205 RCL6
206 P+S
207 X
208 -
209 RTN calculate 2.tinsulation
210 *LBL7 print or R/S subroutine
211 F0?
212 PRTEX
213 F0?
214 RTN
215 R/S
216 RTN
217 *LBL8 space and clear flag 3 subr
218 F0?
219 SPC
220 CF1
221 CF3
222 RTN
223 GT08

```

NOTE FLAG SET STATUS

PROGRAM 3-4 STRAIGHT WIRE AND LOOP WIRE INDUCTANCE.

Program Description and Equations Used

This program calculates the inductance of straight wire lengths and single square wire loops. The permeability of the wire is taken into account only for the inductance calculation, but not for skin depth; therefore, the inductance calculated is the low frequency inductance.

The calculation of wire inductance can be an important design parameter in some instances. For example, the bonding wire inductance of high speed, wideband hybrid integrated circuits affects circuit performance. Wire self-inductance is also important in the design of high frequency (1000 Hz), high power (megawatt) power conversion equipment such as SCR inverters, choppers, cycloconverters, and phase delay rectifiers.

The inductance of a straight wire increases with permeability and length, and decreases with increasing diameter. The combined effect of permeability, length, and diameter is not described simply, but can be easily solved with a scientific calculator. For example, the inductance of copper wire is strongly influenced by diameter while the inductance of a high permeability wire such as permalloy is relatively unaffected by diameter.

The formulas used herein come from Grover [30], and can also be found in Terman [52]. Two basic formulas are used, one for straight wire, and another for wire loops. These formulas are algebraically manipulated to obtain expressions for each of the four variables; wire diameter (d), wire length (l), relative permeability (μ), and inductance in μ H (L). The program works in the units of centimeters, but the user may input data in either inch or centimeter units.

Figure 3-4.1 shows the definitions of the wire terms.

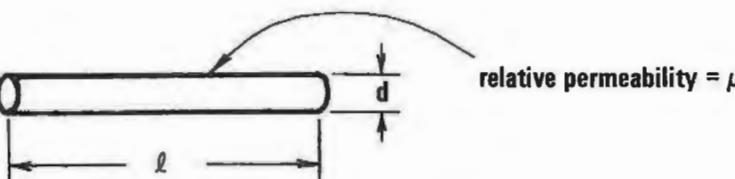


Figure 3-4.1 Straight wire terms.

The formulas for the straight wire case are:

$$L = (2 \times 10^{-3}) \ell \left\{ \ln\left(\frac{4\ell}{d}\right) + \frac{\mu}{4} - 1 \right\}, \mu\text{h} \quad (3-4.1)$$

$$d = \frac{4\ell}{e(L/(2\ell \times 10^{-3}) - \mu/4 + 1)} \quad (3-4.2)$$

$$\mu = 4 \left\{ \frac{L}{2\ell \times 10^{-3}} + 1 - \ln\left(\frac{4\ell}{d}\right) \right\} \quad (3-4.3)$$

To obtain the wire length, a Newton-Raphson iterative solution is employed (see Program 1-3 for details), because the equation for ℓ has a logarithm containing ℓ .

$$\ell = \frac{L}{(2 \times 10^{-3}) \left\{ \ln\left(\frac{4\ell}{d}\right) + \frac{\mu}{4} - 1 \right\}} \quad (3-4.4)$$

The Newton-Raphson solution finds where a function is zero, therefore, let:

$$f(\ell) = \ell - \frac{L}{(2 \times 10^{-3}) \left\{ \ln\left(\frac{4\ell}{d}\right) + \frac{\mu}{4} - 1 \right\}} = 0 \quad (3-4.5)$$

and

$$f'(\ell) = \frac{df(\ell)}{d\ell} = 1 + \frac{L}{(2 \times 10^{-3}) \ell \left\{ \ln\left(\frac{4\ell}{d}\right) + \frac{\mu}{4} - 1 \right\}} \quad (3-4.6)$$

The initial guess for ℓ is 1, and the ℓ value for each succeeding iteration is given by:

$$\ell_{i+1} = \ell_i - \frac{f(\ell_i)}{f'(\ell_i)} \quad (3-4.7)$$

The iteration is terminated when:

$$\left| \ell_{i+1} - \ell_i \right| < 10^{-6} \quad (3-4.8)$$

Figure 3-4.2 shows the definitions of the loop wire terms.

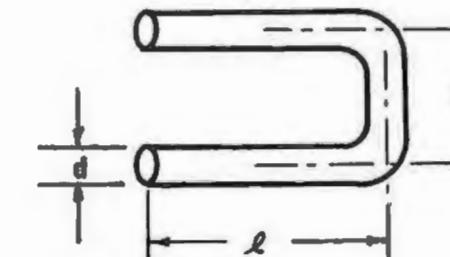


Figure 3-4.2 Loop wire terms.

The formulas for the loop wire case are:

$$L = (4 \times 10^{-3}) \ell \left\{ \ln\left(\frac{2D}{d}\right) + \frac{\mu}{4} - \frac{D}{\ell} \right\}, \mu\text{h} \quad (3-4.9)$$

$$d = \frac{2D}{e(L/(4 \times 10^{-3})\ell - \mu/4 + D/\ell)} \quad (3-4.10)$$

$$\ell = \frac{\frac{L}{4 \times 10^{-3}} + D}{\ln\left(\frac{2D}{d}\right) + \frac{\mu}{4}} \quad (3-4.11)$$

$$\mu = 4 \left\{ \frac{L}{4 \times 10^{-3}\ell} + \frac{D}{\ell} - \ln\left(\frac{2D}{d}\right) \right\} \quad (3-4.12)$$

Keys "a" through "d" set up the dimension units to be used for input or output (inches or centimeters), and the configuration (straight wire or loop wire). When the loop wire configuration is selected (key "c"), the loop separation, D , must also be entered via key "c."

Keys "A" through "D" provide the program input/output functions. Use of these keys following numeric input signals an input to the program. Use of these keys without numeric entry, or following the clear key (E) signals an output is required from the program. Flag 3 is used to indicate input or output within the program.

STRAIGHT WIRE AND LOOP WIRE INDUCTANCE				
centimeter units	inch units	wire loop, enter D	straight wire	
wire diam d	wire length <i>l</i>	permeability μ	inductance L	clear input mode

STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
1	Load both sides of data card			
2	Select dimension units a) centimeter units b) inch units		<input type="checkbox"/> f <input type="checkbox"/> A <input type="checkbox"/> f <input type="checkbox"/> B	1.000 2.540
3	Select configuration a) wire loop, load loop separation b) straight wire	D	<input type="checkbox"/> f <input type="checkbox"/> O <input type="checkbox"/> f <input type="checkbox"/> D	
4	To calculate wire diameter, d a) load wire length b) load wire permeability c) load required inductance d) start solution	ℓ μ $L, \mu\text{h}$	<input type="checkbox"/> B <input type="checkbox"/> C <input type="checkbox"/> D <input type="checkbox"/> A	d
5	To calculate wire length, ℓ a) load wire diameter b) load wire permeability c) load required inductance d) start solution execution	d μ $L, \mu\text{h}$	<input type="checkbox"/> A <input type="checkbox"/> C <input type="checkbox"/> D <input type="checkbox"/> B	ℓ
6	To calculate permeability, μ a) load wire diameter b) load wire length c) load required inductance d) start solution execution	d ℓ $L, \mu\text{h}$	<input type="checkbox"/> A <input type="checkbox"/> B <input type="checkbox"/> D <input type="checkbox"/> C	μ
7	To calculate inductance, L a) load wire diameter b) load wire length c) load permeability d) start solution execution	d ℓ μ	<input type="checkbox"/> A <input type="checkbox"/> B <input type="checkbox"/> C <input type="checkbox"/> D	$L, \mu\text{h}$
8	To clear input mode (reset flag 3)		<input type="checkbox"/> E	

Example 3-4.1

Find the inductance of a straight gold wire 0.001 inch in diameter and 0.3 inch long (a hybrid integrated circuit interconnect wire).

66E4	set inches
66E9	set straight wire mode
.001 66E4	load wire diameter in inches
.300 66E5	load wire length in inches
1.000 66E3	load wire relative permeability
66E8	calculate inductance
0.010 ***	inductance in microhenries

Example 3-4.2

Find the length of a 4/0 copper cable (.528 in diam) having an inductance of 6 microhenries

GSB_b set inches
GSPJ set straight wire mode
.528 GSBA load wire diameter
1.000 GSBC load relative permaability of wire
6.000 GSBD load required inductance
GSBB calculate wire length*
182.258 *** length, inches

12.000 ÷
15.158 *** length, feet

*Computation time takes about 1 minute.

Program Listing I

Example 3-4.3

A pair of 4/0 wires run 20 feet between a capacitor module and an inverter module in an ac traction motor controller. The wire separation is twice the wire diameter. What parasitic inductance does the wire add in series with the capacitors? 4/0 wire is .528 inches in diameter.

GSB6 .528 SETT 1.056 *** GSB6 .528 GSEA 20.000 ENT1 12.000 X 240.000 *** GSB5 1.000 GSBC GSED 3.373 ***	set inch mode calculate and enter the wire separation, and select wire loop configuration load wire diameter in inches calculate and load wire length in inches load permeability of wire calculate inductance of wire loop inductance, microhenries
---	---

If the maximum parasitic inductance that can be tolerated is 2 microhenries, how long can the feeder wires be if the other parameters don't change?

2.000 GSB0 GSBB 120.948 ***	load required inductance in μ H calculate loop length loop length, inches
-----------------------------------	---

12.000 X
10.873 *** loop length, feet

REGISTERS									
0 diameter cm	1 length cm	2 $\mu/4$	3	4 wire separation, cm	5 inductance L	6	7 scratch	$8 2 \times 10^{-3}$	$9 1 \text{ or } 2.54$
S0	S1	S2	S3	S4	S5	S6	S7	S8	S9
A	B	C	D	E	scratch	I	index		

```

001 *LBL0 SET CM UNIT MODE
002 EEX
003 ST09 store cm -> cm conversion
004 RTN
005 *LBLb SET INCH UNIT MODE
006 2
007 .
008 5 store in -> cm conversion
009 4
010 ST09
011 RTN
012 *LBLc LOAD WIRE LOOP SEPARATION
013 SF0 indicate wire loop mode
014 CF3
015 4 goto data entry subroutine
016 GT00
017 *LBLd SET STRAIGHT WIRE MODE
018 CF0 indicate straight wire mode
019 RTN
020 *LBLA I/O OF WIRE DIAMETER, d
021 2
022 EEX
023 CHS store 0.002
024 3
025 ST08
026 R↓ recover input
027 0
028 F3? if numeric input,
029 GT00 goto data input subroutine
030 F8? jump if wire loop mode
031 GT01
032 RCL1 calculate and store d for
033 4 straight wire case:
034 X
035 GSB6
036 +
037 RCL2  $d = \frac{4l}{\left(\frac{l}{2 \times 10^{-3}} - \frac{\mu}{4} + 1\right)}$ 
038 -
039 ex
040 ÷
041 ST08
042 GT07 goto unit conversion & print
043 *LBL1 calculate and store d for
044 GSB8 loop wire case
045 GSB6
046 X
047 2
048 ÷
049 -
050 ex
051 RCL4  $d = \frac{2D}{\left(\frac{l}{4 \times 10^{-3}} - \frac{\mu}{4} + \frac{D}{l}\right)}$ 
052 X
053 ENT1
054 +
055 ST00
056 GT07 goto unit conv and print
057 *LBLB I/O OF WIRE LENGTH, l
058 EEX
059 F3? if numeric input,
060 GT00 goto input subroutine
061 F0? jump if loop wire mode
062 GT01 store "1" for initial guess
063 ST01
064 *LBL4 Newton-Raphson loop start
065 RCL1
066 4 calculate and store f(l):
067 X
068 RCL0
069 ÷
070 LN
071 EEX
072 -  $\ln\left(\frac{4l}{d}\right) + \frac{\mu}{4} - 1$ 
073 RCL2
074 +
075 F2? test for subroutine exit
076 RTN
077 ST0E
078 RCL8 finish f(l) calculation
079 X
080 1/X
081 RCL5  $f(l) = l - \frac{L}{2 \times 10^{-3} \left\{ \ln\left(\frac{4l}{d}\right) + \frac{\mu}{4} - 1 \right\}}$ 
082 X
083 CHS
084 RCL1
085 +
086 ST07 calculate and apply f'(l):
087 RCL5
088 RCL8
089 RCL1
090 X
091 RCL6  $f'(l) = 1 + \frac{L}{(2 \times 10^{-3} l) \left\{ \ln\left(\frac{4l}{d}\right) + \frac{\mu}{4} - 1 \right\}^2}$ 
092 X2
093 X
094 ÷
095 EEX
096 +
097 ST=7 calculate correction
098 RCL7
099 ST-1 apply correction
100 ABS
101 EEX
102 CHS
103 6
104 X?Y?
105 GT04
106 RCL1
107 GT07 recall and print
108 *LBL1 calculate l for loop wire
109 RCL5
110 RCL8

```

Program Listing II

LABELS					FLAGS	SET STATUS								
A	d	B	l	C	μ	D	L	E	clear input	0	wire loop	FLAGS	TRIG	DISP
^a cm units	^b inch units	^c wire loop	^d straight wire	^e 0	^f 1					0	ON	DEG	FIX	■
⁰ data entry	¹ used	² output routine w/o unit conv	³ partial calc of loop wire μ	⁴ Newton - Raphson loop	⁵ subr 4 exit	⁶ 2	⁷ 3	⁸ 4	⁹ calc of ln(4a/D)μ/4-1	¹⁰ 1	OFF	GRAD	SCI	
5	6 calc L/(.002 l)	7 output routine w/ unit conv	8 calc of μ/4 - D/l	9 calc of ln(4a/D)μ/4-1	10 data entry	2	3	4	5	3	■	RAD	ENG	

```

111 ENT↑
112 +
113 ÷
114 RCL4
115 +
116 RCL4
117 ENT↑
118 +
119 RCL0
120 ÷
121 LN
122 RCL2
123 +
124 ÷
125 STO1 store l
126 *LBL7 unit conversion & prt subr
127 RCL9 recall unit conversion
128 ÷
129 *LBL2 print and space subroutine
130 PRTX -- can be R/S statement
131 SPC
132 RTN
133 *LBLC I/O OF PERMEABILITY, μ
134 4
135 ÷
136 RCL9
137 ÷ undo unit conversion
138 2
139 F3? if numeric input, goto
140 GT00 data input subroutine
141 F0? jump if wire loop mode
142 GT03
143 GSB6
144 +
145 RCL1 start calculation for
146 4 straight wire
147 GT01
148 *LBL3 loop wire calculation
149 GSB6
150 2 L
151 ÷ 4l × 10-3
152 RCL4
153 RCL1 D
154 ÷ l
155 +
156 RCL4 D
157 2
158 *LBL1 common calculation routine
159 ×
160 RCL0
161 ÷
162 LN
163 -
164 STO2 store μ/4
165 4
166 X calculate μ
167 GT02 goto print and space subr
168 *LBLD I/O OF INDUCTANCE, L
169 RCL9 undo unit conversion
170 ÷
171 5 if numeric input, goto
172 F3? data input subroutine
173 GT00
174 F0? jump if loop wire mode
175 GT03
176 SF2 calc: ln(4l) + μ/4 - 1
177 GSB4
178 GT01 jump
179 *LBL3 calculate:
180 RCL4
181 ENT↑
182 +
183 RCL0
184 ÷ 2 { ln(2D) + μ/4 - D/l }
185 LN
186 GSB8
187 +
188 ENT↑
189 +
190 *LBL1 common inductance calculation
191 RCL8
192 X × (2l × 10-3)
193 RCL1
194 X
195 STO5 store inductance
196 GT02 goto print and space subr
197 *LBL0 data input subroutine
198 STO1 store register index
199 R4 recover input
200 RCL9
201 X apply unit conversion and
202 STO1 store entry
203 RTN return to main program
204 *LBL6 subroutine to calculate:
205 EEX
206 RCL5
207 RCL8
208 ÷
209 RCL1
210 ÷
211 RTN
212 *LBL8 subroutine to calculate:
213 RCL2
214 RCL4
215 RCL1 μ
216 ÷ 4 - D/d
217 -
218 RTN
219 *LBL6 CLEAR INPUT MODE
220 CF3
221 RTN

```

PROGRAM 3-5 AIR-CORE SINGLE-LAYER INDUCTOR DESIGN.

Program Description and Equations Used

This program uses Wheeler's equation [55] to solve for the various parameters relating to single-layer, air-core inductor design. The basic form of Wheeler's equation is:

$$L(\mu\text{H}) = \frac{a^2 n^2}{9a + 10l} \quad (\text{use inch dimensions}) \quad (3-5.1)$$

This equation provides answers within 1% accuracy for all values of $2a/l$ less than 3, and the results will be about 4% low when $2a/l = 5$ (short coils).

There are five parameters that can be used to describe an air-core inductor: the coil radius in inches (a), the coil length in inches (l), the number of turns (n), the winding pitch ($p = l/n$), and the inductance in microhenries (L). Of this set of five parameters, only four are independent since l , n, and p are interrelated; hence, given any three independent parameters, the fourth independent parameter, and the remaining dependent parameter can be found. For example, L can be calculated given a, l, and n, or a, n, and p.

Wheeler's equation may be algebraically manipulated to yield the other independent variables.

Solving for l given a, n, and L:

$$l = \frac{a^2 n^2 - 9a L}{10 L} \quad (3-5.2)$$

Solving for l given n and p:

$$l = n \cdot p \quad (3-5.3)$$

Solving for n given a, l, and L:

$$n = \frac{1}{a} \sqrt{L(9a + 10l)} \quad (3-5.4)$$

Solving for n given a, p, and L: find quadratic solution of

$$a^2n^2 - 10Lpn - 9aL = 0 \quad (3-5.5)$$

Solving for p given ℓ and n:

$$p = \ell/n \quad (3-5.6)$$

Solving for p given a, n, and L:

$$p = \frac{1}{10n} \left\{ \frac{a^2n^2}{L} - 9a \right\} \quad (3-5.7)$$

Solving for L given a, n, and p:

$$L = \frac{a^2n^2}{9a + 10np} \quad (3-5.8)$$

Solving for a given ℓ , n, and L: find quadratic solution of

$$n^2a^2 - 9La = 10\ell L = 0 \quad (3-5.9)$$

The program uses these equations as follows. The appropriate input keys are assumed to have been executed prior to an output request. Label "A" inputs or outputs the coil radius in inches, a. The input is stored in R0, and Eq. (3-5.9) is used for output.

Label "B" inputs or outputs the number of turns, n. The input is stored in R1, and if p was previously entered, ℓ is calculated using Eq. (3-5.3). For output, Eq. (3-5.5) is used if p, ℓ , and a are specified, otherwise, Eq. (3-5.4) is used.

Label "C" inputs or outputs the coil length, ℓ . For input, the coil length is stored in R2, flag 0 is cleared, and a new p is calculated and stored using Eq. (3-5.6). For output, if p has been previously entered, use Eq. (3-5.3), otherwise use Eq. (3-5.2).

Label "D" inputs or outputs the winding pitch, p. For input, the new pitch is stored in R3, flag 0 is set, and new ℓ is calculated with Eq. (3-5.3). For output, Eq. (3-5.6) is used.

Label "E" inputs or outputs the coil inductance, L, in microhenries. For input, the value is stored in R4. For output, Eq. (3-5.1) is used, and the new inductance value stored.

Label "c" calculates the wire diameter given the wire AWG with heavy insulation. The wire diameter over heavy insulation bears an

exponential relationship to the wire gauge:

$$\text{Diameter (inches)} = k_1 \cdot e^{k_2 \cdot \text{AWG}} \quad (3-5.10)$$

where $k_1 = 0.31373$

and $k_2 = -.109788$

On the first execution of this routine, the constants k_1 and k_2 are stored into R8 and R9 respectively. Flag 2 is initially set after magnetic card reading to indicate constant storage required, and is reset upon test.

Label "d" calculates the AWG of the wire given the diameter over the insulation in inches:

$$\text{AWG} = \frac{1}{k_2} \cdot \ln \left\{ \frac{\text{Diameter}}{k_1} \right\} \quad (3-5.11)$$

Label "e" is used to clear flag 3 to indicate data output desired.

Keys "A" through "E" leave flag 3 cleared after the associated routine finishes, i.e., data output mode is set unless further numeric entry is made.

The routines under keys "d" and "e" do not alter the state of flag 3. For example, one may load the wire AWG, use key "c" to convert to wire diameter, and then use key "D" to load this value as the winding pitch (close wound coils).

Highest coil Q's are generally obtained when the space between the wires equals the wire diameter (pitch equals twice the wire diameter). Callendar's equation [13] can be used to estimate the Q of a coil with this pitch:

$$Q = \frac{\sqrt{\text{freq in Hz}}}{\frac{2.71}{a} + \frac{2.13}{\ell}} \quad (\text{use inch dimensions}) \quad (3-5.12)$$

For RF coils where the skin depth is less than the wire diameter, Callendar's equation is accurate to within a few percent. For close wound coils, the calculated Q will be high by a factor of 1.9.

HP-67 users may want to make the following program changes to make the final number in the display unambiguous. For example, label "C" causes both the number of turns and the coil length to be printed


User Instructions

with the coil length being displayed last. To change the program so only the number of turns is displayed and printed, change lines 122 through 126 of the program as follows:

```


122 RCL3
123 x
124 ST0E
125 RCL1
126 GT0E

```

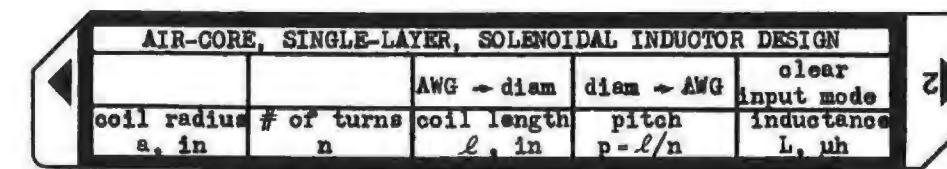

STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
1	Load both sides of program card			
2	Select problem type:			
a)	to find L & p given a, n, & l			
i)	load the coil radius	a, in	A	
ii)	load the number of turns	n	B	
iii)	load the coil length	l, in	C	
iv)	calculate the coil inductance		E	L, μ H
v)	calculate the winding pitch		D	p, in/T
b)	to find L & l given a, n, & p			
i)	load the coil radius	a, in	A	
ii)	load the number of turns	n	B	
iii)	load the winding pitch	p, in/T	D	
iv)	calculate the coil inductance		E	L, μ H
v)	calculate the coil length		C	l, in
c)	to find n & p given a, l, & L			
i)	load the coil radius	a, in	A	
ii)	load a dummy value for n*	l	B	
iii)	load the winding length	l, in	C	
iv)	load desired inductance	L, μ H	E	
v)	calculate the # of turns and the winding pitch		B	n, turns p, in/T
d)	to find n & l given a, n, & L			
i)	load the coil radius	a, in	A	
ii)	load the winding pitch	p, in/T	D	
iii)	load desired inductance	L, μ H	E	
iv)	calculate the number of turns and the winding length		B	n, turns l, in
e)	to find l & p given a, n, & L			
i)	load the coil radius	a, in	A	
ii)	load the desired number of turns	n	B	
iii)	load the desired inductance	L, μ H	E	
iv)	calculate the inductor length **		C	l, in
v)	calculate the winding pitch		D	p, in/T

User Instructions

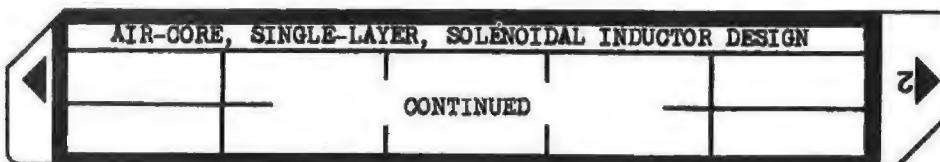

STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
2	f) to find a & ℓ given n , p , & L			
	i) load the desired number of turns	n	B	
	ii) load the desired winding pitch	p , in/T	D	
	iii) load the desired inductance	L , μ h	E	
	iv) calculate the coil radius		A	a , in
	v) calculate the coil length		C	ℓ , in
	g) to find a & p given n , ℓ , & L			
	i) load the desired number of turns	n	B	
	ii) load the desired coil length	ℓ , in	C	
	iii) load the desired inductance	L , μ h	E	
	iv) calculate the coil radius		A	a , in
	v) calculate the winding pitch		D	p , in/T
3	Go back to any part of step 2, or stop			
4	To convert wire AWG to diameter over heavy (class 2) insulation	AWG	f O	diam, in
5	To convert wire diameter over heavy insulation to AWG	diam, in	f D	AWG
6	To clear input mode, i.e., to request output after numeric operations have been performed from the keyboard		f E	
	Notes:			
	* $p = \ell/n$, a non-zero n is required for proper program operation. The dummy n is replaced with the calculated n under label B.			
	** A negative value for the inductor length means the required inductance cannot be realized with the chosen radius and number of turns. Either increase n or a .			

Example 3-5.1

An air-core coil is to be wound in a $\frac{1}{2}$ inch form using #18 AWG HF wire at a pitch of twice the wire diameter. What number of turns are required for an inductance of 500 nanohenry (0.5μ h), and what will the winding length be?

.250 GSER	load coil radius in inches
18.000 GSBe	load wire AWG
0.043 ***	wire diameter over HF insulation
2.000 GSED	calculate winding pitch ($2 \times$ diam)
.500 GSBE	load winding pitch
GSBB	load required inductance in microhenry
8.958 ***	calculate turns and coil length
0.776 ***	number of turns (use 9 turns)
	coil length in inches

Example 3-5.2

A 6 turn coil on a 6 inch form is closewound with #4/0 wire. The wire is 0.750 inches over the insulation. What is the coil inductance and length?

3.000 GSBA	load the coil radius in inches
6.000 GSBE	load the number of turns
.750 GSBD	load winding pitch
GSBE	calculate inductance
4.500 ***	inductance in microhenries
GSEC	calculate coil length
4.500 ***	coil length in inches

Program Listing I

001	*LBLA	I/O OF COIL RADIUS, a	→ 053	*LBL1	calculate and store
002	F3?	jump if numeric entry	054	RCL1	
003	GT08		055	RCL3	$\ell = n(\ell/n)$
004	RCL1		056	x	
005	X2	use quadratic equation	057	ST02	
006	ST05	to find a in:	058	GT08	
007	9		059	*LBL0	goto print and space subr
008	RCL4	$a^2n^2 - 9aL - 10\ell L = 0$	060	F3?	I/O OF COIL PITCH, p
009	x		061	GT08	jump if numeric entry
010	CHS		062	RCL2	calculate and store
011	ST06		063	RCL1	
012	RCL2		064	÷	$p = \ell/n$
013	RCL4		065	ST03	
014	x		066	GT08	goto print and space subr
015	EEX		067	*LBL0	
016	1		068	ST03	store p
017	x		069	RCL1	calculate and store
018	CHS		070	x	$\ell = p \cdot n$
019	ST07		071	ST02	
020	GSB9	gosub quadratic solution	072	SF0	indicate p entered last
021	ST08	store a	073	RTN	
022	GT08	goto print & space subr	074	*LBLB	I/O OF COIL TURNS, n
023	*LBL0	coil radius data input	075	F3?	jump if numeric entry
024	ST00	store coil radius	076	GT08	
025	RTN	return control to keyboard	077	F0?	jump if p entered last
026	*LBL0	I/O OF COIL LENGTH,	078	GT01	
027	F3?	jump if numeric entry	079	GSB3	
028	GT08		080	RCL4	
029	F0?		081	x	
030	GT01	jump if p entered last	082	÷X	
031	RCL0	calculate and store:	083	RCL0	
032	RCL1		084	÷	$n = \frac{1}{a} \sqrt{L(9a - 10\ell)}$
033	x		085	ST01	
034	X2		086	PRTX	
035	RCL4		087	1/X	
036	÷		088	RCL2	
037	RCL0	$\ell = \frac{1}{10} \left(\frac{a^2 n^2}{L} - 9a \right)$	089	x	
038	9		090	ST03	
039	x		091	GT08	
040	-		092	*LBL1	calculate and store n from
041	EEX		093	RCL0	quadratic solution to:
042	1		094	X2	
043	÷		095	ST05	
044	ST02		096	RCL3	
045	GT08	goto print and space subr	097	RCL4	
046	*LBL0		098	x	
047	CFO	indicate ℓ entered last	099	EEX	
048	ST02	store ℓ	100	1	
049	RCL1	calculate and store	101	x	
050	÷		102	CHS	
051	ST03	$p = \ell/n$	103	ST06	
052	RTN		104	RCL0	
			105	RCL4	
			106	x	
					$a^2 n^2 - 10Lpn - 9aL = 0$

REGISTERS

REGISTERS															
0	a	i	n	2	ℓ	3	p	4	L	quadratic	equation	terms	wire	AVNG	constants
S0	S1		S2		S3		S4			5 a	6 b	7 c	8 k ₁	9 k ₂	
A	B		C		D		E		I						

Program Listing II

NOTE FLAG SET STATUS

107	9		160	*LBL3	9a + 10ℓ calculation subr
108	x		161	RCL0	
109	CHS		162	9	
110	ST07		163	x	
111	GSB9		164	RCL2	
112	ST01		165	EEX	
113	PRTX		166	1	
114	RCL3		167	x	
115	x		168	+	
116	ST02		169	RTN	
117	GT08				
118	*LBL0		170	*LBL0	<u>AWG → WIRE DIAMETER</u>
119	ST01	<u>store number of turns</u>	171	F2?	<u>constant initialization</u>
120	F0?	<u>jump if p entered last</u>	172	GSB2	<u>needed?</u>
121	GT00		173	RCL9	
122	RTN		174	x	
123	*LBL0		175	e ^x	$\text{diameter} = k_1 \cdot e^{k_2 \cdot \text{AWG}}$
124	RCL3	<u>calculate and store new</u>	176	RCL8	
125	x	<u>coil length</u>	177	x	
126	ST02		178	GT08	
127	RTN				
128	*LBL1	<u>I/O OF INDUCTANCE, L (μh)</u>	179	*LBL1	<u>WIRE DIAMETER → AWG</u>
129	F3?	<u>jump if numeric entry</u>	180	F2?	<u>constant initialization</u>
130	GT00		181	GSB2	<u>needed?</u>
131	RCL0		182	RCL8	
132	RCL1	<u>use Wheeler's equation</u>	183	=	
133	x	<u>to calculate inductance</u>	184	LH	
134	x ²	<u>(Eq. (3-5.1)):</u>	185	RCL9	$\text{AWG} = \frac{1}{k_2} \ln \left\{ \frac{\text{diameter}}{k_1} \right\}$
135	GSB3	$L = \frac{a^2 n^2}{9a + 10L}$	186	=	
136	=		187	INT	
137	ST04		188	GT08	
138	*LBL2	<u>print and space subroutine</u>	189	*LBL2	<u>constant initialization</u>
139	PRTX		190	.	
140	SPC		191	3	
141	RTN		192	1	
142	*LBL0		193	3	
143	ST04	<u>store inductance input</u>	194	0	
144	RTN		195	4	
145	*LBL9	<u>quadratic equation solution</u>	196	ST08	<u>store k₁</u>
146	RCL5	<u>subroutine.</u>	197	R4	<u>recover x register</u>
147	ST=6		198	.	
148	ST=7	<u>If ax² + bx + c = 0</u>	199	1	
149	2		200	0	
150	ST=6	<u>then the positive root is:</u>	201	9	
151	RCL6		202	7	
152	CHS		203	3	
153	ENT↑	$x = -\frac{b}{2a} + \sqrt{\frac{b^2}{4a^2} + \frac{c}{a}}$	204	3	
154	x ²		205	CHS	
155	RCL7		206	ST09	<u>store k₂</u>
156	-		207	R4	<u>recover x register</u>
157	JX		208	RTN	
158	+				
159	RTN		209	*LBL1	<u>CLEAR INPUT MODE</u>
			210	CF3	
			211	RTN	

NOTE: Print statements are located at steps 086 and 139 and may be changed to R/S if desired. **NOTE FLAG SET STATUS**

LABELS

LABELS						FLAGS	SET STATUS		
A I/O coil radius	B I/O coil length	C I/O # of turns	D I/O pitch	E I/O inductance	F entered last	FLAGS	TRIG	DISP	
a	b	c	d	e	1	ON 0	DEG	FIX	
0 local label	1 Local Label	2 constant storage	3 $9a + 10b$	4	2 store coefficients	OFF 1	GRAD	SCI	
5	6	7	8 print & space	9 quadratic solution	3 data entry	RAD 2	RAD	ENG	
						3	n 3		

PROGRAM 3-6 AIR-CORE MULTILAYER INDUCTOR DESIGN.

Program Description and Equations Used

This program uses a modification of Bunet's formula [11], Eq. (3-6.1), to design air-core, multilayer solenoidal inductors (inch dimensions).

$$L \text{ } (\mu\text{H}) = \frac{a^2 n^2}{9a + 10l + 8.4c + 3.2 c l/a} \quad (3-6.1)$$

The coil dimensions are shown in Fig. 3-6.1, and the range of usefulness of the program can be ascertained from Table 3-6.1.

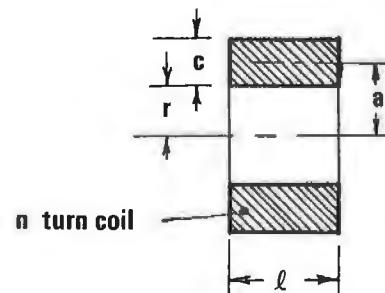


Figure 3-6.1 Multilayer coil dimensions.

Table 3-6.1 Accuracy estimates for Bunet's equation.

c/a ratio	2a/l ratio for 1% accuracy	other accuracies 2a/l %
1/20	≤ 3	5 4
1/5	≤ 5	10 2
1/2	≤ 2	5 3
1/1	≤ 1.5	5 5

The modification to Eq. (3-6.1) consists of replacing the mid-coil radius, a , by the inner radius, r :

$$a = r + \frac{c}{2} \quad (3-6.2)$$

The coil is generally wound on a coil form, hence, r and ℓ are known from the coil form dimensions. The coil mid-radius, a , is dependent upon the coil buildup, and is generally not known at the inception of the design.

If the wire and insulation occupy a box as shown in Fig. 3-6.2,

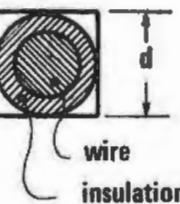


Figure 3-6.2 Wire cross-section.

then the total area occupied by n turns of this wire would be:

$$A_{\text{total}} = n \cdot d^2 \quad (3-6.3)$$

This area is also expressible in terms of the coil dimensions:

$$A_{\text{total}} = c \cdot \ell \quad (3-6.4)$$

Hence,

$$n \cdot d^2 = c \cdot \ell \quad (3-6.5)$$

or

$$c = \frac{n \cdot d^2}{\ell} \quad (3-6.6)$$

A fifth order polynomial in n may be derived to yield the number of turns of wire with diameter d , given the required inductance, L , the coil inner radius, r , and the coil width, ℓ . Taking Eq. (3-6.1), multiplying both sides by the denominator term, and clearing fractions yields:

$$a^3 n^2 - L \{ 9a^2 + (10\ell + 8.4c) a + 3.2c\ell \} = 0 \quad (3-6.7)$$

Substituting Eq. (3-6.2) for a , and Eq. (3-6.6) for c , and collecting terms in like powers of n results in the following 5th order polynomial equation:

$$f(n) = An^5 + Bn^4 + Cn^3 + Dn^2 - En - F = 0 \quad (3-6.8)$$

$$A = \left(\frac{d^2}{2\ell} \right)^3 \quad (3-6.9)$$

$$B = 3r \left(\frac{d^2}{2\ell} \right)^2 \quad (3-6.10)$$

$$C = 3r^2 \left(\frac{d^2}{2\ell} \right) \quad (3-6.11)$$

$$D = r^3 - \left(\frac{d^2}{2\ell} \right)^2 (25.8 L) \quad (3-6.12)$$

$$E = L \left\{ \frac{d^2}{2\ell} (34.8r + 10\ell) + 3.2d^2 \right\} \quad (3-6.13)$$

$$F = rL (10\ell + 9r) \quad (3-6.14)$$

The Newton-Raphson iterative procedure described in Program 1-3 is used to find the largest positive real root for n in Eq. (3-6.8). If the initial guess for n is larger than the largest root, the method will converge to the largest root when the function is a polynomial as in the present case. An initial guess of 10000 turns is used. If a larger number of turns is expected, the user may want to increase the initial guess which is located at step 084 of the program.

If r , c , ℓ , and L are specified, then the solution for n becomes somewhat simpler. Since r and c are both known, a can be calculated from Eq. (3-6.2). With this calculation, all parameters except n are known in Eq. (3-6.1), and n becomes:

$$n = \frac{1}{a} \left\{ L(9a + 10 + c(8.4) + 3.2\ell/a) \right\}^{1/2} \quad (3-6.15)$$

Once n has been calculated, the wire diameter, d , can be calculated from Eq. (3-6.6) as given below:

$$d = \sqrt{\frac{c\ell}{n}} \quad (3-6.16)$$

So far, the two cases for the number of turns have been derived. Likewise, there are two cases for the calculation of L . Given r , ℓ , c , and n , Eqs. (3-6.2) and (3-6.1) may be used to calculate L . If the wire diameter, d , had been specified instead of the coil thickness, c , then



User Instructions

Eqs. (3-6.6) and (3-6.1) are used to calculate L.

Program constants

Since all program steps were used to code the program equations, no room remains for the program constants. These constants are recorded on another magnetic card, and are loaded after the program magnetic card loading. Load the following registers, and record the data on both sides of the data card (2 WDATA commands):

8.4 → R7
3.2 → R8
0.0 → R9

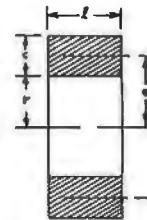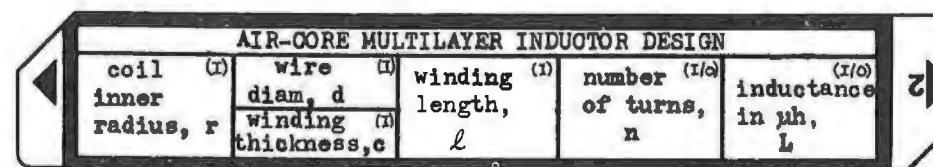

Program Listing I

Example 3-6.1

Find the number of turns of #24 HF wire (0.0224 inches over insulation) to be wound on a bobbin that has a 0.3 inch inner radius and is 0.5 inch wide to obtain an inductance of 200 microhenries. Also find the coil thickness.

.30 GSB4 load bobbin inner radius (in)

.0224 GSB4 load wire diameter over insulation (in)

.50 GSB1 load bobbin width (in)

200.00 GSB4 load inductance required (μh)

GSB5 calculate # of turns & coil thickness*

122.65 *** number of turns (use 123)

0.1231 *** coil thickness, inches

Example 3-6.2

Calculate the inductance of an 18 turn coil of 4/0 wire with 6 turns per layer wound on a 6 inch diameter form. 4/0 wire is 0.75 inch over the insulation.

3.00 GSB4 load coil inner radius (in)

.75 GSB4 load wire diameter over insulation (in)

6.00 calculate coil width:

4.50 *** coil turns per layer x thickness per turn

GSB4 load coil width

18.00 GSB4 load number of turns

GSB4 calculate inductance

50.6345 *** inductance in microhenries

001	*LBLA	LOAD COIL INNER RADIUS	057	058	8
002	ST01		059	RCL1	calculate and store n ¹ coef
003	GT09		060	x	
004	*LBLB	LOAD COIL THICKNESS	061	RCL9	
005	SF0	indicate thickness loaded	062	RCL3	
006	ST02	store thickness	063	GSB4	
007	GT09	goto OF3, space & return	064	RCLI	$E = L \left\{ \frac{d^2}{2\ell} (34.8r + 10\ell) + 3.2d^2 \right\}$
008	*LBLK	LOAD WIRE DIAMETER	065	x	
009	CF0	indicate wire diam. loaded	066	RCL8	
010	ST06	store wire diameter	067	RCL6	
011	GT09	goto OF3, space & return	068	X ²	
012	*LBLC	LOAD WINDING LENGTH	069	GSB4	
013	ST03	store	070	RCL4	
014	GT09	goto OF3, space, & return	071	x	
015	*LBLD	I/O OF COIL TURNS	072	ST0E	
016	F3?	if input, jump	073	RCL9	
017	GT00		074	RCL3	
018	F0?	if coil thickness loaded,	075	x	calculate and store n ⁰ coef
019	GT01	use other routine	076	9	
020	RCL6	calculate n given r, ℓ, d, and L	077	RCL1	
021	X ²		078	GSB4	
022	RCL3		079	RCL4	
023	ENT↑		080	RCL1	
024	+	calculate and temporarily	081	GSB5	
025	÷	store d ² /(2ℓ)	082	ST01	
026	ST01		083	EEX	setup initial guess for n
027	3	calculate and store n ⁵ coef	084	4	in Newton-Raphson soln
028	Y ^x	$A = \{d^2/(2\ell)\}^3$	085	ST05	Newton-Raphson start
029	ST0A		086	*LBL8	
030	RCLI		087	RCL5	
031	X ²	calculate and store n ⁴ coef	088	ENT↑	
032	RCL1		089	ENT↑	
033	3	$B = 3r \left(\frac{d^2}{2\ell} \right)^2$	090	ENT↑	
034	GSB5		091	RCLA	calculate and store
035	ST0B		092	x	$f(n_i) = An_i^6 + Bn_i^4 + Cn_i^3 + Dn_i^2 - En_i - F$
036	RCLI	calculate and store n ³ coef	093	RCLB	
037	RCL1		094	+	
038	X ²		095	x	
039	3	$O = 3r^2 \left(\frac{d^2}{2\ell} \right)$	096	RCLC	
040	GSB5		097	+	
041	ST0C		098	x	
042	RCLI		099	RCLD	
043	3		100	+	
044	Y ^x	calculate and store n ² coef	101	x	
045	2		102	RCLE	
046	5		103	-	
047	.	$D = r^3 \left(\frac{d^2}{2\ell} \right)^2 (25.8 \cdot L)$	104	x	
048	8		105	RCLI	
049	RCLI		106	-	
050	X ²		107	ST02	
051	RCL4		108	CLX	
052	GSB5		109	RCL5	calculate
053	-		110	RCLA	$f'(n_i) = 5An_i^5 + 4Bn_i^3 + 3Cn_i^2 + 2Dn_i - E$
054	ST0D		111	5	
055	3		112	GSB5	
056	4				
		REGISTERS			
0	a	1 r	2 c	3 ℓ	4 L
S0	S1	S2	S3	S4	S5
A	A	B	B	C	C
5	n	6 d	7 8.4	8 3.2	9 10
S6	S7	S8	S9		
D	D	E	E	I	F

* Requires about a minute to compute.

Program Listing II

```

113 RCLB
114   4
115   X
116   +
117   X
118 RCLC
119   3
120   X
121   +
122   X
123 RCLD
124 ENT†
125   +
126   +
127   X
128 RCLE
129 -
130 ST=2 calc & store f(n1)/f'(n1)
131 RCL2 apply correction:
132 ST=5 n1+1 = n1 - f(n1)/f'(n1)
133 ABS
134 . test for loop exit
135   1
136 X?Y?
137 GT08
138 RCL6
139 X2
140 RCL5 can be R/S statement
141 PRTX print n
142 X
143 RCL3 calculate, print and store
144 ÷ coil thickness, c:
145 ST02 c = nd2/l
146 GT02
147 *LBL0 input storage routine for
148 ST05 number of turns input
149 GT09 goto CF3, space and return
150 *LBL1 calculate the number of turns
151 GSB3 given r, l, c, and L
152 RCL4
153 X
154 JX n =  $\frac{1}{a} \left\{ L(9a + 10l + 8.4c + 3.2 \frac{cl}{a}) \right\}^{\frac{1}{2}}$ 
155 RCL0
156 ÷
157 ST05
158 PRTX can be R/S statement
159 1/X
160 RCL2
161 RCL3
162 GSB5
163 JX
164 ST06
165 GT02
166 *LBL2 I/O OF INDUCTANCE
167 ST04 store inductance entry
168 F3?

LABELS
A Load inner radius
B Load winding thickness
C Load winding Length
D I/o number of turns
E I/o inductance
F Set for winding thickness
G Flags
H Set Status
I Trig
J Disp

0 local Loop destination
1 Local Label
2 print & space subroutine
3 Inductance subroutine
4 X, + subroutine
5 X, X subroutine
6 Space & rtn subroutine
7 turns subroutine
8 data entry
9 space & rtn subroutine
10 data entry
11 data entry
12 data entry
168 data entry
169 GT09 jump if input
170 F0? if winding thickness loaded,
171 GT01 skip thickness calculation
172 RCL6
173 X2 calculate and store
174 RCL3 thickness:
175 ÷
176 RCL5 c = nd2/l
177 X
178 ST02
179 *LBL1
180 GSB3 calculate and store
181 1/X inductance:
182 RCL0
183 RCL5 L =  $\frac{a^2 n^2}{9a + 10l + 8.4c + 3.2 cl/a}$ 
184 X
185 X2
186 X
187 ST04
188 *LBL2 print and space subroutine
189 DSP4
190 PRTX ← can be R/S statement
191 DSP2
192 *LBL3 OP3 and space subroutine
193 CF3
194 SPC
195 RTN
196 *LBL4 inductance factor
197 RCL1 calculation subroutine
198 RCL2
199 2 calculate and store:
200 ÷ a = r + c/2
201 +
202 ST00
203 9
204 X
205 RCL3 calculate:
206 RCL9
207 GSB4 9a + 10l + 8.4c + 3.2  $\frac{cl}{a}$ 
208 RCL7
209 RCL8
210 RCL0
211 ÷
212 RCL3
213 GSB4
214 RCL2
215 *LBL5 X, + subroutine
216 X
217 +
218 RTN
219 *LBL6 X, X subroutine
220 X
221 X
222 RTN

```

PROGRAM 3-7 CYLINDRICAL SOLENOID DESIGN.

Program Description and Equations Used

This program provides the coil winding particulars and the coil electrical characteristics given the specifications for a cylindrical solenoid. These specifications are:

- 1) Minimum plunger attractive force in pounds (F),
- 2) Initial air gap length in inches (l_{air}),
- 3) Maximum flux density in the air gap (B_{max}) in gauss,
- 4) Maximum coil current density in amperes/in² (Δ),
- 5) Maximum coil buildup, or thickness, (w) in inches,
- 6) Coil excitation voltage (E) in volts, or current (I) in amperes,
- 7) Optionally, the magnetic path area (A_{iron}) in inches², the magnetic path length (l_{iron}) in inches, and the magnetic permeability (μ).

The length of the magnetic path is assumed to be zero unless step 7 is exercised.

The characteristics that the program calculates are:

- 1) Plunger diameter in inches (D_p),
- 2) Number of turns in the coil (N),
- 3) Coil wire AWG using class 2 or heavy insulation,
- 4) Coil length in inches (l_{coil}),
- 5) Coil inductance in henries (L),
- 6) Coil resistance in ohms (R),
- 7) Coil power dissipation in watts (P),
- 8) Actual B in the core and in the air-gap, and
- 9) Actual F.

With the maximum flux density in the air gap and plunger attractive force specified, the area of the air gap can be calculated from:

$$A_{air} = F \cdot k_1 / (B_{air}^2) \quad (3-7.1)$$

where k_1 is the constant of proportionality relating flux density in the air gap to pressure in pounds/in²

$$k_1 = 1.73 \times 10^6 \quad (3-7.2)$$

If the plunger area is assumed equal to the air gap area, the plunger diameter can be calculated using:

$$D_p = 2 \cdot \left(\frac{A_{air}}{\pi} \right)^{\frac{1}{2}} \quad (3-7.3)$$

Once the plunger diameter is known, then a value for the winding thickness may be loaded into the program. The smallest dimension of the winding should not exceed 3 inches to allow adequate thermal conduction for the heat generated with the coil, thus avoiding high internal coil temperatures. If the program calculates a short coil length, then the thickness is not restrained. A long coil restrains the coil thickness to 3 inches or less. Several iterations of the program solution may be required until satisfactory values for coil length and width (thickness) are found.

Given the excitation voltage, inverse current density in the coil (M) in circular mils per ampere, and the coil dimensions as defined by Fig. 3-7.1, the number of turns required is given by Eq. (3-7.4). The derivation of this equation is given later.

$$N = E \cdot M / (\pi (D_p + w)) \quad (3-7.4)$$

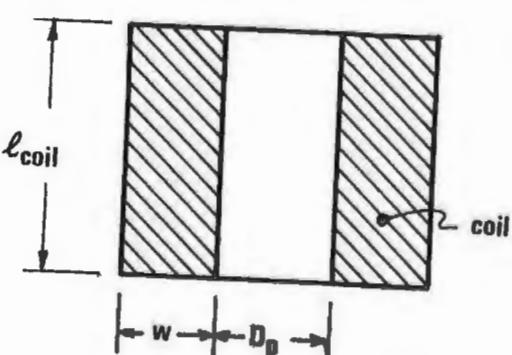


Figure 3-7.1 Solenoid coil dimensions.

If the coil is excited with a current, then the number of turns is:

$$N = (NI)/I \quad (3-7.5)$$

where NI is the coil ampere-turns which is calculated from B_{max} later.

The cross-sectional area of the coil ($w \cdot l_{coil}$) consists of current carrying wire and noncurrent carrying insulation and space. The shape factor (sf) is the ratio of the current carrying area to the total area of the coil. If the wire plus insulation is assumed to occupy a square with side d as shown in Fig. 3-6.2, and the winding cross-section is occupied by N of these squares, then the shape factor is:

$$sf = \frac{\pi}{4} \left\{ \frac{\text{diameter of bare wire}}{d} \right\}^2 \quad (3-7.6)$$

The diameters of both the bare wire and the wire with insulation bear exponential relationships to the wire AWG as given by Eq. (3-2.1). Substituting these relationships into Eq. (3-7.6) yields:

$$sf = \frac{\pi}{4} \left\{ \frac{a'}{a} e^{AWG(b' - b)} \right\}^2 \quad (3-7.7)$$

where

$$\frac{\pi}{4} \left\{ \frac{a'}{a} \right\}^2 = .8418900745 \quad (3-7.8a)$$

$$2(b' - b) = -1.21690938 \times 10^{-2} \quad (3-7.8b)$$

The coil has N wires each carrying in current, I ; thus the current density in the coil is:

$$\Delta = (NI)/(sf \cdot l_{coil} \cdot w) \quad (3-7.9)$$

where Δ is specified by the user through M :

$$k_2 = M \cdot \Delta = (\text{cir-mils}/A)(A/\text{in}^2) = (4 \times 10^6)/\pi \quad (3-7.10)$$

Solving for the coil length between Eqs. (3-7.9) and (3-7.10) yields:

$$l_{coil} = (NI \cdot M) / (sf \cdot k_2 \cdot w) \quad (3-7.11)$$

The coil ampere-turns, NI , is calculated from B_{max} using the "Ohm's law" of magnetics:

$$\text{MMF} = \phi \cdot R \quad (3-7.12)$$

where ϕ is the flux and is continuous throughout the magnetic and air paths and is analogous to electric current. The reluctance, R , is the magnetic resistance, and the magnetomotive force, MMF, is the magnetic "voltage" source. The total reluctance is the sum of the individual reluctances making up the magnetic circuit and the MMF is proportional to the current in the coil:

$$\text{MMF} = 0.4\mu NI \quad (3-7.13a)$$

$$R = \sum_i \frac{\ell_i}{\mu_i A_i} \quad (3-7.13b)$$

The electromagnet model used by this program has two sections, the magnetic path, and the air gap. Usually the air gap reluctance is the dominant term. Noting that the relative permeability for air is unity, and

$$\phi = B_{\text{iron}} A_{\text{iron}} = B_{\text{max}} A_{\text{air}} \quad (3-7.14)$$

then solving Eq. (3-7.12) for NI yields:

$$NI = \frac{B_{\text{max}} A_{\text{air}}}{A_{\text{iron}}} \left\{ \frac{\ell_{\text{iron}}}{\mu_{\text{iron}}} + \ell_{\text{air}} \frac{A_{\text{iron}}}{A_{\text{air}}} \right\} \frac{k_3}{0.4\pi} \quad (3-7.15)$$

where $k_3 = 2.54$, the inch to centimeter conversion ratio. The iron area, A_{iron} , refers to the smallest iron area, which may not be next to the air gap.

An iterative method is required to find the wire AWG and coil length. An initial shape factor of 0.5 is assumed, the coil length is obtained using Eq. (3-7.11). The wire diameter over insulation is obtained using

$$d = (w \cdot \ell_{\text{coil}} / N)^{1/2} \quad (3-7.16)$$

The wire AWG is obtained from the wire diameter over insulation from Eq. (3-2.1), and a new shape factor calculated from the AWG using Eq. (3-7.7). The new shape factor replaces the old shape factor and the calculations run again. The iteration is terminated when the new and old shape factors agree within .001.

The coil physical dimensions and number of turns have now been

determined, and other electrical characteristics can be calculated.

$$L = \frac{0.4\pi \cdot N^2 \cdot A_{\text{iron}} \cdot k_3 \times 10^{-8}}{\ell_{\text{iron}} + \ell_{\text{air}} \frac{A_{\text{iron}}}{A_{\text{air}}}} \quad (3-7.17)$$

$$R = (R/\ell) (\text{mean turn}) (N) \quad (3-7.18)$$

where R/ℓ is obtained from:

$$R/\ell, (\text{ohms/inch}) = k_4 \cdot e^{k_5 \cdot \text{AWG}} \quad (3-7.19)$$

hence,

$$R = N \cdot \pi \cdot (D_p + w) \cdot k_4 \cdot e^{k_5 \cdot \text{AWG}} \quad (3-7.20)$$

For the coil temperature at 60°C, the constants are:

$$\pi \cdot k_4 = 2.9185212367 \times 10^{-5}$$

$$k_5 = 0.2317635483$$

If the coil excitation is a constant voltage, then the coil current will have to be recalculated due to the downward rounding of the wire size to the nearest integral value:

$$I = \frac{E}{R} \quad (3-7.21)$$

The power dissipated in the coil is:

$$P = I^2 R \quad (3-7.22)$$

If constant voltage excitation is used, the peak flux density (B_{max}) and initial plunger attractive force will be slightly larger than the initial values again due to the downward rounding of the wire AWG. The larger wire will have lower resistance causing higher coil current and a higher NI product. Equations (3-7.15) and (3-7.1) are rearranged and used to find B_{iron} and F .

$$B_{\text{iron}} = \frac{0.4\pi NI}{\left\{ \frac{\ell_{\text{iron}}}{\mu_{\text{iron}}} + \ell_{\text{air}} \frac{A_{\text{iron}}}{A_{\text{air}}} \right\} k_3} \quad (3-7.23)$$

$$F = \frac{B_{\max}^2 \cdot A_{\text{air}}}{k_1} = \frac{(B_{\text{iron}} \cdot A_{\text{iron}})^2}{k_1 \cdot A_{\text{air}}} \quad (3-7.24)$$

In addition to the program card, a data card is necessary to load the registers with these constants:

μ_0 default:	500	→ R ₅
B_{\max} default:	15000	→ R ₆
Initial shape factor:	0.5	→ R _E
$(\pi/4)(a'/a)$:	0.8418900745	→ S ₀
$2(b' - b)$:	$-1.216909380 \times 10^{-2}$	→ S ₁
a:	$3.130387015 \times 10^{-1}$	→ S ₂
b:	$-1.097333787 \times 10^{-1}$	→ S ₃
$\pi \cdot k_4$:	$2.985212367 \times 10^{-5}$	→ S ₄
k_5 :	$2.317635483 \times 10^{-1}$	→ S ₅
k_3 :	2.54	→ S ₆
$k_2 = \frac{4}{\pi} \times 10^6$:	1.273239545×10^6	→ S ₇
k_1 :	1.73×10^6	→ S ₈
M default:	1000	→ S ₉

If the user wants to work in centimeter units instead of inch units, then a different set of constants can be loaded. All constants are the same except for the following:

a:	$7.951183018 \times 10^{-1}$	→ S ₂
$\pi \cdot k_4$:	$1.175280459 \times 10^{-5}$	→ S ₄
k_3 :	1.0	→ S ₆
k_2 :	5.012754114×10^5	→ S ₇
k_1 :	1.11613×10^7	→ S ₈

The inverse current density, M, is now in hybrid units. The circular-mils/A must be multiplied by 2.54 before entry, and the current density, Δ, is in A/cm². The plunger attractive force is still in pounds. If this force is desired in kilograms, change k₁ as follows:

$$k_1: \quad 2.46064 \times 10^7 \rightarrow S_8$$

stop at the data output points, change the "print" statements to "R/S" statements at the following line numbers: 047, 084, 131, 144, 160, 176, 180, 185, and 194.

3-7 User Instructions

CYLINDRICAL SOLENOID DESIGN							
Bmax in air gap	air gap	I	Liron Airon	I	+ Volts or I - Amps	load M	I/A air mils
Force, lbs	I	calculate pole diameter	I	winding width	I	M A	calculate coil design and electrical parameters

STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
1	Load both sides of program card and both sides of data card			
2	Load force required (in pounds) at maximum air gap (plunger all the way out)	F	A	
3	Load maximum flux in the iron (gauss) and the air gap in inches	B _{max} l _{air}	ENT f A	
4	Optional, load magnetic circuit parameters: a) load magnetic path length b) load magnetic path minimum area c) load relative permeability	l _{iron} , in A _{iron} , in ² μ	ENT ENT f B	
	If this step is not executed, the program will use A _{iron} = A _{air} and l _{iron} = 0			
5	Calculate pole diameter To change the pole diameter, change B _{max} , a larger B _{max} will result in a smaller pole. B _{max} is material dependent, and generally should not exceed 15000 gauss.		B	pole diameter in inches
6	Load winding thickness	w, in	C	
7	Load excitation voltage or current a) excitation voltage b) excitation current (note neg value)	E, V -I, A	f C f C	
8	Load a value for M, the inverse coil current density in circular-mils per ampere. If no value is loaded, a default value of 1000 will be used. Execution of this step without numeric entry causes currently stored value to be printed and displayed.	M	f D	M Δ

User Instructions

CYLINDRICAL SOLENOID DESIGN

CONTINUED

Example 3-7.1

Figure 3-7.2 shows a plunger-type, iron-clad cylindrical solenoid. Design the solenoid to have a 1 inch travel and exert an initial pull of 500 pounds when connected to a 55 volt dc source. The initial flux density in the iron shall be 7000 gauss, and the coil inverse current density shall be 700 circular-mils/A. Assume all the reluctance to be in the air gap.

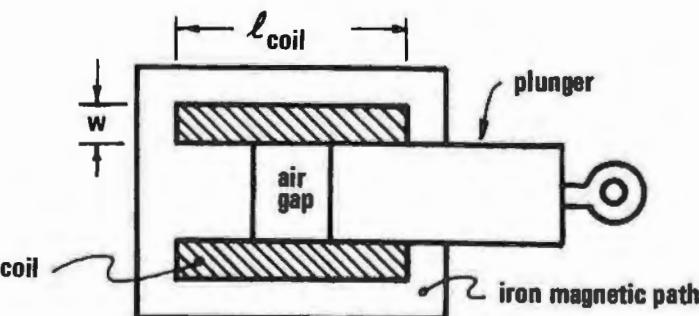


Figure 3-7.2 Plunger-type, iron-clad cylindrical solenoid.

```

500.00 GSBI load initial force required in pounds (F)
7000.00 ENT1 load maximum B field in gauss ( $B_{max}$ )
1.00 GSBA load  $\ell_{air}$ 
6855 calculate plunger diameter required ( $D_p$ )
4.74 *** plunger diameter in inches

5.00 GSBC load winding width in inches (w)
55.00 GSBD load excitation voltage in volts (E)
700.00 GSBD load inverse current density, M, in cir-mils/A
700.00 *** M
1815.51 ***  $\Delta$ , A/in2

GSBE calculate coil design and electrical parameters
1563.00 *** N, the number of turns
12.00 *** AWG of wire with heavy or class 2 insulation
3.57 *** coil length in inches ( $\ell_{coil}$ )
1.41 *** coil inductance in henries (L)
5.98 *** coil resistance in ohms (R)
512.43 *** coil power dissipation in watts (P)
7296.69 *** actual maximum flux density in the iron
7296.69 ***  $B_{max}$ , the flux density in the air gap
543.26 *** F, the plunger attractive force actually achieved

```

Example 3-7.2

A small solenoid is needed which has 0.050 inch travel, exerts an initial pull of 5 pounds, and is used intermittently with a 0.10 duty cycle. The coil excitation current is 3 A, and an initial flux density of 6000 gauss is to be used. Because of the intermittent duty cycle, an M of 100 cir-mils/A is used. The magnetic path is 1.5 inches long, has a cross-sectional area of 0.4 inch², and has a relative permeability of 500. Investigate the solenoid design with and without consideration for the magnetic path reluctance. A much more thorough analysis can be done with Program 3-8.

```

5.000 GSBI load initial force required in pounds (F)
6000.000 ENT1 load maximum flux density in gauss ( $B_{max}$ )
.050 GSBC load initial air gap in inches ( $\ell_{air}$ )
GSBF calculate plunger diameter in inches ( $D_p$ )
0.553 ***  $D_p$ 

.250 GSBC load winding width in inches (w)
-3.000 GSBD load excitation current in A (-I)
100.000 GSBD load inverse current density in cir-mils/A (M)
100.000 *** M
12732.395 ***  $\Delta$ , A/inch2

GSBE calculate coil design etc. without considering iron path
202.000 *** the number of turns (N)
25.000 *** AWG of coil wire with heavy insulation
6.308 *** coil length in inches ( $\ell_{coil}$ )
0.006 *** coil inductance in henries (L)
1.598 *** coil resistance in ohms (R)
14.311 *** coil power dissipation in watts (P)
5996.237 *** maximum flux density in the iron, gauss
5996.237 ***  $B_{max}$ , maximum flux density in the air gap, gauss
4.994 *** actual initial force, F, in pounds

Rerun program with magnetic (iron) path considered

1.500 ENT1 load magnetic path length in inches
.400 ENT1 load magnetic path area in inches2
500.000 GSBIk load relative magnetic permeability

GSBE calculate coil design and electrical parameters
209.000 *** N
25.000 *** AWG
0.319 ***  $\ell_{coil}$ 
0.006 *** L
1.645 *** R
14.807 *** P
3597.060 *** B in iron area defined
5988.202 *** B in air gap and in iron pole pieces
4.980 *** F

```

Derivation of Equations Used. The number of coil turns can be calculated from the applied voltage, the desired inverse current density, and the coil inner diameter and thickness. Conveniently, copper has a resistance of 1 ohm per circular mil per inch of length at 60°C; therefore, with a uniform coil temperature of 60°C, the wire resistance is:

$$R = \frac{\ell_w}{M} \quad (3-7.24)$$

where ℓ_w is the winding wire length in the coil in inches, and m is the wire cross-sectional area in circular mils. If M is defined as the inverse current density in circular-mils/A, then the cross-section of a wire carrying a current I is:

$$m = M \cdot I \quad (3-7.25)$$

Since

$$R = \frac{E}{I}, \text{ (Ohm's law)} \quad (3-7.26)$$

then

$$\frac{E}{I} = \frac{\ell_w}{M \cdot I} \quad (3-7.27)$$

Rearranging Eq. (3-7.27) and cancelling I yields:

$$E = \frac{\ell_w}{M} \quad (3-7.28)$$

The winding wire length can be found by multiplying the mean turn length by the number of turns:

$$\ell_w = N \cdot \pi \cdot (D_p + w) \quad (3-7.29)$$

where Fig. 3-7.1 defines the coil dimensions D_p and w . Substituting Eq. (3-7.29) into Eq. (3-7.28) and solving for N yields:

$$N = \frac{E \cdot M}{\pi(D_p + w)} \quad (3-7.30)$$

The best reference on the subject known to the author is rather old [47] since it was first published in 1924.

Program Listing I

001	*LBLA	LOAD FORCE REQUIRED	056	X
002	ST07		057	RCL3
003	RTN		058	=
004	*LBLB	LOAD B_{max} & ℓ_{air}	059	GSB9
005	ST05		060	=
006	R↓		061	ST0A
007	ST08		062	RCL9
008	GT05	goto CF3 and return subr	063	X<0?
009	*LBLB	CALCULATE POLE DIAMETER, D_p	064	GT00
010	RCL7		065	P2S
011	RCL8		066	RCL9
012	X ²		067	P2S
013	÷	$A_{air} = \frac{F \cdot k_1}{B_{air}^2}$	068	X
014	P2S		069	RCLD
015	RCL8		070	RCL0
016	P2S		071	+
017	X		072	Pi
018	ST06	store air gap area	073	X
019	F1?	minimum magnetic area equals	074	÷
020	ST03	aerogap area if flag 1 is set	075	GT01
021	4		076	*LBL0
022	X		077	RCLA
023	Pi	$D_p = \sqrt{\frac{4 \cdot A_{air}}{\pi}}$	078	X ² Y
024	÷		079	=
025	JX		080	CHS
026	ST0D	store pole diameter	081	*LBL1
027	GT04	goto prt, spc, & OF3 subr	082	INT
028	*LBL6	LOAD liron & Airon & μ	083	ST01
029	CF1	indicate magnetic path used	084	PRTX
030	ST04		085	*LBL7
031	R↓		086	RCLA
032	ST03	store data	087	RCLE
033	R↓		088	=
034	ST02		089	RCL0
035	RTN		090	=
036	*LBLC	LOAD WINDING WIDTH, w	091	P2S
037	ST06		092	RCL9
038	RTN		093	X
039	*LBLc	LOAD COIL EXCITATION,	094	RCL7
040	ST09	+E, or -I	095	P2S
041	GT05	goto CF3 and return subr	096	=
042	*LBLC	I/O OF CIRCULAR-MILS/AMP, M	097	ST01
043	P2S	interchange registers	098	RCLI
044	F3?	store input if present	099	1/X
045	ST09		100	RCL0
046	RCL9	recall and print M	101	X
047	PRTX		102	RCL1
048	RCL7	calculate and print Δ :	103	X
049	X ² Y	$\Delta = \frac{M}{k_2}$	104	JX
050	÷		105	P2S
051	P2S		106	RCL2
052	GT04	goto prt, spc, & OF3 subr	107	=
053	*LBLB	CALCULATE MAIN OUTPUT	108	LN
054	RCL8		109	RCL3
055	RCL6		110	=
REGISTERS				
0	w	¹ ℓ_{coil}	² ℓ_{iron}	³ A_{iron}
S0	$\frac{\pi}{4} \left(\frac{a'}{a} \right)^2 S_1 2(b' - b)$	S2 a	S3 b	S4 $\pi \cdot k_4$
A	N_I, I	B AWG	C R	D D_p
				E sf
				F I N
				G $k_3 = 2.54$
				H $k_2 = \frac{4 \times 10^6}{\pi}$
				I $k_1 = 1.73 \times 10^6$
				J M

Program Listing II

NOTE FLAG SET STATUS

111	STOE		166	*LBL0	calculate and print coil power dissipation using Eq. (3-7.21):
112	RCL1	calculate shape factor using Eq. (3-7.7):	167	ABS	
113	x		168	STOA	
114	e ^x		169	X ²	
115	RCL0	$sf = \frac{\pi}{4} \left(\frac{a'}{a}\right)^2 e^{AWG \cdot 2(b' - b)}$	170	RCLC	$P = I^2 R$
116	P ² S		171	x	
117	x		172	PRTX	
118	RCL0	recall old sf and store new sf	173	GSB9	calculate and print new B_{iron} using Eq. (3-7.22):
119	X ² Y		174	RCLA	$B_{iron} = \frac{0.4\pi NI}{k_3}$
120	STOE		175	x	$\frac{l_{iron}}{\mu_{iron}} + \frac{l_{air} \cdot A_{iron}}{A_{air}}$
121			176	RCLI	
122	ABS		177	x	
123	EEX	test for loop exit	178	PRTX	
124	CHS		179	RCL3	calculate and print:
125	3		180	x	
126	X ² Y?		181	RCL6	$B_{max} = \frac{B_{iron} \cdot A_{iron}}{A_{air}}$
127	GT07		182	÷	
128	RCLB		183	PRTX	
129	INT	print & store integral AWG	184	X ²	calculate and print new F using Eq. (3-7.23):
130	STOB		185	RCL6	$F = \frac{B_{max}^2 \cdot A_{air}}{k_4}$
131	PRTX		186	x	
132	RCL1	recall and print the number of turns indicate k ₃ on top	187	P ² S	
133	PRTX		188	RCL8	
134	SF2		189	P ² S	
135	GSB9	calculate and print inductance using Eq. (3-7.17)	190	÷	
136	RCLI		191	*LBL4	print, spc, CF3 subroutine
137	X ²		192	PRTX	
138	x		193	SPC	
139	RCL3	$L = \frac{0.4\pi \cdot N^2 \cdot A_{iron} \cdot k_3 \cdot 10^{-8}}{l_{iron} + l_{air} \cdot A_{iron}}$	194	*LBL5	CF3 and return subroutine
140	x		195	CF3	
141	EEX		196	RTN	
142	8		197	*LBL9	magnetics subroutine to calculate:
143	÷		198	RCL2	
144	PRTX		199	RCL4	
145	RCLB	calculate and print resistance using Eq. (3-7.20)	200	÷	
146	P ² S		201	RCL5	
147	RCL5		202	RCL3	$\frac{0.4\pi}{l_{iron} + l_{air} \cdot A_{iron}} \cdot k_3(F2-1)$
148	x		203	x	
149	e ^x		204	RCL6	$\frac{l_{iron}}{\mu_{iron}} + \frac{l_{air} \cdot A_{iron}}{A_{air}} \cdot k_3(F2-0)$
150	RCL4		205	÷	
151	P ² S	$R = N\pi(D_p + w) k_4 e^{k_5 \cdot AWG}$	206	+	
152	x		207	1/X	
153	RCLD		208	7	generates 0.4π in 3 steps
154	RCL0		209	2	
155	+		210	D+R	
156	x		211	x	
157	RCL1		212	P ² S	
158	x		213	RCL6	
159	STOC		214	P ² S	
160	PRTX		215	F2?	
161	RCL9		216	1/X	
162	X<0?	test for current excitation	217	÷	
163	GT00		218	RTN	
164	RCLC	calculate current using Ohm's law			
165	÷				
NOTE FLAG SET STATUS					
LABELS		FLAGS	SET STATUS		
^a load F	^b calc D _p	^c load w	^d load M	^e basic coil & elec params	0
^a B _{max} t air gap	^b l _{iron} t A _{iron} t μ	^c load +E, -I	^d	^e 1 magnetic path data not loaded	
⁰ Local label	¹ Local label	²	³	⁴ output routine order	1 magnetic path data not loaded
⁵ CF3, RTN	⁶	⁷ SF iteration routine	⁸	⁹ subroutine	2 conversion order
				³ data entry	3 data entry n=2
FLAGS TRIG DISP					
0	ON OFF	DEG ■	FIX ■		
1	■	GRAD RAD	SCI ENG		
2	■				
3	■				

PROGRAM 3-8 CYLINDRICAL SOLENOID ANALYSIS.

Program Description and Equations Used

This program analyzes a cylindrical coil solenoid, or other magnetic circuits having many parts of varying reluctance. The information required to run the program is as follows:

- 1) The air gap in inches (l_{air}),
- 2) The number of turns in the coil (N),
- 3) The AWG of the coil wire,
- 4) The length of the coil in inches (l_{coil}),
- 5) The coil inner diameter in inches (ID_{coil}),
- 6) The plunger outer diameter in inches (OD_p),
- 7) The plunger inner diameter in inches if the plunger is hollow (ID_p),
- 8) The length, area, and permeability of each different magnetic section (l_{iron} , A_{iron} , μ),
- 8a) If the magnetic section is a cylindrical shell with axial flux flow, the height (h), the ID which may be zero, the OD, and the permeability (μ), can be entered, and the reluctance and cross-sectional area will be returned and automatically loaded into the program,
- 8b) If the magnetic section consists of a disc (or washer) with radial flux flow, the thickness (t), the ID, the OD, and the permeability can be entered, and the reluctance and minimum cross-sectional area will be returned and automatically loaded into the program, and
- 9) The coil excitation in either volts or amperes (E or -I).

The program will then calculate the following parameters:

- 1) Reluctance and area of each different magnetic section (μ & A_{iron}),
- 2) Coil inductance and resistance (R and L),
- 3) Coil circular-mils/A, A/in², and power dissipation M, Δ , & P),
- 4) The flux density in the air gap, and in the magnetic section with the smallest cross-sectional area (B_{air} , B_{iron}), and
- 5) The plunger attractive force in pounds (F).

This program uses the Ohm's law of magnetics as given by Eqs. (3-7.12) and (3-7.13), which combined yield:

$$0.4\pi NI = \emptyset \cdot \sum_i \frac{\ell_i}{\mu_i A_i} \quad (3-8.1)$$

As magnetic path data is entered, the program keeps a running sum of the reluctances, $\frac{\ell_i}{\mu_i A_i}$, and also stores the smallest magnetic area. The iron part will saturate first where the area is the smallest, and the flux density (B) the highest. The total flux can be found from Eq. (3-8.1):

$$\emptyset = \frac{0.4\mu N I k_3}{\sum_i \frac{\ell_i}{\mu_i A_i} + \frac{\ell_{air}}{A_{air}}} \quad (3-8.2)$$

where

$$A_{air} = \frac{\pi}{4} (OD_p^2 - ID_p^2) \quad (3-8.3)$$

$$k_3 = 2.54$$

The plunger attractive force is found in terms of the flux:

$$F = \frac{\emptyset^2}{k_1 \cdot k_3 \cdot A_{air}} \quad (3-8.4)$$

where the air gap area is in inches² and the constant k_1 is:

$$k_1 = 1.73 \times 10^6$$

The inductance of the N turn coil wound on the magnetic circuit is:

$$L = \frac{N^2 k_3}{10^8} \left\{ \frac{0.4\pi}{\sum_{iron} \frac{\ell_i}{\mu_i A_i} + \frac{\ell_{air}}{A_{air}}} \right\} \quad (3-8.5)$$

This expression is basically derived in Eqs. (3-1.1) through (3-1.10).

The coil width (w) can be expressed in terms of the coil length (ℓ_{coil}), the number of turns (N), and the wire AWG. The wire is assumed to occupy a box as shown in Fig. 3-6.2.

$$coil area = w \cdot \ell_{coil} = N \cdot (\text{wire diameter})^2 \quad (3-8.6)$$

Substituting the exponential relationship between AWG and wire diameter given by Eq. (3-5.10) yields:

$$w = \frac{N}{\ell_{coil}} \left(a \cdot e^{b \cdot \text{AWG}} \right)^2 \quad (3-8.7)$$

The coil resistance can now be calculated using Eq. (3-7.20):

$$R = N \cdot \pi (ID_{coil} + w) (k_4 e^{k_5 \cdot \text{AWG}})$$

The coil power dissipation is:

$$P = I^2 R \quad (3-8.8)$$

If voltage excitation is used, the coil current is calculated using Ohm's law, then the power dissipation is calculated.

The coil circular mils per A is given by:

$$M = 10^6 \cdot \underbrace{\left(a' \cdot e^{b' \cdot \text{AWG}} \right)^2}_{\text{wire area in circular mils}} / I \quad (3-8.9)$$

The coil current density in A/in² is given by Eq. (3-8.10), i.e.:

$$\Delta = \frac{k_2}{M} \quad (3-8.10)$$

Two commonly encountered part shapes in the magnetic path are the cylindrical shell as shown in Fig. 3-8.1 and the disc or washer as shown in Fig. 3-8.2. Two subroutines are provided to calculate the reluctance and minimum cross-sectional area of these two shapes.

Subroutine 1, thin cylindrical shell with permeability μ .

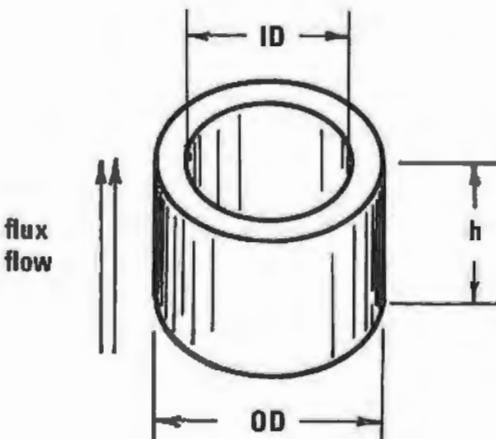


Figure 3-8.1 Thin cylindrical shell.

The cross-sectional area is given by Eq. (3-8.3) and the reluctance is:

$$R = \frac{h}{\mu A}$$

This subroutine output becomes the input for the program coding under label B, and the reluctance is calculated under label B. The subroutine output is stored in the stack in the same format as data entered from the keyboard for arbitrary magnetic section, i.e.:

stack register	contents
t	not used
z	h
y	cross-sectional area
x	permeability

Subroutine 2, disc or washer with radial flux flow.

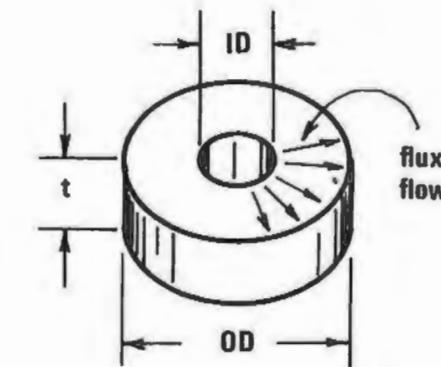


Figure 3-8.2 Disc or washer with radial flux flow.

The disc is composed of an infinite number of annular shells each with infinitesimal thickness dr. The cross-sectional area of each annulus is $2\pi rt$. In this instance, the summation of Eq. (3-8.1) is expressed as an integral:

$$R = \sum \frac{l}{\mu A} = \frac{1}{\mu t} \int_{r_1}^{r_2} \frac{dr}{2\pi r} = \frac{\ln(OD/ID)}{2\pi t \mu} \quad (3-8.11)$$

$$r_1 = \frac{ID}{2}$$

The disc has the smallest cross-sectional area at the inner diameter, hence:

$$A = A' = \pi \cdot ID \cdot t \quad (3-8.12)$$

This subroutine output becomes the input for the program coding under label B. The data format used with label B is the equivalent length of a constant cross-section magnetic path, the path area, and the path permeability. The equivalent length having the above reluctance and

User Instructions

cross-sectional area A' is:

$$\ell = \mu A' \cdot R = \left(\frac{\pi \cdot ID \cdot t \cdot \mu}{2\pi \cdot t \cdot \mu} \right) \cdot \ell \ln \frac{OD}{ID} = \frac{ID}{2} \ell \ln \frac{OD}{ID} \quad (3-8.13)$$

Subroutine 2 output is transferred to the program coding under label B using the stack in the same way that subroutine 1 operates.


In addition to the program card, a data card is required to load the registers with the program constants. All registers contain zero except for the following:

a' for AWG	$3.241013109 \times 10^{-1}$	$\rightarrow S_0$
b' for AWG	$-1.158179256 \times 10^{-1}$	$\rightarrow S_1$
a for AWG	$3.130387015 \times 10^{-1}$	$\rightarrow S_2$
b for AWG	$-1.097333787 \times 10^{-1}$	$\rightarrow S_3$
$\pi \cdot k_4$ for resistance	$2.985212367 \times 10^{-5}$	$\rightarrow S_4$
k_5 for resistance	$2.317635483 \times 10^{-1}$	$\rightarrow S_5$
$k_3, \text{cm} \rightarrow \text{inch}$	2.54	$\rightarrow S_6$
$k_2, 4/\pi \times 10^6$	1.273239545×10^6	$\rightarrow S_7$
k_1	1.73×10^6	$\rightarrow S_8$

If metric units are preferred, i.e., linear dimensions in cm, force in kg, current density in A/cm² and inverse current density in hybrid units (circular mil-milli-centimeter/A), change the following constants.


a' for AWG	$8.232173297 \times 10^{-1}$	$\rightarrow S_0$
a for AWG	$7.951183108 \times 10^{-1}$	$\rightarrow S_2$
$\pi \cdot k_4$ for resistance	$1.175280459 \times 10^{-5}$	$\rightarrow S_4$
$k_3, \text{cm} \rightarrow \text{cm}$	1.0	$\rightarrow S_6$
$k_2, 4/(2.54\pi) \times 10^6$	5.012754114×10^5	$\rightarrow S_7$
k_1	2.4606×10^7	$\rightarrow S_8$

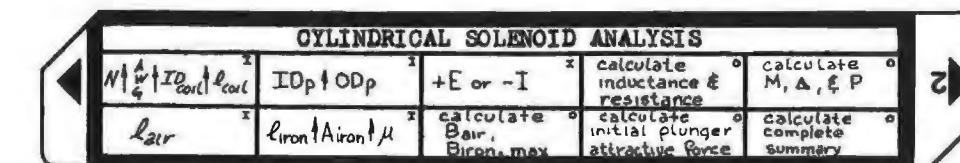HP-67 users may want the program to stop instead of executing a "print" statement. This can be accomplished by changing the "print" statements to "R/S" statements at the following line numbers: 102, 105, 124, and 130. To continue program execution after a stop, key a "R/S" command from the keyboard.



STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
1	Load both sides of program card and both sides of data card			
2	Load air gap length in inches	l_{air}	A	
3	Load plunger ID and OD in inches. The ID can be zero if the plunger is solid	ID _p OD _p	ENT↑ f B	
4	Load coil parameters: number of wire turns in coil wire AWG coil ID in inches coil length in inches	N AWG ID _{coil} l _{coil}	ENT↑ ENT↑ ENT↑ f A	
5	Load coil excitation voltage excitation in volts current excitation in A (note minus)	E -I	f Q f Q	
6	Optional step, the main source of reluctance in the magnetic path is the air gap. For added accuracy, the length, area, and permeability of each magnetic section may be entered: effective magnetic path length in inches effective magnetic path area in inches ² magnetic permeability of path	l_{iron} A _{iron} μ	ENT↑ ENT↑ B A	
	If the magnetic section is either a cylindrical shell or a disc, then a subroutine can be used to calculate and enter the above parameters from the section dimensions. For cylindrical shells with axial flux flow:			
	load shell height in inches load shell ID in inches (may be zero) load shell OD in inches load shell permeability	h ID OD μ	ENT↑ ENT↑ ENT↑ GSB 1 A	

3-8 User Instructions

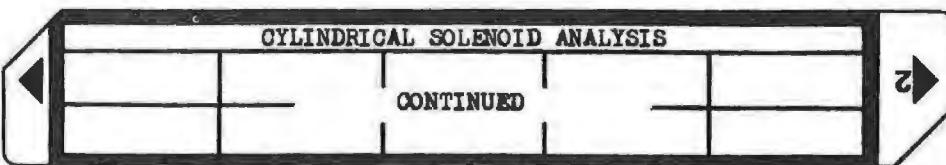

STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
6	continued For discs with radial flux flow: load disc thickness in inches load disc ID in inches load disc OD in inches load permeability of material	t ID OD μ	ENT↑ ENT↑ ENT↑ GSB 2	R A
	Repeat step 6 for each separate magnetic section in the magnetic circuit.			
7	To calculate the flux density in the air gap and in the smallest iron cross-sectional area (the smallest area has the highest flux dens) If step 6 is omitted, $B_{iron} = 0$, $A_{iron} = A_{air}$ is assumed, hence, $B_{iron} = B_{air}$	0		B_{air}, G B_{iron}, G
8	To calculate the initial plunger attractive force in pounds	D		F
9	To calculate the electrical inductance and resistance at 60°C of the coil	f D		L, h R, ohms
10	To calculate the coil M, Δ , and power dissipation	f E		M, $\frac{cir-mils}{A}$ $\Delta, A/in^2$ P, watts
11	To calculate all the information contained in steps 8, 9, 10, and 11	E		L, h R, ohms M, $\frac{cir-mils}{A}$ $\Delta, A/in^2$ P, watts B_{air}, G B_{iron}, G F, lbs
12	To run a new case, goto step 1 and start over			

Example 3-8.1

The cylindrical solenoid shown in cross-section by Fig. 3-8.3 has the following characteristics:

- 1) The coil is 150 turns of #24 AWG HF wire,
- 2) 0.5 A excitation current flows through the coil, and
- 3) The magnetic materials are 1010 mild carbon steel.

For the analysis, neglect the force required to compress the return spring.

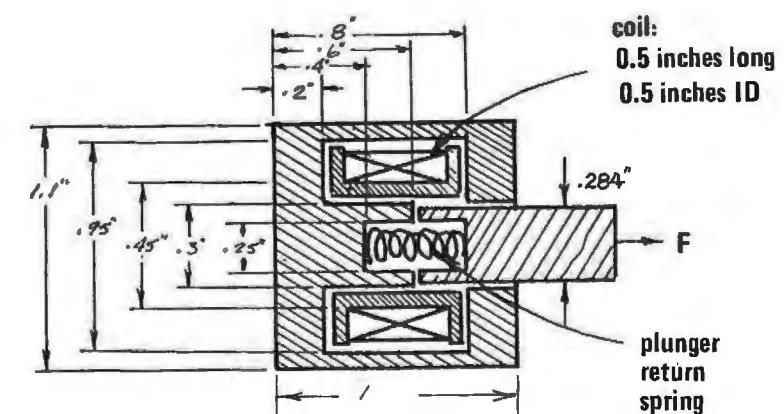


Figure 3-8.3 Cylindrical solenoid construction.

Analyze the solenoid and determine its electrical and magnetic characteristics. Also analyze the solenoid for the same characteristics if the coil is excited by 0.6 Vdc.

The analysis is begun by breaking down the solenoid into its component geometric shapes as shown by Fig. 3-8.4.

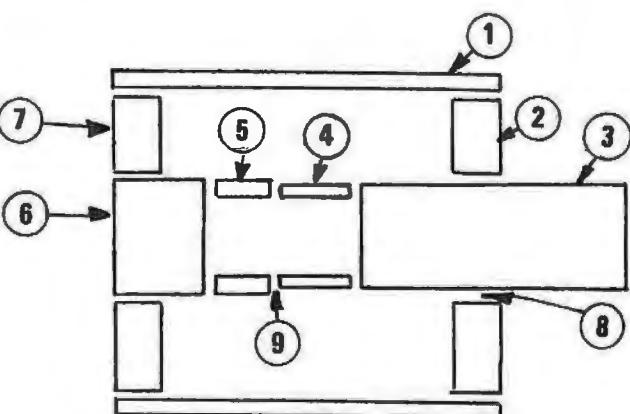


Figure 3-8.4 Component geometric shapes of solenoid.

The component geometric shapes of the solenoid are as follows:

- 1) Cylindrical shell, 1.0" long, 0.95" ID, 1.1" OD, and $\mu = 1000$,
- 2) Disc, 0.2" thick, 0.3" ID, 0.95" OD, and $\mu = 1000$,
- 3) Solid cylinder, 0.2" long (active magnetic part), 0.0" ID, 0.284" OD, and $\mu = 1000$,
- 4) Cylindrical shell, 0.2" long, 0.25" ID, 0.284" OD, and $\mu = 1000$,
- 5) Cylindrical shell, 0.2" long, 0.25" ID, 0.3" OD, and $\mu = 1000$,
- 6) Solid cylinder, 0.4" long, 0.0" ID, 0.3" OD, and $\mu = 1000$,
- 7) Disc, 0.2" thick, 0.3" ID, 0.95" OD, and $\mu = 1000$,
- 8) Disc (air gap), 0.2" thick, 0.284" ID, 0.3" OD, and $\mu = 1$,
- 9) Operating air gap, 0.005" thick, 0.25" ID, 0.284" OD, & $\mu = 1$.

The air gap data is loaded, and the complete summary calculated, then the magnetic path component parts are loaded and the summary run again to show the difference that the magnetic circuit reluctance makes on the electrical and magnetic characteristics. This sequence is repeated with the coil excitation at 0.6 Vdc.

HP-97 PRINTOUT FOR EXAMPLE 3-8.1

		GSBE calc all params	
.005 GSBA load l_{air}	solid cylinder .2 ENT↑ length	1.661-03 *** L, h	
150. ENT↑ load N	0. ENT↑ ID	759.9-03 *** R, ohms	
24. ENT↑ load AWG	.284 ENT↑ OD	809.2+00 *** M, cir-mils/A	
.5 ENT↑ load ID	1000. GSB1 u	1.574+03 *** Δ, A/in ²	
.5 GSBa load l_{coil}	3.157-03 *** R	190.0-03 *** P, watts	
	63.35-03 *** area		
.25 ENT↑ load ID _p	cylindrical shell .2 ENT↑ length	6.019+03 *** max Biron	
.284 GSBb load OD _p	.25 ENT↑ ID	6.019+03 *** Bair, G	
-.5 GSBc load -I	.284 ENT↑ OD	298.6-03 *** F, pounds	
	1000. GSB1 μ		
	calc all * GSBE parameters		
2.048-03 *** L, h	14.03-03 *** R		
759.9-03 *** R, ohms	14.26-03 *** area		
809.2+00 *** M, cir-mils/A	cylindrical shell .2 ENT↑ length		
1.574+03 *** Δ, A/in ²	.25 ENT↑ ID		
190.0-03 *** P, watts	.3 ENT↑ OD		
7.421+03 *** max Biron	1000. GSB1 μ		
7.421+03 *** Bair, G	9.260-03 *** R		
453.9-03 *** F, pounds	21.60-03 *** area		
	solid cylinder .4 ENT↑ length		
	0. ENT↑ ID		
	.3 ENT↑ OD		
	1000. GSB1 μ		
	* Magnetic reluctance is assumed zero since flag 0 is set. Flag 0 is cleared under label B.		
	load magnetic path data		
	disc .2 ENT↑ thickness		
	.95 ENT↑ ID		
	1.1 ENT↑ OD		
	1000. GSB2 μ		
4.141-03 *** R	917.3-06 *** R		
241.5-03 *** area	188.5-03 *** min area		
	disc .2 ENT↑ thickness		
	.3 ENT↑ ID		
	.95 ENT↑ OD		
	1000. GSB2 μ		
	disc .2 ENT↑ thickness		
	.284 ENT↑ ID		
	.3 ENT↑ OD		
	1. GSB2 μ		
917.3-06 *** R	43.62-03 *** R		
188.5-03 *** area	178.4-03 *** min area		
	744.6-03 *** F, pounds		

Look at voltage excitation. Set flag 0 so magnetic reluctance is ignored and calculate electrical & magnetic parameters.

SF0
.6 GSBc load E

GSBE calc params
2.048-03 *** L, h
759.9-03 *** R, ohms

512.4+00 *** M, cir-mils/A
2.485+03 *** Δ, A/in²
473.7-03 *** P, watts

11.72+03 *** max Biron
11.72+03 *** Bair, G

1.132+00 *** F, pounds
Clear flag 0 to use magnetic reluctance.

CF0
GSBE calc params
1.661-03 *** L, h
759.9-03 *** R, ohms

512.4+00 *** M, cir-mils/A
2.485+03 *** Δ, A/in²
473.7-03 *** P, watts

9.505+03 *** max Biron
9.505+03 *** Bair, G

43.62-03 *** R
178.4-03 *** min area
744.6-03 *** F, pounds

Program Listing I

001 *LBLA	LOAD AIR GAP IN INCHES								
002 ST02	store entry								
003 GT00	goto space and return								
004 *LBLa	LOAD N & AWG & ID _{coil} & coil								
005 ST01	store coil length								
006 R↓	recover and store ID _{coil}								
007 ST0D	recover and store AWG								
009 ST0B	recover and store N								
010 ST0E	recover and store ID _{coil}								
012 GT00	goto space and return								
013 *LBL2	SUBROUTINE FOR DISC								
014 R↓									
015 X2Y									
016 ST0I									
017 ÷									
018 LN	$\ell_{\text{effective}} = \frac{\text{ID}}{2} \ln \frac{\text{OD}}{\text{ID}}$								
019 RCLI									
020 X									
021 2									
022 ÷									
023 X2Y									
024 RCLI									
025 X	$A_{\min} = \pi \cdot \text{ID} \cdot t$								
026 Pi									
027 X									
028 R↑	recover μ								
029 *LBLB	LOAD l _{iron} & A _{iron} & μ								
030 X2Y	store μ								
031 ST0I									
032 F0?	store l _{iron} on first execution of this routine								
033 ST04									
034 X									
035 ÷									
036 SPC	$R_i = \frac{l_{\text{iron}}}{M_i \cdot A_{\min}}$								
037 PRTX									
038 ST+5	add R _i to Σ								
039 RCL4	test to see if present area is smaller than minimum stored area, if so, store present area								
040 RCLI									
041 X2Y?									
042 ST04									
043 CF0	indicate magnetic params								
044 GSB8	print area and space								
045 GT00	goto space and return								
046 *LBLb	LOAD ID _p & OD _p								
047 GSB4	calculate and store annular area								
048 ST03									
049 GT00	goto space and return								
NOTE:	The "print" statements at line numbers 037, 102, 105, 124, and 130 may be changed to "R/S" statements if desired.								
REGISTERS									
0 W	¹ l _{coil}	² l _{air}	³ A _{air}	⁴ min A _{iron}	⁵ $\sum R_i$	⁶ ϕ	⁷ scratch	⁸ I	⁹ E
S0 a'	b'	s2 a	s3 b	s4 π k ₄	s5 k ₅	s6 k ₃	s7 k ₂	s8 k ₁	s9
A NI	B AWG	C R	D coil OD	E N	F scratchpad				

050 *LBLC CALCULATE B_{air} and B_{iron}
 051 GSB6 calculate R, I, and NI
 052 GSB9 calc $(0.4\pi/k_3)/(\sum R_i + l_{\text{air}}/\lambda_{\text{air}})$
 053 RCL4 use A_{air} if magnetic params not entered, otherwise use
 054 F0? min A_{iron}
 055 RCL3 take reciprocal area
 056 1/X
 057 RCLI calculate and print φ
 058 RCLA using Eq. (3-7.2)
 059 X
 060 ST06
 061 X calculate and prints:
 062 P2S
 063 RCL6
 064 P2S
 065 X² $B_{\text{iron}, \max} = \frac{\phi}{\min A_{\text{iron}} \cdot k_3}$
 066 ST0I
 067 ÷
 068 PRTX
 069 RCL6 calculate and prints:
 070 RCL3
 071 ÷
 072 RCLI $B_{\max} = \frac{\phi}{A_{\text{air}} \cdot k_3}$
 073 ÷
 074 GT08
 075 *LBL0 PRINT COMPLETE SUMMARY
 076 GSBd
 077 GSBe
 078 GSBC
 079 *LBLD CALCULATE AND PRINT F
 080 GSB6
 081 SF2
 082 GSB9
 083 RCLA
 084 X
 085 X²
 086 RCL3 $F = \frac{\phi^2}{k_1 \cdot k_3^4 \cdot A_{\text{air}}}$
 087 ÷
 088 P2S
 089 RCL8
 090 P2S
 091 ÷
 092 GT08
 093 *LBLd CALCULATE AND PRINT L & R
 094 GSB6
 095 GSB9
 096 RCLE
 097 X²
 098 X $L = \frac{N^2 k_3}{10^8} \cdot \frac{0.4\pi}{\sum R_i + \frac{l_{\text{air}}}{A_{\text{air}}}}$
 099 EEX
 100 8
 101 ÷
 102 PRTX
 103 RCLC recall and print resistance

Program Listing II

NOTE FLAG SET STATUS

104 *LBL8	print and space subroutine	159 *LBL6	subr to calc R, I, and NI
105 PRTX		160 P2S	
106 GT00		161 RCL2	
107 *LBLc LOAD COIL EXCITATION		162 RCL3	
108 ST09		163 GSB3	
109 *LBL0 space and return subroutine		164 X ²	$W = \frac{N}{l_{\text{coil}}} (a \cdot e^{b \cdot \text{AWG}})^2$
110 SPC		165 RCLE	
111 RTN		166 X	
112 *LBLe CALCULATE AND PRINT M, P		167 RCL1	
113 GSB6		168 ÷	
114 P2S		169 ST00	
115 RCL0		170 RCLD	
116 RCL1		171 +	
117 GSB3		172 RCLE	
118 X ²		173 X	
119 RCL8	$M = 10^6 (a' e^{b' \cdot \text{AWG}})^2$	174 P2S	
120 ÷		175 RCL4	$R = N\pi (ID_{\text{coil}} + W) k_4 e^{k_5 \cdot \text{AWG}}$
121 EEX		176 RCL5	
122 6		177 GSB3	
123 X		178 X	
124 PRTX		179 ST0C	
125 1/X		180 RCL9	
126 P2S		181 X2Y?	test for current excitation
127 RCL7	$\Delta = \frac{k_2}{M}$	182 GT08	
128 P2S		183 ÷	I = E/R
129 X		184 1/X	
130 PRTX		185 *LBL0 jump destination	
131 RCL8		186 ABS	store I
132 X ²		187 ST08	
133 RCLC	P = I ² R	188 RCLE	calculate and store NI
134 X		189 X	
135 GT08		190 ST0A	
136 *LBL1 CYLINDRICAL SHELL SUBR		191 RTN	
137 ST0I		192 *LBL9 magnetics subroutine	
138 R↓		193 7	
139 GSB4		194 2	0.4π
140 RCLI		195 D→R	
141 GT0B		196 RCL2	
142 *LBL3 subroutine to calculate:		197 RCL3	
143 P2S		198 ÷	
144 RCLB		199 RCL5	
145 X $R_x \cdot \text{AWG}$		200 F0?	
146 e ^x		201 CLX	
147 X		202 +	
148 RTN		203 ÷	
149 *LBL4 subroutine to calculate:		204 P2S	$\frac{0.4\pi}{\sum R_i + \frac{l_{\text{air}}}{A_{\text{air}}}} \cdot \frac{k_3}{k_3}$
150 X ²		205 RCL6	$(F_2=0)$
151 X2Y		206 P2S	
152 X ²		207 F2?	
153 -		208 1/X	
154 Pi	$\text{Area} = \frac{\pi}{4} (OD^2 - ID^2)$	209 X	
155 X		210 ST0I	
156 4		211 RTN	return to main program
157 ÷			
158 RTN			

NOTE FLAG SET STATUS

LABELS	FLAGS	SET STATUS
A l _{air}	B l _{iron} A _{iron} I μ	C calculate B _{air} max B _{iron}
a A A l _{iron} l _{air}	b ID _p OD _p	c calc F
0 local label	1 cylindrical section entry	d calc L, R
5	2 section entry	e calc M, A, & P
	3 wire size subroutine	f complete summary
	4 circular section area	0 magnetic parameters entered
	5 subroutine	1
	6 R I & NI subroutine	ON OFF users choice
	7	2 0 1 2 3
	8 print & space subroutine	DEG GRAD RAD
	9 magnetics calc subr	FIX SCI ENG n 3

PROGRAM 3-9 MAGNETIC RELUCTANCE OF TAPERED CYLINDRICAL SECTIONS.

Program Description and Equations Used

This program calculates the magnetic reluctance of tapered cylindrical sections with axial flux flow as shown by Fig. 3-9.1. The magnetic reluctance is analogous to electrical resistance, and is used in the Ohm's law of magnetics as given by Eq. (3-8.1).

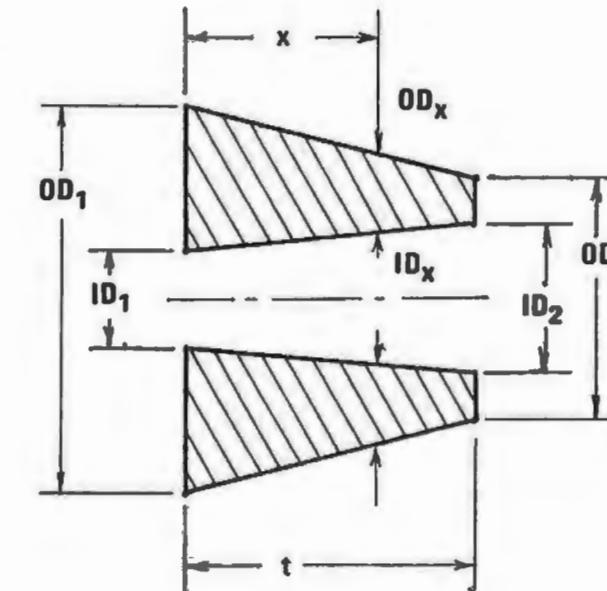


Figure 3-9.1 Tapered cylindrical section and dimensions.

Consider the section to be composed of an infinite number of washers each of infinitesimal thickness dx , then the reluctance of a washer is:

$$dR = dx / (\mu \cdot A_x) \quad (3-9.1)$$

where

$$A_x = (\pi/4)(OD_x^2 - ID_x^2) \quad (3-9.2)$$

The inner and outer diameters at location x can be found by linearly interpolating between the known end diameters:

$$ID_x = ID_1 + (1/t)(ID_2 - ID_1) \cdot x \quad (3-9.3)$$

$$OD_x = OD_1 + (1/t)(OD_2 - OD_1) \cdot x \quad (3-9.4)$$

Substituting Eqs. (3-9.3) and (3-9.4) into Eq. (3-9.2) and collecting like powers of x results in a quadratic:

$$A_x = (\pi/4)(a + bx + cx^2) \quad (3-9.5)$$

where

$$a = OD_1^2 - ID_1^2$$

$$b = (2/t)\{OD_1(OD_2 - OD_1) - ID_1(ID_2 - ID_1)\}$$

$$c = (1/t^2)\{(OD_2 - OD_1)^2 - (ID_2 - ID_1)^2\}$$

hence,

$$\mathcal{R} = \frac{4}{\mu \pi} \int_0^t \frac{dx}{a + bx + cx^2} \quad (3-9.6)$$

The result of this integration can have any one of three forms; let

$$q = b^2 - 4ac \quad (3-9.7)$$

and

$$r = (2cx + b) / \sqrt{|q|} \quad (3-9.8)$$

then if $q > 0$ and $|r| < 1$, the solution is:

$$\mathcal{R} = -\frac{8}{\mu \pi \sqrt{|q|}} \tanh^{-1} r \quad (3-9.9)$$


if $q > 0$ and $|r| \geq 1$, the solution is:

$$\mathcal{R} = \frac{4}{\mu \pi \sqrt{|q|}} \ell n \left(\frac{r - 1}{r + 1} \right) \quad (3-9.10)$$

if $q < 0$, the solution for all r is:

$$\mathcal{R} = \frac{8}{\mu \pi \sqrt{|q|}} \tan^{-1} r \quad (3-9.11)$$

User Instructions

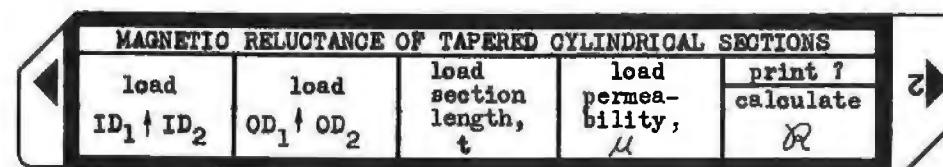

STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
1	Load both sides of the magnetic card			
2	Select print/ no-print option		f E f E f E ;	0 (no prt) 1 (print) 0 (no prt) ;
3	Load inner diameters	ID1* ID2*	ENT↑ A	
4	Load outer diameters	OD1* OD2*	ENT↑ B	
5	Load section length	t*	C	
6	Load magnetic permeability of material		D	
7	Calculate reluctance		E	R **
	Notes			
	* Any units of the users choosing may be used as long as the same unit is used throughout. If the reluctance is going to be loaded into Program 3-7, then inch units should be used.			
	** The units of reluctance are in inverse dimension units, i.e., inches ⁻¹ , cm ⁻¹ , ft ⁻¹ , etc.			

Program Listing I

Example 3-9.1

Given the conical section shown in Fig. 3-9.2, calculate the reluctance in inch units.

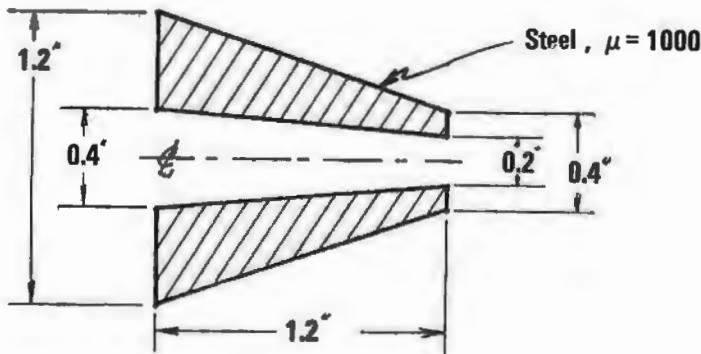


Figure 3-9.2 Tapered conical section.

```

.2 ENT1 ID1
.4 GSBH ID2

.4 ENT1 OD1
.2 GSBH OD2

.12 GSBG t

1000. GSBC μ

GSBE calculate reluctance
3.872E-03 Rt in-1

```

LOAD ID ₁ ↑ ID ₂		CALCULATE RELUCTANCE	
001	*LBLA		calculate and stores
002	ST01		
003	R↓	store entries	(OD ₂ - OD ₁) ²
004	ST00		
005	GT00	goto space and return subr	calculate and retain in stk:
006	*LBLB	LOAD OD ₁ ↓ OD ₂	OD ₁ (OD ₂ - OD ₁)
007	ST03		
008	R↓	store entries	calculate w/ register arith:
009	ST02		(OD ₂ - OD ₁) ² - (ID ₂ - ID ₁) ²
010	GT00	goto space and return subr	calculate and store b:
011	*LBLC	LOAD SECTION LENGTH	$\frac{2}{t} \{ OD_1(OD_2 - OD_1) - ID_1(ID_2 - ID_1) \}$
012	ST04		
013	GT00		
014	*LBLD	LOAD PERMEABILITY	finish c calculation
015	ST05		calculate and store q:
016	*LBL0	space and return subroutine	$q = b^2 - 4ac$
017	SPC		
018	RTN		
019	*LBL0	CALCULATE RELUCTANCE	
020	RCL3	calculate and stores	
021	RCL2		
022	-		
023	X2		
024	ST08		
025	LSTX		
026	RCL2		
027	X		
028	RCL1		
029	RCL0		
030	-		
031	ENT↑		
032	X2		
033	ST-8		
034	R↓		
035	RCL0		
036	X		
037	-		
038	ENT↑		
039	+		
040	RCL4		
041	÷		
042	ST07		
043	RCL4		
044	X2		
045	ST÷8		
046	RCL7	calculate and store q:	
047	X2		
048	RCL2		
049	X2		
050	RCL0		
051	X2		
052	-		
053	RCL8		
054	X		
055	4		
056	X		
057	-		
058	ST06		
059	AES	calculate and store:	
060	JX	$\sqrt{ q }$	
061	ST0A	calculate and store:	
062	RCL4		
063	GSB0		
064	ST09		
065	CLX	$\int_a^t \frac{dx}{a + bx + cx^2}$	
066	GSB0		
067	ST-9		
REGISTERS			
0	ID ₁	ID ₂	OD ₁
S0	S1	S2	S3
A	$\sqrt{ q }$	B	q
		C	$2cx + b$
		D	
		E	R
		F	I
		G	C
		H	S
		I	S

Program Listing II

					LABELS	FLAGS	SET STATUS		
A Load ID ₁ ↑ID ₂	B Load OD ₁ ↑OD ₂	C Load t	D Load permeability	E calculate reluctance	0 r > 1	FLAGS	TRIG	DISP	
a	b	c	d	e print / R/S toggle	0 r > 1	0 ON	DEG	FIX	
0 local label	1 subroutine destination	2 subroutine destination	3 print / R/S destination	4	1 print	1 OFF	GRAD	SCI	
5	6	7	8	9	2	2 RAD	RAD	ENG	
					3	3	n	3	

Flag 1 should be set (cleared) before magnetic card recording depending upon the user's desire for the program to normally be in the print (R/S) mode after the card read.

Part 4

HIGH FREQUENCY CIRCUIT DESIGN

PROGRAM 4-1 BILATERAL TRANSISTOR AMPLIFIER DESIGN USING S PARAMETERS.

Program Description and Equations Used

When s_{12} , the reverse transmission coefficient, cannot be reduced to near zero using unilateral design methods,* or the unilateral figure of merit is not sufficiently near zero, the bilateral design method must be used. Since s_{12} is related to the capacitive reactance of the transistor base-collector capacity, and this reactance becomes smaller as frequency increases, the bilateral design requirement generally occurs when the amplifier is to be used at UHF frequencies and above.

The bilateral stability factor, K, is computed using Eq. (4-1.1). For the amplifier to be unconditionally stable, K must be greater than one, and the magnitudes of s_{11} and s_{22} must be smaller than one. Since s_{11} and s_{22} are reflection coefficients, this last requirement implies that the input and output impedances are positive. Unconditional stability means the amplifier will not oscillate for any choice of input and output terminations.

$$K = \frac{1 + |\Delta|^2 - |s_{11}| - |s_{22}|}{2 |s_{21} \cdot s_{12}|} \quad (4-1.1)$$

$$\Delta = s_{11} \cdot s_{22} - s_{21} \cdot s_{12} \quad (4-1.2)$$

When K is less than one, the amplifier will oscillate with certain source and load impedances, hence, these impedances must be carefully selected. The HP EE pac Program 18 will calculate the stability circles to aid in the termination impedance selection.

The scattering parameters are:

- s_{11} is the input reflection coefficient,
- s_{12} is the reverse transmission coefficient,
- s_{21} is the forward transmission coefficient, and
- s_{22} is the output reflection coefficient.

* See the HP EE pac Program 16 for unilateral design methods.

Scattering parameters are obtained from reflection coefficient measurements applied to a two port network with both ports loaded with a reference impedance, Z_0 , which is typically 50 ohms resistive. The reflection coefficient is defined by Eq. (1-1.2). For a more comprehensive discussion of s parameters, see Froehner [24], HP application note 95 [32], or Carson [15].

If the proposed amplifier is unconditionally stable, then the maximum gain can be calculated using Eq. (4-1.3)

$$G_{\max} = \left| \frac{s_{21}}{s_{12}} \right| \cdot (K \pm \sqrt{K^2 - 1}) \quad (4-1.3)$$

The negative sign is used when B_1 is positive and vice-versa:

$$B_1 = 1 + |s_{11}|^2 - |s_{22}|^2 - |\Delta|^2 \quad (4-1.4)$$

The source and load reflection coefficients necessary to provide G_{\max} are given by Eqs. (4-1.5) and (4-1.6). These loads present a conjugate match to the transistor.

$$\rho_{MS} = C_1 * \frac{B_1 \pm \sqrt{B_1^2 - 4|C_1|^2}}{2|C_1|^2} \quad (4-1.5)$$

$$\rho_{ML} = C_2 * \frac{B_2 \pm \sqrt{B_2^2 - 4|C_2|^2}}{2|C_2|^2} \quad (4-1.6)$$

$$B_2 = 1 + |s_{22}|^2 - |s_{11}|^2 - |\Delta|^2 \quad (4-1.7)$$

$$C_1 = s_{11} - \Delta * s_{22}^* \quad (4-1.8)$$

$$C_2 = s_{22} - \Delta * s_{11}^* \quad (4-1.9)$$


The minus sign in Eqs. (4-1.5) and (4-1.6) is used when B_1 is positive and vice-versa. The asterisk (*) means the complex conjugate, i.e., the sign of the imaginary part is reversed, or the sign of the angle is reversed for rectangular or polar formats respectively.

Equations (4-1.5) and (4-1.6) are used to calculate reflection coefficients. The corresponding impedances can be obtained if Eq. (1-1.2) is rearranged to provide Z_L in terms of Z_s :

$$Z_L = Z_0 \frac{1 + \rho}{1 - \rho} \quad (4-1.10)$$

This routine is contained under label E of the program.

User Instructions

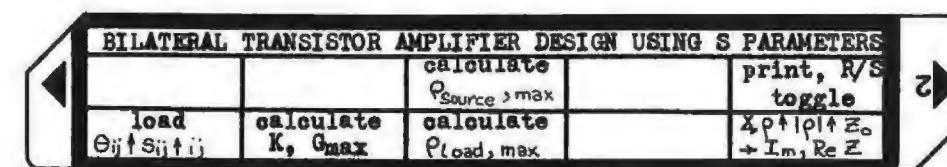

STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
1	Load both sides of magnetic card			
2	Select print or R/S option		f E f E f E	0 (R/S) 1 (print) 0 (R/S) ⋮
3	Load elements of s parameter matrix for $ij = 11, 12, 21, 22$ (any order)			
a)	load angle of s_{ij} in degrees	Θ_{ij}	ENT↑	
b)	load magnitude of s_{ij}	$ s_{ij} $	ENT↓	
c)	load subscript	ij	A	
4	Calculate stability factor and maximum gain		B	K G_{\max}, dB
5	Calculate angle and magnitude of load reflection coefficient to obtain G_{\max}		C	$X\rho_{ML}$ $ \rho_{ML} $
	Calculate real and imaginary parts of load impedance	Z_0	E	$\text{Re } Z_L$ $\text{Im } Z_L$
6	Calculate angle and magnitude of source reflection coefficient to obtain G_{\max}		f C	$X\rho_{MS}$ $ \rho_{MS} $
	Calculate real and imaginary parts of source impedance	Z_0	E	$\text{Re } Z_S$ $\text{Im } Z_S$
7	Calculate real and imaginary parts of impedances corresponding to a reflection coefficient and Z_0	ρ $ \rho $ Z_0	ENT↑ ENT↓ E	$\text{Re } Z$ $\text{Im } Z$

Example 4-1.1

Given a 2N3570 transistor operating at $I_c = 4 \text{ mA}$ and $V_{ce} = 10 \text{ V}$ and having the following s parameters at 750 MHz,

$$\begin{bmatrix} s_{11} & s_{12} \\ s_{21} & s_{22} \end{bmatrix} = \begin{bmatrix} 0.277 \angle -59^\circ & 0.078 \angle 93^\circ \\ 1.920 \angle 60^\circ & 0.848 \angle -31^\circ \end{bmatrix}$$

calculate the stability factor, the maximum power gain in dB, the source reflection coefficient and impedance to obtain G_{\max} , and the load reflection coefficient and impedance to obtain G_{\max} .

PROGRAM INPUT	PROGRAM OUTPUT
-59.000 ENT [†] θ ₁₁ , angle in degrees .277 ENT [†] s ₁₁ , magnitude 11. GSBA ij	GSBB calculate K & G _{max} 1.033+00 *** K > 1, uncond stable 12.61+00 *** G _{max} , dB
.03.000 ENT [†] θ ₁₂ .078 ENT [†] s ₁₂ 12. GSBR ij	GSBc calculate ρ _{MS} 135.4+00 *** √ρ _{MS} , degrees 729.8+03 *** ρ _{MS}
64.000 ENT [†] θ ₂₁ 1.920 ENT [†] s ₂₁ 21. GSBR ij	GSPE calculate Z _S 9.063+00 *** Re Z _S , ohms 19.36+00 *** Im Z _S , ohms
-31.000 ENT [†] θ ₂₂ .848 ENT [†] s ₂₂ 22. GSBR ij	GSBC calculate ρ _{ML} 33.85+00 *** √ρ _{ML} , degrees 551.1+03 *** ρ _{ML}
	GSBE calculate Z _L 14.53+00 *** Re Z _L , ohms 263.1+00 *** Im Z _L , ohms

Program Listing I

41

```

001 *LBLA LOAD 0ij↑sij↑ij
002 ENT↑
003 +
004 2 calculate storage register
005 1 index
006 -
007 ST01
008 R↓ recover and store s1j
009 ST01 increment register index
010 ISZI
011 R↓ recover and store Gij
012 ST01
013 GT03 goto space and return
014 *LBLB CALCULATE K, Gmax
015 RCL2 calculate and store s11·s22
016 RCL1
017 RCLD
018 RCLE
019 GSB9
020 ST06 |s11·s22|
021 R↓
022 ST07 X s11 s22
023 RCL4 calculate and store:
024 RCL3
025 RCLB
026 RCLC
027 GSB9 Δ = s11·s22 - s12·s21
028 CHS
029 RCL7
030 RCL6
031 GSB8
032 ST06 |Δ|
033 R↓
034 ST07 X Δ
035 RCLD finish K calculation
036 RCL1
037 GSB7 B1 = |s11|2 - |s22|2 - |Δ|2 + 1
038 RCL6
039 X2
040 EEX
041 +
042 RCL1
043 X2
044 -
045 RCLD
046 X2
047 -
048 RCL3 1 + |Δ|2 - |s11|2 - |s22|2
049 RCLB
050 X
051 ABS
052 ENT↑
053 +
054 ÷
055 ST09 K =  $\frac{1 + |\Delta|^2 - |s_{11}|^2 - |s_{22}|^2}{2 |s_{21} \cdot s_{12}|}$ 
056 GSB5 goto print routine
057 X2 calculate Gmax
058 LSTX
059 X#Y
060 EEX
061 -
062 JX
063 RCL5 Gmax =  $\left| \frac{s_{21}}{s_{12}} \right| \cdot (K \pm \sqrt{K^2 - 1})$ 
064 X - used when B1 is +
065 -
066 RCLB
067 X
068 RCL3
069 ÷
070 ABS convert Gmax to dB power
071 LOG gain
072 EEX
073 1
074 X
075 GT00 goto print and space subr
076 *LBLc CALCULATE ρsource, max
077 RCL7 calculate - Δ · s22
078 RCL6
079 RCLD
080 RCLE
081 CHS
082 GSB9
083 CHS
084 RCL2 recall s11
085 RCL1
086 GSB2 calc and print √ρsource, max
087 RCLD |s22|
088 RCL1 |s11|
089 GSB7 calc |s11|2 - |s22|2 - |Δ|2 + 1 = B1
090 GT01 jump
091 *LBLc CALCULATE ρload, max
092 RCL7 calculate - Δ · s11
093 RCL6
094 RCL1
095 RCL2
096 CHS
097 GSB9
098 CHS
099 RCLE
100 RCLD recall s22
101 GSB2 calc and print √ρload, max
102 RCL1 |s11|
103 RCLD |s22|
104 GSB7 calc |s22|2 - |s11|2 - |Δ|2 - 1 = B2
105 *LBL1 calculate refl coef mag
106 RCLA - X B
107 RCL8 |B|
108 RCL0 |C|
109 ENT↑
110 +

```

REGISTERS

0 C	1 s ₁₁	2 X s ₁₁	3 s ₁₂	4 X s ₁₂	5 sign(B ₁)	6 scratch, Δ	7 scratch, X Δ	8 scratch, B ₂ or B ₁	9 K
S0 Re ρ	S1 Im ρ	S2 Z _o , Z _s	S3 X Z _s	S4	S5	S6	S7	S8	S9
A X C*, X B	B s ₂₁	C X s ₂₁	D s ₂₂	E X s ₂₂	I index				

Program Listing II

LABELS		FLAGS		SET STATUS	
A $\alpha_{ij} + s_{ij} \uparrow ij$	B $\rightarrow K, G_{max}$	C $\rightarrow P_{mL}$	D	E $\rho \uparrow Z_0 \rightarrow Z$	0 print
a	b	c $\rightarrow P_{mg}$	d	e	1
0 prt, spc, rtn subroutine	1 local label w/ C, FC	2 subroutine w/ C, FC	3 space, rtn	4	2
5 print, R/S subroutine	6 R/S lock	7 subroutine	8 complex add	9 complex multiply	3
					0 ■ 1 2 3
					DEG ■ GRAD RAD ENG ■ n 3
					FIX

PROGRAM 4-2 UHF OSCILLATOR DESIGN USING S PARAMETERS.

Program Description and Equations Used

At UHF frequencies, the interelement capacities of a UHF transistor can function as the feedback elements to allow the device to oscillate when connected to an external tuned circuit (usually a $\frac{1}{4}$ -wave transmission line section). The emitter circuit is generally left unbypassed while the base circuit is bypassed with a capacitor to provide an ac ground. The collector-emitter capacity provides the necessary feedback to allow the collector to exhibit negative output impedance and oscillate with the external tuned circuit.

The program starts with the common base s parameters, reverses the port ordering so the collector is the input, and calculates the reflection coefficient of the "input." If the magnitude of the reflection coefficient is greater than one, the real part of the input impedance will be negative. The routine under label E provides the conversion from reflection coefficient to impedance, while the routine under label e provides the reverse conversion.

Equation (4-2.1) calculates the input reflection coefficient when the output port is loaded with R_L as shown by Fig. 4-2.1. Equation (4-2.1) holds for any transistor configuration.

$$s_{11}' = s_{11} + \frac{s_{12} \cdot s_{21} \cdot \rho_L}{1 - s_{22} \cdot \rho_L} \quad (4-2.1)$$

where ρ_L is defined by Eq. (1-1.2) with $Z_r = R_L$.

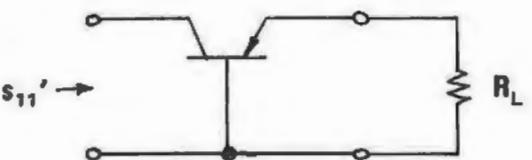


Figure 4-2.1 Common base transistor with collector as input port.

If the tuned source is connected to the collector, and the reflection coefficient of the source is denoted ρ_s , the circuit will oscillate if:

$$\rho_s \cdot s_{11}' \geq 1 \quad (4-2.2)$$

This equation is used in reverse to calculate the source reflection coefficient necessary for oscillation, i.e.:

$$\rho_s = \frac{1}{s_{11}'} \quad (4-2.3)$$

This reflection coefficient can be converted to its equivalent impedance using Eq. (4-1.10). The "Q," or quality factor, of this impedance is the ratio of the imaginary part to the real part, i.e.:

$$Q = \frac{\text{Im } Z_s}{\text{Re } Z_s} \quad (4-2.4)$$

The transistor negative input impedance can also be used to make a reflection amplifier if a circulator is used to separate the input from the output. The noise figure will be poor because of the large unby-passed emitter resistance.


For more information see the HP Journal [33], or HP application note number 95 [32].

Notes for User Instructions. Most UHF transistors are four lead devices (emitter, base, collector, and case). The case is electrically isolated from the transistor, in fact, the transistor chip is so small that it is mounted on the end of the collector lead inside the case. Because

of the fourth element, the case, the parasitic capacities from it to the other leads will introduce errors into the common-emitter to common-base s parameter conversion. See G. Bodway's article [9] on characterization of transistors by means of three port scattering parameters as one way of dealing with this problem.

If the common base s parameters are available, or can be measured, they are the highly preferred form of data input for the program. Common-base parameters notwithstanding, the common-emitter conversion can be used with the knowledge that s_{11}' will not be very accurate.

User Instructions

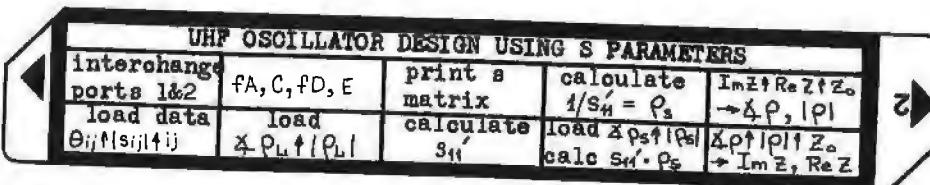

STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
1	Load both sides of program card or load Program 4-3 if parameter conversion reqd			
2	Load s parameters. If already in common base form, goto step 10 after executing this step.			
a)	load angle of scattering parameter	θ_{ij}	ENT↑	
b)	load magnitude of scattering parameter	$ s_{ij} $	ENT↑	
c)	load subscript of scattering parameter	ij	A	
	Repeat this step for $ij = 11, 12, 21, 22$ in any order			
3	To convert common emitter s parameters to common base, load EE1-06A, parameter conversions: s → Y, G, Z, H. (see notes in step 16)			
4	Convert s parameters to Y parameters	Z_o	B	
5	Load Program 4-3 to convert common emitter Y parameters to common base Y parameters			
6	Perform CE to CB conversion		B	
7	Reload EE1-06A to convert Y parameters back to s parameters			
8	Convert Y parameters to s parameters	Z_o	f B	
9	Reload both sides of this program card (4-2)			
10	Calculate load reflection coefficient			
a)	load imaginary part of Z_{emitter}	Im Z _L	ENT↑	
b)	load real part of Z_{emitter}	Re Z _L	ENT↑	
c)	load reference impedance	Z_o	f E	$\frac{1}{\rho_L}$, ρ _L

User Instructions



STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
11	Enter load reflection coefficient (if step 10 is used, the reflection coefficient magnitude and angle are already in the stack--- use key "B" alone)	$\frac{1}{\rho_L}$, ρ _L	ENT↑ B	
12	Interchange port ordering 1↔2		f A	
13	Calculate s_{11}'		C	$\frac{1}{s_{11}'}$, s ₁₁ '
14	Calculate $\rho_s = 1/s_{11}'$		f D	$\frac{1}{s_{11}'}$, 1/s ₁₁ '
15	Convert ρ_s to Z_s : enter reference impedance	Z_o	E	Im Z _s , Re Z _s
	To find the minimum resonator Q		+	Q _{min}
16	The lead reflection coefficient is not erased when Program 4-3 or EE1-06A is used, hence, for another case, the keystrokes in steps 12, 13, 14, and 15 are contained in user definable key fB, therefore, for another case, do steps 1 through 9, then execute fB		f B	
	* In HP EE pac (supplied by HP)			

Example 4-2.1

A UHF oscillator using a RCA 2N5179 transistor is to operate between 300 MHz and 400 MHz. The transistor is to be operated at 1.5 mA collector current and 4 volts V_{ce} per the manufacturer's recommendations. At 300 MHz the common-emitter y parameters are:

$$\begin{bmatrix} ((6.5 + j9.0) \times 10^{-3}) & (-j1.35 \times 10^{-3}) \\ ((32 - j32) \times 10^{-3}) & ((0.25 + j2.6) \times 10^{-3}) \end{bmatrix}$$

and at 400 MHz the common-emitter y parameters are:

$$\begin{bmatrix} ((9.2 + j10.7) \times 10^{-3}) & (-j1.8 \times 10^{-3}) \\ ((25 - j34) \times 10^{-3}) & ((0.3 + j4.0) \times 10^{-3}) \end{bmatrix}$$

The proposed oscillator schematic is shown in Fig. 4-2.2, and biasing networks have been added to achieve the manufacturer's recommended bias. The 100 ohm resistor in series with the RFC lowers the Q of the resonant circuit formed by the RFC and the coax capacity so the circuit will not preferentially oscillate at that lower frequency.

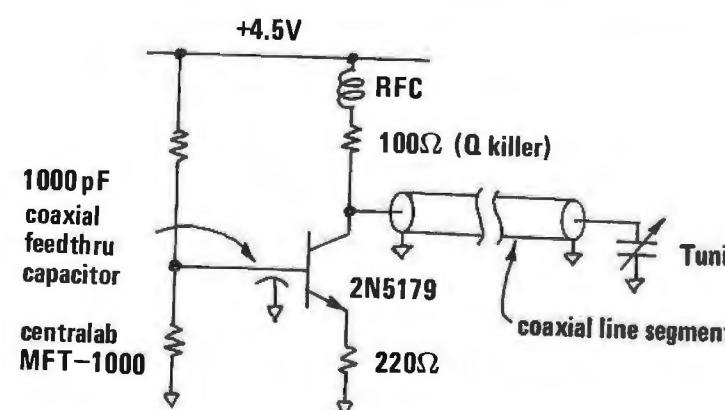


Figure 4-2.2 Oscillator schematic for Example 4-2.1.

HP-97 PRINTOUT FOR EXAMPLE 4-2.1, 300MHz CASE

Load Program 4-3 & load y params	Load Program EEL-06A (EE pac)
1. GSBe select y parameters	50. GSBB load reference Z & convert y params to s parameters
5. ENT1 Im load y_{ie} and 6.5 →P Re convert to polar format	
1. -03 x	
11. GSBA ij	
-90. ENT1 Θ load y_{re} in mag polar format	load this program (Program 4-2)
1. 35-03	
12. GSBA ij	
-32. ENT1 Im load y_{fe} and CHS Re convert to polar format	GSBe print s parameters
1. -03 x	147.6+00 *** $\Re s_{11}$
21. GSBA ij	464.4-03 *** $ s_{11} $
2.6 ENT1 Im load y_{oe} and .25 →P Re convert to polar format	93.63+00 *** $\Re s_{12}$
1. -03 x	41.01-03 *** $ s_{12} $
22. GSBA ij	-27.41+00 *** $\Re s_{21}$
	1.404+00 *** $ s_{21} $
	-10.62+00 *** $\Re s_{22}$
	1.024+00 *** $ s_{22} $
54.16+00 *** $\Re y_{11}$ or $\Re y_{ie}$ 11.10-03 *** $ y_{11} $ or $ y_{ie} $	load R_L and calculate Q_L using 50 ohm Z_0
-90.00+00 *** $\Re y_{12}$ or $\Re y_{re}$ 1.350-03 *** $ y_{12} $ or $ y_{re} $	0. ENT1 Im R_L
-45.00+00 *** $\Re y_{21}$ or $\Re y_{fe}$ 45.25-03 *** $ y_{21} $ or $ y_{fe} $	220. ENT1 Re R_L
84.51+00 *** $\Re y_{22}$ or $\Re y_{oe}$ 2.612-03 *** $ y_{22} $ or $ y_{oe} $	50. GSBe Z_0
	0.000+00 *** $\Re Q_L$
	629.6-03 *** $ Q_L $
	GSBB load Q_L into program
	GSBB execute design
	-9.018+00 *** $\Re s_{11}'$
	1.027+00 *** $ s_{11}' $
	9.018+00 *** $\Re 1/s_{11}'$
	973.4-03 *** $ 1/s_{11}' $
	616.0+00 *** $\Im Z_L$ for $Z_0 = 50 \Omega$
	105.9+00 *** $\Re Z_L$
	5.817+00 *** $Q_{min} = \Im Z_L / \Re Z_L$
	GSBE OE → OB conversion
	GSBE print stored params
-29.31+00 *** $\Re y_{1b}$ 44.44-03 *** $ y_{1b} $	
78.69+00 *** $\Re y_{rb}$ -1.275-03 *** $ y_{rb} $	
-42.35+00 *** $\Re y_{fb}$ -43.64-03 *** $ y_{fb} $	
84.51+00 *** $\Re y_{ob}$ 2.612-03 *** $ y_{ob} $	

A transmission line segment is designed to provide the load reactance of $j616$ ohms to resonate at 300 MHz. The real part of the load reactance is ignored since the Q of the resonant line will be much larger than the minimum Q required. The amplitude of the oscillation will increase until the amplifier becomes non-linear and its power gain is reduced to the point that Eq. (4-2.2) is satisfied with the equals sign.

Because of the high load reactance required, a high Z_o in the resonant line is desired. For the transmission line, use a #12 AWG wire spaced 0.25" off a ground plane as shown by Fig. 4-2.3.

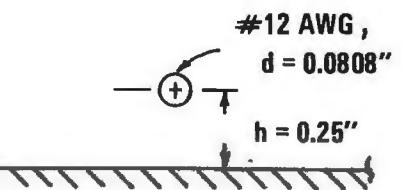


Figure 4-2.3 Air dielectric transmission line.

The characteristic impedance, Z_o , of this line is:

$$Z_o = \frac{138}{\sqrt{\epsilon_r}} \log \frac{4h}{d} \quad (4-2.5)$$

where ϵ_r is the relative dielectric constant of the dielectric, and is unity for air. Using this ϵ_r , and the d and h shown in Fig. 4-2.3, the characteristic impedance of the line is 150.6 ohms.

If the trimmer capacitor at the far end of the line is a 1 - 10 pF piston trimmer, its reactance with 10 pF at 300 MHz is:

$$X_c = -j/(2\pi f C) = -j53.05 \text{ ohms} \quad (4-2.6)$$

The length of transmission line that transforms $-j53.05$ ohms to $j616$ ohms is needed. Equation (1-1.1) can be manipulated to provide the solution for line length i.e.:

$$e^{2\gamma\ell} = \frac{\rho}{\rho_t} \quad (4-2.7)$$

where ρ_t is defined by Eq. (1-2.7). Since the transmission line load impedance is purely imaginary, as is the required input impedance, and the line is essentially lossless, the expressions for the reflection coefficients are the ratios of complex conjugates, and Eq. (4-2.7) can be reduced to the following forms:

$$\ell = \frac{\lambda}{2\pi} \left\{ \tan^{-1} \left(\frac{j \cdot Z_r}{Z_o} \right) - \tan^{-1} \left(\frac{j \cdot Z_s}{Z_o} \right) \right\} \quad (4-2.8)$$

where

$$\gamma = j\beta = j \frac{2\pi}{\lambda}$$

Using Eq. (4-2.8) with $Z_r = -j53.05$ ohms, $Z_s = 616$ ohms, $Z_o = 150.6$ ohms, and $\lambda = 3 \times 10^8 / \text{freq} = 1 \text{ meter} = 39.27 \text{ inches}$ yields $\ell = 10.46 \text{ inches}$. This length is too long to be practical. If capacity is added to the transistor collector circuit, less inductance will be required from the transmission line stub, and a shorter stub can be used. If 10 pF is added from the collector to ground, the susceptance of this capacitor will be:

$$B = 2\pi f C = (2\pi)(300 \times 10^6)(10^{-11}) = 18.85 \text{ mmho}$$

This susceptance is subtracted from the susceptance required from the transmission line stub to obtain the new transmission line susceptance and hence, input reactance:

$$B_{\text{line}} = \frac{-1}{616} - 0.01885 = -0.02047 \text{ mho}$$

or

$$X_{\text{line}} = \frac{-1}{B_{\text{line}}} = 48.84 \text{ ohms}$$

Using Eq. (4-2.8) with $Z_s = j48.84$ and the other parameters unchanged yields $\ell = 4.09$ inches, which is much more practical. With this line length, the trimmer capacitor value for oscillation at 400 MHz is calculated as shown by the HP-97 printout in Fig. (4-2.5). Again, neglecting the real part of Z_L , and accommodating the susceptance of the additional 10 pF at the transistor collector, the line must present a reactance of 36.22 ohms to the collector. Using Eq. (4-2.8) and solving for Z_r given $\ell = 4.09$ inches, $\lambda = 29.53$ inches, $Z_s = j36.22$ ohms and $Z_o = 150.6$ ohms yields $Z_r = -j110.8$ ohms. At 400 MHz, $-j110.8$ ohms is the

reactance of a 3.6 pF capacitor, which is within the tuning range of the piston trimmer capacitor. The complete schematic of the oscillator is shown in Fig. 4-2.4, which was breadboarded and does oscillate over the 300 to 400 MHz range. This type of oscillator is often used as the local oscillator in UHF tv tuners.

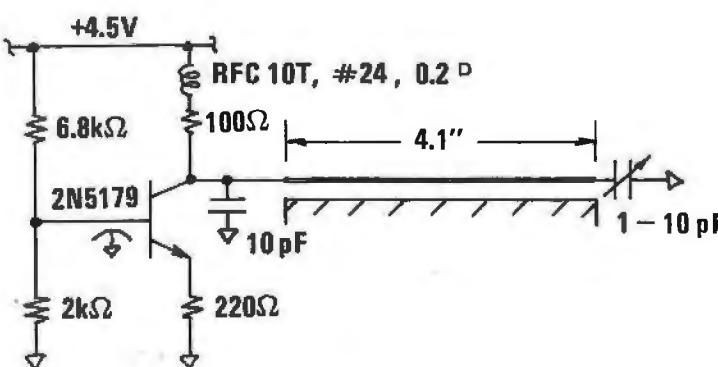


Figure 4-2.4 UHF oscillator schematic.

Load Program 4-3 and load y params		Load Program EEL-06A (EE pac)	
1. GSBe select y parameters		50. GSBe load reference Z & convert y parameters to s parameters	
10.7 ENT†	Im y _{ie}		
9.2 +P	Re y _{ie}		
1.-03 X			
11. GSBA ij			
-90. ENT†	y _{re}	GSBe print s parameters	
1.8-03 ENT†	y _{re}	139.2+00 *** 4s ₁₁	
12. GSBA ij		450.8-03 *** s ₁₁	
-34. ENT†	Im y _{fe}	95.19+00 *** 4s ₁₂	
25. +P	Re y _{fe}	77.48-03 *** s ₁₂	
1.-03 X			
21. GSBA ij		-36.90+00 *** 4s ₂₁	
4. ENT†	Im y _{oe}	1.369+00 *** s ₂₁	
.3 +P	Re y _{oe}	-15.96+00 *** 4s ₂₂	
1.-03 X		1.059+00 *** s ₂₂	
22. GSBA ij			
load R _L and calc P _L using 50 ohm Z _o			
GSBE print stored values			
49.31+00 ***	4y _{ie}	0. ENT† Im R _L	
14.11-03 ***	y _{ie}	220. ENT† Re R _L	
-90.00+00 ***	4y _{re}	50. GSBe Z _o	
1.800-03 ***	y _{re}	0.000+00 *** 4P _L	
625.6-03 ***	P _L	625.6-03 *** P _L	
GSBB load P _L into program			
GSBB execute design			
85.71+00 ***	4y _{fe}	-13.06+00 *** 4s ₁₁ '	
4.011-03 ***	y _{fe}	1.067+00 *** s ₁₁ '	
GSBB convert CE -> CB			
GSBE print CB values			
-31.45+00 ***	4y _{ib}	13.06+00 *** 41/s ₁₁ '	
40.44-03 ***	y _{ib}	937.0-03 *** 1/s ₁₁ '	
403.8+00 ***	Im Z _L for Z _o = 50		
116.3+00 ***	Re Z _L		
82.23+00 ***	4y _{rb}	3.471+00 *** Q _{min} = Im Z _L / Re Z _L	
-2.220-03 ***	y _{rb}		
-49.86+00 ***	4y _{fb}		
-39.24-03 ***	y _{fb}		
85.71+00 ***	4y _{ob}		
4.011-03 ***	y _{ob}		

Fig. 4-2.5 HP-97 printout for 400 MHz case.

Program Listing I

```

001 *LBLA LOAD S PARAMETERS
002 ENT1
003 +
004 2 calculate storage index
005 1
006 -
007 ST01
008 R↓ recover and store S11
009 ST01
010 ISZ1 increment index
011 R↓ recover and store S11
012 ST01
013 GT09 goto space and return
014 *LBLB ENTER LOAD REFLECTION COEF
015 ST06 store magnitude
016 X↑Y
017 ST07 store angle
018 GT09 goto space and return
019 *LBLC CALCULATE S11'
020 RCL3 |S11|
021 ST08
022 RCL4 ×S12
023 ST09 ×S12
024 RCLB |S11' = S11 +  $\frac{S_{12}S_{21}P_L}{1 - S_{22}P_L}$ 
025 STX8
026 RCLC ×S21
027 ST+9
028 RCL6 |PL1|
029 STX8
030 RCL7 ×PL
031 ST+9
032 RCL6 ×S22
033 RCL7 ×P
034 +
035 RCLD |S22|
036 RCL6 |PL|
037 X
038 CHS
039 +R
040 EEX
041 +
042 +P 1 - S22 · PL
043 ST+8
044 X↑Y
045 ST-9
046 RCL9 }  $\frac{S_{12} \cdot S_{21} \cdot P_L}{1 - S_{22} \cdot P_L}$  in polar
047 RCL8 } coordinates
048 +R
049 ST08 }  $\frac{S_{12} \cdot S_{21} \cdot P_L}{1 - S_{22} \cdot P_L}$  in rect
050 X↑Y coordinates
051 ST09
052 RCL2 S11
053 RCL1
054 +R
055 ST+8

```

REGISTERS

0	1 S ₁₁	2 ×S ₁₁	3 S ₁₂	4 ×S ₁₂	5	6 P _{L1}	7 ×P _L	8 scratch	9 scratch
S0 scratch	S1 scratch	S2 Im P _L	S3 Re P _L	S4 Z _o , Z _o	S5 scratch, X _{Z_o}	S6 scratch	S7	S8	S9
A	B S ₂₁	C ×S ₂₁	D S ₂₂	E ×S ₂₂	I index				

```

056 X↑Y
057 ST+9
058 RCL9 } S11 -  $\frac{S_{12} \cdot S_{21} \cdot P_L}{1 - S_{22} \cdot P_L}$  rect
059 RCL8 }
060 +P
061 ST08 } S11 -  $\frac{S_{12} \cdot S_{21} \cdot P_L}{1 - S_{22} \cdot P_L}$  polar
062 X↑Y
063 ST09
064 GT08 goto print subroutine
065 *LBLD CALCULATE P · S11' GIVEN P
066 P↑S
067 ST08 |P|
068 X↑Y
069 ST01 ×P
070 P↑S
071 RCL9 ×S11' 
072 RCL8 |S11'|
073 P↑S
074 STX8 |P| · |S11'|
075 X↑Y
076 ST+1 ×P + ×S11' 
077 RCL8
078 RCL1
079 P↑S
080 GT08 goto print subroutine
081 *LBLD CALCULATE 1/S11' 
082 1/X reciprocate magnitude
083 X↑Y
084 CHS change sign of angle
085 GT08 goto print subroutine
086 *LBLE CALCO Re, Im Z GIVEN XP!|P|↑Zo
087 P↑S
088 ST04 Zo
089 R↓
090 +R
091 ST02 Re P Z = Zo  $\frac{1 + P}{1 - P}$ 
092 EEX
093 + 1 + Re P
094 X↑Y
095 ST03 Im P
096 X↑Y
097 +P H + P1
098 STX4
099 X↑Y } Zo · (1 + P)
100 ST05
101 RCL3
102 CHS
103 EEX
104 RCL2
105 -
106 +P 1 - P
107 ST+4
108 X↑Y } calc Z
109 ST-5
110 RCL5

```

Program Listing II

```

111 RCL4
112 P↑S
113 +R
114 X↑Y
115 GT08 goto print subroutine
116 *LBLF CALCO 4P, |P| GIVEN Im Zo Re Zo
117 P↑S
118 ST04 Zo
119 R↓
120 ST03 Re Z
121 R↓
122 ST02 Im Z  $P = \frac{Z - Z_o}{Z + Z_o}$ 
123 R↑
124 R↑
125 - Zo - Re Z
126 +P
127 ST05 |Zo - Z|
128 X↑Y
129 ST06 ×(Zo - Z)
130 RCL2
131 RCL3
132 RCL4
133 +
134 +P |Zo + Z|
135 ST+5
136 X↑Y
137 ST-6
138 RCL5 |P|
139 RCL6 ×P
140 P↑S
141 GT08 goto print subroutine
142 *LBLG INTERCHANGE PORTS 1 AND 2
143 RCL6
144 RCL2
145 ST05 ×S11 ↔ ×S22
146 X↑Y
147 ST02
148 RCLD
149 RCL1
150 ST08 |S11| ↔ |S22|
151 X↑Y
152 ST01
153 RCLC
154 RCL4
155 ST05 ×S12 ↔ ×S21
156 X↑Y
157 ST04
158 RCLB
159 RCL3
160 ST08 |S12| ↔ |S21|
161 X↑Y
162 ST03
163 GT07 goto R/S lookup
164 *LBLH EXECUTE FA, 0, FD, 50 E
165 GSBA

```

Notes:

Flag 0 controls the print or R/S decision. It should be set or reset to reflect the users choice of printed output, or program halts for output respectively at the time the magnetic card is recorded.

LABELS					FLAGS		SET STATUS		
A Load S parameters	B Enter load reflection coef	C calculate S ₁₁ '	D calculate S ₁₁ ' · P	E P, Z _o → Z	0 print	FLAGS	TRIG	DISP	
a interchange ports 1&2	b fA, C, FD, E	c print s matrix	d calculate 1/S ₁₁ '	e Z _o , Z _o → P	1	ON OFF	DEG ■	FIX SCI	
0	1	2	3	4	2	1	GRAD RAD	ENG ■	
5 print or R/S subroutine	6	7 R/S Lockup	8 print & space subroutine	9 space subroutine	3	2	n 3		

PROGRAM 4-3 TRANSISTOR CONFIGURATION CONVERSION.

Program Description and Equations Used

This program allows conversion between common emitter, common base, and common collector configurations of transistor h parameters or y parameters, as well as conversions between the h and the y parameters.

The configuration conversions is done by operating on the y parameters and converting to and from the h parameters for data input and output. To make the program operate in either h or y parameters, the conversion process is skipped for the y parameter case. Label 7 of the program contains the coding that accomplishes the h to y, or y to h conversion. Label 7 is called at the beginning and end of the configuration conversion, and flag 0 is used to indicate whether or not the subroutine under label 7 should be skipped or not.

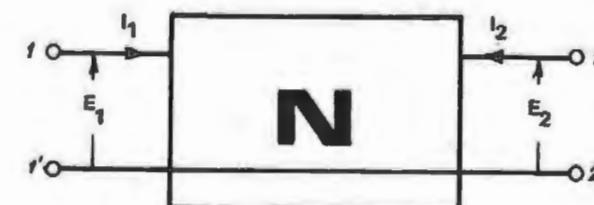


Figure 4-3.1 Two-port network conventions.

Given a two-port network with port voltages and currents as defined by Fig. 4-3.1, the y and h parameters are defined as follows:

h parameters

$$\begin{bmatrix} E_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \cdot \begin{bmatrix} I_1 \\ E_2 \end{bmatrix} \quad (4-3.1)$$

y parameters

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \cdot \begin{bmatrix} E_1 \\ E_2 \end{bmatrix} \quad (4-3.2)$$

The network ports correspondence to the transistor elements is shown in Table 4-3.1.

Table 4-3.1 Transistor 2-port correspondences

Configuration	1	1' or 2'	2
CE	B	E	C
CB	E	B	C
CC	B	C	E

The h parameters are converted to y parameters with the following transformation [15]:

$$\begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} = \frac{1}{h_{11}} \begin{bmatrix} 1, & -h_{12} \\ h_{21}, & h_{11}h_{22} - h_{12}h_{21} \end{bmatrix} \quad (4-3.3)$$

Likewise, the y parameters are converted to h parameters in similar fashion:

$$\begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} = \frac{1}{y_{11}} \cdot \begin{bmatrix} 1, & -y_{12} \\ y_{21}, & y_{11}y_{22} - y_{21}y_{12} \end{bmatrix} \quad (4-3.4)$$

Since the form of both conversions is identical, the same subroutine is used for both conversions (subroutine 7).

The y matrix representing the present transistor configuration is

transformed into another y matrix representing the new transistor configuration. This new matrix is designated y' for clarity. These transformations are:

For CE \rightarrow CB or CB \rightarrow CE,

(4-3.5)

$$\begin{bmatrix} y_{11}' & y_{12}' \\ y_{21}' & y_{22}' \end{bmatrix} = \begin{bmatrix} \{y_{11} + y_{22} + y_{12} + y_{21}\} & \{-(y_{12} + y_{22})\} \\ \{-(y_{21} + y_{22})\} & \{y_{11}\} \end{bmatrix}$$

For CC \rightarrow CE or CE \rightarrow CC,

(4-3.6)

$$\begin{bmatrix} y_{11}' & y_{12}' \\ y_{21}' & y_{22}' \end{bmatrix} = \begin{bmatrix} \{\, y_{11} \, \} \, \{ \, -(y_{11} + y_{12}) \, \} \\ \{-(y_{11} + y_{21})\} \, \{ y_{11} + y_{22} + y_{21} + y_{12} \} \end{bmatrix}$$

For CC \rightarrow CB,

(4-3.7)

$$\begin{bmatrix} y_{11}' & y_{12}' \\ y_{21}' & y_{22}' \end{bmatrix} = \begin{bmatrix} \{\, y_{22} \, \} \, \{ \, -(y_{21} + y_{22}) \, \} \\ \{-(y_{12} + y_{22})\} \, \{ y_{11} + y_{12} + y_{21} + y_{22} \} \end{bmatrix}$$

For CB \rightarrow CC,

(4-3.8)

$$\begin{bmatrix} y_{11}' & y_{12}' \\ y_{21}' & y_{22}' \end{bmatrix} = \begin{bmatrix} \{y_{11} + y_{22} + y_{21} + y_{12}\} \, \{-(y_{11} + y_{21})\} \\ \{-(y_{11} + y_{12})\} \, \{y_{11}\} \end{bmatrix}$$


After the respective conversion is complete, the y' matrix has replaced the y matrix in storage.

In looking over the various conversions, one will notice similarities in the operations used. There are four basic operations used to perform all the conversions:

User Instructions

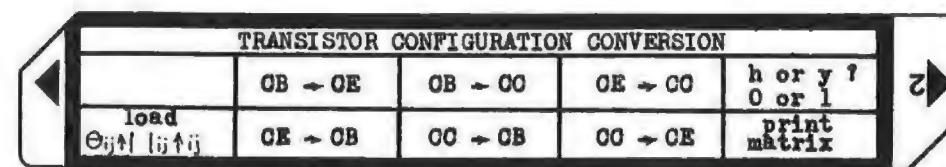- 1) no change;
- 2) $(y_{11} \text{ or } y_{22}) + y_{12}$;
- 3) $(y_{11} \text{ or } y_{22}) + y_{21}$; and
- 4) $y_{11} + y_{22} + y_{12} + y_{21}$.

The choice between y_{11} and y_{22} or y_{12} and y_{21} can be taken care of by interchanging the appropriate y matrix elements prior to these calculations. This matrix reordering is accomplished under label 3. The matrix conversion calculation is done under label 6 (two places); thus, these subroutines are selectively used to achieve all conversions.



STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
1	Load both sides of program card			
2	Select h or y matrix mode a) h parameters b) y parameters	0 1	f E f E	0 1
3	Load matrix to be converted a) angle of h_{ij} or y_{ij} b) magnitude of h_{ij} or y_{ij} c) subscript	θ_{ij} $ _{ij}$ ij	ENT↑ ENT↑ A	
	repeat this step for $ij = 11, 12, 21, 22$ in any order			
4	Select conversion desired a) common emitter to common base b) common base to common emitter c) common collector to common base d) common base to common collector e) common collector to common emitter f) common emitter to common collector	B f B C f C D f D		
5	Print converted matrix	E		θ_{11} $ _{11}$ θ_{12} $ _{12}$ θ_{21} $ _{21}$ θ_{22} $ _{22}$

Example 4-3.1

Convert the following common collector h parameter matrix to a common base h parameter matrix:

$$\begin{bmatrix} h_{ic} & h_{rc} \\ h_{fc} & h_{oc} \end{bmatrix} = \begin{bmatrix} 1000 + 40^\circ & 10^{-4} + -50^\circ \\ 100 + 40^\circ & 50 \times 10^{-6} + 0 \end{bmatrix}$$

PROGRAM INPUT	PROGRAM OUTPUT
40. ENT* Δh_{ic}	8. GSB8 select h parameters
1000. ENT1 $ h_{ic} $	
11. GSB8 ij	GSBC execute CC \rightarrow CB conv
-50. ENT* Δh_{rc}	GSBE print stored matrix
1. -04 ENT1 $ h_{rc} $	-9.97 + 00 *** Δh_{ib}
12. GSB8 ij	22.66 + 03 *** $ h_{ib} $
40. ENT* Δh_{fc}	-5.967 + 00 *** Δh_{rb}
100. ENT1 $ h_{fc} $	2.261 + 03 *** $ h_{rb} $
21. GSB8 ij	
8. ENT* Δh_{oc}	-179.3 + 00 *** Δh_{fb}
56. -06 ENT1 $ h_{oc} $	1.000 + 00 *** $ h_{fb} $
22. GSB8 ij	-45.37 + 00 *** Δh_{oc}
	1.130 - 03 *** $ h_{oc} $

Common base h parameter matrix from HP-97 output:

$$\begin{bmatrix} h_{ib} & h_{rb} \\ h_{fb} & h_{ob} \end{bmatrix} = \begin{bmatrix} 22600 + -9.971^\circ & 2261 + -9.967^\circ \\ 1.000 + -179.9^\circ & 1.130 \times 10^{-3} + -49.97^\circ \end{bmatrix}$$

Program Listing I

001 *LBLA	LOAD MATRIX ELEMENTS,	056 RCLD	calculate and store:
002 ENT1		057 GSB8	
003 +	calculate storage index	058 CHS	
004 2	from subscript	059 ST03	$y_{12}' = -(y_{12} + y_{22})$
005 1		060 X \leftrightarrow Y	
006 -		061 ST04	
007 ST01		062 X \leftrightarrow Y	
008 RJ	recover and store $ l_{ij} $	063 RCLC	
009 ST01		064 RCLB	
010 IS21	increment storage index	065 GSB8	calculate and store:
011 RJ	recover and store θ_{ij}	066 RCLE	
012 ST01		067 RCLD	
013 GT04	return control to keyboard	068 GSB8	
014 *LBLC	CONVERT CC \rightarrow CB PARAMETERS	069 CHS	
015 GSB8	take [h] \rightarrow [y] \rightarrow [y']	070 RCL2	$y_{11}' = -y_{22} + (y_{21} + y_{12}') + y_{11}$
016 *LBL3	reorder matrix elements	071 RCL1	
017 RCL1		072 GSB8	$= y_{11} + y_{12} + y_{21} + y_{22}$
018 RCLD		073 ST01	
019 ST01	$ l_{11} \Rightarrow l_{22} $	074 R \downarrow	
020 R \downarrow		075 ST02	
021 ST0D		076 RTN	
022 RCL3		077 *LBLd	CONVERT CE \rightarrow CO PARAMETERS
023 RCLB		078 *LBLD	CONVERT CO \rightarrow CE PARAMETERS
024 ST03	$ l_{12} \Rightarrow l_{21} $	079 GSB6	take [h] \rightarrow [y] \rightarrow [y']
025 R \downarrow		080 GT07	convert [y'] \rightarrow [h]
026 ST0B		081 *LBLc	CONVERT CB \rightarrow CO PARAMETERS
027 RCL2		082 GSB6	take [h] \rightarrow [y] \rightarrow [y']
028 RCLE		083 GT03	reorder matrix elements
029 ST02	$\theta_{11} \Rightarrow \theta_{22}$	084 *LBL6	
030 R \downarrow		085 GSB7	transform [h] \rightarrow [y]
031 ST0E		086 RCL2	
032 RCL4		087 RCL1	calculate and store:
033 RCLC		088 RCL4	
034 ST04	$\theta_{12} \Rightarrow \theta_{21}$	089 RCL3	
035 R \downarrow		090 GSB8	
036 ST0C		091 CHS	$y_{12}' = -(y_{11} + y_{12})$
037 GT07	convert y' \rightarrow h	092 ST03	
038 *LBLK	CONVERT OB \rightarrow CE PARAMETERS	093 R \downarrow	
039 *LBLB	CONVERT CE \rightarrow OB PARAMETERS	094 ST04	
040 GSB6	take [h] \rightarrow [y] \rightarrow [y']	095 RCL2	
041 GT07	convert [y'] \rightarrow [h]	096 RCL1	calculate and store:
042 *LBL6		097 RCLC	
043 GSB7	convert h params to y params	098 RCLB	
044 RCLC		099 GSB8	
045 RCLB	calculate and store:	100 CHS	$y_{21}' = -(y_{11} + y_{21})$
046 RCLE		101 ST0B	
047 RCLD		102 X \leftrightarrow Y	
048 GSB8		103 ST0C	
049 CHS	$y_{21}' = -(y_{21} + y_{22})$	104 X \leftrightarrow Y	
050 ST0B		105 RCL4	
051 R \downarrow		106 RCL3	calculate and store:
052 ST0C		107 GSB8	
053 RCL4		108 RCL2	
054 RCL3		109 RCL1	$y_{22}' = y_{11} + y_{12} + y_{21} + y_{22}$
055 RCLE		110 GSB8	
REGISTERS			
0	1	$ l_{11} $	2 θ_{11}
S0	S1	S2	S3
A	B	$ l_{21} $	C θ_{21}
D	E	$ l_{22} $	F θ_{22}
	I		index

Program Listing II

LABELS					FLAGS	SET STATUS		
A load data	B CE → CB	C CC → CB	D CC → CE	E print matrix	0 set for y	FLAGS	TRIG	DISP
a	b CB → CE	c CB → CC	d CE → CC	e select y or h	1	0 ■	DEG ■	FIX
0	1	2	3 rearrange matrix	4 space & rtn subroutine	2	1	GRAD	SCI
5 print subroutine	6 [h] → [h']	7 [h] ≠ [y]	8 complex add	9 complex multiply	3	2	RAD	ENG ■
						3		n 3

```

111 CHS
112 RCLC
113 RCLD
114 GSB8
115 STOD
116 R↓
117 STOE
118 RTN return to main program
119 *LBL7 subroutine to convert [y]≠[h]
120 F0? if flag 0 is set
121 RTN
122 RCL2
123 RCL1 given:
124 RCLD
125 RCLE
126 GSB9
127 ST06
128 R↓
129 ST07
130 RCL4 calculate and store the determinant of A:
131 RCL3
132 RCLB
133 RCLC
134 GSB9
135 CHS
136 RCL7
137 RCL6
138 GSB8
139 ST06
140 R↓
141 ST07
142 RCL2 calculate and store:
143 CHS
144 ST02
145 RCL1
146 1/X
147 ST01
148 RCL3
149 CHS
150 RCL4
151 GSB9
152 ST03
153 R↓
154 ST04
155 RCL2
156 RCL1 calculate and store:
157 RCLB
158 RCLC
159 GSB9
160 ST08
161 R↓
162 ST0C
163 RCL2
164 RCL1
165 RCL6
166 RCL7 calculate and store:
167 GSB9
168 STOD
169 R↓
170 STOE a22' = ΔA
171 RTN return to subroutine call
172 GT02 goto R/S lockup
173 *LBL8 complex addition subroutine
174 +R input and output are in polar co-ordinates
175 R↓
176 R↓
177 +R
178 X≠Y
179 R↓
180 +
181 R↓
182 +
183 R↑
184 +P
185 RTN
186 *LBL9 complex multiply subroutine
187 R↓ input and output are in polar co-ordinates
188 X
189 R↓
190 +
191 R↑
192 +R
193 +P
194 RTN
195 *LBL0 PRINT STORED MATRIX
196 RCL1
197 RCL2
198 GSB5
199 RCL3
200 RCL4
201 GSB5
202 RCLB
203 RCLC
204 GSB5
205 RCLD
206 RCLE
207 *LBL5 print subroutine
208 PRTX-- or R/S
209 X≠Y
210 PRTX-- or R/S
211 *LBL4 space and return subroutine
212 SPC
213 RTN
214 *LBL2 R/S lockup subroutine
215 R/S
216 GT02
217 *LBL6 SELECT y OR h PARAMETERS
218 CFB
219 X>0? set flag 0 if "1" entered
220 SF0
221 RTN return to keyboard control

```

PROGRAM 4-4 COMPLEX 2x2 MATRIX OPERATIONS – PART 1.

Program Description and Equations Used

This program is one of two programs to manipulate complex 2x2 matrices. When dealing with high frequency amplifiers employing feedback, and input and output networks, one way of obtaining the overall amplifier response is to operate on the matrices that describe these 2-port networks. Shunt feedback may be included within the transistor transfer matrix through Y matrix addition. Y matrices can be converted to Z matrices using the complex matrix inverse routine. Series feedback is included by adding Z matrices. The input and output networks are included by multiplying ABCD (transmission) matrices.

This program will perform matrix addition ($A + B \rightarrow A$), subtraction ($A - B \rightarrow A$), multiplication ($AB \rightarrow A$), and interchange ($A \leftrightarrow B$) with 2x2 matrices having complex coefficients. Data entry and output may be in either rectangular or polar format. All data stored and used by the program is in rectangular format. If flag 1 is set, polar format is indicated and the data is converted to and from rectangular format upon data input or output respectively.

The program operation is very straightforward, and matrix operations are done in the conventional manner. Two subroutines are used, one for complex addition and the other for complex multiplication. See [6], [14] for matrix algebra details.

Both this program and the companion program (Program 4-5) share common register storage allocations; thus, matrix manipulations requiring functions contained in different programs are easily accommodated.

Matrix addition and subtraction:

$$\begin{bmatrix} a_{11} & a_{12} \\ a_{21} & a_{22} \end{bmatrix} \pm \begin{bmatrix} b_{11} & b_{12} \\ b_{21} & b_{22} \end{bmatrix} = \begin{bmatrix} r_{11} & r_{12} \\ r_{21} & r_{22} \end{bmatrix}$$

$$r_{11} = a_{11} \pm b_{11}$$

$$r_{22} = a_{22} \pm b_{22}$$

$$r_{21} = a_{21} \pm b_{21}$$

$$r_{12} = a_{12} \pm b_{12}$$

The R matrix replaces the A matrix at the completion of the routine.

Matrix multiplication:

$$\begin{bmatrix} a_{11} & a_{12} \\ a_{21} & a_{22} \end{bmatrix} \times \begin{bmatrix} b_{11} & b_{12} \\ b_{21} & b_{22} \end{bmatrix} = \begin{bmatrix} r_{11} & r_{12} \\ r_{21} & r_{22} \end{bmatrix}$$

$$r_{11} = a_{11} b_{11} + a_{12} b_{21}$$

$$r_{12} = a_{11} b_{12} + a_{12} b_{22}$$


$$r_{21} = a_{21} b_{11} + a_{22} b_{21}$$

$$r_{22} = a_{21} b_{12} + a_{22} b_{22}$$

Again, the R matrix replaces the A matrix at the completion of the routine.

Matrix interchange:
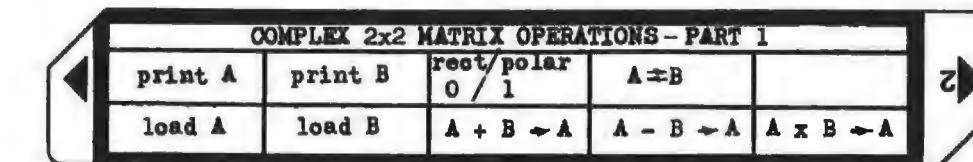
$$\begin{bmatrix} a_{11} & a_{12} \\ a_{21} & a_{22} \end{bmatrix} \leftrightarrow \begin{bmatrix} b_{11} & b_{12} \\ b_{21} & b_{22} \end{bmatrix} \quad \begin{array}{l} a_{11} \rightleftharpoons b_{11} \\ a_{12} \rightleftharpoons b_{12} \\ a_{21} \rightleftharpoons b_{21} \\ a_{22} \rightleftharpoons b_{22} \end{array}$$



STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
1	Load both sides of the program card			
2	Select polar or rectangular format		f 0 f 0 f 0	0 (rect) 1 (polar) 0 (rect) ⋮
3	Load A matrix in selected format (step 2) rectangular format shown here		ENT ↴ ENT ↴ A	
a)	imaginary part of matrix element	Im a _{ij}		
b)	real part of matrix element	Re a _{ij}		
c)	load element subscript	ij		
Do this step for subscripts 11, 12, 21, 22 in any order.				
4	Load B matrix in selected format (step 2) polar format shown here		ENT ↴ ENT ↴ B	
a)	load angle of matrix element	∠ b _{ij}		
b)	load magnitude of matrix element	b _{ij}		
c)	load element subscript	ij		
Do this step for subscripts 11, 12, 21, 22 in any order				
5	To print matrices in chosen format (say polar)		f *	X ₁₁ X ₁₂ X ₂₁ X ₂₂
a)	A matrix -- use f A			
b)	B matrix -- use f B			



Example 4-4.

Give

$$A = \begin{bmatrix} (3 + j4) & (4 + j5) \\ (5 + j6) & (2 + j4) \end{bmatrix}, \quad B = \begin{bmatrix} (4 + j5) & (5 + j6) \\ (6 + j7) & (7 + j8) \end{bmatrix}$$

Load the above matrices, store them on a data card, then perform A + B, A - B, and A x B. The HP-97 printout for the matrix loading is shown below, and the program output is shown on the next page. The B matrix is loaded in scrambled order to demonstrate the free form loading feature of the program.

HP-97 PRINTOUT FOR EXAMPLE 4-4-1 INPUT

A MATRIX LOADING	B MATRIX LOADING
4.00 ENT† Im a ₁₁	6.00 ENT† Im b ₁₂
3.00 ENT† Re a ₁₁	5.00 ENT† Re b ₁₂
11.00 GSBA ij	12.00 GSBB ij
5.00 ENT† Im a ₁₂	7.00 ENT† Im b ₂₁
4.00 ENT† Re a ₁₂	6.00 ENT† Re b ₂₁
12.00 GSBA ij	21.00 GSBB ij
6.00 ENT† Im a ₂₁	8.00 ENT† Im b ₂₂
5.00 ENT† Re a ₂₁	7.00 ENT† Re b ₂₂
21.00 GSBA ij	22.00 GSBB ij
4.00 ENT† Im a ₂₂	5.00 ENT† Im b ₁₁
3.00 ENT† Re a ₂₂	4.00 ENT† Re b ₁₁
22.00 GSBA ij	11.00 GSBB ij

HP-97 PRINTOUT FOR EXAMPLE 4-4.1 OUTPUT

GSBa print A matrix 4.00 *** Im a ₁₁ 3.00 *** Re a ₁₁	GSBC execute matrix addition GSBa print resultant matrix 9.00 *** Im r ₁₁ 7.00 *** Re r ₁₁
5.00 *** Im a ₁₂ 4.00 *** Re a ₁₂	11.00 *** Im r ₁₂ Note that 9.00 *** Re r ₁₂ the R matrix has replaced the A matrix in storage.
6.00 *** Im a ₂₁ 5.00 *** Re a ₂₁	13.00 *** Im r ₂₁ 11.00 *** Re r ₂₁
4.00 *** Im a ₂₂ 2.00 *** Re a ₂₂	12.00 *** Im r ₂₂ 9.00 *** Re r ₂₂
<hr/>	
GSBb print B matrix 5.00 *** Im b ₁₁ 4.00 *** Re b ₁₁	Reload A and B matrices by reading data card.
6.00 *** Im b ₁₂ 5.00 *** Re b ₁₂	GSBD execute mat subtraction
7.00 *** Im b ₂₁ 6.00 *** Re b ₂₁	GSBa print resultant matrix -1.00 *** Im r ₁₁ -1.00 *** Re r ₁₁
8.00 *** Im b ₂₂ 7.00 *** Re b ₂₂	-1.00 *** Im r ₁₂ -1.00 *** Re r ₁₂
<hr/>	
	-1.00 *** Im r ₂₁ -1.00 *** Re r ₂₁
<hr/>	
	-4.00 *** Im r ₂₂ -5.00 *** Re r ₂₂
<hr/>	
	Reload A and B matrices by reading data card.
<hr/>	
	GSBE exec mat multiplication
<hr/>	
	GSBa print resultant matrix 89.00 *** Im r ₁₁ -15.00 *** Re r ₁₁
<hr/>	
	105.00 *** Im r ₁₂ -21.00 *** Re r ₁₂
<hr/>	
	87.00 *** Im r ₂₁ -26.00 *** Re r ₂₁
<hr/>	
	104.00 *** Im r ₂₂ -29.00 *** Re r ₂₂

Example 4-4.2

Because the resultant matrix replaces the A matrix in storage, operations may be chained. This example demonstrates that chaining ability starting with the A and B matrices given in Example 4-4.1.

GSBE execute matrix multiplication: A x B → A
GSBC execute matrix addition: AB + B → A
GSBd execute matrix interchange: AB + B ↛ B
GSBE execute matrix multiplication: B(AB + B) → A
GSBa print resultant A matrix
651.00 *** Im a ₁₁ -1194.00 *** Re a ₁₁
792.00 *** Im a ₁₂ -1401.00 *** Re a ₁₂
957.00 *** Im a ₂₁ -1640.00 *** Re a ₂₁
1162.00 *** Im a ₂₂ -1923.00 *** Re a ₂₂

The same data can be outputted (printed) in polar format using the polar-rectangular toggle under label "c" to bring a 1 to the display.

GSBc } use polar-rectangular selection toggle
GSBc }
GSBa print A matrix in polar format
151.40 *** a ₁₁ 1359.94 *** a ₁₁
150.52 *** a ₁₂ 1609.37 *** a ₁₂
149.73 *** a ₂₁ 1898.80 *** a ₂₁
148.86 *** a ₂₂ 2246.81 *** a ₂₂

Program Listing I

```

001 *LBLA LOAD MATRIX A
002 SF2 indicate matrix A
003 *LBLB LOAD MATRIX B
004 1
005 2
006 - calculate storage register
007 X>0? location from subscript
008 8
009 X>0?
010 -
011 ENT↑
012 +
013 3
014 +
015 EEX
016 F2?
017 CLX
018 +
019 R↓
020 F1? if polar data, convert
021 →R to rectangular format
022 R↑ recover storage index
023 GSB8 store matrix element
024 GT01 goto space and return
025 *LBLa PRINT MATRIX A
026 EEX initialize index register
027 STOI for matrix A
→028 GT0e jump
029 *LBLb PRINT MATRIX B
030 2 initialize index register
031 STOI for matrix B
→032 *LBLc matrix print subroutine
033 GSB4 recall matrix element
034 F1? convert to polar format
035 →P if flag 1 is set
036 X↑Y
037 PRTX print matrix element
038 X↑Y as complex quantity
039 PRTX ←(may be R/S statements
040 SPC if desired)
041 ISZI increment index by 2
042 ISZI
043 8
044 RCLI
045 X≤Y? test for loop exit
→046 GT0e
047 GT01 goto space and return
048 *LBLD ADD A AND B MATRICES
049 CF0 indicate matrix addition
→050 GT0C jump
051 *LBLE SUBTRACT A AND B MATRICES
052 SF0 indicate matrix subtraction
→053 *LBLC
054 8 initialize index register
055 STOI

```

003 *LBLB LOAD MATRIX B

056 *LBL0 matrix add/subtract subr

057 GSB4 recall matrix B element

058 F0? change sign of element parts if subtraction is indicated

059 CHS

060 X↑Y

061 F0?

062 CHS

063 X↑Y

064 DSZI decrement index

065 GSB4 recall matrix A element

066 GSB2 perform complex addition

067 GSB5 store result as matrix A

068 DSZI decrement index and

069 GT00 test for loop exit

070 GT01 goto space and return

071 *LBLF MATRIX MULTIPLICATION

072 1 calculate and temporarily store:

073 2

074 SF2

075 GSB7

076 3

077 6

078 GSB7

079 9

080 GSB8

081 1 calculate and temporarily store:

082 4

083 SF2

084 GSB7

085 3

086 8

087 GSB7

088 STOA

089 X↑Y

090 STOB

091 2 calculate and temporarily store:

092 5

093 SF2

094 GSB7

095 7

096 6

097 GSB7

098 STOC

099 X↑Y

100 STOD

101 4 calculate and store:

102 5

103 SF2

104 GSB7

105 7

106 8

107 GSB7

108 7

109 GSB8

$a_{11} \cdot b_{11} + a_{12} \cdot b_{21} = r_{11}$

$a_{11} \cdot b_{12} + a_{12} \cdot b_{22} = r_{12}$

$a_{21} \cdot b_{11} + a_{22} \cdot b_{21} = r_{21}$

$a_{21} \cdot b_{12} + a_{22} \cdot b_{22} = r_{22}$

REGISTERS

⁰ scratch	¹ Re a ₁₁	² Re b ₁₁	³ Re a ₁₂	⁴ Re b ₁₂	⁵ Re s ₂₁	⁶ Re b ₂₁	⁷ Re a ₂₂	⁸ Re b ₂₂	⁹ temp Re r ₁₁
S0 scratch	S1 Im a ₁₁	S2 Im b ₁₁	S3 Im a ₁₂	S4 Im b ₁₂	S5 Im s ₂₁	S6 Im b ₂₁	S7 Im a ₂₂	S8 Im b ₂₂	S9 temp Im r ₁₁
A temporary Re r ₁₂	B temporary Im r ₁₂	C temporary Re r ₂₁	D temporary Im R ₂₁	E scratchpad	I index				

Program Listing II

```

110 9
111 GSB9
112 EEX
113 GSB8
114 RCLB
115 RCLA
116 3
117 GSB8
118 RCLD
119 RCLC
120 5
121 GSB8
122 *LBL1 space and return subroutine
123 SPC
124 RTN
125 *LBL2 complex add subroutine
126 X↑Y
127 R↓
128 +
129 RCLB
130 RCLI
131 FRC
132 EEX
133 1
134 X
135 GSB9
136 STOE
137 R↓
138 STOI
139 R↑
140 ENT↑
141 R↑
142 X
143 R↑
144 RCLI
145 X↑Y
146 X
147 LSTX
148 R↓
149 -
150 R↑
151 RCLE
152 X
153 R↑
154 RCLI
155 X
156 +
157 X↑Y
158 F2?
159 GT07 jump if first product
160 0 recall first product
161 GSB9 from scratchpad storage

```

$r_{11} \rightarrow a_{11}$

$r_{12} \rightarrow a_{12}$

$r_{21} \rightarrow a_{21}$

$r_{11} \rightarrow a_{11}$

$r_{12} \rightarrow a_{12}$

$r_{21} \rightarrow a_{21}$

$r_{22} \rightarrow a_{22}$

$a_{11} \cdot b_{11} + a_{12} \cdot b_{21} = r_{11}$

$a_{11} \cdot b_{12} + a_{12} \cdot b_{22} = r_{12}$

$a_{21} \cdot b_{11} + a_{22} \cdot b_{21} = r_{21}$

$a_{21} \cdot b_{12} + a_{22} \cdot b_{22} = r_{22}$

LABELS					FLAGS		SET STATUS	
A Load A	B Load B	C A+B→A	D A-B→A	E Ax B→A	0 subtract	FLAGS	TRIG	DISP
a print A	b print B	c polar/rect 1 / 0	d A±B	e print loop start	1 polar	ON OFF	DEG	SCI
0 matrix add/subtract	1 space& rtn	2 complex addition	3	4 complex recall	2 don't continue summation	1	GRAD	ENG
5 complex store	6 A±B subroutine	7 matrix multiplication	8 store index & complex sto	9 store index & complex rel	3	2	RAD	■
						3		n 3

PROGRAM 4-5 COMPLEX 2x2 MATRIX OPERATIONS – PART 2.

Program Description and Equations Used

This program is the second of two programs to manipulate complex 2x2 matrices. This program will perform matrix inverse ($A^{-1} \rightarrow A$), matrix transpose ($A^T \rightarrow A$), matrix complex conjugate ($A^* \rightarrow A$), and matrix interchange ($A \leftrightarrow B$). Because the resultant matrix from the matrix operation replaces the A matrix, chaining of matrix operations without data re-entry is easily done.

This program shares common register storage with Program 4-4, hence, matrix operations that require concatenation of routines contained in two different programs can be done without reloading any previous data.

The user may elect to work in either the polar or the rectangular co-ordinate systems, however, all data is stored in rectangular format. If flag 1 is set, the input data is converted from polar to rectangular, and vice-versa for output.

The algorithms used are:

Matrix inverse:

$$A^{-1} = \frac{1}{|A|} \begin{bmatrix} a_{22} & -a_{12} \\ -a_{21} & a_{11} \end{bmatrix} \quad (4-5.1)$$

where $|A|$ is the determinant of A,

$$|A| = a_{11} \cdot a_{22} - a_{21} \cdot a_{12} \quad (4-5.2)$$

Matrix transpose:

$$A^T = \begin{bmatrix} a_{11} & a_{21} \\ a_{12} & a_{22} \end{bmatrix}. \quad (4-5.3)$$

User Instructions

Matrix complex conjugate:


$$A^* = \begin{bmatrix} a & * \\ 11 & 12 \\ a & * \\ 21 & 22 \end{bmatrix}$$

Matrix interchange, see Eq. (4-4.3).

COMPLEX 2x2 MATRIX OPERATIONS - PART 2

print A	print B	polar/rect 1/0	$A \pm B$	calculate $ A $
load A	load B	$A^{-1} \rightarrow A$	$A^T \rightarrow A$	$A^* \rightarrow A$

STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
1	Load both sides of the program card			
2	Select polar or rectangular format		f 0 f 0 f 0 ⋮	0 (rect) 1 (polar) 0 (rect) ⋮
3	Load matrix A in selected format (rect shown)			
	a) load imaginary part of matrix element	Im a_{ij}	ENT	
	b) load real part of matrix element	Re a_{ij}	ENT	
	c) load subscript of matrix element	ij	A	
	Repeat this step for ij 11, 12, 21, 22 in any order.			
4	Load matrix B in selected format (polar used)			
	a) load angle of matrix element	$\angle b_{ij}$	ENT	
	b) load magnitude of matrix element	$ b_{ij} $	ENT	
	c) load subscript of matrix element	ij	B	
	Repeat this step for ij 11, 12, 21, 22 in any order.			
5	To print matrices in chosen format (say polar)			
	a) A matrix -- use f A		f *	X_{11}
	b) B matrix -- use f B			$ _{11}$
				X_{12}
				$ _{12}$
				X_{21}
				$ _{21}$
				X_{22}
				$ _{22}$

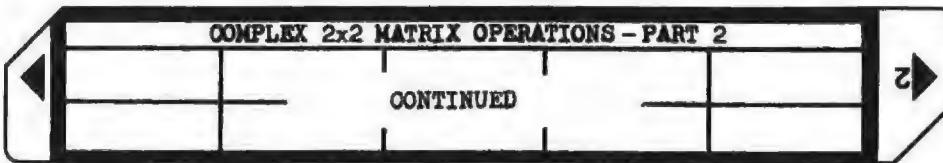

Example 4-5.

Given the A and B matrices of Example 4-4.1, calculate $B^{-1}AB$. The loading of the A and B matrices is shown in Example 4-4.1, and is omitted here for brevity (they were actually loaded from the magnetic data card from Program 4-4).

Load Program 4-4, and load A and B matrices

GSBE form AB → A

Load this program (Program 4-5)

GSEa interchange AB and

GSBC form $B^{-1} \rightarrow A$

Reload Program 4-

GSBE form $B^{-1}AB \rightarrow A$

GSBa print result

-54.50 来来来 Im a_{12}
-55.25 来来来 Re a_{12}

$$\begin{array}{lll} 49.50 & \text{***} & \text{Im } a_{21} \\ 45.75 & \text{***} & \text{Re } a_{21} \end{array}$$

$$56.25 \quad *** \quad \text{Im } a_{22} \\ 53.00 \quad *** \quad \text{Re } a_{22}$$

Program Listing I

```

001 *LBLA LOAD MATRIX A
002 SF2 indicate matrix A
003 *LBLB LOAD MATRIX B
004 1
005 2
006 -
007 X>?
008 8 calculate storage register
009 X>? location from subscript
010 -
011 ENT†
012 +
013 3
014 +
015 EEX
016 F2?
017 CLK
018 +
019 R↓
020 F1? if polar data, convert
021 →R to rectangular format
022 R↑ recover storage index
023 GSB8 store matrix element
024 GT01 goto space and return subr
025 *LBLa PRINT MATRIX A
026 EEX initialize index register
027 ST01 for matrix A
028 GT07 jump
029 *LBLb PRINT MATRIX B
030 2 initialize index register
031 ST01 for matrix B
032 *LBL7 matrix print subroutine
033 GSB4 recall matrix element
034 GSB0 print matrix element
035 ISZI increment index by 2
036 ISZI
037 8
038 RCLI test for loop exit
039 X≤Y?
040 GT07
041 GT01 goto space and return subr
042 *LBLc CALCULATE DETERMINANT OF A
043 SF2 indicate determinant calc
044 *LBLd CALCULATE A MATRIX INVERSE
045 EEX
046 GSB9 calculate and scratchpad
047 7 store a11·a22
048 GSB9
049 GSB3
050 9
051 GSB8
052 3
053 GSB9 calculate a21·a12 and
054 5 subtract from a11·a22 which
055 GSB8 is stored
056 9
057 GSB9
058 GSB2
059 F2? if determinant calculation
060 GT00 goto print routine
061 →P
062 1/X calculate and store 1/|AI|
063 X=Y
064 CHS
065 X=Y
066 →R
067 9
068 GSB8
069 3 calculate and store:
070 GSB9
071 9
072 GSB8 - a12 → a12
073 3
074 GSB8
075 5 calculate and store:
076 GSB9
077 9
078 GSB8 - a21 → a12
079 5
080 GSB8
081 EEX
082 GSB9
083 ST0A
084 X=Y
085 ST0B
086 7
087 GSB9
088 9 a22 → a11
089 GSB9
090 GSB3
091 EEX
092 GSB8
093 RCLB
094 RCLA
095 9 calculate and store:
096 GSB9
097 GSB3
098 7 a11 → a22
099 GSB8
100 GT01
101 *LBLe multiply and change sign
102 GSB9 subroutine
103 GSB3
104 CHS
105 X=Y
106 CHS
107 X=Y
108 RTN

```

REGISTERS

0 scratchpad	1 Re a ₁₁	2 Re b ₁₁	3 Re a ₁₂	4 Re b ₁₂	5 Re a ₂₁	6 Re b ₂₁	7 Re a ₂₂	8 Re b ₂₂	9 Re 1/ AI
S0 scratchpad	S1 Im a ₁₁	S2 Im b ₁₁	S3 Im a ₁₂	S4 Im b ₁₂	S5 Im a ₂₁	S6 Im b ₂₁	S7 Im a ₂₂	S8 Im b ₂₂	S9 Im 1/ AI
A scratchpad	B scratchpad	C	D	E scratchpad	I index / scratch				

Program Listing II

```

109 *LBL0 common output subroutine
110 F1? convert to polar if required
111 →P
112 X=Y print both parts of a
113 PRTX complex number
114 X=Y (may be R/S statements
115 PRTX if desired)
116 GT01 goto space and return subr
117 *LBL2 complex add subroutine
118 X=Y
119 R↓
120 +
121 R↓
122 +
123 R↑
124 RTN
125 *LBL3 complex multiply subroutine
126 ST0E
127 R↓
128 ST0I
129 R↓
130 ENT†
131 R↑
132 X
133 R↑
134 RCLI
135 X=Y
136 X
137 LSTX
138 R↓
139 -
140 R↑
141 RCLC
142 X
143 R↑
144 RCLI
145 X
146 +
147 X=Y
148 RTN
149 *LBLc POLAR/RECTANGULAR TOGGLE
150 CF1 indicate rectangular format
151 CLX and place a zero in display
152 RTN return to keyboard control
153 *LBLd
154 SF1 indicate polar format and
155 EEX place a one in the display
156 RTN return to keyboard control
157 *LBLd MATRIX INTERCHANGE
158 8 initialize index
159 ST01
160 *LBLe loop start
161 GSB4 recall corresponding
162 DSZI matrix elements
163 GSB4
164 ISZI
165 GSB5
166 DSZI interchange and store
167 R↓ corresponding matrix
168 R↑ elements
169 GSB5
170 DSZI decrement index and
171 GT06 test for loop exit
172 GT01 goto space and return subr
173 *LBLD CALCULATE MATRIX A TRANSPOSE
174 3 recall and scratchpad store
175 GSB9 a12
176 ST0A
177 X=Y
178 ST0B
179 5 recall a21 and store in
180 GSB9 a12 location
181 3
182 GSB8
183 RCLB
184 RCLA recall a12 from scratchpad
185 5 and store in a21 location
186 GSB8
187 GT01 goto space and return subr
188 *LBL9 store recall index subr
189 ST0I
190 R↓
191 *LBL4 complex recall subroutine
192 P↑S
193 RCLI
194 P↑S
195 RCLI
196 RTN
197 *LBL8 store storage index subr
198 ST0I
199 R↓
200 *LBL5 complex storage subroutine
201 ST0I
202 X=Y
203 P↑S
204 ST0I
205 P↑S
206 RTN
207 *LBLc CALCULATE MAT A COMPLEX CONJ
208 P↑S reverse the sign of the
209 1 imaginary parts of the
210 CHS matrix elements
211 STX7
212 STX5
213 STX3
214 STX1
215 P↑S
216 *LBL1 space and return subroutine
217 SPC
218 RTN

```

LABELS					FLAGS	SET STATUS		
A load A	B load B	C A ⁻¹ →A	D A ^T →A	E A*→A	0	FLAGS	TRIG	DISP
a print A	b print B	c polar/rect	d A ⁼ B	e calc AI	f polar	ON OFF	users choice	
0 complex print	1 space & return	2 complex add	3 complex multiply	4 complex recall	5 used with	0	DEG	FIX
5 complex store	6 A ⁼ B subroutine	7 common print routine	8 sto index & cmplx store	9 store index & cmplx ret	3	1	GRAD	SCI
						2	RAD	ENG
						3		n

Part 5
ENGINEERING
MATHEMATICS

PROGRAM 5-1 ELLIPTIC INTEGRALS AND FUNCTIONS.

Program Description and Equations Used

This program calculates complete elliptic integrals of the first kind and the following elliptic functions: elliptic sine ($\text{sn}(u,k)$), elliptic cosine ($\text{cn}(u,k)$), elliptic delta ($\text{dn}(u,k)$), and elliptic amplitude ($\text{am}(u,k)$).

The elliptic integral of the first kind is defined by Eq. (5-1.1), and the complete elliptic integral of the first kind is defined by Eq. (5-1.2), which can be evaluated using the infinite product shown in Eqs. (5-1.3) through (5-1.6). The product is terminated when k_m becomes smaller than 10^{-10} . Generally this condition is achieved after the 3rd term of the series, hence, the series converges rapidly. As the modulus, k , approaches 1, more iterations are required, e.g., $K(.9) = 2.280549137$ requires 4 iterations and $K(.999) = 4.495596396$ requires 5 iterations.

$$u(\phi, k) = \int_0^\phi (1 - k^2 \sin^2 x)^{-\frac{1}{2}} dx \quad (5-1.1)$$

$$K(k) = u(\frac{\pi}{2}, k) \quad (5-1.2)$$

$$K(k) = \frac{\pi}{2} \prod_{m=0}^{\infty} (1 + k_{m+1}) \quad (5-1.3)$$

$$k_{m+1} = (1 - k_m^2) / (1 + k_m^2) \quad (5-1.4)$$

$$k_m' = \sqrt{1 - k_m^2} \quad (5-1.5)$$

$$k_0 \equiv k \quad (5-1.6)$$

The elliptic modulus, k , is commonly expressed three different ways, which leads to some degree of confusion. In the Abramowitz and Stegun tables of elliptic functions [1], the parameters m and θ are used where $m = k^2$, and $\theta = \sin^{-1} k$. The parameter θ is called the modular angle.

The elliptic sine is an elliptic function, and is defined in a somewhat reverse manner from the elliptic integral. Referring to Eq. 5-1.1, given the input $u(\phi, k)$, the limit of integration, ϕ must be found to satisfy the equality, then $\text{sn}(u, k) = \sin \phi$. Likewise, the elliptic cosine is defined; $\text{cn}(u, k) = \cos \phi$. Notice that when $k = 0$, the elliptic sine equals the trigonometric sine and likewise for the respective cosines.

The descending Landen transformation [12], [46] is used to calculate the elliptic sine. Starting with an initial value for $\text{sn}(u_r, k_r)$ as given by Eq. (5-1.7), Eq. (5-1.8) is recursively used to find $\text{sn}(u_0, k_0)$ which is the answer.

$$\operatorname{sn}(u_{m+1}, k_{m+1}) = \sin\left(\frac{\pi u_0}{2K(k)}\right) \quad (5-1.7)$$

$$\operatorname{sn}(u_{r-1}, k_{r-1}) = \frac{(1 + k_r) \operatorname{sn}(u_r, k_r)}{1 + k_r \operatorname{sn}^2(u_r, k_r)} \quad (5-1.8)$$

where

$c = m+1, m, \dots, 1$

and k_r is obtained from storage, and was calculated from Eq. (5-1.4) during the complete elliptic integral calculation.

The descending Landen transformation is also the basis for Darlington's elliptic filter algorithms (Program 2-15).

The other elliptic functions are calculated from the elliptic sine as follows:

$$cn(u,k) = (1 - sn^2(u,k))^{\frac{1}{2}} \quad (5-19)$$

$$dn(u,k) = (1 - k^2 \cdot sn^2(u,k))^{\frac{1}{2}} \quad (5-1.10)$$

$$\operatorname{am}(u, k) = \sin^{-1} \operatorname{sn}(u, k) = \emptyset \quad (5-1-11)$$

User Instructions

ELLIPTIC INTEGRALS AND FUNCTIONS				
complete elliptic integral, $K(k)$	elliptic sine $sn(u,k)$, $u \uparrow k$	elliptic cosine $cn(u,k)$, $u \uparrow k$	elliptic delta $dn(u,k)$, $u \uparrow k$	print ? elliptic amplitude $am(u,k)$, $u \uparrow k$

Example 5-1.1

Evaluate the following elliptic functions and compare with Abramowitz and Stegun [1] Tables 17.1 and 17.5.

$$K(k); k = \sqrt{0.9}$$

$$\text{sn}(3.09448898, \sin 88^\circ)$$

HP-97 printout

```

.9 JX
9.486832981-01 *** calculate k
GSBA
2.578092113+00 *** K(k)

3.09448898 ENT4 load u
86. DEG
SIN calculate k = sin 88°
9.993908270-01 *** sin 88°
558E
9.961546961-01 *** sn(3.09448898, sin 88°)

DEG
SIN calculate and print  $\phi = \sin^{-1} \text{sn}(u, k)$ 
8.500000000+00 ***
```

From Table 17.1 (p. 608 of [1]), $K(m)$ for $m = 0.9$ is:

$$K(m) = 2.57809211334173$$

Rounded to ten significant figures, this figure agrees identically with the program output.

From Table 17.5 (p. 615 of [1]), the elliptic integral of the first kind for $\alpha = 88^\circ$, $\phi = 85^\circ$ is 3.09448898. The program output differs by 1 part in 8.5×10^9 , which exceeds the precision of the input.

5-1 Program Listing I

001 *LBLA COMPUTE COMPLETE ELLIPTIC INT	045 *LBLB CALCULATE ELLIPTIC SINE
002 GSB2 calculate K(k)	046 GSB3 calculate $\text{sn}(u, k)$
003 GT09 goto output routine	047 GT09 goto output routine
004 *LBL2 K(k) calculation subroutine	048 *LBL3 $\text{sn}(u, k)$ calculation subr
005 ST00 store k	049 ST02 store k
006 PI calculate and store:	050 R↓ receiver and store u
007 2	051 ST03 calculate $K(k)$
008 ÷ $\frac{\pi}{2} \rightarrow R1$	052 RCL2
009 ST01	053 GSB2
010 EEX	054 DSZI
011 1 $10 \rightarrow R8$	055 RAD
012 ST08	056 RCL3
013 ST01	057 PI form and store initial
014 EEX sn value for descending	058 X Landen transformations:
015 CHS	059 RCL1 $\text{sn}(u_{m+1}, k_{m+1}) = \text{sn} \left\{ \frac{\pi u_m}{2 K(k)} \right\}$
016 1 $10^{-10} \rightarrow R9$	060 ENT↑
017 0	061 +
018 ST09	062 ÷
019 *LBL0 K(k) loop start	063 SIN
020 EEX calculate and store:	064 ST04 transformation loop start
021 RCL0	065 *LBL1 recursively use descending
022 X ² - Landen transformation to	066 RCL1 find $\text{sn}(u_0, k_0)$:
023 - $k'_m = (1 - k_m^2)^{\frac{1}{2}}$	067 EEX $\text{sn}(u_{r-1}, k_{r-1}) = \frac{(1+k_r) \text{sn}(u_r, k_r)}{1 + \text{sn}^2(u_r, k_r)}$
024 JX	068 +
025 ST07	069 RCL4
026 CHS calculate and store:	070 X
027 EEX	071 RCL1
028 +	072 RCL4
029 RCL7 $k_{m+1}' = \frac{1 - k_m'}{1 + k_m'}$	073 X ²
030 EEX	074 X
031 +	075 EEX
032 ÷	076 +
033 ST00	077 ÷
034 ST01 store k_r for descending	078 ST04
035 ISZI Landen transformation	079 DSZI
036 EEX	080 RCL1
037 +	081 RCL8 test for loop exit
038 STX1 form $\pi (1 + k_{m+1})$	082 X \leq Y?
039 RCL9	083 GT01
040 RCL0	084 RCL4 recall $\text{sn}(u, k)$
041 X \geq Y?	085 RTN return to main program
042 GT00	
043 RCL1	
044 RTN	

REGISTERS									
0 k_i	1 $K(k)$	2 k_o	3 u_o	4 $\text{sn}(u, k)$	5	6	7 scratch	8 10	9 10^{-10}
S0 k_1	S1 k_2	S2 k_3	S3 k_4	S4 k_5	S5 k_6	S6	S7	S8	S9
A	B	C	D	E	F	G	H	I	J

Program Listing II

```

086 *LBL0 CALCULATE ELLIPTIC COSINE
087 GSB3 calculate sn(u,k)
088 GT06 convert to cn(u,k) & output
089 *LBL0 CALCULATE ELLIPTIC DELTA
090 GSB3 calculate sn(u,k)
091 RCL2 form k-sn(u,k) and convert
092 X to dn(u,k) then output
093 *LBL6 routine to calculate:
094 X2
095 CHS
096 EEX
097 +
098 JX
099 GT09 goto output routine
100 *LBL0 CALCULATE ELLIPTIC AMPLITUDE
101 GSB3 calculate sn(u,k)
102 SIN convert to sm(u,k)
103 *LBL9 output subroutine
104 F02
105 PRTX print and space if
106 F02 flag 0 is set
107 SPC
108 RTN return to main program
109 *LBL7 R/S lockup routine
110 R/S
111 GT07
112 *LBL0 PRINT - R/S TOGGLE
113 F02 jump if flag 0 is set
114 GT08
115 SF0 set flag 0 and place a 1
116 EEX in the display
117 GT07 goto R/S lockup routine
118 *LBL8
119 CF0 clear flag 0 and place a
120 CLX 0 in the display
121 RTN return control to keyboard

```

Flag 0 should be set (cleared) prior to magnetic card recording depending whether the user normally wants the program in the print (R/S) mode.

LABELS					FLAGS	SET STATUS		
A K(k)	B sn(u,k)	C cn(u,k)	D dn(u,k)	E am(u,k)	0 print	FLAGS	TRIG	DISP
a	b	c	d	e	print toggle	ON OFF 0 <input type="checkbox"/> <input checked="" type="checkbox"/>	DEG 1 2 3	SCI RAD <input checked="" type="checkbox"/> ENG n. 9
0 K(k) Loop	1 sn loop	2 K(k)	3 sn(u,k)	4	1	2		
5	6 $\sqrt{1-x^2}$	7 R/S lock	8 print toggle	9 print or R/S	3			

PROGRAM 5-2 BESSEL FUNCTIONS AND FM OR PHASE MODULATION SPECTRA.

Program Description and Equations Used

This program will calculate the magnitude of the spectral lines arising from a frequency of phase sine-wave modulation process. In addition, the power in the higher sidebands is calculated which can be used to help define the bandwidths necessary for a communication channel carrying frequency division multiplexed data with either frequency modulation (FM), or phase modulation (PM) on the individual subcarriers. Phase modulation is often used to transmit digital data with preconditioning such as Manchester biphasic coding, or doublet modulation.

The spectra of both frequency modulated and phase modulated signals are the same when expressed as a function of the modulation index, m . The modulation index for the FM case is:

$$m_f = \frac{\text{peak carrier deviation from nominal frequency}}{\text{modulation frequency}}$$

Notice that the FM modulation index is modulation frequency dependent.

The modulation index for the PM case is:

$$m_p = \left\{ \begin{array}{l} \text{carrier phase shift in radians produced by the} \\ \text{modulating frequency.} \end{array} \right.$$

Also notice that the PM modulation index is modulation frequency independent.

The carrier and carrier sideband levels are described in terms of Bessel functions with the modulation index as the argument. The spacing of the sidebands is equal to the modulating frequency. For example, with a modulation index of 5 and a modulation frequency of 15 kHz, the FM or PM spectra is:

carrier amplitude	$J_0(5)$,
first sideband pair	$J_1(5)$,
second sideband pair	$J_2(5)$,
	⋮
n-th sideband pair	$J_n(5)$.

Figure 5-2.1 shows the above concept graphically.

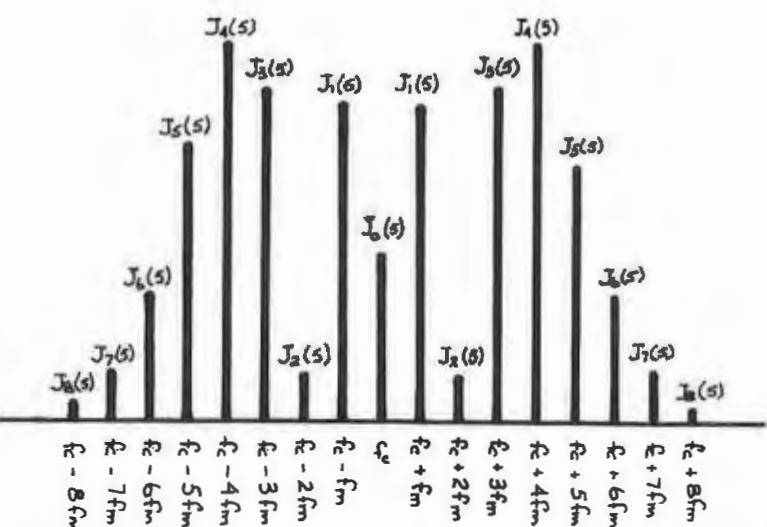


Figure 5-2.1 FM or PM modulation spectra.

A Bessel function identity allows the power remaining in the higher sidebands to be calculated. With FM or PM, all the sidebands carry modulation information in somewhat redundant form. If the higher order sidebands are removed by filtering, the modulation information can still be recovered, but the effective power will be reduced hence, the signal-to-noise ratio decreased; some distortion will also be introduced.

The Bessel function identity is:

$$J_0^2(m) + 2 \sum_{i=1}^{\infty} J_i^2(m) = 1 \quad (5-2.1)$$

The summation is broken into 2 parts and the equation rearranged:

$$\sum_{i=n+1}^{\infty} J_i^2(m) = \frac{1}{2}(1 - J_0^2(m)) - \sum_{i=1}^n J_i^2(m) \quad (5-2.2)$$

Therefore, if the magnitudes of the first n sidebands are known, then the power in the higher sidebands may be calculated since power is proportional to magnitude squared.

When the modulating signal contains 2 sinewaves of different frequencies and amplitudes superposition does not hold, since the resulting

spectra is represented by the products of the Bessel functions of the individual spectra. Let m_1 be the modulation index for modulation frequency f_1 , and likewise, m_2 for f_2 , then the combined modulation spectral components will be as shown in Table 5-2.1.

Table 5-2.1 Spectra for combined modulation

Spectral Component	frequency of component	amplitude of component
Carrier	f_c	$J_0(m_1) \cdot J_0(m_2)$
Simple sidebands of	$f_c \pm f_1$	$J_1(m_1) \cdot J_0(m_2)$
	$f_c \pm f_2$	$J_0(m_1) \cdot J_1(m_2)$
	$f_c \pm 2f_1$	$J_2(m_1) \cdot J_0(m_2)$
	$f_c \pm 2f_2$	$J_0(m_1) \cdot J_2(m_2)$
	\vdots	\vdots
Intermodulation	$f_c \pm f_1 \pm f_2$	$J_1(m_1) \cdot J_1(m_2)$
	$f_c \pm f_1 \pm 2f_2$	$J_1(m_1) \cdot J_2(m_2)$
	$f_c \pm 2f_1 \pm f_2$	$J_2(m_1) \cdot J_1(m_2)$
	\vdots	\vdots

The Bessel function of the first kind is easily evaluated using the summation of an infinite series; however, for values of m larger than 10, computational difficulties arise because of small differences between big numbers, i.e., using Eq. (5-2.3), Table 5-2.2 shows the individual terms for $n=0$ and $m=20$.

$$J_n(m) = \left(\frac{m}{2}\right)^n \sum_{i=0}^{\infty} \frac{\left(-\frac{m^2}{4}\right)^i}{i!(i+n)!} = \left(\frac{m}{2}\right)^n \sum_{i=0}^{\infty} T_j \quad (5-2.3)$$

Table 5-2.2

Infinite series terms.	
1.000000000	T_0
-100.0000000	T_1
2500.000000	
-27777.77778	
173611.1111	
-694444.4444	T_5
1929012.346	
-3936759.889	
6151187.327	
-7594058.428	
7594058.428	T_{10}
-6276081.347	
4358389.823	
-2578928.890	
1315780.046	
-584791.1313	T_{15}
228434.0357	
-79042.91893	
24395.96263	
-6757.884387	
1689.471097	T_{20}
-383.1000219	
79.15289702	
-14.96274047	
2.597697998	
-0.415631680	T_{25}
0.061483976	
-0.008434016	
0.001075767	
-0.000127915	
0.000014213	T_{30}
-0.000001479	
0.000000144	
-0.000000013	
0.000000001	

The computed $J_0(20)$ by this method is 0.166021646. Because the range of the numbers exceed 10^{10} , the least significant figures have been lost. Even though the summation was carried out until $T_i < 10^{-9}$, the answer is only accurate to 2 significant figures. The correct answer to $J_0(20)$ is 0.1670246646, which is computed by a slower, less direct method shown next.

and the constant of proportionality for $J_0(m)$, i.e., given

$$T_1(m) = \frac{2}{m}(i+1) \cdot T_{i+1}(m) - T_{i+2}(m) \quad (5-2.5)$$

then, the minimum starting index is

$$i_{\min} = 2 \cdot \text{INT}\left(\frac{6 + \max(n, z) + (9z/(z+2))}{2}\right) \quad (5-2.6)$$

which for $n=0$ may be reduced to

$$i_{\min} = 2 \cdot \text{INT}\left(\frac{z^2 + 17z + 12}{2(z+2)}\right) \quad (5-2.7)$$

where

$$z = 3m/2 \quad (5-2.8)$$

and "INT" means the integral part of the expression. The constant of proportionality is given by Eq. (5-2.9)

$$k = T_0(m) + 2 \sum_{j=1}^{\frac{i_{\min}}{2}} T_{2j}(m) \quad (5-2.9)$$

The first two Bessel functions are then:

$$J_0(m) = \frac{T_0(m)}{k} \quad (5-2.10)$$

$$J_1(m) = \frac{T_1(m)}{k} \quad (5-2.11)$$


With $J_0(m)$ and $J_1(m)$ and the recursion relationship given by Eq. (5-2.4), all the higher order Bessel functions may be evaluated.

Equation (5-2.4) is the recursion relationship for Bessel functions of the first kind.

$$J_n(m) = \frac{2}{m} (n-1) \cdot J_{n-1}(m) - J_{n-2}(m) \quad (5-2.4)$$

All Bessel functions approach zero as the order becomes large. This characteristic can be used to compute Bessel functions. If $T_{n+2}(m) = 0$ and $T_{n+1}(m) = 10^{-9}$, the recursion relationship can be run backwards to arrive at a result that is proportional to $J_0(m)$. Abramowitz and Stegun [1] has the relations for the minimum starting index

User Instructions

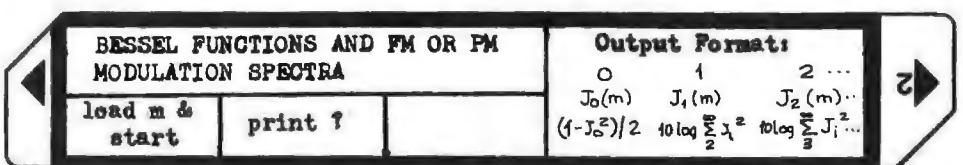

STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
1	Load both sides of program card			
2	Select print/no-print (R/S) option		B B B ⋮	0 (R/S) 1 (print) 0 (R/S) ⋮
3	Load modulation index and start remaining power in higher sidebands in dB	m 10 log $\sum_i J_i^2(m)$	A	0 J ₀ (m) (1 - J ₀ ²)/2 1 J ₁ (m) 2 J ₂ (m) 10 log $\sum_i J_i^2(m)$
4	To stop analysis (print mode selected)		R/S	

Example 5-2.1

The 400 MHz carrier from a navigation satellite is phase modulated with a 400 Hz sinewave causing 60 degrees peak modulation. What is the modulation index, and what are the amplitudes of the PM sidebands?

The modulation index is the peak modulation expressed in radians:

$$m_p = 2\pi (60/360) = 1.0472 \text{ radians} \quad (5-2.12)$$

HP-97 PRINTOUT FOR EXAMPLE 5-2.1

60. D+F
GSEA load modulation index and start

0.	*** carrier
0.744072	*** J ₀ (m)
0.223176	*** (1 - J ₀ ² (m))/2
1.	*** first sideband, f _c ± f _m
0.455051	*** J ₁ (m)
-11.4	*** relative power in higher sidebands in dB
2.	*** second sideband, f _c ± 2f _m
0.124972	*** J ₂ (m)
-26.4	***
3.	***
0.022322	*** J ₃ (m)
-44.0	***
4.	***
0.002964	*** J ₄ (m)
-63.5	***
5.	***
0.000513	*** J ₅ (m)
-84.5	***

Notice that 99% of the power is contained in the carrier and the first two sidebands (-26.4 dB = 0.23% remaining power in higher sidebands).

Example 5-2.2

Calculate the sideband structure of a commercial FM station transmitting a 15 kHz signal with 75 kHz peak carrier deviation. The modulation index is:

$$m_f = 75000/15000 = 5$$

(5-2.13)

HP-97 PRINTOUT FOR EXAMPLE 5-2.2

5. GSEH load m_f & start	
6. *** carrier	6. ***
-0.177537 *** $J_0(m)$	0.131049 *** $J_6(m)$
0.484236 *** $(1 - J_0^2(m))/2$	-21.6 ***
7. *** first sidebands	7. ***
-0.327579 *** $J_1(m)$	0.053376 *** $J_7(m)$
-1.1 *** power (dB) outside	-31.2 ***
8. *** 2nd sideband pair	8. ***
0.046565 *** $J_2(m)$	0.018405 *** $J_8(m)$
-1.1 ***	-41.7 ***
9. ***	9. ***
0.364631 *** $J_3(m)$	0.065520 *** $J_9(m)$
-3.0 ***	-53.3 ***
10. ***	10. ***
0.391232 *** $J_4(m)$	0.001466 *** $J_{10}(m)$
-7.4 ***	-65.7 ***
11. ***	11. ***
0.261141 *** $J_5(m)$	
-13.6 ***	

Notice that one-half the power is contained in the first 3 sidebands and 99% of the power is contained in the first 6 sidebands.

The sideband structure for this example is shown in Fig. 5-2.1.

Program Listing I

```

001 *LBLA LOAD m AND START
002 ST00 store m
003 F0?
004 SPC double space if flag 0 set
005 F0?
006 SPC
007 j calculate minimum starting
008 . index plus two
009 5
010 x
011 ENT↑
012 ENT↑
013 ENT↑
014 1
015 7
016 +
017 x
018 2
019 ÷  $i_{\text{min}} = 2 \cdot \text{int} \left\{ \frac{Z^2 + 17Z + 12}{2(Z+2)} \right\}$ 
020 6
021 +
022 X2Y
023 2
024 +
025 ÷
026 INT
027 ENT↑
028 +
029 2
030 +
031 ST01
032 2
033 RCL0 calculate and store 2/m
034 ÷
035 ST02
036 CLX
037 ST0E initialize  $T_{i+2}$  and  $\sum T_{2j}(m)$ 
038 ST09
039 EEX
040 CHS
041 9 initialize  $T_{i+1}$ 
042 ST0D
043 *LBL0 calculate  $T_1$  and  $T_0$ 
044 GSB1 calculate and store  $\sum T_{2j}$ 
045 ST+9
046 CF2 execute recursion formula
047 GSB1
048 F2?
049 GT00 test for loop exit
050 CLX initialize i
051 ST01
052 GSB7 print j
053 RCLC calculate and print  $J_0(m)$ 
054 RCL9
055 ENT↑
056 +
057 RCLC  $J_0(m) = \frac{T_0(m)}{k}$ 
058 -
059 ST02
060 ÷
061 ST01
062 GSB6
063 X2 calculate, store and print:
064 CHS
065 EEX
066 +
067 2
068 ÷
069 ST05
070 GSB9
071 IS2I increment and print i
072 GSB7
073 RCLD calculate, store, and print
074 CHS  $J_1(m)$ 
075 RCL2
076 ÷
077 ST02  $J_1(m) = \frac{T_1(m)}{k}$ 
078 GSB6
079 X2
080 CHS calculate and print power
081 ST06 in higher sidebands
082 RCL5 using Eq. (5-2.2)
083 +
084 GSB8

```

REGISTERS									
0 m	1 $J_0(m), T_{n+1}(m)$	2 $K^2, J_1(m), J_n(m)$	3	4	5 $(1 - J_0^2)/2$	6 $\sum_{i=1}^n J_i^2(m)$	7	8	9 $\sum T_{2j}(m)$
S0	S1	S2	S3	S4	S5	S6	S7	S8	S9
A n	B $2/m$	C	D T_i, T_{i+1}	E T_{i+1}, T_{i+2}	F i, n				

Program Listing II

LABELS		FLAGS		SET STATUS	
A load m and start	B R/S - print toggle	C	D	E	0 print
a	b	c	d	e	1
0 J ₀ & J ₁ calc Loop	1 J ₀ & J ₁ calc loop	2 output calc loop	3 R/S - print toggle	4 R/S lockup	2 loop exit
5	6 dep6, print	7 dsp0, prt I	8 10 log, dep1	9 print & space	3

Note:
Flag 0 should be set or reset prior to magnetic card recording to cause the program to initially be in the print or R/S mode respectively as users desire.

```

085 *LBL2 loop to calc Bessel function
086 RCL1 Jn-2
087 CHS
088 RCL2 Jn-1
089 STO1
090 RCLB 2/m
091 X
092 RCLI n-1 Jn(m) =  $\frac{2}{m} (n-1) J_{n-1}(m) - J_{n-2}(m)$ 
093 X
094 +
095 STO2 Jn
096 ISZI increment n
097 GSB7
098 RCL2
099 GSB6 recall and print Jn(m)
100 X2
101 ST-6 calculate and print power
    in higher sidebands
102 RCL6
103 RCL5
104 +
105 GSB8
106 GT02
107 *LBL1 Ti(m) recursion subroutine
108 DSZI
109 SF2
110 RCLC Ti+2
111 CHS
112 RCLI i+1
113 RCLB 2/m
114 X
115 RCLD Ti+4 Ti(m) =  $\frac{2}{m} (i-1) T_{i+4}(m) - T_{i+2}(m)$ 
116 STOE
117 X
118 +
119 STOD Ti
120 RTN
121 *LBL6 print in dsp 6 subroutine
122 DSP6
123 STO6
124 *LBL7 print index in dsp 0 subr
125 DSP0
126 PCL1
127 *LBL8
128 F0?
129 PRTX
130 F0?
131 RTN
132 R/S
133 FTn stop and await R/S command
134 *LBL8 calculate & prt 10-log subr
135 RCL5
136 =
137 LOG
138 EEY
139 1
140 A
141 DSP1 set display format
142 RND
143 *LBL9 print and space if flag 0
    is set, otherwise stop
144 F0?
145 PRTX
146 F0?
147 SFC
148 F0?
149 RTN
150 R/S
151 RTN
152 GT04 program block
153 *LBL0 PRINT-R/S TOGGLE
154 F0?
155 ST05 jump if flag 0 is set
156 SF0 set flag 0 and place
    a one in the display
157 EEY
158 GT04 goto R/S lookup routine
159 *LBL3
160 CF0 clear flag 0 and place a
    zero in the display
161 CLX
162 *LBL4 R/S lookup routine
163 R/S
164 GT04

```

PROGRAM 5-3 CURVE FITTING BY THE CUBIC SPLINE METHOD.

Program Description and Equations Used

This program will fit a cubic spline interpolating curve through 2 to 9 equally spaced points [31]. The cubic spline represents the shape of the curve that would be generated if a clock spring were threaded through the data points. This technique is often used by draftsmen to draw a smooth curve through given points. The shape of such a curve looks natural, and is generally the shape one would attempt to draw by hand.

Let the ordinates, y_i , be given at $x_i = x_1 + (i-1) \cdot h$, where $i = 1, 2, \dots, n$, and h is the point spacing. Furthermore, let $y(x)$ be the interpolating curve that is fitted to these points, and let y'_i and y''_i represent the first and second derivatives of $y(x)$ evaluated at $x = x_i$. $y(x)$ may be represented piecewise where the function and its first and second derivatives are matched at the boundaries. The first and last segments of the interpolating curve may have their first and second derivatives specified by the user. The individual cubic interpolating polynomial $f_i(x)$ can be expressed in terms of the ordinates y_i and y_{i+1} , and either their first or second derivatives. Both forms will provide the same $y(x)$, but the second derivative form requires simpler calculations.

Assume the third derivative, $y'''(x)$, is constant in each interval,

h. This assumption implies that $y'''(x)$ is linear in x , i.e.,

$$f_i'''(x) = y''_i \left\{ 1 - \frac{x - x_i}{h} \right\} + y''_{i+1} \left\{ \frac{x - x_i}{h} \right\} \quad (5-3.1)$$

Equation (5-3.1) is integrated twice with respect to x , and the constants of integration chosen so the boundary conditions are met to the extent that $f_i(x_i) = y_i$ ($i = 1, 2, \dots, n-1$), and $f_{i-1}(x_i) - y_i$ ($i = 2, 3, \dots, n$). The results of this integration yield:

$$\begin{aligned}f_i(x) &= y_i(1 - (x-x_i)/h) + y_{i+1}(x-x_i)/h \\&\quad - (h^2/6)(y_i'') \left[1 - (x-x_i)/h - (1 - (x-x_i)/h)^3 \right] \\&\quad - (h^2/6)(y_{i+1}'') \left[(x-x_i)/h - ((x-x_i)/h)^3 \right]\end{aligned}\quad (5-3.2)$$

Since the first and second derivatives of the function must also match at the boundaries, Eq. (5-3.2) is differentiated with respect to x and evaluated at x_i :

$$f_i'(x_i) = (y_{i+1} - y_i)/h - (h/6)(2y_i'' + y_{i-1}'') \quad (5-3.3)$$

and

$$f_{i-1}'(x_i) = (y_i - y_{i-1})/h + (h/6)(y_{i-1}'' + 2y_i'') \quad (5-3.4)$$

Equating Eqs. (5-3.3) and (5-3.4) implying boundary match yields:

$$h \cdot y_{i-1}'' = 4h \cdot y_i'' + h \cdot y_{i-1}'' = (6/h)(y_{i-1} - 2y_i + y_{i+1}) \quad (5-3.5)$$

where

$$i = 2, 3, \dots, n-1.$$

This equation set represents $n-2$ equations in n unknowns. If the starting and ending second derivatives are specified (y_1'' and y_n''), then the number of unknowns is reduced by 2, and a solution exists to the equation set. This equation set may be expressed in matrix notation:

$$\begin{bmatrix} 4 & 1 & 0 & 0 & \dots & 0 \\ 1 & 4 & 1 & 0 & \dots & 0 \\ 0 & 1 & 4 & 1 & 0 & \dots \\ \vdots & \vdots & \vdots & \vdots & \ddots & \vdots \\ 0 & \dots & 0 & 1 & 4 & 1 \\ 0 & 0 & \dots & 0 & 1 & 4 \end{bmatrix} \begin{bmatrix} y_2'' \\ y_3'' \\ \vdots \\ y_{n-2}'' \\ y_{n-1}'' \end{bmatrix} = \begin{bmatrix} (6/h^2)(y_1 - 2y_2 + y_3) - y_1'' \\ (6/h^2)(y_2 - 2y_3 + y_4) \\ (6/h^2)(y_3 - 2y_4 + y_5) \\ \vdots \\ (6/h^2)(y_{n-2} - 2y_{n-1} + y_n) - y_n'' \end{bmatrix} \quad (5-3.6)$$

Because of the tridiagonal characteristic of Eq. (5-3.6), a Gauss reduction is an effective method for finding the values of the various second derivatives. Let,

$$d_i = (6/h^2)(y_{i-1} - 2y_i + y_{i+1}) \quad (5-3.7)$$

and select $y_1'' = y_n'' = 0$ (another common selection is $y_1'' = y_2''/2$ and $y_n'' = y_{n-1}''/2$). If a recursion relationship is defined thus:

$$i^4 = 1/(4 - i-1^4) \text{ for } i = , 1, \dots, n-1 \quad (5-3.8)$$

i.e.,

$$0^4 = 1/4 = 0.25$$

$$1^4 (1/3.75 = 0.2666^-$$

$$2^4 = 1/(4 - 1^4) = .267857143$$

.

.

.

then the Gauss reduced matrix becomes:

$$\begin{bmatrix} (1/0^4) & 1 & 0 & \dots & \dots & 0 \\ 0 & (1/1^4) & 1 & \dots & \dots & 0 \\ 0 & 0 & (1/2^4) & \dots & \dots & 0 \\ \vdots & \vdots & \vdots & \ddots & \vdots & \vdots \\ 0 & \dots & 0 & 0 & (1/n-3^4) & \vdots \\ & & & & & y_{n-1}'' \end{bmatrix} \begin{bmatrix} y_2'' \\ \vdots \\ y_{n-1}'' \end{bmatrix} = \begin{bmatrix} d_2 \\ d_3 - 0^4 \cdot d_2 \\ d_4 - 1^4(d_3 - 0^4 \cdot d_2) \\ \vdots \\ \vdots \\ \vdots \end{bmatrix} \quad (5-3.9)$$

Equation (5-3.9) is evaluated by the program as shown by the flowchart in Fig. 5-3.1.

User Instructions

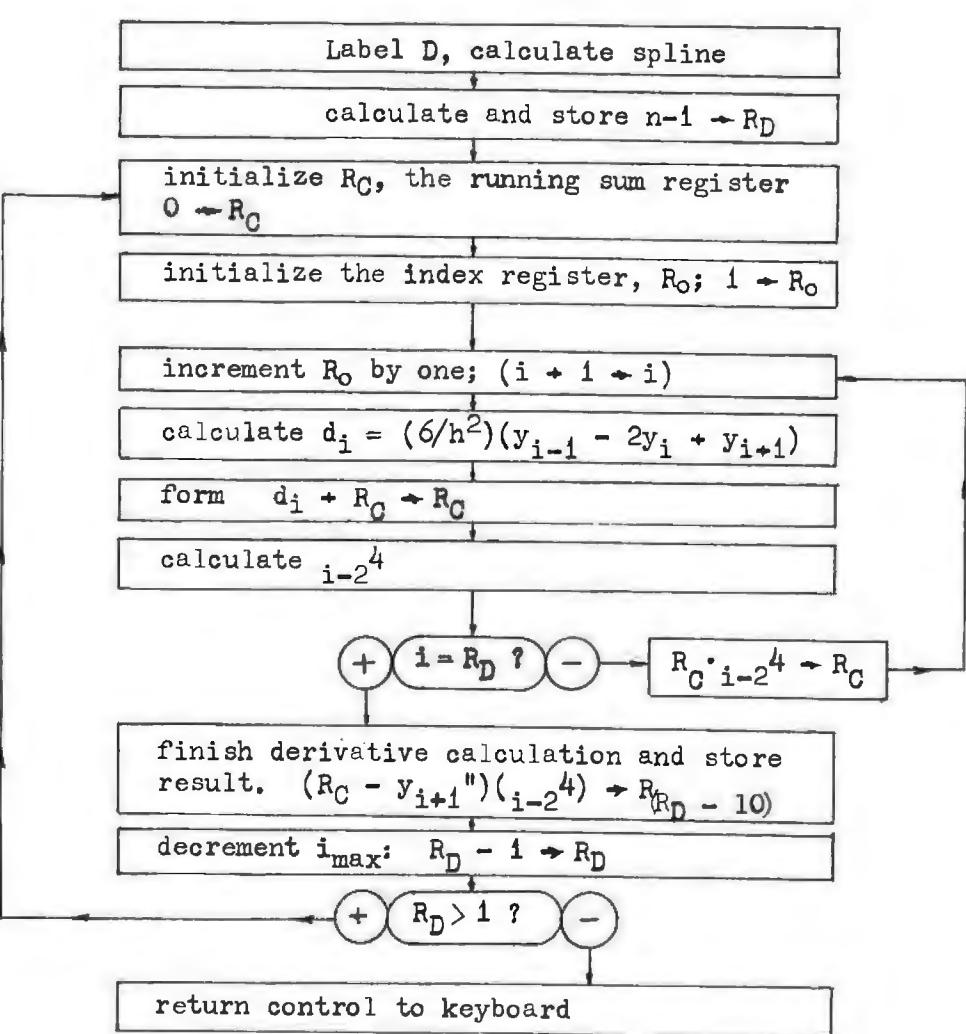


Figure 5-3.1 Flowchart of Gauss reduction algorithm.

CURVE FITTING BY THE CUBIC SPLINE METHOD				
Δx	start sweep			x_1
number of points	load h	load data, y_1	calculate spline	$x \rightarrow \hat{y}$

STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
1	Load both sides of magnetic card			
2	Load the number of data points	n	A	
3	Load h, the x interval	h	B	
4	Load y data	y_1 y_2 . . y_{n-1} y_n	C D E F G	2 3 n
5	Calculate spline		D	
6	Load first x point	x_1	F E	
7	Execute single point interpolation	x	E	\hat{y}
	Step 7 may be used any number of times			
8	For linear sweep in x and corresponding interpolation of y: a) Load sweep point spacing b) Start sweep	Δx	F A F B	x_1 \hat{y}_1 $x_1 + \Delta x$ \hat{y} $x_1 + 2\Delta x$ \hat{y} . . $x_1 + (n-1)\Delta x$ \hat{y}

Example 5-3.1

Fit a cubic spline interpolating curve to the data given in Table 5-3.1. Provide the output sweep with x increments of 0.1.

Table 5-3.1 Data for cubic spline interpolation.

x	1	2	3	4	5	6	7	8	9
y	0	5	9	7	4	3	5	8	9

The HP-97 printer output is shown on the next page, and the interpolated output is plotted in Fig. 5-3.2. The bold points represent the given data.

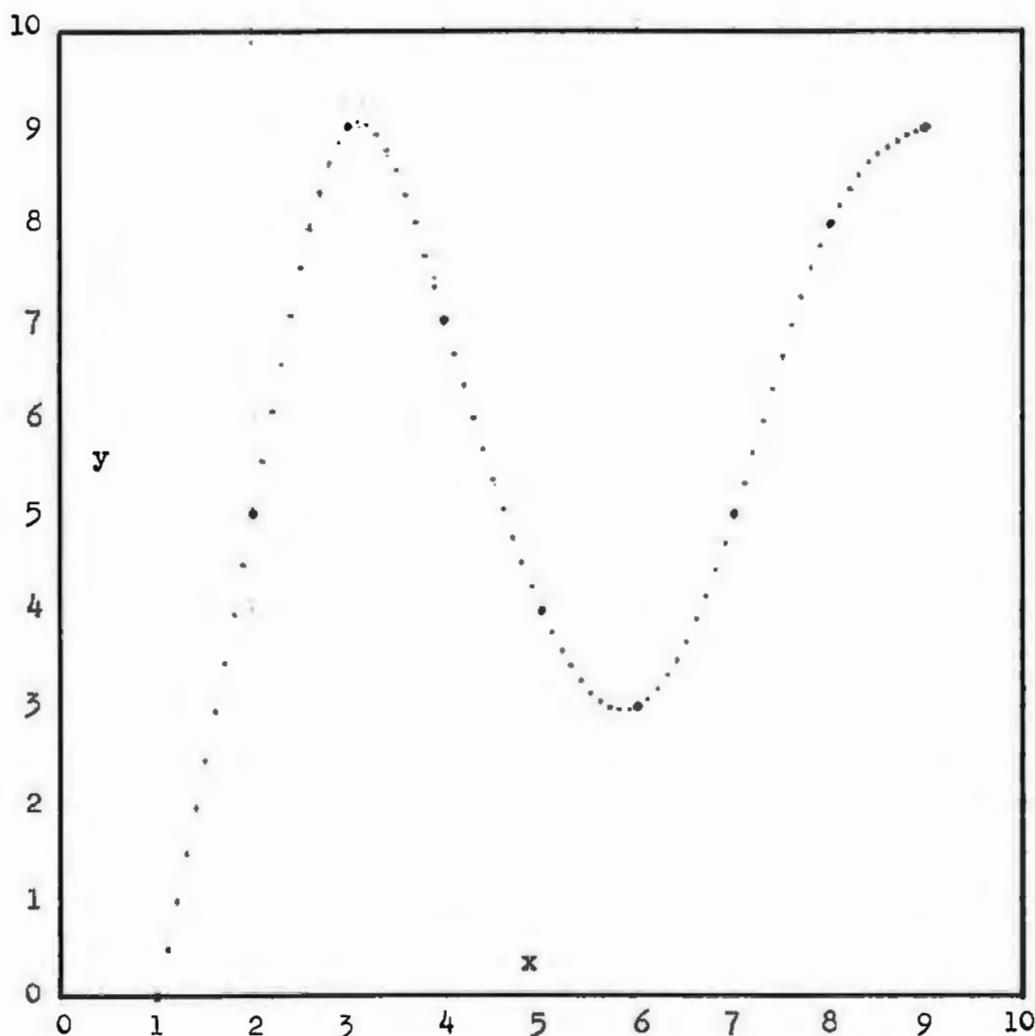


Figure 5-3.2 Cubic spline interpolation of given data.

HP-97 PRINTOUT FOR EXAMPLE 5-3.1

PROGRAM INPUT									
9.000 GSBA	load number of data points								
1.000 GSBB	load h, the x interval								
0.000 GSBC	load y data points								
0.000 GSBC	y1								
5.000 GSBC	y2								
9.000 GSBC	y3								
7.000 GSBC	y4								
4.000 GSBC	y5								
3.000 GSBC	y6								
5.000 GSBC	y7								
8.000 GSBC	y8								
9.000 GSBC	y9								
GSBD execute spline calculation									
1.000 GSBe	load x ₁ , the first x point								
.100 GSBa	load x interval for output sweep								
GSBb	start sweep								
PROGRAM OUTPUT									
1.000	2.000	3.000	4.000	5.000	6.000	7.000	8.000	9.000	
0.000	5.000	9.000	7.000	4.000	3.000	5.000	8.000	9.000	
1.100	2.100	3.100	4.100	5.100	6.100	7.100	8.100	x	
0.486	5.530	9.059	6.658	3.783	3.073	5.315	8.196	y	
1.200	2.200	3.200	4.200	5.200	6.200	7.200	8.200		
0.974	6.058	9.035	6.320	3.587	3.180	5.639	8.361		
1.300	2.300	3.300	4.300	5.300	6.300	7.300	8.300		
1.463	6.574	8.938	5.990	3.415	3.318	5.968	8.500		
1.400	2.400	3.400	4.400	5.400	6.400	7.400	8.400		
1.954	7.067	8.776	5.667	3.267	3.487	6.297	8.615		
1.500	2.500	3.500	4.500	5.500	6.500	7.500	8.500		
2.449	7.529	8.560	5.354	3.147	3.683	6.621	8.710		
1.600	2.600	3.600	4.600	5.600	6.600	7.600	8.600		
2.947	7.948	8.300	5.053	3.054	3.905	6.935	8.788		
1.700	2.700	3.700	4.700	5.700	6.700	7.700	8.700		
3.451	8.315	8.004	4.766	2.992	4.149	7.235	8.853		
1.800	2.800	3.800	4.800	5.800	6.800	7.800	8.800		
3.961	8.619	7.682	4.493	2.961	4.415	7.515	8.907		
1.900	2.900	3.900	4.900	5.900	6.900	7.900	8.900		
4.477	8.851	7.344	4.237	2.963	4.699	7.772	8.955		

Program Listing I

5-3

001	*LBLA	<u>LOAD # OF DATA POINTS</u>
002	STO A	<u>store number of data points</u>
003	EEX	<u>set y_n to zero</u>
004	1	
005	+	
006	STO I	
007	CLX	
008	STO I	
009	EEX	<u>initialize index register</u>
010	STO I	
011	RTN	
012	*LBLB	<u>LOAD n, THE x POINT SEPARATION</u>
013	STO B	
014	RTN	
015	*LBLC	<u>LOAD y DATA</u>
016	STO I	<u>store y data</u>
017	ISZ I	<u>increment storage index</u>
018	RCLI	<u>recall index to display</u>
019	RTN	<u>return control to keyboard</u>
020	*LBLD	<u>CALCULATE SPLINE</u>
021	RCL A	<u>calculate and store n-1</u>
022	EEX	
023	-	
024	STOD	
025	*LBL E	<u>spline outer loop</u>
026	CLX	<u>initialize running sum</u>
027	STOC	
028	EEX	
029	STOB	<u>initialize index register</u>
030	*LBL I	<u>spline inner loop</u>
031	EEX	<u>increment and store index</u>
032	ST+0	
033	RCL O	
034	EEX	
035	+	
036	STOI	
037	RCL I	<u>calculate d_i</u>
038	DSZ I	
039	RCL I	
040	ENT↑	
041	+	
042	-	
043	DSZ I	
044	PCL I	
045	+	
046	6	$d_i = \frac{6}{h^2} (y_{i-1} - 2y_i + y_{i+1})$
047	X	
048	RCL R	
049	X ²	
050	÷	
051	RCL C	
052	-	$d_i - R_c \rightarrow R_c$
053	STOC	
054	RCL O	
055	2	

REGISTERS									
0 Ax for sweep £ scratchpad	1 Y_1	2 Y_2	3 Y_3	4 Y_4	5 Y_5	6 Y_6	7 Y_7	8 Y_8	9 Y_9
S0 X_1	S1 current-x for sweep	S2 Y'_2	S3 Y''_3	S4 Y''_4	S5 Y'_5	S6 Y''_6	S7 Y'_7	S8 Y''_8	S9 $Y''_9 = 0$
A n	B h	C scratchpad	D index	E scratchpad	F index	G scratchpad	H index	I scratchpad	J index

Program Listing II

5-

110	*LBL _E	<u>LOAD FIRST x POINT (x₁ value)</u>	165	1	generate 0 if first interval
111	P _{#S}	<u>store data</u>	166	1	otherwise generate 1
112	ST00		167	-	(frees up one register)
113	P _{#S}		168	ENT↑	
114	FT08		169	X#0?	
115	*LBL _E	<u>CALCULATE y ESTIMATE, x → y</u>	170	=	
116	P _{#S}		171	X=0?	
117	RCL0	x - x ₁	172	P↓	
118	P _{#S}		173	X	<u>compute running sum</u>
119	-		174	+	
120	RCLB		175	6	<u>calculate</u>
121	÷	$\frac{x - x_1}{h} \rightarrow R_C$	176	÷	$\frac{h^2}{6}$
122	STOC		177	RCL _E	
123	INT		178	X ²	
124	EEX	$1 + \text{INT}\left(\frac{x - x_1}{h}\right) \rightarrow R_I$	179	X	
125	+		180	CHS	<u>finish running sum calc</u>
126	STOI		181	RCLC	
127	RCLC		182	+	
128	-	$\frac{x_{i+1} - x}{h} \rightarrow R_D$	183	PRTX	<u>print y estimate</u>
129	STOD		184	SPC	(may be R/S statement)
130	RCLI		185	GT08	goto R/S lockup
131	X	$\frac{x_{i+1} - x}{h} y_i$	186	*LBL _D	<u>LOAD x FOR SWEEP</u>
132	RCLC		187	ST00	
133	RCLI		188	GT08	goto R/S lockup
134	EEX	$\frac{x - x_i}{h} \rightarrow R_E$	189	*LBL _E	<u>START LINEAR SWEEP</u>
135	-		190	SPC	
136	-		191	RCL0	
137	STOE		192	CHS	
138	ISZ1		193	P _{#S}	
139	RCL _I		194	RCL0	<u>initialize registers</u>
140	×	$(y_{i+1}) \frac{x - x_i}{h} + (y_i) \frac{x_{i+1} - x}{h} \rightarrow R_C$	195	+	
141	+		196	STO!	
142	STOC		197	P _{#S}	
143	RCL _E		198	*LBL _I	
144	RCL _E		199	RCL0	
145	3	$\frac{x - x_i}{h} - \left\{ \frac{x - x_i}{h} \right\}^3$	200	P _{#S}	<u>increment x value</u>
146	YX		201	STO!	
147	-		202	RCL1	
148	RCL _T		203	RCL0	
149	EEX		204	P _{#S}	
150	1		205	RCLA	
151	+	$(y_{i+1}'') \left\{ \frac{x - x_i}{h} - \left(\frac{x - x_i}{h} \right)^3 \right\}$	206	EEX	<u>calculate largest x value</u>
152	STOI		207	-	
153	R↓		208	RCLB	
154	RCL _I		209	X	
155	X		210	+	
156	RCLD		211	X _i Y	
157	RCLD		212	X>Y?	<u>test for loop exit</u>
158	3	$\frac{x_{i+1} - x}{h} - \left(\frac{x_{i+1} - x}{h} \right)^3$	213	GT08-	(may be R/S statement)
159	YX		214	PRTX	<u>print current x value</u>
160	-		215	GSBE-	<u>calc and print y estimate</u>
161	DSZ1		216	GT09-	
162	RCL _I	$(y_i'') \left\{ \frac{x_{i+1} - x}{h} - \left(\frac{x_{i+1} - x}{h} \right)^3 \right\}$	217	*LBL _S	<u>R/S lockup subroutine</u>
163	X		218	RTN	
164	RCL _T		219	GT08	

LABELS					FLAGS		SET STATUS		
A load nbr of data points	B load h, the x interval	C load y data	D calculate spline	E $x \rightarrow y$	0		FLAGS	TRIG	DISP
a load Δx for sweep	b Start sweep	c	d	e load first x point	1		ON OFF	USERS	CHOICE
0 loop destination	1 loop destination	2 initialize i;4 & scratch	3 calculate i;4	4 gaves reduction	2		0	DEG	FIX
5	6	7	8	9 loop destination	3		1	GRAD	SCI
							2	RAD	ENG
							3	n	_____

PROGRAM 5-4 LEAST SQUARES CURVE-FIT TO AN EXPONENTIAL FUNCTION.

Program Description and Equations Used

Many processes both in electrical engineering and in physics have behavior that can be described by an exponential law, e.g., the voltage across a capacitor being charged through a series resistor asymptotically approaches the charging voltage in an exponential manner. When time constants are to be determined from oscilloscope photographs of these phenomena, only part of the entire waveform is available, and some error is introduced transferring the photograph data into numbers. If these errors are random, then a least squares fit can help remove them.

The equation form for the exponential function is given by:

$$x = a(1 - e^{-bt}) \quad (5-4.1)$$

Let d_i represent the difference between the measured point, x_i , and the exponential curve as shown by Fig. 5-4.1 and Eq. (5-4.2).

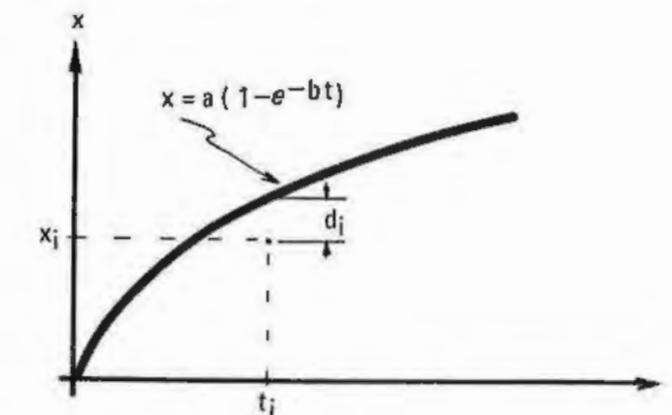


Figure 5-4.1 Exponential function.

$$d_i = x_i - a(1 - e^{-bt_i}) \quad (5-4.2)$$

The object of a least squares fit is to minimize the sum of the

squares of the deviations as implied by Eq. (5-4.3).

$$S = \sum_i d_i^2 = \sum_i (x_i - a(1 - e^{-bt_i}))^2 \quad (5-4.3)$$

The minimum can be found by setting the derivatives of Eq. (5-4.3) to zero, i.e.:

$$\frac{\partial S}{\partial a} = 0, \quad \frac{\partial S}{\partial b} = 0$$

or

$$\frac{\partial S}{\partial a} = -2 \sum_i \{x_i - a(1 - e^{-bt_i})\} \cdot (1 - e^{-bt_i}) = 0 \quad (5-4.4)$$

$$\frac{\partial S}{\partial b} = -2a \sum_i \{x_i - a(1 - e^{-bt_i})\} \cdot (t_i \cdot e^{-bt_i}) = 0 \quad (5-4.5)$$

Equations (5-4.4) and (5-4.5) represent 2 equations in 2 unknowns, a and b . Equation (5-4.4) is solved for a as shown in Eq. (5-4.6) and substituted into Eq. (5-4.5) to yield Eq. (5-4.7)

$$a = \frac{\sum_i x_i (1 - e^{-bt_i})}{\sum_i (1 - e^{-bt_i})^2} \quad (5-4.6)$$

$$g(b) \triangleq \sum_i x_i \cdot t_i e^{-bt_i} \sum_i (1 - e^{-bt_i})^2 - \sum_i x_i (1 - e^{-bt_i}) \sum_i t_i \cdot e^{-bt_i} (1 - e^{-bt_i}) = 0 \quad (5-4.7)$$

To simplify things, the various sums in Eq. (5-4.7) are assigned numbers in the same respective order as they appear.

$$g(b) = \Sigma_1 \Sigma_2 - \Sigma_3 \Sigma_4 = 0 \quad (5-4.8)$$

The object is to find b so $g(b) = 0$. Since Eq. (5-4.7) is nonlinear, an iterative solution is employed to find b . Wegstein's method [29] is used and is flowcharted in Fig. 5-4.2. This method is chosen because no derivatives are required and the convergence is very rapid.

Basically Wegstein's method is Esperti's method where one curve is a straight line (see Program 2-9 for Esperti's method). Equation (5-4.8) will have to be modified as Wegstein's method finds the solution to $f(b) = b$, therefore, let $f(b)$ be as shown in Eq. (5-4.9)

$$f(b) = \frac{\Sigma_3 \Sigma_4}{\Sigma_2} - \Sigma_1 + b \quad (5.4-9)$$

The reason for this form is to try and avoid the small difference between big numbers problem. It is advisable to keep b between 0.1 and 10 for best accuracy. If the data is on a microsecond time scale, enter the time as though it were in seconds and denormalize b after it has been calculated. Likewise for millisecond data.

After b has been found by iteration, a is obtained by using Eq. (5-4.6), which can be expressed in terms of the numbered sums:

$$a = \frac{\Sigma_3}{\Sigma_2} \quad (5.4-10)$$

User Instructions

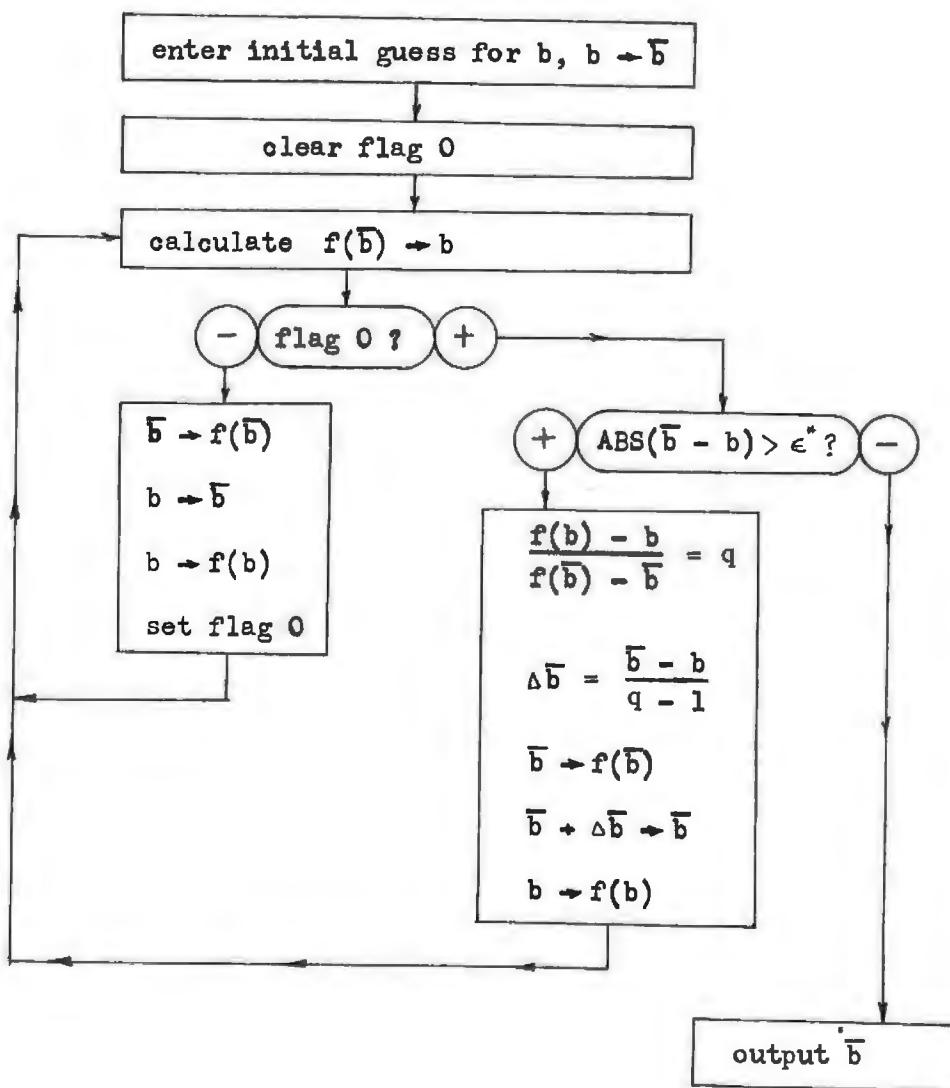
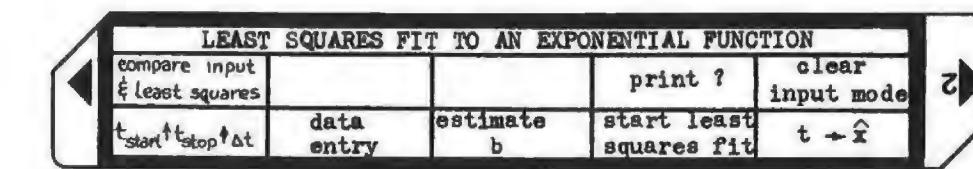


Figure 5-4.2 Flowchart for Wegstein's method.

* For this program, ϵ is chosen at $10^{-6} \cdot \bar{b}$ 

STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
1	Load both sides of magnetic card			
2	Select print or R/S option (toggle)		<input type="checkbox"/> f <input type="checkbox"/> D <input type="checkbox"/> f <input type="checkbox"/> D <input type="checkbox"/> f <input type="checkbox"/> D	0 (R/S) 1 (print) 0 (R/S) ⋮
3	Load t_{start} , t_{stop} , and t a) time of first data point b) time of last data point c) data point spacing	t_{start} t_{stop} Δt	<input type="checkbox"/> ENT <input type="checkbox"/> ENT <input type="checkbox"/> A	
4	Load data (10 points maximum) load x at t_{start} load x at $t_{start} + \Delta t$ ⋮ load last data point	x_1 x_2 ⋮ x_n	<input type="checkbox"/> B <input type="checkbox"/> B ⋮ <input type="checkbox"/> B	t_{start} $t_{start} + \Delta t$ $t_{start} + 2\Delta t$ ⋮ t_{stop} $t_{stop} + \Delta t$
5	Load estimate for b ($0.1 \leq b \leq 10$) To examine the currently stored value for b, key "C" without numeric entry. The input mode can be cleared with keys "f", "R".	$b_{estimate}$	<input type="checkbox"/> C	
6	To clear input mode (used with step 5)		<input type="checkbox"/> f <input type="checkbox"/> E	
7	Start least squared fit		<input type="checkbox"/> D	a b space
8	Optional; compare input data with least squares fit data		<input type="checkbox"/> f <input type="checkbox"/> A	t_{start} x_1 \hat{x}_1 ⋮
9	Calculate linear estimate for x given t	t	<input type="checkbox"/> E	\hat{x}

Example 5-4.1

A constant voltage was suddenly connected to the field of a large dc traction motor, and an oscilloscope photograph taken of the current. The field time constant is needed to determine loop stability in the overall motor control loop. Table 5-4.1 shows the field current as read from the oscilloscope photo as a function of time.

Table 5-4.1 Motor field current vs. time.

time, seconds	0.1	0.2	0.3	0.4	0.5	0.6	0.7
current, amps	10	18	26	33	39	45	50

Assuming the field to be a simple series LR circuit, find the time constant and the asymptotic field current.

HP-97 PRINTOUT FOR EXAMPLE 5-4.1

.100 ENT† load starting time	GSBa compare input & least squares
.700 ENT† load stopping time	0.100 *** time
.100 GSBA load time increment	10.000 *** I(t) input
	3.587 *** I(t) from least sqs
GSBB setup for data entry	
10.000 GSBB load I(.1)	0.200 ***
18.000 GSBB load I(.2)	18.000 ***
26.000 GSBB load I(.3)	18.211 ***
33.000 GSBB load I(.4)	
39.000 GSBB load I(.5)	0.300 ***
45.000 GSBB load I(.6)	26.000 ***
50.000 GSBB load I(.7)	25.971 ***
1.000 GSBC load b estimate	0.400 ***
	33.000 ***
GSBD start least sqrs fit	32.953 ***
95.569 *** a (asymptotic current)	0.500 ***
1.057 *** b (1/γ, time constant)	39.000 ***
γ = 1/1.057 = 0.9461 seconds	39.234 ***
	0.600 ***
	45.000 ***
	44.885 ***
	0.700 ***
	50.000 ***
	49.969 ***

Program Listing I

001 *LBLA	LOAD t _{start} , t _{stop} , Δt	056 RCL5							
002 ST00	store entries	057 RCL6							
003 R4		058 X							
004 ST00		059 RCL7							
005 R4		060 X							
006 ST0C		061 ST+4							
007 GT0e	goto OF3 and R/S lockup subr	062 GT00 goto summation loop start							
008 *LBLC	LOAD b ESTIMATE	063 *LBL3 start Wegstein solution							
009 F3?	if numeric input, store data	064 RCL3							
010 ST0B		065 RCL4							
011 RCLB	recall b estimate to display	066 X							
012 GT06	goto R/S lockup subroutine	067 RCL2							
013 *LBLD	START LEAST SQUARES CALC	068 ÷							
014 CF0	indicate first time thru loop	069 RCL1							
015 *LBL9	outer loop start	070 -							
016 CLX	initialize sums:	071 F0?							
017 ST01	0 → Σ ₁ → Σ ₂ → Σ ₃ → Σ ₄	072 GT01 jump if not first time							
018 ST02		through loop							
019 ST03		073 RCLB b → f(b)							
020 ST04		074 ST0E							
021 9	initialize index	075 +							
022 ST01		076 ST08 b → b → f(b)							
023 R ⁻¹ C		077 ST0B							
024 RCL8	initialize time register	078 ST09							
025 -		079 SF0 not first time thru loop							
026 ST05		080 GT09 goto outer loop start							
027 *LBL0	summation loop start	081 *LBL1 jump destination							
028 ISZI	increment index	082 RCLB							
029 RCL0	increment time	083 +							
030 ST+5		084 ST08							
031 RCLD		085 RCLB							
032 RCL5	test for loop exit	086 -							
033 X>Y?		087 RCLB ABS { $\frac{\bar{b} - b}{\bar{b}}$ }							
034 GT03		088 ÷							
035 RCLB		089 ABS							
036 X	e ^{-bt_i}	090 EEX							
037 CHS		091 CHS							
038 e ^x		092 6 test for loop exit							
039 ST06		093 X>Y?							
040 CHS	1 - e ^{-bt_i}	094 GT02							
041 EEX		095 RCL9							
042 +		096 RCL8							
043 ST07		097 -							
044 X ²	$\Sigma_2 + (1 - e^{-bt_i})^2 \rightarrow \Sigma_2$	098 RCL6 q _b = $\frac{f(b) - b}{f(\bar{b}) - \bar{b}}$							
045 ST+2		099 RCL8							
046 RCLi		100 -							
047 RCL5	$\Sigma_1 + x_i \cdot t_i \cdot e^{-bt_i} \rightarrow \Sigma_1$	101 ÷							
048 X		102 ST0A							
049 RCL6		103 RCLB							
050 X		104 ST0E							
051 ST+1		105 RCL8							
052 RCLi		106 -							
053 RCL7	$\Sigma_3 + x_i (1 - e^{-bt_i}) \rightarrow \Sigma_3$	107 RCL6							
054 X		108 EEX							
055 ST+3		109 -							
		110 ÷							
REGISTERS									
0 Δt	1 Σ ₁	2 Σ ₂	3 Σ ₃	4 Σ ₄	5 t _i	6 e ^{-bt_i}	7 1 - e ^{-bt_i}	8 b	9 f(b)
S0 x ₀	S1 x ₁	S2 x ₂	S3 x ₃	S4 x ₄	S5 x ₅	S6 x ₆	S7 x ₇	S8 x ₈	S9 x ₉
A a, q	B \bar{b}	C t _{start}	D t _{stop}	E f(\bar{b})	F Index				

Program Listing II

<pre> 111 RCLB 112 + 113 STOB 114 RCL8 115 STO9 116 GT09 goto outer loop start 117 *LBL2 Wegstein output 118 F1? 119 SPC 120 RCL3 121 RCL2 122 = 123 STOA 124 GSB5 gosub print or R/S subr 125 RCLB recall b 126 GT04 goto print and space subr 127 *LBLc COMPARE INPUT & LEAST SQRS 128 RCLC 129 RCL0 setup time register and index register 130 - 131 STO1 132 9 133 S101 134 *LBL7 loop start 135 ISZI increment register index 136 RCL0 increment time index 137 S1 138 RCL 139 RCL5 140 X>Y? 141 ST06 142 GSB5 143 RCLI 144 GSB5 145 R+ 146 GSBE calculate and output least squares estimate 147 GT07 goto loop start 148 *LBL8 LEAST SQUARES ESTIMATE 149 RCLB calculate: 150 X 151 CHS 152 e^X 153 CHS 154 1 155 + 156 RCLA 157 X 158 *LBL4 print and space subroutine 159 GSB5 gosub print or R/S subr 160 F1? 161 SPC space if print mode set 162 GT0e goto OF3 and R/S lockup subr </pre>		<pre> 163 *LBL5 print or R/S subroutine 164 F1? 165 PRTX print and return if flag 1 is set, otherwise 166 F1? 167 RTN 168 R/S stop and await R/S command 169 RTN 170 *LBLB LOAD DATA 171 9 initialize register index 172 STOI 173 *LBL8 data storage loop start 174 ISZI increment register index 175 RCLI 176 EEX calculate time for x(t) 177 1 178 - 179 RCL0 180 X 181 RCLC 182 + 183 R/S display time & await entry 184 *LBLB data storage 185 STOI store data 186 GT08 goto loop start 187 *LBLc CF3 and R/S lockup subr 188 CF3 clear flag 3 189 *LBL8 R/S lockup subroutine 190 RTN 191 GT06 192 *LELd PRINT OR R/S TOGGLE 193 CF1 clear flag 1 for R/S mode 194 CLX and place a zero in display 195 RTN return control to keyboard 196 *LBLd toggle continued 197 SF1 set flag 1 for print mode 198 EEX and place a one in display 199 PTN return control to keyboard </pre>																									
LABELS																											
A load times	B load data	C load b estimate	D start least squares																								
a output summary	b	c	d print toggle																								
0 form sums	1 Wegstein major loop	2 Wegstein output	e clear flag 3																								
5 print or R/S	6 R/S lock	7 summary loop	f print																								
FLAGS																											
SET STATUS																											
<table border="1" style="width: 100%; border-collapse: collapse;"> <thead> <tr> <th style="width: 50%;">FLAGS</th><th style="width: 50%;">TRIG</th></tr> </thead> <tbody> <tr> <td>ON</td><td>DEG</td></tr> <tr> <td>OFF</td><td>FIX</td></tr> <tr> <td>0</td><td>GRAD</td></tr> <tr> <td>1</td><td>SCI</td></tr> <tr> <td>2</td><td>ENG</td></tr> <tr> <td>3</td><td>n</td></tr> </tbody> </table>		FLAGS	TRIG	ON	DEG	OFF	FIX	0	GRAD	1	SCI	2	ENG	3	n	<table border="1" style="width: 100%; border-collapse: collapse;"> <thead> <tr> <th style="width: 50%;">DISP</th><th style="width: 50%;">USERS CHOICE</th></tr> </thead> <tbody> <tr> <td>DEG</td><td>FIX</td></tr> <tr> <td>GRAD</td><td>SCI</td></tr> <tr> <td>RAD</td><td>ENG</td></tr> <tr> <td>n</td><td></td></tr> </tbody> </table>		DISP	USERS CHOICE	DEG	FIX	GRAD	SCI	RAD	ENG	n	
FLAGS	TRIG																										
ON	DEG																										
OFF	FIX																										
0	GRAD																										
1	SCI																										
2	ENG																										
3	n																										
DISP	USERS CHOICE																										
DEG	FIX																										
GRAD	SCI																										
RAD	ENG																										
n																											

LIST OF ABBREVIATIONS

Note:
Flag one should be set or reset
prior to magnetic card recording
depending whether the user wishes the
program to normally come up in print
or R/S mode after the card read.
Step 2 can be skipped in this instance.

LIST OF ABBREVIATIONS

alternative or alternate	alt	destination	dest
amplifier	amp	diameter	diam
approximately	approx	display	dsp
arithmetic	arith	distance	dist
attenuation	atten	electrical	elect
		elements	elts
bandpass	BP	enter	ent
bandstop	BS	Equation(s)	Eq(s).
bandwidth	BW	equivalent	equiv
branch	br	evaluation	eval
Butterworth	Buttr	even part of (.)	Ev(.)
		execute	exec
calculation or calculate	calc		
capacitor	cap	feedback	fdbk
Chebyshev	Cheb	Figure	Fig.
circuit	ckt	format	fmt
clear	clr	frequency	freq
coaxial	coax	function	fcn
coefficient	coef		
complex	cmplx	go substitute	go sub
conductance	cond	go to	gto
conjugate	conj		
conversion	conv	henry	h
co-ordinates	co-ords	highpass	HP
decibel	dB	imaginary	imag
decibel ripple	dBR	increment	incr
denominator	den	initialize	init
denormalization	denorm	input/output	I/O
density	dens	integral	int

label	lbl	resistance	resist
level	lvl	return	rtn
linear	lin	review	revu
loop	lp	root sum square	RSS
lowpass	LP	root mean square	RMS
matrix	mat	secondary	sec
minimum	min	section	sect
multiplication	mult	solution	soln
		space	spc
negative	neg	specification(s)	spec(s)
numerator	num	square	sq
		starting frequency	f _{st}
odd part of(·)	Odd(·)	stopping frequency	f _{sp}
order	ord	store	sto
		subroutine	subr
page	pg, p	sweep	swp
parameters	params		
peak	pk	temporary	temp
polynomial	poly	terminating,	term
preamplifier	preamp	terminal, or	
primary	pri	termination	
print	prt	through	thru
program	pgm	toggle	tog
		total	tot
recall	rcl	transform	xfrm
rectangular	rect	transformer	xfmr
reflection	refl	transistor	xstr
register(s)	reg(s)	transmitter	xmit
required	reqd	transmission	xmsn
		trigonometric	trig

BIBLIOGRAPHY

- 1 Abramowitz, M., and Stegun, I., Handbook of Mathematical Functions with Formulas, Graphs, and Mathematical Tables, AMS #55, Nat'l Bur. of Stds., Washington, D.C., 1972.
- 2 Amstutz, P., "Elliptic Approximation and Elliptic Filter Design on Small Computers," IEEE Trans. on Ckts. and Systems, vol CAS-25, Dec. 1978, pp. 1001-1011.
- 3 Antoniou, A., "Realization of Gyrators Using Operational Amplifiers and Their Use in RC Active Network Synthesis," Proc IRE (London), vol 116, Nov. 1969, pp. 1838-1850.
- 4 Bashkow, T.R., ch 26 in Mathematical Methods for Digital Computers, Eds. Ralston, A., and Wilf, H., Wiley, N.Y., 1960.
- 5 Belevitch, V., "Tchebycheff Filter and Amplifier Networks," Wireless Engineer, vol 29, April 1952, pp. 106-110.
- 6 Bell, W., Matrices for Scientists and Engineers, Van Nostrand Reinhold, N.Y., 1975.
- 7 Bennett, W.R., "Transmission Network," U.S. Pat 1,849,656, 15 March 1932.
- 8 Blinchikoff, H., and Zverev, A., Filtering in the Time and Frequency Domains, Wiley-Interscience, N.Y., 1976.
- 9 Bodway, G.E., "Circuit Design and Characterization of Transistors by Means of Three Port Scattering Parameters," Microwave Journal, vol 11, no. 15, May 1968.
- 10 Bruton, L., "Network Transfer Functions Using the Concept of Frequency Dependent Negative Resistance," IEEE Trans. on Ckt. Theory, vol CT-16, Aug. 1969, pp. 406-408.
- 11 Bumet, P., "On the Self Inductance of Circular Cylindrical Coils," Revue General de l'Electricite, Tome xlivi, no. 4, Jan. 1938, p. 99.
- 12 Byrd, P., and Friedman, M., Handbook of Elliptic Integrals for Engineers and Physicists, Springer-Verlag, N.Y., 1954.
- 13 Callendar, M., "Q of Solenoid Coils," Wireless Engineer, vol 24, June 1947, p. 185.

- 14 Carnahan, B., Luther, H., Wilkes, J., Applied Numerical Methods, Wiley, N.Y., 1969.
- 15 Carson, R.S., High Frequency Amplifiers, Wiley-Interscience, N.Y., 1975.
- 16 Cohn, S., "Direct Coupled Resonator Filters," Proc. IRE, vol 40, Feb. 1957, pp. 186-196.
- 17 Daniels, R., Approximation Methods for Electronic Filter Design, McGraw-Hill, N.Y., 1974.
- 18 Darlington, S., "Simple Algorithms for Elliptic Filters and a Generalization Thereof," session 3 of IEEE Int. Symp. on Ckts. and Systems Proc., May 1978, pp. 35-39.
- 19 Daryanani, G., Principles of Active Network Synthesis and Design, Wiley, N.Y., 1976.
- 20 Deliyannis, T., "High-Q Factor Circuit with Reduced Sensitivity," Electronic Letters, vol 4, Dec. 1968, p. 577.
- 21 Dishal, M., "Design of Dissapative Band-Pass Filters Producing Exact Amplitude-Frequency Characteristics," Proc IRE, vol 37, Sept. 1949, pp. 1050-1069.
- 22 Doyle, W., "Lossless Butterworth Ladder Networks Operating Between Arbitrary Resistances," J. Math. Phys., vol 37, no. 1, April 1958, pp. 29-37.
- 23 Fano, R.M., "Theoretical Limitations on the Broadband Matching of Arbitrary Impedances," J. Franklin Inst., vol 249, Jan. 1950, pp. 57-83, and vol 249, Feb. 1950, pp. 139-154.
- 24 Froehner, W.H., "Quick Amplifier Design with Scattering Parameters," Electronics Magazine, 16 Oct. 1967.
- 25 Fortescue, Standard Handbook for Electrical Engineers, McGraw-Hill, N.Y., 1922 5th ed., p. 413.
- 26 Geffe, P.R., Designers Guide to Active Filters, Cahners Pub. Co., Boston, MA., 1974.
- 27 Geffe, P.R., "Microcomputer-Aided Filter Design," IEEE Ckts. and Systems Magazine, vol 1, no. 1, Jan. 1979, pp. 5-8.
- 28 Green, E., Amplitude-Frequency Characteristics of Ladder Networks, Marconi's Wireless Telegraph Co. Ltd., Essex, England, 1954.
- 29 Grove, W.E., Brief Numerical Methods, Prentice-Hall, Englewood Cliffs, N.J., 1966.
- 30 Grover, F.W., Inductance Calculations, Working Formulas and Tables, D. Van Nostrand, N.Y., 1946.

- 31 Hamming, R., Numerical Methods for Scientists and Engineers, second edition, McGraw-Hill, N.Y., 1973.
- 32 Hewlett-Packard Application note #95, "S parameters . . . Circuit Analysis and Design," Hewlett-Packard Co., Sept. 1968.
- 33 Hewlett-Packard Journal, "S Parameters for Faster, More Accurate Network Design," vol 18, no. 6, Feb. 1967, p. 3-7.
- 34 Kawakami, M., "Nomographs for Butterworth and Chebyshev Filters," IEEE Trans. on Ckt. Theory, vol CT-10, June 1963, pp. 288-289.
- 35 Kerwin, W., and Heulsman, L., "Design of High Performance Active RC Band Pass Filters," 1966 IEEE Int. Conv. Rec., vol 14, part 10, pp. 74-80.
- 36 Lee, R., Electronic Transformers and Circuits, second ed., Wiley, N.Y., 1961.
- 37 Matthaei, G., "Synthesis of Tchebycheff Impedance-Matching Networks, Filters, and Interstages," IRE Trans. on Ckt. Theory, vol CT-3, Sept. 1956, pp. 163-172.
- 38 Moschytz, G., "Second-Order Pole-Zero Selection for n-th Order Minimum Sensitivity Networks," IEEE Trans. on Ckt. Theory, vol CT-17, Nov. 1970, pp. 527-534.
- 39 Norton, E.L., "Constant Resistance Networks with Applications to Filter Groups," BSTJ, vol 16, April 1937, pp. 178-193.
- 40 Orchard, H.J., "Formulae for Ladder Filters," Wireless Engineer, vol 30, Jan. 1953, pp. 3-5.
- 41 Orchard, H.J., "Computation of Elliptic Functions of Rational Fractions of a Quarter period," IRE Trans. on Ckt. Theory, vol CT-5, Dec. 1958, pp. 352-355.
- 42 Orchard, H.J., and Sheahan, D.F., "Inductorless Bandpass Filters," IEEE Jour. of Solid State Ckts., vol SC-5, June 1970, pp. 108-118.
- 43 Potter, J., and Fich, S., Theory of Networks and Lines, Prentice-Hall, Englewood Cliffs, N.J., 1963.
- 44 Reference Data for Electrical Engineers, Fourth Ed., ITT Corp., New York, N.Y., 1959.
- 45 Saal, R., and Ulbrich, E., "On the Design of Filters by Synthesis," IRE Trans. on Ckt. Theory, vol CT-5, Dec. 1958, pp. 284-327.
- 46 Skwirzynski, J., and Zdunek, J., "Note on Calculation of Ladder Coefficients for Symmetrical and Inverse Impedance Filters on a Digital Computer," IRE Trans. on Ckt. Theory, vol CT-5, Dec. 1958, pp. 328-332.

- 47 Still, A.F., Elements of Electrical Design, McGraw-Hill, N.Y., 1932.
- 48 Szentirmai, G., "Synthesis of Multiple Feedback Active Filters," BSTJ, vol 52, April 1973, pp. 527-555.
- 49 Temes, G., and La Patra, J., Circuit Synthesis and Design, McGraw-Hill, N.Y., 1977.
- 50 Temes, G., and Mitra, S., Eds., Modern Filter Theory and Design, Wiley-Interscience, N.Y., 1973.
- 51 Takahasi, H., "On the Ladder-Type Filter Network with Tchebycheff Response," J. Inst. Elec. Commun. Engrs., Japan, vol 34, Feb 1951, (In Japanese).
- 52 Terman, F.E., Radio Engineers Handbook, McGraw-Hill, N.Y., 1943.
- 53 Weinberg, L., Network Analysis and Synthesis, McGraw-Hill, N.Y., 1962.
- 54 Weinberg, L., and Slepian, P., "Takahasi's Results on Techbycheff and Butterworth Ladder Networks," IRE Trans. on Ckt. Theory, vol CT-7, June 1960, pp. 88-101.
- 55 Wheeler, H.A., "Simple Inductance Formulas for Radio Coils," Proc IRE, vol 16, no. 10, Oct 1928, p. 1398 and subsequent discussion in vol 17, no. 3, March 1929, p. 580.
- 56 White, D.R.J., A Handbook on Electrical Filters, Don White Consultants, Gainesville, VA., 1963.
- 57 Yengst, W.C., Procedures of Modern Network Synthesis, Macmillan, N.Y., 1964.
- 58 Zverev, A.I., Handbook of Filter Synthesis, Wiley, N.Y., 1967.

INDEX

INDEX

- Abramowitz, M., 290, 332, 276, 478, 484
Active filters, 41-84, 233-280
Air gap, 337, 391, 400
Amstutz, P., 293
Analysis:
 active networks, 41-84, 268-269
 LC filters, 97-108
 LRC filters, 75-96
Antoniou, A., 202
Approximation:
 Butterworth, 129-140
 Chebyshev, 129-140
 elliptic, 281-296
 narrowband, 185-216
 maximally flat *see* Butterworth
AWG of wire, 347, 375

Balanced structure, 178, 180
Ball, J., 3
Bandpass transformations, 165-166, 185-216, 299
Bandstop transformations, 166-168, 299
Bartlett's bisection theorem, 101
Bashkow, T.R., 87
Belevitch, V., 154
Bell, W.W., 455
Bennett, W.R., 154

Bessel functions, 476, 481
Bilateral:
 amplifier design, 427
 network, 163, 185, 199, 217, 233
Biquad circuits, 235
Bodway, G., 435
Bruton, L., 156
Bunet, P., 383
Butterworth approximation, 129-130, 134, 136-137, 146, 155, 233, 245-246
Byrd, P., 292, 476

Callendar, M., 375
Capacitance of transformers, 353
Carnahan, B., 455
Carson, R.S., 428
Cascade synthesis, 235
Characteristic function, 287, 309
Chebyshev rational function:
 definition, 287-289
 relation to elliptic functions, 293-294
Closed loop gain, 255
Coaxial cable *see* Transmission Line
Coefficient matching technique, 256-256
Coefficient sensitivity, *see* Sensitivity
Cohn, S., 171, 185, 199
Cubic spline, 491-493

Daniels, R., 281, 287, 291, 297
 Darlington, S., 293, 325
 Daryanani, G., 254, 255, 272
 Delay (of Butterworth and Chebyshev filters), 141-152
 Decomposition into second order function, 235, 267
 Deliyannis, T., 235, 267
 Dishal, M., 171, 185
 Doyle, W., 22
Elliptic filter:
 attenuation, 297-299
 characteristic function, 326
 degree, calculation of, 283, 293
 examples, 303, 304, 313, 314
 loss function, 298
 natural modes, 309-311, 326
 transformation to produce loss pole at infinity, 283-284
Elliptic functions:
 sine (sn), 292, 476
 cosine (cn), 476
 delta (an), 476
 amplitude (am), 476
Elliptic integrals, 292, 475
Equiripple filters, 309-324
Esperti's method, 237-238
Even part (Ev), 318

Fano, R.M., 121
Feedback factor, 267
Feldtkeller equation, 287, 309
Ferromagnetic cores, 337
Fich, S., 36

Fortescue, 253
Fourier series for elliptic sine, 292
Frequency normalization, 163-164
Frequency-dependent-negative-resistance (FDNR), 156
Friedman, M., 292, 476
Froehner, W.H., 428

Gain-bandwidth of op-amps, 267
Gain, open loop, 49-54, 268, 271, 272
Gain-bandwidth product, 272
Gain sensitivity, 271
Geffe, P.R., 272, 293
Green, E., 154
Grove, W.E., *see* Wegstein's method
Grover, F.W., 365
Gyrator, Antoniou, 202

Hamming, R.W., 3, 491
Heulsman, L., 235
Highpass transformation 142-143, 164-165
h parameters, 447

Inductance:
 leakage, 353
 of aircore coils, 373, 383
 of solenoids, 395
 of straight wires, 366
 of wire loops, 367
 open circuit, 338
 quality factor (Q), 375
Inductors:
 active, 202-203
 passive, 337-352

Input bias current, 260
Input noise, 109
Input offset voltage, 260

Jacobian elliptic functions, 475
Johnson noise, 109

.Kawakami, M., 129, 133, 134
Kerwin, W., 235

Ladder networks, 41, 76, 80, 83, 101, 103, 109
Landen, descending transformation, 292, 476, 479,
LaPatra, J., 235
Least squares fit, 501-503
Low-pass approximation, *see* Approximation
Loss function, 297-299
Luther, H.A., 455

Magnetic path, 337
Magnetic saturation, 344
Matrix algebra, 447-471
Matthaei, G., 121
Möbius transformation, 283-284, 299
Modular elliptic function, 292
Moschytz, G., 309

Natural modes:
 of Butterworth filters, 146
 of Chebyshev filters, 148
 of elliptic filters, 328
 of equiripple filters, 309-312
 of maximally flat filters, 146
Negative feedback biquad, 267

Network, two port, 447
Newton's method (Newton-Raphson iteration), 57
Nodal analysis, 56, 258
Normalized lowpass filter, 153-162
Norton, E., 154, 211

Offset voltage, 260
Open loop gain, 41, 45, 50, 51, 52, 54, 55, 268, 276
Orchard, H.J., 154, 202, 293
Ordering of biquads, 244
Oscillator (design with s parameters), 433

Passband:
 bandpass filter, 131
 bandstop filter, 167
 highpass filter, 142-143, 253
 lowpass filter, 147-148
Passive networks:
 analysis, 75-108
 LC filter, 153-216
 transformation, 217-232
 transmission lines, 13-40
Permeability, 337
Phase delay, 142
Pole frequency, ω_n , definition, 234
Pole Q, definition, 234
Poles, complex conjugate, 234
Positive feedback biquads *see* Sallen and Key
Potter, J.I., 36
Power dissipated in coil, 395

Q enhancement, 270
Q factor of inductors, 375
Quadrangle symmetry, 316

Quality of roots:
 Butterworth, 234
 Chebyshev, 234

Rational function, Chebyshev, 289

Reflection coefficient, 14, 15, 32, 286, 298, 313, 428

Reluctance, 393-394, 419

RC-CR transformations, 253-254

Saal, R., 299, 305

Sallen, R.P., and Key, E.L., 234

Scaling component values, 163-164

Secant iteration method, 318-320

Second order functions, 44, 59, 234-235

Sensitivity of biquads, Deli-yannis, 270, 271

Sheehan, D., 156, 202

Short circuit (*y*) parameters, 447-448

Skwirzinski, J., 476

Slepian, P., 154

Smith, J.M., 3

Solenoid design and analysis, 391-418

Solenoid pull in force, 391

s parameters 427

Stegun, I., 290, 332, 476, 478, 484

Still, A.F., 402

Stopband, 167

Szentirmai, G., 156, 235, 255, 267

Takahasi, H., 154

Temes, G., 235

Terman, F.E., 365

Transfer function - definition, 7

Transformations:
 gyrator, 202
 lowpass to bandpass, 165
 lowpass to bandstop, 166
 lowpass to highpass, 164
 Möbius, 283-284, 299
 Norton, 223
 RC-CR, 253-254
 Wye-delta, 217

Transformers:
 capacity, 355
 design, 337
 ideal, 227
 leakage inductance, 353
 wire size, 347

Transistors:
 configuration conversion, 449
 parameter conversion, 447

Transmission line:
 input impedance, 14
 propagation constant, 14
 reflection coefficient, 14, 15, 32
 transmission function, 32

Tuning LC filters, 193, 204-205

Two-port network, 447

Uhlbrich, E., 299, 305

Unilateral design method, 427

Weinberg, L., 154, 156

Wegstein's method, 502

Wheeler, H.A., 373

Wilkes, J.O., 455

Wire, AWG, 347, 375

White, D.R.J., 168, 185, 186, 199

Yengst, W.C., 101

y parameters, 448

Zeros of transfer function, 310, 318

Zdunek, J., 476

z parameters, 455

Zverev, A.I., 224, 283, 286, 290, 314